

Total No. of Questions :12]

SEAT No. :

**P4218**

**[5459]-6**

[Total No. of Pages : 4

**S.E. (E & TC/ Electronics)**

**POWER DEVICES & MACHINES**

**(2008 Pattern) (204185) (Semester - I)**

*Time : 3 Hours]*

*[Max. Marks : 100*

*Instructions to the candidates:*

- 1) *Answer three questions from section-I and three questions from section-II.*
- 2) *Answer to the two sections should be written in separate answer books.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Assume suitable data, if necessary.*

**SECTION-I**

**Q1) a)** Draw and explain reverse characteristics of power diode with mathematical analysis. **[9]**

b) Draw constitution diagram of IGBT and explain its switching characteristics. **[9]**

OR

**Q2) a)** Why UJT triggering is preferred? Draw and explain line synchronised UJT triggering circuit for S.C.R. **[9]**

b) The reverse recovery time of power diode is 5  $\mu$  sec and rate of fall of diode current is 80 A/ $\mu$  sec. If softness factor is 0.5, determine **[9]**

i)  $t_a$  and  $t_b$

ii) Peak inverse current ( $I_{RR}$ )

iii) Storage charge ( $S_{RR}$ )

**Q3) a)** Draw and explain two transistor analogy of SCR and derive an expression for anode current. **[8]**

b) Design UJT triggering circuit with the following UJT data:  $R_{BB}=5k\Omega$ ,  $n=0.72$ ,  $I_p=0.6$  MA,  $V_p=18$  V,  $V_v=I_v=2.5$  MA, normal leakage current=4.2 MA. Frequency of pulses is 2kHz,  $C=0.04\mu$ f. **[8]**

OR

**P.T.O.**

**Q4) a)** Explain different triggering modes of triac with proper later diagrams. With two modes are more sensitive. [8]

**b)** Describe following ratings as applicable to SCR [8]

i) Surge current rating

ii)  $I^2t$  rating

iii)  $\frac{dv}{dt}$  rating

iv)  $\frac{di}{dt}$  rating

**Q5) a)** Describe the working of single phase fully controlled bridge converter for R-L load in the following modes [8]

i) Rectifying mode

ii) Inversion mode

Also derive an expression for average output voltage.

**b)** Draw and explain single phase AC voltage controller for 'R' load with wave forms. Derive an expression for its output voltage. [8]

OR

**Q6) a)** A single phase semi converter is operated from 120 V, 50Hz and load resistance is  $10\Omega$ . IP the average output voltage is 25% of maximum possible average output voltage, calculate: [8]

i) Decay angle ( $\alpha$ )

ii) RMS and average output current

**b)** Explain with neat diagram and wave forms the working of three phase AC voltage controller with resistive load. [8]

## SECTION-II

- Q7)** a) Draw and explain step down chopper for 'R' load. Derive the expression for average and rms output voltages. [9]
- b) A step down DC chopper has resistive load  $R=15\ \Omega$  and input voltage  $V_{dc}=200V$ . When chopper remains on its voltage drop is 2.5 V. The chopper frequency is 1kHz. IP duty cycle is 50% find: [9]
- i) Average output voltage
  - ii) RMS output voltage
  - iii) Chopper efficiency
  - iv) Effective input resistance of chopper.

OR

- Q8)** a) With neat circuit diagram and necessary wave forms, explain the operation of single phase bridge Inverter with 'R' load. [9]
- b) Single phase full bridge Inverter has resistive load of  $R=3\ \Omega$  and input voltage = 50V [9]
- Calculate:
- i) RMS output voltage at fundamental frequency
  - ii) Output power ( $P_o$ )
  - iii) Average and peak currents of each thyristor

- Q9)** a) Explain torque-current and torque-speed characteristics of DC shunt motor. [8]
- b) Derive an expression for torque of DC motor obtain condition-for maximum power. [8]

OR

**Q10)a)** Explain torque-speed characteristics of three phase Induction motor.[8]

b) Explain different methods of speed control of three phase induction motor. [8]

**Q11)a)** What is an auto transpower, explain its working with neat diagram. List its advantages and draw books. [8]

b) What is a stepper motor. Explain the working of stepper motor with neat diagram. [8]

OR

**Q12)a)** Explain construction, working of BLDC motor with the characteristics.[8]

b) Draw and explain various types of 3 phase transformer connection in details. [8]

