

**[5460]-15**  
**T.E. (E & TC)**  
**NETWORK SYNTHESIS AND FILTER DESIGN**  
**(2008 Pattern)**

Time : 3 Hours]

[Max. Marks : 100

**Instructions to the candidates:**

- 1) Answers to the two sections should be written in separate books.
- 2) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8, Q.9 or Q.10, Q.11 or Q.12.
- 3) Use of electronic pocket calculator is allowed.
- 4) Figures to the right side indicate full marks.
- 5) Assume Suitable data if necessary.

**SECTION - I**

- Q1)** a) List the properties of positive real function. [6]  
 b) Determine whether the polynomials  $F(s)$  are Hurwitz [8]  
 i)  $F(s) = s^4 + s^3 + 5s^2 + 3s + 4$   
 ii)  $F(s) = s^4 + s^3 + 2s^2 + 3s + 2$   
 c) For a two port network, define all the transfer functions. [4]

OR

- Q2)** a) Explain the significance of poles and zeros in network synthesis. Also discuss effect of poles and zeros on response. [6]  
 b) Determine whether the following function is positive real function [4]

$$Z(S) = \frac{s^2 + 1}{s^3 + 4s}$$

- c) For the network shown in Fig. 1, find current transfer ratio  $\alpha_{12}(s)$  and transfer impedance  $Z_{21}(s)$ . [8]

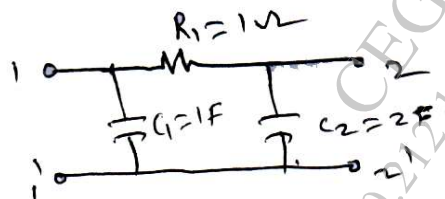


Fig. 1

- Q3) a)** Synthesize the following one port network function in both foster forms [8]

$$Z(S) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- b) Synthesize the following one port network function in both Cauer forms [8]

$$Z(S) = \frac{3(s + 2)(s + 4)}{s(s + 3)}$$

OR

- Q4) a)** List properties of one port RC driving point impedance function. [6]  
b) Indicate with reasons which of the following driving point functions are RC, LC or RL. Out of that realize only RL function in first foster and first Cauer forms. [10]

i)  $Z(S) = \frac{s^3 + 2.6s}{s^4 + 4s^2 + 3}$

ii)  $Y(S) = \frac{s^2 + 2.5s}{s^2 + 5s + 6}$

iii)  $Y(S) = \frac{2(s + 1)(s + 3)}{(s + 2)(s + 6)}$

- Q5) a)** Define constant resistance network. For a constant resistance Lattice or Bridge T network prove that  $Z_a Z_b = R^2$  [8]

- b) Synthesize  $Z_{21}(S) = \frac{s^3}{s^3 + 3s^2 + 4s + 2}$  as a LC ladder with  $1 \Omega$  termination. [8]

OR

- Q6) a)** Synthesize the all pass function. [6]

$$\frac{V_o}{V_{in}} = \frac{s^2 - 2s + 2}{s^2 + 2s + 2} \text{ as a lattice network terminated into } 1\Omega.$$

- b) Synthesize voltage ratio

$$\frac{V_2}{V_1} = \frac{s + 2}{s + 3}$$

as a constant resistance bridge T network terminated by  $1\Omega$ . [6]

- c) Identify the zeroes of transmission for the network in Fig.2. [4]

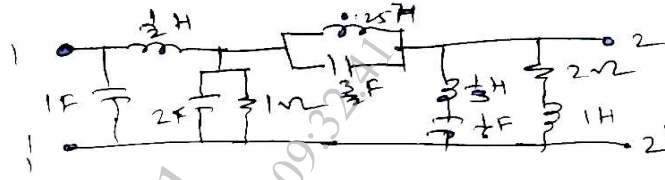


Fig. 2

## SECTION - II

- Q7) a)** Explain the need and concept of magnitude and frequency normalization in context with filter designing. [6]
- b)** Realize a third order Butterworth low pass filter transfer impedance terminated in load of  $500 \Omega$  with a cut off frequency of  $10^4$  rad/sec. Also convert it into high pass of same specifications. [12]

OR

- Q8) a)** Compare Butterworth and Chebyshev approximation. [6]
- b)** Design a Chebyshev approximated low pass filter with not more than 1 dB ripple in pass band and 20 dB attenuation at 2 rad/sec. [12]
- Q9) a)** What are different biquad feedback topologies used in active filter design. [8]
- b)** Synthesize a 2<sup>nd</sup> order high pass filter having cut off frequency 1kHz using the Sallen and Key circuit based on positive feedback. [8]

OR

- Q10) a)** What is cascade approach in active filter synthesis? Explain in detail and list its advantages. [8]
- b)** Design a second order Butterworth low pass active filter having upper cut off frequency 1kHz. [8]

- Q11) a)** Define sensitivity and its significance. Derive the property of sensitivity,

$$S_x^{y_1+y_2} = \frac{y_1 S_x^{y_1} + y_2 S_x^{y_2}}{y_1 + y_2}. \quad [8]$$

- b) Find the transfer function ( $V_2/I_1$ ) of a passive network shown in Fig.3. Also compute the sensitivities of  $K$ ,  $\omega_p$  and  $Q_p$  with respect to elements. [8]

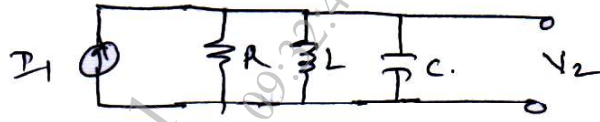


Fig. 3

OR

- Q12)a)** Describe the properties of op-amp such as dynamic range, slew rate, offset voltage, input bias and input offset currents and common mode signal in context of filter design. [8]

- b) Derive the sensitivity properties : [8]

i)  $S_x^{y^n} = nS_x^y$

ii)  $S_x^y = \frac{1}{n} S_x^y$

iii)  $S_x^y = S_p^y S_x^p$

iv)  $S_x^{pq} = S_x^p + S_x^q$

