

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4857]-1083

S.E. (I.T.) (First Semester) EXAMINATION, 2015
DIGITAL ELECTRONICS AND LOGIC DESIGN
(2012 PATTERN)

Time : Two Hours**Maximum Marks : 50**

- N.B. :—** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
- (ii) Neat diagrams must be drawn wherever necessary.
- (iii) Figures to the right side indicate full marks.
- (iv) Assume suitable data, if necessary.

1. (a) Convert the following numbers, show all steps : [6]
- (i) $(2598.675)_{10} = (\quad)_{16}$
- (ii) $(110101.101010)_2 = (\quad)_8$
- (iii) $(A72E)_{16} = (\quad)_8$
- (b) Draw and explain CMOS Non-inverting buffer. [6]

Or

2. (a) Design full Subtractor using Decoder IC 74138. [6]
- (b) Explain the following TTL characteristics. [6]
- (i) Noise Immunity
- (ii) High level input voltage (V_{IH})
- (iii) Figure of Merit

P.T.O.

3. (a) What is race around condition ? Explain with the help of timing diagram. How is it removed using Flip-flop. [7]

(b) Draw and explain 3-bit ring counter. [6]

Or

4. (a) Design a sequence generator to generate the sequence10110using IC 74194. [7]

(b) Design MOD-11 Up counter using IC 74191. [6]

5. (a) Design the following functions using PLA. [6]

$$F1 = \sum m (1, 3, 5)$$

$$F2 = \sum m (5, 6, 7)$$

(b) Draw and explain block diagram of CPLD. [6]

Or

6. (a) Explain the difference between CPLD and FPGA. [6]


(b) Design 4 : 1 Multiplexer using PAL. [6]

7. (a) Explain the difference between data flow and behavioural modeling. [7]

(b) Write entity and architecture of D Flip-flop with clear input using behavioural modeling. [6]

Or

 8. (a) Write entity and architecture of following circuit using structural modeling. [7]



- (b) What is VHDL ? Draw the structure of VHDL module and explain various components of it. [6]