

Total No. of Questions : 6]

SEAT No. :

P536

[Total No. of Pages : 2

TE/Insem/APR-128
T.E. (Electronics Engineering)
PLC AND APPLICATION
(2015 Pattern) (Semester - II)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates :

- 1) *Answer Q.1 or Q.2, Q.3 or Q.4 and Q.5 or Q.6.*
- 2) *Figures to the right indicate full marks.*
- 3) *Assume suitable data, if necessary.*

Q1) a) Write short note on : **[6]**

- i) Programming word level logic instruction
- ii) Principle of Operation of PLC

b) Differentiate PLC Vs Computer. **[4]**

OR

Q2) a) What is PLC? Draw and Explain block diagram of PLC? **[6]**

- b) Draw the Gate Logic, Relay ladder Logic and PLC ladder diagram for given equation.

$Y=AB+CD$ **[4]**

Q3) a) List different types of switches which are interface with PLC input module. Explain any one switch. **[6]**

b) Write short note on branch instruction. **[4]**

OR

Q4) a) List different types of output Devices which are interface with PLC Output module. Explain any one in detail. **[6]**

b) Write Short Note on PLC Programming Languages. **[4]**

P.T.O.

Q5) a) Blinking Indicator Lights are used quite extensively in industry. Design a circuit in which two lights are flashed alternately every after 5 seconds. Draw PLC ladder Diagram. [6]

b) List various types of comparison Function used in PLC. Explain any one in detail. [4]

OR

Q6) a) List various types of Timers used in PLC. Explain any one in detail. [6]

b) The Start Switch Starts Motor 1 and 10 seconds later motor 2 starts. The Stop switch stops motor 1 and 15 seconds later motor 2 stops. Draw PLC ladder diagram for the above statement. [4]
