

Total No. of Questions : 6]

SEAT No. :

P531

[Total No. of Pages : 2

TE/Insem/APR-119
T.E. (E & Tc Engineering)
POWER ELECTRONICS
(2015 Pattern) (Semester - II)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6.
- 2) Figures to the right indicate full marks.

Q1) a) Explain following rating of SCR, [6]

- i) Holding current
- ii) Latching current
- iii) V_{BO}
- iv) V_{RRM}

b) Draw the V-I characteristics of IGBT. Mark & explain various operating regions & SOA of the IGBT. [4]

OR

Q2) a) Explain how the following devices can be operated as switch with necessary driving conditions. [6]

- i) SCR
- ii) IGBT

b) Draw & Explain switching characteristics of SCR. [4]

Q3) a) With the help of neat circuit diagram and waveforms, explain the operation of 1ϕ Full-converter for $\alpha = 30 \text{ deg.}$ and $\alpha = 60 \text{ deg.}$ with R load. [5]

b) Draw & Explain the single phase dual converter. Explain the 4 quadrant operation of dual converter. [5]

OR

Q4) a) Explain effect of source Inductance on the performance of 1Φ full converter. Derive the expression for average output voltage? [4]

b) In a single phase semi converter with highly inductive load is feed from $120V$ RMS ac mains & fired at $\alpha = 90 \text{ deg.}$, Calculate [6]

- i) Average Load voltage
- ii) RMS Load Voltage
- iii) Displacement factor

P.T.O.

- Q5) a)** With the help of neat circuit diagram and waveforms, explain the working of single phase bridge inverter for R load. Derive the expression for RMS output voltage. [6]
- b)** Explain Single pulse PWM & Sinusoidal PWM control technique for 1ϕ inverter. [4]

OR

- Q6) a)** With the help of neat circuit diagram and waveform explain the working of 3ϕ voltage source inverter R load with 120° conduction mode. [6]
- b)** With the Fourier expression, explain what are the harmonics presents in the output of single phase 50 Hz square wave inverter with R-L Load? Calculate RMS value 1^{st} , 3^{rd} , and 5^{th} harmonic if the dc supply is 48 Volts? [4]

