

Total No. of Questions : 6]

SEAT No. :

**P19**

[Total No. of Pages : 2

**Oct./TE/Insem. - 17**

**T.E. (Electronics)**

**NETWORK SYNTHESIS**

**(2012 Course) (Semester - I) (304205) (Elective - II)**

*Time : 1 Hour]*

*[Max. Marks : 30*

*Instructions to the candidates:*

- 1) Answer Q1 or Q2, Q3 or Q4 and Q5 or Q6.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of calculator is allowed.
- 5) Assume suitable data, if necessary.

**Q1) a)** Explain the physical significance of poles and zeros. **[5]**

b) Test the function is Hurwitz polynomial or not. **[5]**

$$F(s) = s^4 + s^3 + 2s^2 + 3s + 2$$

OR

**Q2) a)** Explain the following removal operation, **[6]**

i) Removal of pole at  $S = \infty$  from the functions

ii) Removal of pole at  $S = 0$  from the functions.

b) Test whether  $F(s) = \frac{s^2 + 1}{s^3 + 4s}$  is positive real function. **[4]**

**Q3) a)** State the properties of RC Driving point function of one port network. **[4]**

b) Synthesize the following function using Foster - I and Cauer - I form

$$Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)} \quad \text{[6]}$$

OR

**Q4) a)** State the properties of LC Driving point function of one port network. **[4]**

b) Synthesize the following function using partial fraction expansion method.

$$F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2} \quad \text{[6]}$$

**P.T.O.**

**Q5) a)** Write a short note on Zeros of transmission. [4]

b) Realize the following function, [6]

$$Z_{21} = \frac{s^3}{s^3 + 3s^2 + 4s + 2}$$

OR

**Q6) a)** Give the properties of the Transfer function. [4]

b) Realize the following function as symmetrical constant resistance lattice network terminated by  $1\Omega$ . [6]

$$\frac{V_o}{V_s} = \frac{1s^2 - 3s + 2}{2s^2 + 3s + 2}$$

