



K. K. Wagh Institute of Engineering Education & Research, Nashik
(An Autonomous Institute From A.Y. 2022-23)

SUMMER-2024	
Exam Seat No.:	
Academic Year:2023-2024	Semester:III
Class:SY	Program:B.Tech
Branch Code:ETC	Pattern:2022
Name of Course:Digital System Design Using HDL	Course Code:ETC222003
Max. Marks:60	Duration:2.30 Hrs.

Instructions: Candidates should read carefully the instructions printed on the Question Paper and on the cover page of the Answer Book, which is provided for their use.

1. This question paper contains 02 page(s).
2. Answer to each new question is to be started on a new page.
3. Assume suitable data wherever required, but justify it.
4. Draw the neat labelled diagrams, wherever necessary.
5. The last columns indicates the Course Outcome and level of Blooms Taxonomy of the Question/sub-question.

Question No. 1 Attempt following Question

- 1a) Design 1:16 demultiplexer using 1:8 demultiplexer (6) CO1

Question No. 2 Attempt following Question

- 2a) Design MOD 6 UP counter and explain with the help of waveforms (6) CO2

Question No. 3 Attempt following Question

- 3a) What is an ASM chart? Give its advantages and applications (8) CO3

OR

- 3b) Design a circuit which follows following sequence 0-3-6-4-1-2-7-0 (8) CO3

- 3c) Design sequence generator to generate the following string of sequence 110011.... (8) CO3

OR

- 3d) Compare mealy and Moore machines. What is the lock out condition? And explain how to avoid it. (8) CO3

Question No. 4 Attempt following Question

- 4a) List and explain data types in VHDL with examples (8) CO4

OR

- 4b) What is an entity and architecture? Write VHDL program for 8:1 multiplexer (8) CO4

- 4c) With example explain the syntax of while and case statement in VHDL (8) CO4

OR

- 4d) What are different digital logic families? Give classification of logic families and explain it (8) CO4

Question No. 5 Attempt following Question

- 5a) Write short notes on VHDL test bench (8) CO5

OR

- 5b) Write a VHDL program for SR flip flop (8) CO5

- 5c) Write VHDL code for the 2 bit comparator and also write a test bench for it (8) CO5

OR

- 5d) Write note on different modeling styles in VHDL along with an example (8) CO5

XXXXXXXXXXXXXXXXXXXXXXXXXXXX