



	InSem Examination-IISummer2024		
	Exam Seat No.:		
	Academic Year:2023-2024	Semester:IV	
	Name of Programme: S.Y.B.Tech Electrical	Pattern:2022	
	Name of Course: Electrical Network Analysis	Course Code:ELE222011	
	Max. Marks:30	Duration:1 hr	

	<p><b>Instructions:</b> Candidates should read carefully the instructions printed on the Question Paper and on the cover page of the Answer Book, which is provided for their use.</p> <ol style="list-style-type: none"><li>1. This question paper contains 2 page(s).</li><li>2. Answer to each new question is to be started on a new page.</li><li>3. Assume suitable data wherever required, but justify it.</li><li>4. Draw the neat labelled diagrams, wherever necessary.</li><li>5. The last columns indicates the Course Outcome and level of Blooms Taxonomy of the Question/sub-question.</li></ol>	
--	---	--


**Question No. 1 Attempt following Question**

- a) List all independent and dependent sources. Draw their symbols and explain the concept of source transformation (7) CO1

**OR**


- b) Explain the concept of 1) Supermesh 2) Supernode (7) CO1

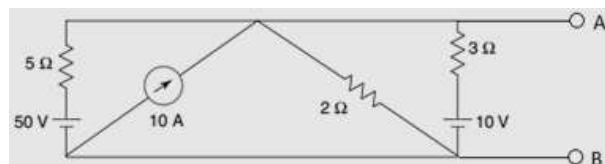- c) Reduce the network shown in figure into a single voltage source and a single resistor between terminals A and B (8) CO2



**OR**

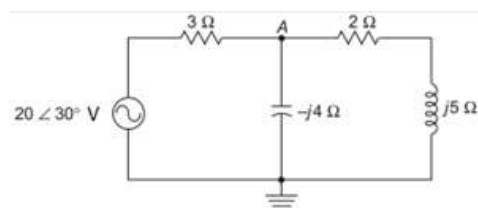
- d) For the circuit shown in Figure, determine the voltage at node A (8) CO2



**Question No. 2 Attempt following Question**

- a) Use Thevenin's theorem to find the current in 3 Ohm resistor


(7) CO2

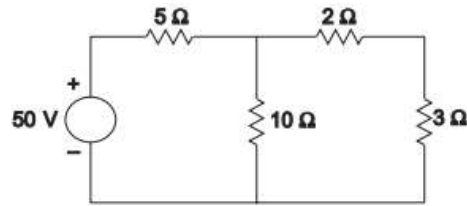

**OR**

- b) Find the current through the 2 Ohm resistor by Mesh analysis

(7) CO2

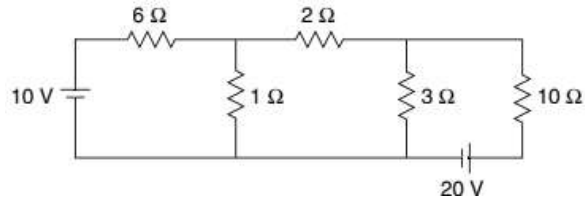

- c) State and explain Maximum Power Transfer Theorem

(8) CO1

**OR**

- d) State and explain Superposition Theorem

(8) CO1

XXXXXXXXXXXXXXXXXXXXXXXXXXXX