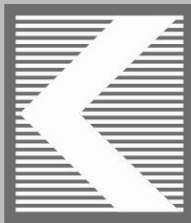




BASIC ELECTRICAL ENGINEERING

WITH LAB MANUAL

S. K. SAHDEV



KHANNA BOOK PUBLISHING CO. (P) LTD.

PUBLISHER OF ENGINEERING AND COMPUTER BOOKS

4C/4344, Ansari Road, Darya Ganj, New Delhi-110002

Phone: 011-23244447-48

Mobile: +91-99109 09320

E-mail: contact@khannabooks.com

Website: www.khannabooks.com

Dear Readers,

To prevent the piracy, this book is secured with HIGH SECURITY HOLOGRAM on the front title cover. In case you don't find the hologram on the front cover title, please write us to at contact@khannabooks.com or whatsapp us at +91-99109 09320 and avail special gift voucher for yourself.

Specimen of Hologram on front Cover title:



Moreover, there is a SPECIAL DISCOUNT COUPON for you with EVERY HOLOGRAM.

How to avail this SPECIAL DISCOUNT:

Step 1: Scratch the hologram

Step 2: Under the scratch area, your "coupon code" is available

Step 3: Logon to www.khannabooks.com

Step 4: Use your "coupon code" in the shopping cart and get your copy at a special discount

Step 5: Enjoy your reading!

ISBN: 978-93-91505-15-8

Book Code: UG005EN

Basic Electrical Engineering

by S. K. Sahdev

[English Edition]

First Edition: 2021

Published by:

Khanna Book Publishing Co. (P) Ltd.

Visit us at: www.khannabooks.com

Write us at: contact@khannabooks.com

CIN: U22110DL1998PTC095547

To view complete list of books,
Please scan the QR Code:



Printed in India.

Copyright © Reserved

No part of this publication may be reproduced, stored in a retrieval system or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording or otherwise without prior permission of the publisher.

This book is sold subject to the condition that it shall not, by way of trade, be lent, re-sold, hired out or otherwise disposed of without the publisher's consent, in any form of binding or cover other than that in which it is published.

Disclaimer: The website links provided by the author in this book are placed for informational, educational & reference purpose only. The Publisher do not endorse these website links or the views of the speaker/ content of the said weblinks. In case of any dispute, all legal matters to be settled under Delhi Jurisdiction only.



प्रो. अनिल डी. सहस्रबुद्धे
अध्यक्ष
Prof. Anil D. Sahasrabudhe
Chairman



सत्यमेव जयते

अखिल भारतीय तकनीकी शिक्षा परिषद्
(भारत सरकार का एक सांविधिक निकाय)
(शिक्षा मंत्रालय, भारत सरकार)
नेल्सन मंडेला मार्ग, वसंत कुंज, नई दिल्ली-110070
दूरभाष : 011-26131498
ई-मेल : chairman@aicte-india.org

ALL INDIA COUNCIL FOR TECHNICAL EDUCATION
(A STATUTORY BODY OF THE GOVT. OF INDIA)
(Ministry of Education, Govt. of India)
Nelson Mandela Marg, Vasant Kunj, New Delhi-110070
Phone : 011-26131498
E-mail : chairman@aicte-india.org

FOREWORD

Engineering has played a very significant role in the progress and expansion of mankind and society for centuries. Engineering ideas that originated in the Indian subcontinent have had a thoughtful impact on the world.


All India Council for Technical Education (AICTE) had always been at the forefront of assisting Technical students in every possible manner since its inception in 1987. The goal of AICTE has been to promote quality Technical Education and thereby take the industry to a greater heights and ultimately turn our dear motherland India into a Modern Developed Nation. It will not be inept to mention here that Engineers are the backbone of the modern society - better the engineers, better the industry, and better the industry, better the country.

NEP 2020 envisages education in regional languages to all, thereby ensuring that each and every student becomes capable and competent enough and is in a position to contribute towards the national growth and development.

One of the spheres where AICTE had been relentlessly working from last few years was to provide high-quality moderately priced books of International standard prepared in various regional languages to all it's Engineering students. These books are not only prepared keeping in mind it's easy language, real life examples, rich contents and but also the industry needs in this everyday changing world. These books are as per AICTE Model Curriculum of Engineering & Technology – 2018.

Eminent Professors from all over India with great knowledge and experience have written these books for the benefit of academic fraternity. AICTE is confident that these books with their rich contents will help technical students master the subjects with greater ease and quality.

AICTE appreciates the hard work of the original authors, coordinators and the translators for their endeavour in making these Engineering subjects more lucid.

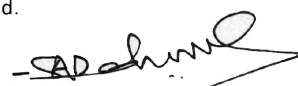
(Anil D. Sahasrabudhe)

Acknowledgement

The author grateful to AICTE for their meticulous planning and execution to publish the technical book for Engineering and Technology students.

I sincerely acknowledge the valuable contributions of the reviewer of the book Prof. Majal Jamel, for making it students' friendly and giving a better shape in an artistic manner.

This book is an outcome of various suggestions of AICTE members, experts and authors who shared their opinion and thoughts to further develop the engineering education in our country.

It is also with great honour that I state that this book is aligned to the AICTE Model Curriculum and in line with the guidelines of National Education Policy (NEP) -2020. Towards promoting education in regional languages, this book is being translated in scheduled Indian regional languages.

Acknowledgements are due to the contributors and different workers in this field whose published books, review articles, papers, photographs, footnotes, references and other valuable information enriched us at the time of writing the book.

Finally, I like to express my sincere thanks to the publishing house, M/s. Khanna Book Publishing Company Private Limited, New Delhi, whose entire team was always ready to cooperate on all the aspects of publishing to make it a wonderful experience.

S. K. Sahdev

Preface

If we look around, we will observe that our day starts with the application of electricity and finishes with the application of electricity. We can't imagine our life without electricity.

In the present scenario, electrical energy has become an integral part of all the engineering applications. Therefore, a course of “**Basic Electrical Engineering**” has been introduced in all the engineering disciplines by all the universities in India and abroad. Usually, this course is taught in first year either in 1st or in 2nd semester.

It is observed that most of the students, particularly the students belonging to the disciplines of civil, mechanical, computers, textile etc. face difficulties in understanding the contents of this course. To keep this in mind, every effort has been made to make the text *students' friendly* by using simple and lucid language.

*The book is prepared as per the **latest model curriculum of All India Council for Technical Education (AICTE)** for the students per-suing UG engineering.*

Each chapter of the book contains much needed text supported by neat and self-spoken diagrams to make the subject matter self-explanatory to a great extent. Many solved and unsolved examples have been added in various chapters to enable the students to attempt different types of questions asked in the examination without any difficulty. Practice Exercises have been added in all the chapters at regular intervals to keep the students regular in their studies. At the end of each chapter Summary, Objective Type Questions, Short-Answer Questions, Test Questions and Unsolved Examples have been added to make the book complete and comprehensive unit in all respects.

The author lay no claim to original research in preparing the text. Materials available in the research work of eminent authors has been used liberally. But the author claims that he has organized the subject matter in very systematic manner. He also claims that the language of the text is lucid, direct and easy to understand.

Although, every care has been taken to eliminate errors, but it is very difficult to claim perfection. I shall be very grateful to the readers (students and teachers) and users of this book if they point out any mistake that might have crept in. Suggestions for the improvement of the book shall be highly appreciated.

S. K. Sahdev

Outcome Based Education

For the implementation of an outcome-based education the first requirement is to develop an outcome-based curriculum and incorporate an outcome-based assessment in the education system. By going through outcome-based assessments evaluators will be able to evaluate whether the students have achieved the outlined standard, specific and measurable outcomes. With the proper incorporation of outcome-based education there will be a definite commitment to achieve a minimum standard for all learners without giving up at any level. At the end of the programme running with the aid of outcome-based education, a student will be able to arrive at the following outcomes:

- PO-1: Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- PO-2: Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- PO-3: Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- PO-4: Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
- PO-5: Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modelling to complex engineering activities with an understanding of the limitations.
- PO-6: The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- PO-7: Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- PO-8: Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- PO-9: Individual and teamwork:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.

- PO-10: Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
- PO-11: Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
- PO-12: Life-long learning:** Recognize the need for and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Course Outcomes

After completion of the course the students will be able to:

CO-1 : To understand and analyse basic electric and magnetic circuits

CO-2 : To study the working principles of electrical machines and power converters.

CO-3 : To introduce the components of low voltage electrical installations.

Course Outcomes	Expected Mapping with Programme Outcomes (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1	3	2	1	1					1	1	1	1
CO-2	2	2	2	2	1	1			1	1	1	1
CO-3	3	1	1	2	2	1	1		1	1	1	1

List of Abbreviations

Abbreviations	Full form
CO	Course Outcome
PO	Programme Outcome
UO	Unit Outcome
C	coulomb
A	ampere
W	watt
EM	electromagnetic
DC	Direct Current
AC	Alternating Current
CRT	Cathode Ray Tube
T	tesla
G	gauss
V	volt
LCR	Inductor-Capacitor-Resistor
BW	Band Width
CRO	Cathode Ray Oscilloscope
Q-factor	Quality factor
GHz	Gigahertz
Oe	Oersted
Wb	weber
Hz	hertz
mH	milli henry
kHz	kilohertz
nC	nano coulomb
nA	nano ampere
Ge	Germanium
<i>emf</i>	electromotive force
<i>mmf</i>	magnetomotive force
μA	micro ampere
μC	micro coulomb
μF	microfarad

List of Symbols

Symbols	Description
e	Electronic charge
ϵ_0	Permittivity of free space
ϵ_r, k	Relative permittivity
ρ	Volume charge density
σ	Surface charge density
λ	Linear charge density
ϕ	Electric flux
E	Electric field intensity
D	Electric displacement
C	Capacitance of a capacitor
χ	Electromagnetic susceptibility
μ_0	Permeability of free space
J	Current density
B	Magnetic induction
H	Magnetic intensity
L	Self-inductance
M	Mutual inductance
S	Reluctance
K	Co-efficient of coupling
I_d	Displacement current
J_d	Displacement current density
U	Electromagnetic energy density
P	Poynting vector
ψ	Wave function
Z	Impedance
f_{res}	Resonant frequency

List of Figures

UNIT - 1		
Fig. 1.1	Symbol of fixed register	3
Fig. 1.2	Carbon-composition resistor	4
Fig. 1.3	Wire-wound resistor	4
Fig. 1.4	Variable carbon-composition resistor	4
Fig. 1.5	Variable wire wound resistor	4
Fig. 1.6	Schematic symbol of variable resistor	4
Fig. 1.7	Symbol of fixed and variable inductors	5
Fig. 1.8	Inductor with magnetic core	5
Fig. 1.9	Inductor with air core	6
Fig. 1.10	Variable inductor with its schematic diagram	6
Fig. 1.11	Symbol of fixed and variable capacitor	7
Fig. 1.12	Paper capacitors	7
Fig. 1.13	Fixed mica capacitor	8
Fig. 1.14	Ceramic capacitor	8
Fig. 1.15	Electrolytic capacitors	8
Fig. 1.16	Variable capacitors	8
Fig. 1.17	Transfer of energy from source to load	9
Fig. 1.18	DC source	9
Fig. 1.19	DC source on load	9
Fig. 1.20	Ideal constant voltage source	10
Fig. 1.21	Real voltage source	11
Fig. 1.22	Ideal current source, its characteristic and symbol	11
Fig. 1.23	Real current source and its characteristic	12
Fig. 1.24	Voltage source, current source	13
Fig. 1.25	Conversion of voltage source to current source and vice-versa	14
Fig. 1.26	Voltage source	14
Fig. 1.27	Equivalent current source	14
Fig. 1.28	DC current source	14
Fig. 1.29	Equivalent voltage source	14
Fig. 1.30	A resistor is connected across a battery	15
Fig. 1.31	Simple DC circuit	16
Fig. 1.32	Three resistor connected in series	16

Fig. 1.33	Three resistor connected in parallel	17
Fig. 1.34	Series parallel circuit	17
Fig. 1.35	Two resistor connected in parallel	17
Fig. 1.36	Circuit diagram	18
Fig. 1.37	Given circuit	18
Fig. 1.38	Simplified view of the given circuit	18
Fig. 1.39	An electric network	19
Fig. 1.40	Five branches meeting at a junction	19
Fig. 1.41	Algebraic signs for emf and voltage drop	20
Fig. 1.42	KVL	20
Fig. 1.43	Given circuit	21
Fig. 1.44	Circuit carrying current	21
Fig. 1.45	Given circuit	22
Fig. 1.46	Circuit carrying current	22
Fig. 1.47	Given circuit	23
Fig. 1.48	Circuit carrying current	23
Fig. 1.49	Given circuit	24
Fig. 1.50	Circuit for solution	24
Fig. 1.51	Given circuit	24
Fig. 1.52	Given circuit	25
Fig. 1.53	Circuit with assumed current	25
Fig. 1.54	Circuit for bridge	26
Fig. 1.55	Given circuit	27
Fig. 1.56	Circuit for solution	27
Fig. 1.57	Given circuit	28
Fig. 1.58	Given circuit	28
Fig. 1.59	Given network	29
Fig. 1.60	Given circuit	29
Fig. 1.61	Given network	29
Fig. 1.62	Given network	29
Fig. 1.63	Given circuit	29
Fig. 1.64	Considering source E1 only	30
Fig. 1.65	Considering source E2 only	30
Fig. 1.66	Given circuit	30
Fig. 1.67	Circuit for solution	30
Fig. 1.68	Considering one source only	30
Fig. 1.69	Considering second source only	31

Fig. 1.70	Considering third source only	31
Fig. 1.71	Given circuit	31
Fig. 1.72	Considering voltage source only	32
Fig. 1.73	Considering current source only	32
Fig. 1.74	Given circuit	32
Fig. 1.75	Figure for numerical problem	33
Fig. 1.76	Figure for numerical problem	33
Fig. 1.77	Given network	34
Fig. 1.78	Given network	34
Fig. 1.79	Given network	34
Fig. 1.80	Given network	35
Fig. 1.81	Circuit to determine E_{th}	35
Fig. 1.82	Circuit to determine R_{th}	35
Fig. 1.83	Thevenin circuit	36
Fig. 1.84	Given network	36
Fig. 1.85	Circuit to determine E_{th}	36
Fig. 1.86	Circuit to determine R_{th}	36
Fig. 1.87	Thevenin circuit	36
Fig. 1.88	Given circuit	36
Fig. 1.89	Circuit to determine E_{th}	37
Fig. 1.90	Circuit to determine R_{th}	37
Fig. 1.91	Thevenin circuit	37
Fig. 1.92	Given circuit	37
Fig. 1.93	Circuit to determine E_{th}	38
Fig. 1.94	Circuit to determine R_{th}	38
Fig. 1.95	Thevenin circuit	38
Fig. 1.96	Given circuit as per data	39
Fig. 1.97	Circuit to determine E_{th}	39
Fig. 1.98	Circuit to determine R_{th}	39
Fig. 1.99	Thevenin circuit	39
Fig. 1.100	Given circuit	40
Fig. 1.101	Circuit to determine E_{th}	40
Fig. 1.102	Circuit to determine R_{th} , simplified circuit	40
Fig. 1.103	Thevenin circuit	41
Fig. 1.104	Given circuit	41
Fig. 1.105	Circuit to determine R_{th}	41
Fig. 1.106	Circuit to determine E_{th}	41

Fig. 1.107	Thevenin circuit	41
Fig. 1.108	Given circuit	42
Fig. 1.109	Given circuit	42
Fig. 1.110	Given circuit	42
Fig. 1.111	Given circuit	42
Fig. 1.112	Given circuit	42
Fig. 1.113	Given circuit	42
Fig. 1.114	Given circuit	43
Fig. 1.115	Circuit to determine R_n	44
Fig. 1.116	Circuit to determine I_n	44
Fig. 1.117	Norton Circuit	44
Fig. 1.118	Given circuit	44
Fig. 1.119	Circuit to determine I_n	44
Fig. 1.120	Circuit to determine R_n	45
Fig. 1.121	Norton Circuit	45
Fig. 1.122	Given circuit	45
Fig. 1.123	Circuit to determine I_n	45
Fig. 1.124	Considering only current source	46
Fig. 1.125	Considering only voltage source	46
Fig. 1.126	Circuit to determine R_n	46
Fig. 1.127	Norton Circuit	46
Fig. 1.128	Closing of RL circuit	47
Fig. 1.129	Opening and short circuiting of RL circuit	49
Fig. 1.130	Graph between current and time	49
Fig. 1.131	Given circuit	51
Fig. 1.132	When S_1 is closed and S_2 is opened	51
Fig. 1.133	When S_2 is closed and S_1 is opened	51
Fig. 1.134	Graph between current and time	52
Fig. 1.135	RL Circuit with switch	53
Fig. 1.136	Closing of RL circuit	53
Fig. 1.137	Graph between current and voltage when circuit is closed	54
Fig. 1.138	Graph between current and t when circuit is opened	54
Fig. 1.139	Charged capacitor with open switch without supply	56
Fig. 1.140	Graph between v and t during discharging of capacitor	56
Fig. 1.141	Graph between i and t during discharging of capacitor	57
Fig. 1.142	Figure for numerical problem	64
Fig. 1.143	Figure for numerical problem	65

Fig. 1.144	Figure for numerical problem	65
Fig. 1.145	Figure for numerical problem	65
Fig. 1.146	Figure for numerical problem	65
Fig. 1.147	Figure for numerical problem	65
Fig. 1.148	Figure for numerical problem	65
Fig. 1.149	Figure for numerical problem	67
Fig. 1.150	Figure for numerical problem	67
Fig. 1.151	Figure for numerical problem	68
Fig. 1.152	Figure for numerical problem	68
UNIT -2		
Fig. 2.1	Alternating voltage and current	80
Fig. 2.2	Wave shape of ac quantities	81
Fig. 2.3	Coil rotating in the stationary magnetic field	82
Fig. 2.4	field rotating in the stationary coil	82
Fig. 2.5	EMF induced in a coil at various instants	83
Fig. 2.6	EMF developed in a rotating coil	84
Fig. 2.7	Wave shape of induced EMF	84
Fig. 2.8	Considering half cycle of an alternating quantity for a symmetrical wave	86
Fig. 2.9	Sinusoidal alternating current	86
Fig. 2.10	Wave shape of an alternating current	87
Fig. 2.11	Square wave of a sinusoidal alternating current	88
Fig. 2.12	Full wave rectified wave	90
Fig. 2.13	Wave diagram	91
Fig. 2.14	Wave shape of periodic current	91
Fig. 2.15	Plotting of sign wave	93
Fig. 2.16	Phasor and wave diagram (single quantity)	93
Fig. 2.17	Phasor and wave diagram (two quantity)	93
Fig. 2.18	Circuit diagram	94
Fig. 2.19	Phasor diagram	95
Fig. 2.20	Phasor representation of three voltages	95
Fig. 2.21	Circuit containing only resistance	96
Fig. 2.22	Phasor and wave diagram	96
Fig. 2.23	Circuit containing pure inductance	97
Fig. 2.24	Phasor and wave diagram	99
Fig. 2.25	Circuit containing pure capacitance	99
Fig. 2.26	Phasor and wave diagram	100
Fig. 2.27	R-L series circuit	102

Fig. 2.28	Phasor diagram	102
Fig. 2.29	Phasor and wave diagram	103
Fig. 2.30	Voltage triangle for an R-L series circuit	104
Fig. 2.31	Impedance triangle	104
Fig. 2.32	Active and reactive component of current	105
Fig. 2.33	Power angle	105
Fig. 2.34	Circuit diagram	107
Fig. 2.35	Phasor diagram	107
Fig. 2.36	Phasor diagram	108
Fig. 2.37	Circuit as per given data	109
Fig. 2.38	R-C series circuit	110
Fig. 2.39	Phasor diagram	110
Fig. 2.40	Phasor and wave diagram	111
Fig. 2.41	Voltage triangle	112
Fig. 2.42	Impedance triangle	112
Fig. 2.43	Circuit diagram	112
Fig. 2.44	Resistance in series	113
Fig. 2.45	Pure inductance in series	113
Fig. 2.46	Pure capacitance in series	114
Fig. 2.47	Circuit diagram	114
Fig. 2.48	Circuit diagram	115
Fig. 2.49	Phasor diagram	115
Fig. 2.50	Impedance triangle $X_L > X_C$	116
Fig. 2.51	Impedance triangle $X_L < X_C$	116
Fig. 2.52	Resonant circuit $X_L = X_C$	117
Fig. 2.53	Graph for X_L and X_C	117
Fig. 2.54	Resonance curve	118
Fig. 2.55	Resonance curve showing band width	119
Fig. 2.56	Circuit as per given data	120
Fig. 2.57	Given circuit	120
Fig. 2.58	Circuit as per data	121
Fig. 2.59	Circuit diagram	121
Fig. 2.60	Circuit diagram	122
Fig. 2.61	Phasor diagram	122
Fig. 2.62	Circuit with given data	123
Fig. 2.63	Parallel AC circuit	125
Fig. 2.64	Phasor diagram	125

Fig. 2.65	Circuit diagram	126
Fig. 2.66	Phasor diagram	126
Fig. 2.67	Circuit diagram	127
Fig. 2.68	Phasor diagram	127
Fig. 2.69	Circuit diagram	128
Fig. 2.70	Parallel resonance circuit	129
Fig. 2.71	Phasor diagram	129
Fig. 2.72	Curve between f and i	130
Fig. 2.73	Generation of 3-phase emfs	134
Fig. 2.74	Three coils representing three phases loaded separately	135
Fig. 2.75	Star connection	136
Fig. 2.76	Relationship between line and phase voltages in star connection	136
Fig. 2.77	Delta connection	137
Fig. 2.78	Relationship between line and phase currents in delta connection	138
Fig. 2.79	Three phase load, connected in star and delta	139
Fig. 2.80	Star connection	140
Fig. 2.81	Delta connection	140
Fig. 2.82	Star connection	140
Fig. 2.83	Star connected balanced load	141
Fig. 2.84	Delta connected load	142
UNIT -3		
Fig. 3.1	Magnet bar with its field	164
Fig. 3.2	B-H curve	167
Fig. 3.3	B-H curve of various magnetic materials	167
Fig. 3.4	B-H curve for non- magnetic materials	167
Fig. 3.5	Transformer	168
Fig. 3.6	Transformer core windings	168
Fig. 3.7	Coupling of primary and secondary	168
Fig. 3.8	L-shaped lamination	170
Fig. 3.9	Staggering of lamination	170
Fig. 3.10	Transformer core with winding	170
Fig. 3.11	E & I lamination	170
Fig. 3.12	Winding placed on core	171
Fig. 3.13	Ideal transformer	172
Fig. 3.14	Sinusoidal flux	172
Fig. 3.15	Resistance of primary and secondary winding	176
Fig. 3.16	Transfer of resistance	177

Fig. 3.17	Inductive reactance of primary and secondary	177
Fig. 3.18	Transfer of reactance	178
Fig. 3.19	Complete circuit diagram of an actual transformer	180
Fig. 3.20	Equivalent circuit of transformer when all the quantities are referred to secondary side	181
Fig. 3.21	Phasor diagram	181
Fig. 3.22	Ordinary two winding and auto transformer	191
Fig. 3.23	Three phase transformer (core-type)	195
Fig. 3.24	Shell type 3-phase transformer	195
Fig. 3.25	Flux distribution in the core of a 3-phase shell type transformer	195
Fig. 3.26	Winding connected in star-star	196
Fig. 3.27	Y-Y connection	196
Fig. 3.28	Winding connected in delta-delta	197
Fig. 3.29	D-D connection	197
Fig. 3.30	Winding connected in delta-star	198
Fig. 3.31	D-Y connection	198
Fig. 3.32	Winding connected in star-delta	198
Fig. 3.33	Y-D connection	198
Fig. 3.34	Distribution transformer	201
UNIT – 4		
Fig. 4.1	Stator	219
Fig. 4.2	Stator stamping	219
Fig. 4.3	Squirrel cage rotor	220
Fig. 4.4	Phasor wound rotor	220
Fig. 4.5	Wave diagram of magnetic flux produced in the stator core	221
Fig. 4.6	Resultant axis of magnetic field at instant t_1	221
Fig. 4.7	Resultant axis of magnetic field at instant t_2	221
Fig. 4.8	Resultant axis of magnetic field at instant t_3	221
Fig. 4.9	Working principle of 3-phase induction motor	222
Fig. 4.10	Field developed in the motor	222
Fig. 4.11	Rotor leakage flux	227
Fig. 4.12	Rotor circuit $X_2 = SX_2S$	227
Fig. 4.13	Rotor circuit X_2 variable	228
Fig. 4.14	Rotor circuit X_2 is fixed to X_2S	228
Fig. 4.15	Rotor equivalent circuit and Phasor diagram	228
Fig. 4.16	Power flow diagram	229
Fig. 4.17	T-s curve	236
Fig. 4.18	Operating region of T-s curve	237
Fig. 4.19	DOL starter	239

Fig. 4.20	Star-delta starter	240
Fig. 4.21	Auto transformer starter	240
Fig. 4.22	Rotor rheostat starter	241
Fig. 4.23	Graph between speed and torque	242
Fig. 4.24	Speed torque curve keeping R_2/S constant	243
Fig. 4.25	Speed- torque characteristic change in supply voltage	244
Fig. 4.26	Speed control by changing number of poles	245
Fig. 4.27	Two-field revolving theory	247
Fig. 4.28	Torque developed by two field	247
Fig. 4.29	Split phase motor	248
Fig. 4.30	Torque-speed curve	249
Fig. 4.31	Capacitor start motor	249
Fig. 4.32	Torque speed characteristic of capacitor start motor	250
Fig. 4.33	Capacitor run motor	250
Fig. 4.34	Capacitor start capacitor run motor	251
Fig. 4.35	Shaded pole motor	251
Fig. 4.36	Flux distribution in the pole during half cycle	252
Fig. 4.37	Torque-speed characteristic of shaded pole motor	252
Fig. 4.38	Circuit diagram of ac series motor	252
Fig. 4.39	Voltage distribution	252
Fig. 4.40	Torque-speed characteristic	253
Fig. 4.41	Universal motor	254
Fig. 4.42	Rotor of Universal motor	254
Fig. 4.43	Circuit diagram	255
Fig. 4.44	Torque developed during positive half cycle	255
Fig. 4.45	Torque developed during negative half cycle	255
Fig. 4.46	Dis-assembled view of DC machine	255
Fig. 4.47	Pole with field winding	256
Fig. 4.48	Stator and armature	257
Fig. 4.49	Armature of DC machine	257
Fig. 4.50	Commutator	258
Fig. 4.51	Magnetic field developed in a dc machine	259
Fig. 4.52	Position of axis of main field and rotor field	259
Fig. 4.53	Torque development	259
Fig. 4.54	(a) Current supplied by source (b) EMF produced due to rotation (back emf)	260
Fig. 4.55	Circuit diagram	260
Fig. 4.56	Circuit of separately excited motor	261
Fig. 4.57	Circuit of shunt motor	261
Fig. 4.58	Circuit of series motor	262

Fig. 4.59	Circuit of compound motor	262
Fig. 4.60	Separately excited dc motor	263
Fig. 4.61	N- I_a characteristic	263
Fig. 4.62	T- I_a characteristic	263
Fig. 4.63	N-T characteristic	263
Fig. 4.64	Ward –leonard method of speed control of separately excited dc motor	264
Fig. 4.65	Generator action	265
Fig. 4.66	Motor action	265
Fig. 4.67	Generation of alternating emf	266
Fig. 4.68	Rotor having number of poles	266
Fig. 4.69	Constructional features of salient pole alternator	267
Fig. 4.70	Parts of an alternators	268
Fig. 4.71	Non-salient pole type alternator	269
Fig. 4.72	Non-salient pole type rotor	269
UNIT – 5		
Fig. 5.1	Linear voltage regulator	301
Fig. 5.2	Buck converter circuit diagram	302
Fig. 5.3	Pictorial view of buck converter The switch is typically a MOSFET, IGBT, or BJT	302
Fig. 5.4	On-state	302
Fig. 5.5	Off-state	302
Fig. 5.6	Evolution of the voltages and currents with time in an ideal buck converter operating in continuous mode	304
Fig. 5.7	Evolution of the voltages and currents with time in an ideal buck converter operating in discontinuous mode	305
Fig. 5.8	Boost converter circuit diagram	307
Fig. 5.9	Pictorial view of boost converter The switch is typically a MOSFET, IGBT, or BJT	307
Fig. 5.10	Boost converter schematic	307
Fig. 5.11	On-state (boost converter) For ideal operation, it is assumed that	308
Fig. 5.12	Off-state (boost converter)	308
Fig. 5.13	Waveforms of voltage and current in a boost converter operating in continuous mode	309
Fig. 5.14	Waveforms of voltage and current in a boost converter operating in discontinuous mode	310
Fig. 5.15	The basic schematic of an inverting buck-boost converter	312
Fig. 5.16	Pictorial view of a buck-boost converter	312
Fig. 5.17	Schematic of a buck-boost converter	312
Fig. 5.18	The two-operating state of a buck-boost converter	313
Fig. 5.19	The basics of the 4-switch topology	313

Fig. 5.20	Transistor working in active (amplifier) mode	316
Fig. 5.21	Transistor working in switch mode	316
Fig. 5.22	Topology of a single phase VSI	317
Fig. 5.23	Topology of a three phase VSI	318
Fig. 5.24	Amplitude modulated wave	321
Fig. 5.25	Frequency modulated wave	322
UNIT - 6		
Fig. 6.1	Circuit with fuse	337
Fig. 6.2	Time-current characteristic of various fuses	337
Fig. 6.3	Switch fuse unit (SFU)	338
Fig. 6.4	Outer view of MCB	339
Fig. 6.5	Internal structure of MCB	339
Fig. 6.6	Operating characteristic of an MCB	340
Fig. 6.7	4-pole ELCB	341
Fig. 6.8	Internal wire diagram of a 2-pole ELCB	341
Fig. 6.9	Circuit for 2-pole ELCB	341
Fig. 6.10	Circuit for 4-pole ELCB	341
Fig. 6.11	100 AMP MCCB Moulded Case Circuit Breakers 100 AMP MCCB 4 pole Electrical Circuit Breakers	342
Fig. 6.12	Porcelain cleats	344
Fig. 6.13	Casing – capping	344
Fig. 6.14	CTS Wiring	345
Fig. 6.15	Conduit wiring	347
Fig. 6.16	Cross-section of a four core LT cable	349
Fig. 6.17	Earthing protects the operator	350
Fig. 6.18	Pipe earthing	352
Fig. 6.19	Plate earthing	352
Fig. 6.20	Lead-acid battery	354
Fig. 6.21	Battery plates and separator	354
Fig. 6.22	Checking of electrolyte	357

Guidelines for Teachers

To implement Outcome Based Education (OBE) knowledge level and skill set of the students should be enhanced. Teachers should take a major responsibility for the proper implementation of OBE. Some of the responsibilities (not limited to) for the teachers in OBE system may be as follows:

- Within reasonable constraint, they should manipulate time to the best advantage of all students.
- They should assess the students only upon certain defined criterion without considering any other potential ineligibility to discriminate them.
- They should try to grow the learning abilities of the students to a certain level before they leave the institute.
- They should try to ensure that all the students are equipped with the quality knowledge as well as competence after they finish their education.
- They should always encourage the students to develop their ultimate performance capabilities.
- They should facilitate and encourage group work and team work to consolidate newer approach.
- They should follow Blooms taxonomy in every part of the assessment.

Bloom's Taxonomy

Level	Teacher should Check	Student should be able to	Possible Mode of Assessment
Creating	Students ability to create	Design or Create	Mini project
Evaluating	Students ability to Justify	Argue or Defend	Assignment
Analysing	Students ability to distinguish	Differentiate or Distinguish	Project/Lab Methodology
Applying	Students ability to use information	Operate or Demonstrate	Technical Presentation/ Demonstration
Understanding	Students ability to explain the ideas	Explain or Classify	Presentation/Seminar
Remembering	Students ability to recall (or remember)	Define or Recall	Quiz

Guidelines for Students

Students should take equal responsibility for implementing the OBE. Some of the responsibilities (not limited to) for the students in OBE system are as follows:

- Students should be well aware of each UO before the start of a unit in each and every course.
- Students should be well aware of each CO before the start of the course.
- Students should be well aware of each PO before the start of the programme.
- Students should think critically and reasonably with proper reflection and action.
- Learning of the students should be connected and integrated with practical and real life consequences.
- Students should be well aware of their competency at every level of OBE.

CONTENTS

<i>Foreword</i>	<i>v</i>
<i>Acknowledgement</i>	<i>vii</i>
<i>Preface</i>	<i>ix</i>
<i>Outcome Based Education</i>	<i>xi</i>
<i>Course Outcomes</i>	<i>xi</i>
<i>Abbreviations and Symbols</i>	<i>xii</i>
<i>List of Figures</i>	<i>xiv</i>
<i>Guidelines for Teachers</i>	<i>xxv</i>
<i>Guidelines for Students</i>	<i>xxv</i>
1. DC CIRCUITS.....	1 - 77
Rationale	1
Unit Outcomes	1
Unit Specific	1
Mapping the Unit Outcomes with the Course Outcomes	2
1.1 Circuit Elements	3
1.2 Resistors	3
1.3 Inductors	5
1.4 Capacitors	7
1.5 Voltage And Current Sources	9
1.6 Internal Resistance	9
1.7 Constant Voltage Source	10
1.7.1 Ideal Constant Voltage Source	10
1.7.2 Real Constant Voltage Source	10
1.8 Constant Current Source	11
1.8.1 Ideal Constant Current Source	11
1.8.2 Real Constant Current Source	12
1.9 Difference Between Voltage Source and Current Source	12
1.10 Source Transformation	13
1.11 Ohm's Law	15

1.12	D.C. Circuits	16
1.13	Series Circuits	16
1.14	Parallel Circuits	16
1.15	Series – Parallel Circuits	17
1.16	Division of Current in Parallel Circuits	17
1.17	Network Terminology	19
1.18	Kirchhoff's Laws	19
1.19	Solution of Network by Kirchhoff's Laws	21
	Practice Exercise	28
1.20	Superposition Theorem	29
	Practice Exercise	34
1.21	Thevenin's Theorem	34
	Practice Exercise	42
1.22	Norton's Theorem	43
1.23	Conversion of Thevenin's Equivalent Into	43
	Practice Exercise	46
1.24	Time Domain Analysis of R_L and R_C Circuits	47
1.25	Analysis of RL Circuits (Closing and Opening of R_L Circuit)	47
1.26	Rise of Current in an Inductive Circuit	47
1.27	Decay of Current in an Inductive Circuit	48
	Practice Exercise	52
1.28	Analysis of Recircuits (Closing of R_C Circuit)	53
1.29	Time Constant	54
1.30	Discharging of A Capacitor	55
	Practice Exercise	58
	Project	59
	Summary	60
	Short Answer Questions	62
	Numerical For Practice	64
	Multi-Choice Questions	66
	Test Questions	69
	Answers To Multi-Choice Questions	71
	Experiment	72
2.	AC CIRCUITS	78 - 161
	Rationale	78
	Unit Outcomes	78

Unit Specific	78
Mapping the Unit Outcomes with the Course Outcomes	78
Interesting Facts	79
Video Resources	79
2.1 Alternating Voltage and Current	80
2.2 Advantages of AC System Over DC System	81
2.3 Difference Between AC and DC	81
2.4 Sinusoidal Alternating Quantity	82
2.5 Generation of Alternating Voltage and Current	82
2.6 Equation of Alternating e.m.f. and Current	84
2.7 Important Terms	85
2.8 Important Relations	85
2.9 Values of Alternating Voltage and Current	85
2.10 Peak Value	86
2.11 Average Value	86
2.12 Average Value of Sinusoidal Current	86
2.13 Effective Or r.m.s. Value	87
2.14 r.m.s. Value of Sinusoidal Current	88
2.15 Form Factor and Peak Factor	89
Practice Exercise	91
2.16 Phasor Representation of Sinusoidal Quantity	92
2.17 Phase and Phase Difference	93
2.18 Addition and Subtraction of Alternating Quantities	94
2.19 A.C. Circuit Containing Only Resistance (R)	96
2.20 A.C. Circuit Containing Pure Inductance (L)	97
2.21 A.C. Circuit Containing Pure Capacitance (C)	99
Practice Exercise	101
2.22 A.C. Series Circuits	102
2.23 R-L Series Circuit	102
2.24 Impedance Triangle	104
2.25 True Power and Reactive Power	104
2.26 Power Factor and Its Importance	105
2.27 Q-Factor of A Coil	106
Practice Exercise	109
2.28 R-C Series Circuit	110
Practice Exercise	114

2.29	R-L-C Series Circuit	115
2.30	Series Resonance	117
2.31	Resonance Curve	118
2.32	Q-Factor of Series Resonant Circuit	119
	Practice Exercise	124
2.33	A.c. Parallel Circuits	125
2.34	Methods of Solving Parallel A.c. Circuits	125
2.35	Phasor (Or Vector) Method	125
	Practice Exercise	128
2.36	Parallel Resonance	129
2.37	Q-Factor of A Parallel Resonant Circuit	130
2.38	Comparison of Series and Parallel Resonant Circuits	131
2.39	Poly-Phase System	132
2.40	Advantages of 3-Phase System Over 1-Phase System	133
2.41	Generation of 3-Phase e.m.f..	133
2.42	Naming the Phases	134
2.43	Phase Sequence	135
2.44	Interconnection of Three-Phases	135
2.45	Star Or Wye (Y) Connection	135
2.46	Mesh Or Delta (D) Connection	136
2.47	Connections of 3-Phase Loads	139
2.48	Power in 3-Phase Circuits	139
	Practice Exercise	142
	Project	143
	Summary	143
	Short Answer Questions	147
	Numerical for Practice	149
	Multi-Choice Questions	152
	Test Questions	155
	Answers To Multi-Choice Questions	157
	Experiment	158
3.	TRANSFORMERS	162 - 216
	Rationale	162
	Unit Outcomes	162
	Unit Specific	162
	Mapping The Unit Outcomes with the Course Outcomes	163

Interesting Facts	163
3.1 Magnet	163
3.2 Types of Magnetic Materials	164
3.3 Electromagnetism	165
3.4 Magnetisation Or B-H Characteristics	167
3.5 Transformer	167
3.6 Working Principle of A Transformer	168
3.7 Transformer Construction	169
3.8 An Ideal Transformer	171
3.9 Transformer on D.C.	172
3.10 E.m.f. Equation	172
Practice Exercise	175
3.11 Practical (Actual) Transformer	176
3.12 Resistance of Transformer Windings	176
3.13 Reactance in Transformer Windings	177
Practice Exercise	180
3.14 Circuit Diagram of an Actual Transformer	180
3.15 Simplified Equivalent Circuit	181
3.16 Expression for No Load Secondary Voltage	181
3.17 Voltage Regulation	183
Practice Exercise	186
3.18 Losses in A Transformer	186
3.19 Efficiency of A Transformer	187
3.20 Condition for Maximum Efficiency	188
Practice Exercise	191
3.21 Auto-Transformer	191
3.22 Three-Phase Transformers	194
3.23 Merits of Three-Phase Transformers	194
3.24 Construction of Three-Phase Transformer	194
3.25 Connections of Three-Phase Transformer	196
3.26 Power Transformer And Its Auxiliaries	201
Project	202
Summary	203
Numerical For Practice	205
Multi-Choice Questions	206

Short Answer Questions	207
Test Questions	208
Answers To Multi-Choice Questions	209
Experiment	210
4. ELECTRICAL MACHINES.....	217- 298
Rationale	217
Unit Outcomes	217
Unit Specific	217
Mapping the Unit Outcomes with the Course Outcomes	218
4.1 Constructional Features of A 3-Phase Induction Motor	219
4.2 Production of Revolving Field	221
4.3 Principle of Operation	222
4.4 Reversal of Direction of Rotation of 3-Phase Induction Motors	223
4.5 Slip	223
4.6 Frequency of Rotor Currents	224
Practice Exercise	225
4.7 Speed of Rotor Field Or M.M.F.	226
4.8 Rotor E.m.f.	226
4.9 Rotor Resistance	227
4.10 Rotor Reactance	227
4.11 Rotor Impedance	227
4.12 Rotor Current and Power Factor	227
4.13 Simplified Equivalent Circuit of Rotor	228
4.14 Losses in An Induction Motor	229
4.15 Power Flow Diagram	229
4.16 Relation Between Rotor Copper Loss, Slip and Rotor Input	230
4.17 Rotor Efficiency	230
Practice Exercise	233
4.18 Torque Developed by an Induction Motor	234
4.19 Condition For Maximum Torque And Equation for Maximum Torque	235
4.20 Starting Torque	235
4.21 Torque-Slip Curve	236
4.22 Torque-Speed Curve and Operating Region	237
Practice Exercise	238
4.23 Necessity of A Starter	238
4.24 Starting Methods of Squirrel Cage Induction Motors	239

4.25	Starting Method of Slip Ring Induction Motors	241
4.26	Speed Control of Induction Motors	242
4.27	Speed Control by Changing The Slip	242
4.28	Speed Control by Changing The Supply Frequency	244
4.29	Speed Control by Changing The Poles	244
4.30	Speed Control by Cascade Method	245
4.31	Applications of Three-Phase Induction Motors	246
4.32	Nature of Field Produced in Single Phase Induction Motors	246
4.33	Torque Produced By 1-Phase Induction Motor	247
4.34	Types of 1-Phase Ac Motors	248
4.35	Split Phase Motors	248
4.36	Capacitor Motors	249
4.37	Shaded Pole Motor	251
4.38	A.C. Series Motor Or Commutator Motor	252
4.39	Universal Motor	253
4.40	D.C. Motor	256
4.41	Main Constructional Features	256
4.42	Armature Resistance	259
4.43	Working Principle of D.C. Motors	259
4.44	Back E.m.f.	260
4.45	Types of D.C. Motors	261
4.46	Characteristics of D.C. Motors	262
4.47	Characteristics of Separately Excited DC Motors	262
4.48	Speed Control of Separately Excited Motors	263
4.49	Speed Regulation	263
4.50	Synchronous Machine	263
4.51	Basic Principles	265
4.52	Production of Sinusoidal Alternating E.m.f.	265
4.53	Relation Between Frequency Speed and Number of Poles	266
4.54	Constructional Features of Synchronous Machines	267
4.55	Advantages of Rotating Field System Over Stationary Field System	269
4.56	Three-Phase Synchronous Machines	270
4.57	E.m.f. Equation	270
	Practice Exercise	273
	Project	273
	Summary	273

Short Answer Questions	277
Numerical for Practice	278
Multi-Choice Questions	280
Test Questions	282
Answers to Multi-Choice Questions	284
Experiment	285
5. POWER CONVERTERS.....	299-332
Rationale	299
Unit Outcomes	300
Unit Specific	300
Mapping The Unit Outcomes With The Course Outcomes	300
Interesting Facts	300
Video Resources	301
5.1 DC-DC Power Converters	301
5.2 Simple Linear Voltage Regulator	301
5.3 Buck Converters	302
5.4 Boost Converters	307
5.5 Buck-Boost Converters	311
5.6 Duty Cycle	314
5.7 Voltage Source Inverters	314
5.8 Conversion of DC Input to AC Output	315
5.9 General Structure of Voltage Source Inverters (VSI)	317
5.10 Modulation	319
5.11 Need of Modulation	319
5.12 Types Of Modulation	319
5.13 Amplitude Modulation	319
5.14 Modulation Factor and Its Significance	320
5.15 Analysis of Amplitude Modulated Wave	320
5.16 Limitations of Amplitude Modulation	322
5.17 Frequency Modulation	322
5.18 Phase Modulation	324
Project	325
Summary	325
Short Answer Questions	326
Multi-Choice Questions	327
Test Questions	328

Answers to Multi-Choice Questions	329
Experiment	330
6. POWER CONVERTERS	333-375
Rationale	333
Unit Outcomes	333
Unit Specific	333
Mapping The Unit Outcomes with the Course Outcomes	334
6.1 Switchgear	335
6.2 Low Voltage Switchgear Or LV Switchgear	336
6.3 Fuse	336
6.4 Switch Fuse Unit (SFU)	338
6.5 Miniature Circuit Breaker (MCB)	338
6.6 Earth Leakage Circuit Breaker (ELCB)	340
6.7 Moulded Case Circuit Breaker (MCCB)	342
6.8 Types of Wires and Cables	343
6.8.1 Types of Wiring	343
6.8.2 Power Rating of Basic House-Hold Equipment:	347
6.9 Classification of Cables	349
6.10 Earthing	349
6.10.1 Purpose of Earthing	349
6.10.2 Equipment Earthing	350
6.10.3 System Earthing	351
6.10.4 Methods of Earthing	352
6.10.5 Double Earthing	353
6.11 Battery	354
6.11.1 Lead-Acid Battery	354
6.11.2 Capacity of A Battery	355
6.11.3 Efficiency of A Battery	355
6.11.4 Charge Indications of A Lead-Acid Battery Or Cell	357
6.11.5 Charging Of Lead-Acid Battery	358
6.11.6 Care and Maintenance of Lead-Acid Batteries	358
6.11.7 Applications Of Lead-Acid Batteries	358
6.12 Nickel-Iron Alkaline Cell	359
6.13 Calculations For Energy Consumption	360
Practice Exercise	361

Summary	361
Short Answer Questions	363
Numerical For Practice	364
Multi-Choice Questions	364
Test Questions	366
Attainment & Gap Analysis	367
Answers to Multi-Choice Questions	367
Experiment	368

1

DC Circuits

RATIONALE

The path for flow of electric current is called electric circuit. The electric circuit is just an arrangement in which electrical energy sources and various elements such as resistor, inductors and capacitors are connected in series, parallel or series-parallel combinations.

For simplification or analysing these circuits, various laws and theorems have been developed. In this chapter, we shall discuss some of the important laws and theorems.

UNIT OUTCOMES

U1-O1: Unit-1 Learning Outcome-1

To know about the active and passive components of an electric circuit, various electrical quantities and their measuring units.

U1-O2: Unit-1 Learning Outcome-2

To know about constant voltage and constant current sources, various laws related to electric networks such as Ohm's Law, Kirchhoff's Laws.

U1-O3: Unit-1 Learning Outcome-3

To analyse various electric networks employing different network theorems such as Thevenin theorem, Norton's theorem, superposition theorem, Delta-star and Star-delta transformation etc.

UNIT SPECIFICS

- Study of main elements of an electric circuit, their measuring units and importance.
- Importance of constant voltage and constant current sources.
- Ohm's law, its limitations and applications.
- Calculations of series, parallel and series-parallel circuits.
- Importance and applications of series, parallel and series-parallel circuits.
- General behaviour of different electric elements employed in an electric network.
- Analyses and designing of electric/electronic circuits by employing:
 - Kirchhoff's law
 - Delta-star or star-delta transformation

- Superposition theorem
- Thevenin's theorem
- Norton's theorem
- Maximum power transfer theorem and its applications.

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES


Unit-1 Outcome	EXPECTED MAPPING WITH COURSE OUTCOMES (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)				
	CO-1	CO-2	CO-3	CO-4	CO-5
U1-O1	3	—	—	—	—
U1-O2	3	—	—	—	—
U1-O3	3	—	—	—	—

Interesting facts

- Most of the people believe that Benjamin Franklin invented electricity. On the contrary, he proved that lightning is a form of electricity. This led to invention of the lightning rod which conducts electricity to the ground in case of lightning strokes.
- The lightning you see during storms is also a form of electricity. It is a discharge of electricity in the atmosphere that can travel around 130,000 miles per hour.
- Electricity plays a major role to determine functioning of your heart. Muscle cells in the heart contract due to electricity. ECG machines used by medical professionals measure the electricity going through the heart. A healthy heart displays a pattern with regular spikes.
- A filament light bulb only uses 10% of its total energy to emit light. The other 90% emits heat(wastage). Whereas LED lamps use 90% of its energy to emit light.
- Even when some of the appliances (desktops, laptops etc.) are switched off, they continue to use electricity.

Video Resources

Videos Links for circuits

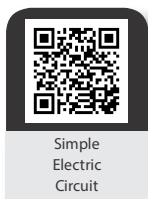

1.1. CIRCUIT ELEMENTS

In general, the circuit elements can be categorised as:

1. Active and passive elements.
 2. Unilateral and bilateral elements.
 3. Linear and non-linear elements.
 4. Lumped and distributed elements.
1. **Active and passive elements:** The elements which supply energy to the circuit or network are called *active elements*. All energy sources (batteries or generators) are the active elements. The elements which receive energy are called *passive elements* (such as resistors, inductors and capacitors).
 2. **Unilateral and Bilateral Elements:** The elements which conduct current in one direction only are called *unilateral elements* such as semiconductor diodes, vacuum tubes, selenium rectifiers etc.

Bilateral elements: The elements which conduct current in both the directions are called *bilateral elements* such as resistors etc. In other words, the elements which behave similarly when current flows through them in either direction are called *bilateral elements*.

3. **Linear and Non-linear Elements:**

Linear Elements: The elements which have V-I characteristics as straight line are called *linear elements* such as resistors.

Non-linear Elements: The elements which do not follow V-I characteristics as straight line are called *non-linear elements*, such as diodes, transistors etc.

4. **Lumped and Distributed Elements.**

Lumped Elements: The elements in which action takes place simultaneously are called *lumped elements*, such as resistors, inductors and capacitors. These elements are smaller in size.

Distributed Elements: The elements in which action for a given cause is not occurring simultaneously at the same instant but it is distributed are called *distributed elements*, such as transmission line which is having distributed resistance, inductance and capacitance along its length.

1.2. RESISTORS

Resistor is a component, used to limit the amount of current or divide the voltage in an electronic circuit. The ability of a resistor to oppose the current is called *resistance*. The unit of resistance R is *ohm* for which the symbol is Ω (the Greek capital letter omega). The schematic symbol of R is shown in fig.1.1.

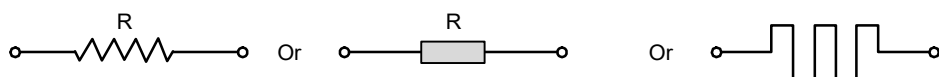


Fig.1.1: Symbol of fixed resistor

Each resistor has two main characteristics *i.e.* its resistance (R) in ohm and its power rating in watt (W). The resistors having wide range of resistance (from a fraction of an ohm to many mega ohm) are available. The power rating may be as low as 1/10 W to as high as several hundred watts. The value of

R is selected to obtain a desired current I or voltage drop IR in the circuit. At the same time wattage of the resistor is selected so that it can dissipate the heat losses without overheating itself.

- **Classification of resistors:** The resistors may be classified as fixed and variable resistors.

Fixed resistors: The resistors which have fixed value of resistance are called *fixed resistors*. These resistors may be carbon composition (shown in fig. 1.2) or wire-wound resistors (shown in fig.1.3)

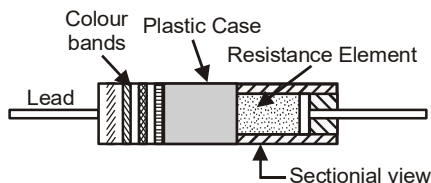


Fig. 1.2: Carbon-composition resistor,

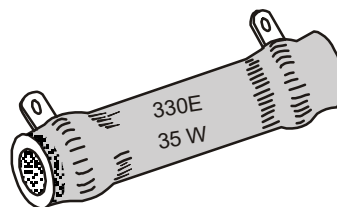


Fig. 1.3: Wire-wound resistor

Variable resistors: The resistors in which value of resistance can be varied as per the need are called *variable resistors*. The variable resistors may be carbon composition resistors (shown in fig. 1.4) or wire-wound resistors (shown in fig.1.5)

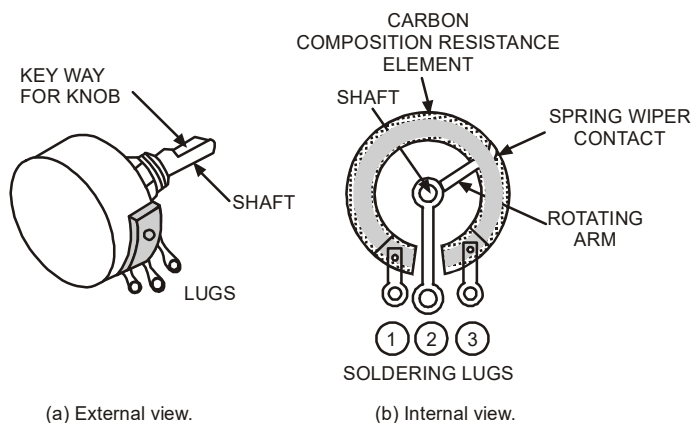


Fig. 1.4: Variable carbon-composition resistor

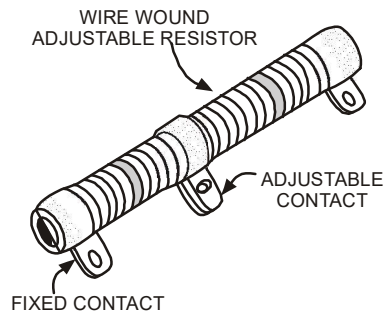


Fig.1.5: Variable wire wound resistor.

The schematic symbol of variable resistor is shown in fig.1.6.

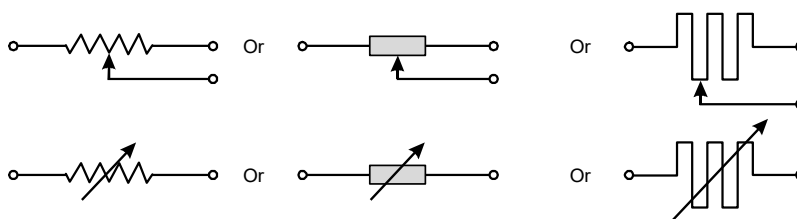


Fig.1.6: Schematic symbol of Variable resistor

The resistance of a wire depends upon:

- (i) its length *i.e.* $R \propto l$
- (ii) its area of cross-section *i.e.* $R \propto \frac{1}{a}$ and
- (iii) nature of material of which the wire is made of *i.e.* $R \propto \frac{l}{a}$ or $R = \rho \frac{l}{a}$

where ρ ('Rho' a Greek letter) is called resistivity of the material. Its unit is ohm-m.

1.3. INDUCTORS

A component that opposes the change of current in circuit is called an *inductor*. The ability of an inductor or coil due to which it opposes the change of current flowing through it is called its *inductance*. The *inductance* of an inductor may also be defined as the ability of an inductor (or coil) to produce voltage when the current varies through it. The unit of inductance is *henry*. The schematic symbol of a fixed and variable inductor is shown in fig.1.7.



Fig.1.7: Symbols of fixed and variable inductors

- **Classification Inductors :** Inductors can be classified broadly as fixed and variable inductors. Different types of inductors are available for different applications some of them are mentioned below.
- **Fixed inductors :** Some of the inductors (or coil) which have fixed inductance are mentioned below:
- **Filter Chokes :** A filter choke or inductor is shown in fig.1.8. It is used to block a.c. signal (voltage) and allows the d.c. signal (voltage) to pass through it.


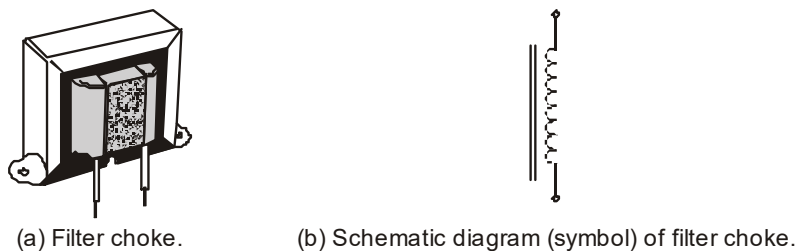


Fig.1.8: Inductor with magnetic core

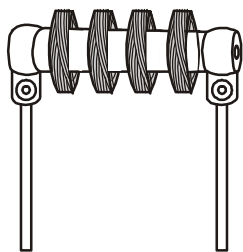- **Radio-Frequency Chokes :** A typical air-core radio-frequency inductor (choke) is shown with its schematic symbol in Fig.1.9.




(a) Radio frequency choke.




(b) Schematic diagram (symbol) of radio frequency choke.

Fig.1.9: Inductor with air core

Variable Inductors : A variable inductors (or coil) is shown in fig.1.10. The inductance of the coil is varied by varying the position of core. When current flows through a coil flux is produced by it which links with its outer turns. If current changes in the coil, the flux linking with its own turns changes and emf is induced in it called self induced emf which is proportional to rate of change of current or flux linkages, *i.e.*

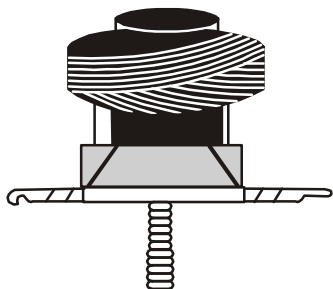

(a) Variable inductor.

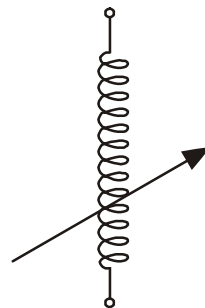

(b) Schematic diagram.

Fig.1.10: Variable inductor with its schematic diagram.

$$e \propto \frac{di}{dt} \quad \text{or} \quad e = L \frac{di}{dt} \quad \text{or} \quad L = \frac{e}{di/dt} \quad \dots\dots\dots(i)$$

Where L is the inductance of the coil.

$$\text{Now} \quad e = N \frac{d\phi}{dt} \quad \text{also} \quad e = L \frac{di}{dt} \quad \therefore \quad L \frac{di}{dt} = N \frac{d\phi}{dt}$$

$$\text{Or} \quad L = \frac{Nd\phi}{di} = \frac{N\phi}{I} \quad \dots\dots\dots(ii)$$

$$L = \frac{N}{I} \times \frac{NI}{l} \times a\mu_o\mu_r = \frac{N^2}{\text{Reluctance}} = \frac{N^2}{l} \times a\mu_o\mu_r \quad \dots\dots\dots(iii)$$

$$L = \frac{e}{di/dt} = \frac{N\phi}{I} = \frac{N^2}{l} \times a\mu_o\mu_r$$

The energy stored in the magnetic field of an inductor is given by the relation

$$W = \frac{1}{2} LI^2 \text{ or } w = \frac{1}{2} Li^2 \text{ joule}$$

Note : Inductance opposes the change of current, therefore, it opposes the alternating current (ac) but does not oppose the direct current (dc)

1.4. CAPACITORS

Two conducting plates separated by an insulating material (or dielectric) forms a *capacitor*. Capacitor has the ability to store electric charge. The capacity of a capacitor to store charge per unit potential difference is called its *capacitance*. The unit of capacitance is farad (*F*). However, the unit farad is too large, the capacitors are specified practically in microfarad (μF) or pico-farad (pF).

A capacitor is a component which offers low impedance to a.c. but very high impedance (resistance) to d.c. The schematic symbol of fixed and variable capacitor (*C*) is shown in Fig.1.11.

Classification of capacitors : The capacitors can also be classified broadly as fixed and variable capacitors. Different types of capacitors are available for different applications.

Fixed capacitors : Some of the capacitor which have fixed capacitance are mentioned below:

- *Paper Capacitors* : In these capacitors, impregnated paper is used as a dielectric.

Paper capacitors are available in a wide range of capacitance and voltage ratings. These capacitors are used in the circuits having frequency less than *radio-frequency*. Such capacitors are shown in fig.1.12.

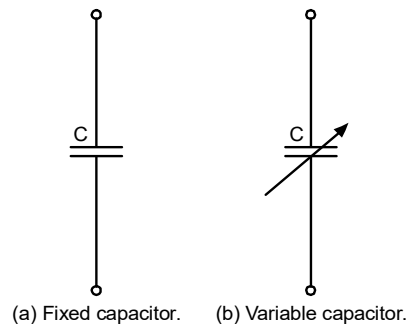


Fig. :1.11: Symbols of fixed and variable capacitors.



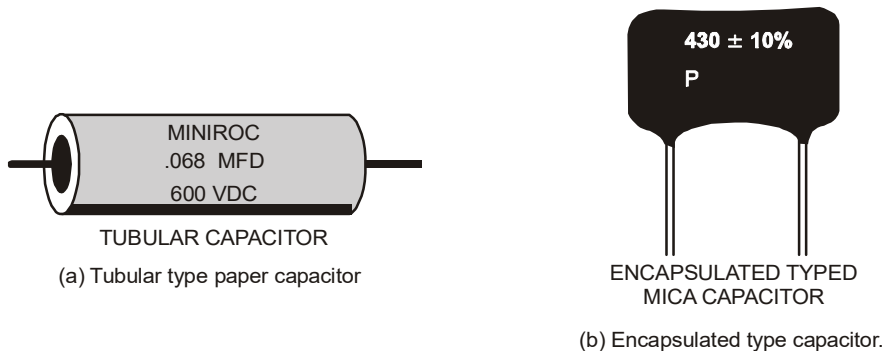


Fig.1.12: Paper Capacitors

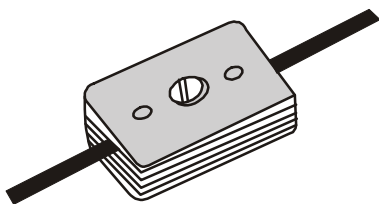- *Mica Capacitors* : In these capacitors, mica is used as a dielectric. These capacitors are used in the circuits operating at radio-frequency. One of such capacitor is shown in fig.1.13




(a) Fixed Mica Capacitor.

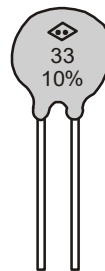


(b) Ceramic Capacitor.

Fig.1.13: Fixes Mica capacitor**Fig.1.14:** Ceramic Capacitors

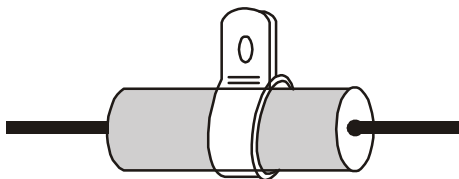- *Ceramic Capacitors* : Ceramic is used as dielectric material in these capacitors. A disc type ceramic capacitor is shown in fig.1.14.
- *Electrolytic Capacitors* : In these capacitors, an electrolyte is used as a dielectric. These are mostly used in the filter section of dc power supplies. Such capacitors are shown in fig.1.15.



Tubular Capacitor

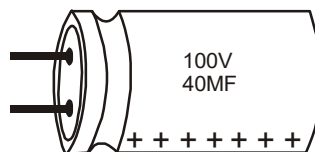


Can type capacitor.


Fig.1.15: Electrolytic Capacitors.

Variable Capacitors

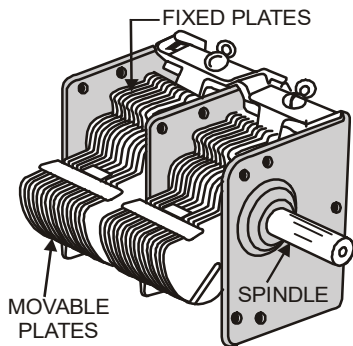The electronic circuits, in which frequency is to be changed as per requirement such as tuning circuits, variable capacitors are used. *Air-gang capacitor* is, shown in fig.1.16(a). and trimmer or padder with mica sheet capacitors are shown in fig.1.16(b). These are the most common variable capacitors.



(a) Air-gang capacitor

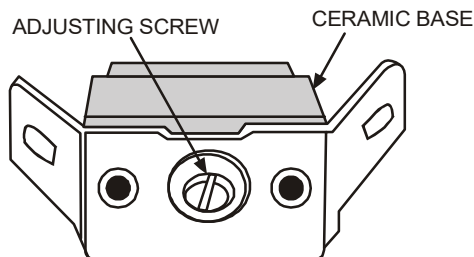

(b) Trimmer or padder capacitor

Fig.1.16: Variable capacitors

The capacitance of a capacitor is defined as charge per unit potential difference, *i.e.*

$$C = \frac{Q}{V} \text{ farad} \quad \text{or} \quad c = \frac{q}{v} \text{ farad}$$

The energy stored in a capacitor is given by the relation

$$W = \frac{1}{2} CV^2 \text{ joule} \quad \text{or} \quad w = \frac{1}{2} cv^2 \text{ joule}$$

1.5. VOLTAGE AND CURRENT SOURCES

To deliver electrical energy to electrical/electronic circuits, a source is required. A load is connected to the source as shown in Fig.1.17. The source may be either a d.c. (direct current) source or an a.c. (alternating current) source.

- **DC Source :** Any device that produces direct voltage continuously and has the ability to deliver current is called a **dc source**, such as batteries, dc generators and dc power supplies (regulated power supplies).
- **AC Source :** Any device that produces alternating voltage continuously and has the ability to deliver current is called an **ac source**, such as alternators and oscillators or signal generators.

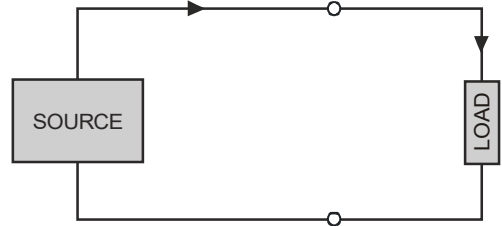


Fig. 1.17: Transfer of energy from source to load

1.6. INTERNAL RESISTANCE

All the sources (battery, dc generator or rectifier type supply) have some internal resistance R_i . The equivalent circuit of a dc source is represented by e.m.f. E in series with internal resistance R_i of the source as shown in fig.1.18.

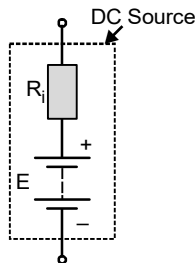


Fig.1.18 : DC Source

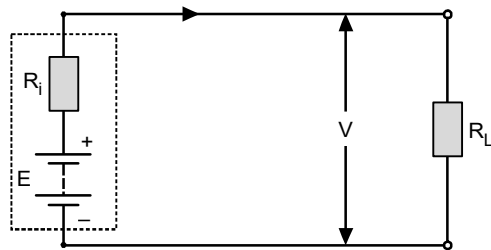


Fig.1.19: DC Source on load

When load (R_L) is connected across the source as shown in fig.1.19.

Load current,
$$I_L = \frac{E}{R_L + R_i}$$

Terminal voltage,
$$V = E - I_L R_i$$

or

$$V = I_L R_L = \frac{E}{R_L + R_i} \times R_L = \frac{E}{1 + R_i / R_L}$$

The voltage across the load terminals is reduced because of the voltage drop in the internal resistance of the source. A source having smaller internal resistance will provide more voltage across the load terminals.

1.7. CONSTANT VOLTAGE SOURCE

An electrical source is called a constant voltage source if it supplies power at almost constant voltage to a load irrespective to its value.

1.7.1. Ideal constant voltage source

An electrical source that can deliver current at constant voltage irrespective of the value of load resistance is called an *ideal constant voltage source*.


It is true only if a voltage source has zero internal resistance. We know,

Terminal voltage,
$$V = \frac{E}{1 + R_i / R_L}$$


Since
$$R_i = \text{zero,}$$

$$V = E$$

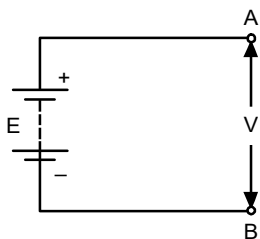An ideal constant voltage source and its characteristics are shown in fig.1.20(a) and 1.20(b) respectively..



(a) Ideal voltage source.

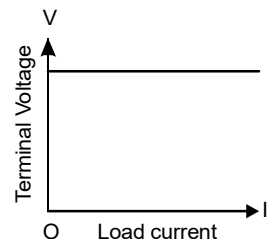

(b) Characteristics of Ideal Voltage Source.

Fig.1.20: Ideal constant voltage source

An ideal constant voltage source is just an idea, it cannot exist in nature. All the voltage sources have some internal resistance (or impedance), although its value may be very small.

1.7.2. Real Constant Voltage Source

All the voltage sources have some internal resistance which limits the current at short circuit. A real voltage source and its characteristics are shown in Fig.1.21(a) and 1.21(b) respectively.

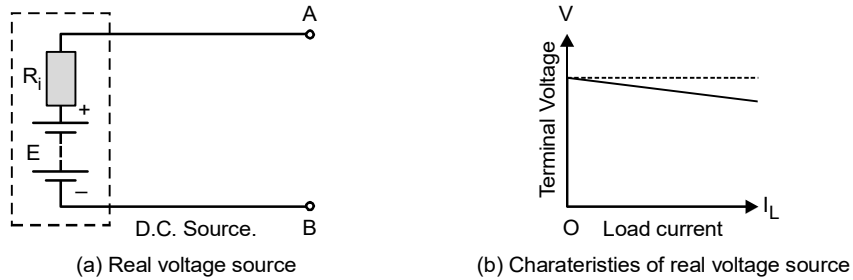


Fig. 1.21: Real Voltage Source

To maintain the terminal voltage of the source almost constant from no-load to full-load, the internal resistance of the source should be very small.

*A voltage source that has very low internal resistance (or impedance) as compared to load resistance (or impedance) is known as a real **constant voltage source**.*

1.8. CONSTANT CURRENT SOURCE

An electrical source is called a constant current source if it supplies power at almost constant current to a load irrespective to its value.

1.8.1. Ideal constant current source

An electrical source that can deliver constant current irrespective of the value of load resistance is called *ideal constant current source*.

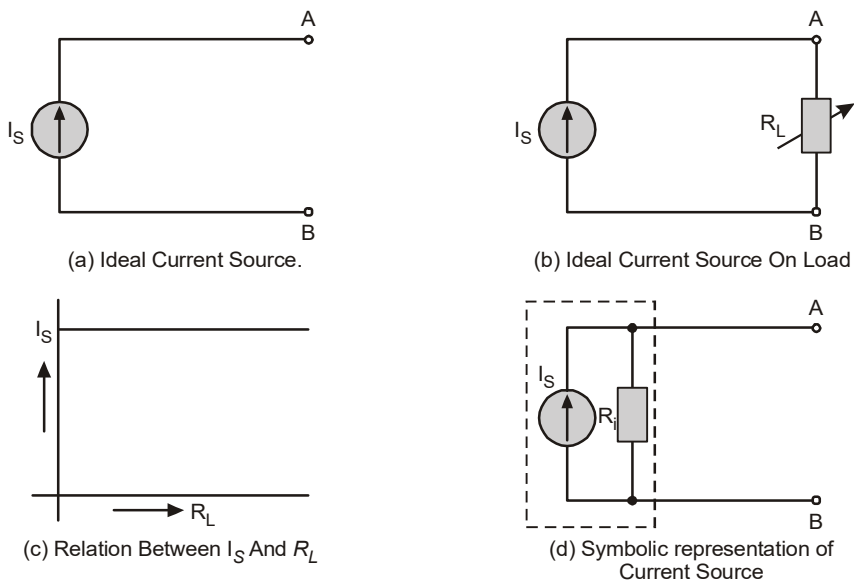


Fig.1.22: Ideal current source, its characteristics and symbol

It is true only if the source has infinite internal resistance.

Since,
$$I = \frac{E}{R_L + R_i} = \frac{E / R_i}{1 + R_L / R_i}$$

i.e. even if $R_L = 0$, $I = \frac{E}{R_i}$

This is only possible, if internal resistance (or impedance) is represented in parallel with the load as shown in fig.1.14(d)

This shows that in this type of source, there will be internal power loss even at no-load. Hence ideal current source is merely an idea and not the real one.

1.8.2. Real constant current source

An ideal constant current source is just idea. A real constant current source is basically a voltage source which delivers almost the same current at all values of load resistance. This is only possible if the source has very high internal resistance *i.e.* $R_i \gg R_L$.

*A source that has very high internal resistance (or impedance) as compared to the load resistance (or impedance) is considered as a **constant current source**.*

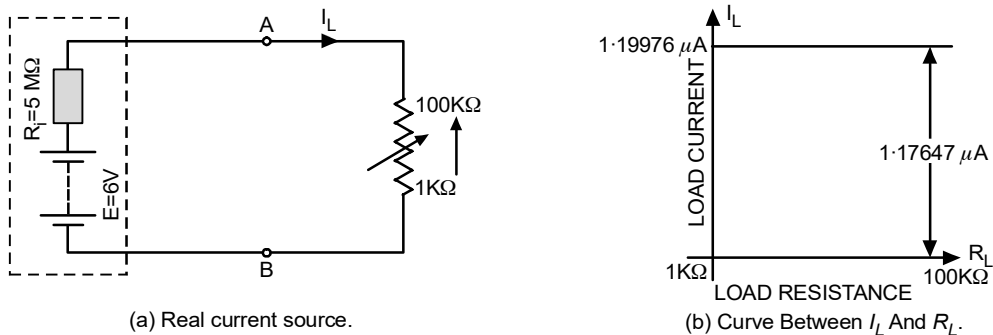


Fig.1.23: Real current source and its characteristics

A real current source having very high internal resistance say $5 \text{ M}\Omega$ with a comparatively low load resistance R_L (say varying from 1 K to 100 K) is shown in Fig.1.23(a). Its characteristics are shown in fig.1.23(b).

This shows that the load current remains almost constant and the source behaves as a constant current source irrespective of the value of load resistance.

1.9. DIFFERENCE BETWEEN VOLTAGE SOURCE AND CURRENT SOURCE

The behaviour of an electrical source depends upon its working conditions. When the value of load resistance (or impedance) is very large as compared to the internal resistance (or impedance) of the source, the source is treated as a voltage source.

Whereas, when the value of load resistance is very small as compared to the internal resistance of the source, the source is treated as a current source.

For instance, consider a 12 V battery with an internal resistance of 0.5 ohm. If the load applied on the battery varies from 1 K Ω to 10 K Ω , the terminal voltage varies from 11.994V to 11.9994

$\left[V = \frac{E}{1 + R_i / R_L} \right]$. The source is considered as constant voltage source.

If the load applied on the battery varies from 1 m Ω to 10 m Ω the current supplied by the battery varies from 23.952 A to 23.529 A $\left[I = \frac{E / R_i}{1 + R_L / R_i} \right]$. The source is considered as constant voltage source.

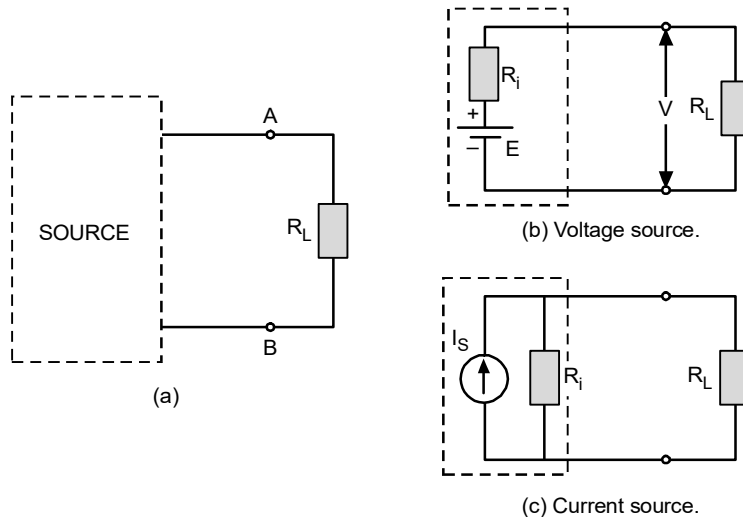


Fig.1.24: Voltage source and current source


Conclusion : It clearly shows that the source is the same but it is considered as a constant voltage source if $R_i \ll R_L$ and the same source is considered as a constant current source If $R_i \gg R_L$. Hence practically, there is *no difference* between constant voltage source and constant current source.

1.10. SOURCE TRANSFORMATION


(CONVERSION OF VOLTAGE SOURCE TO CURRENT SOURCE AND VICE-VERSA)

It has been seen that, the same electrical source behaves as a constant voltage source and as a constant current source. Accordingly the same source can be represented in two different ways as shown in fig. 1.25(b) and 1.25(c) respectively.

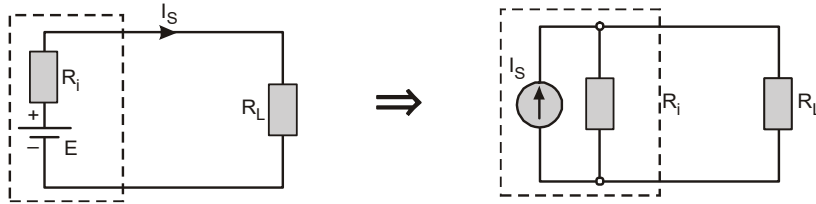Thus, a voltage source can be represented as a current source as shown in fig.1.25(a) and a current source can be represented as a voltage source as shown in fig.1.25(b)




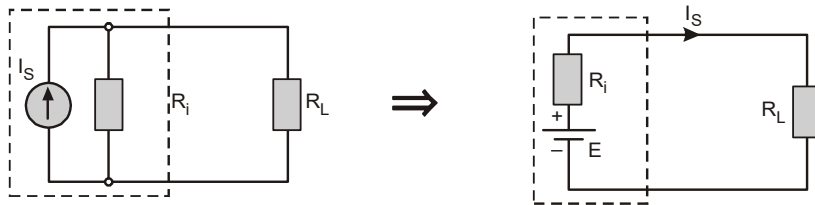
(a) Conversion from voltage source to current source



(b) Conversion from current source to voltage source

Fig.1.25: Conversion of voltage source to current source and vice-versa.

Example 1.1. Fig.1.26 shows a d.c. voltage source having an open circuit voltage of 12 V and an internal resistance of 1 ohm. Obtain its equivalent current source representation.

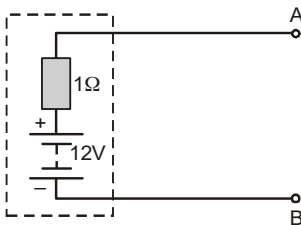
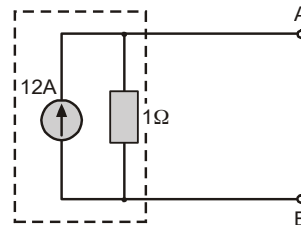
**Fig.1.26:** Voltage Source**Fig.1.27:** Equivalent Current source

Solution. If the terminals A and B of voltage-source are short-circuited, the current supplied by the source,

$$I_S = \frac{E}{R_i} = \frac{12}{1} = 12 \text{ A}$$

In the equivalent current-source representation, the current source is of 12A. The internal resistance of the source is represented in parallel with the current source as shown in Fig.1.27.

Example 1.2. Fig.1.28 shows a d.c. current-source, obtain its equivalent voltage-source representation.

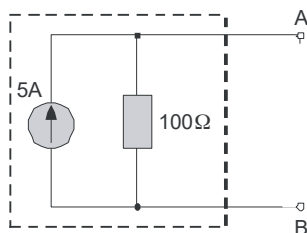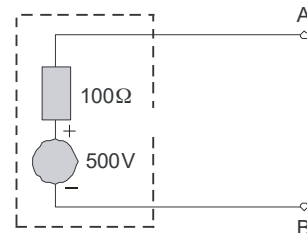**Fig.1.28:** D.C Current Source**Fig.1.29:** Equivalent Voltage Source

Solution. The open circuit voltage of the current source across the terminals A and B .

$$E = I_S R_i = 5 \times 100 = 500 \text{ V}$$

This will be the generated e.m.f. or ideal voltage of the equivalent voltage source representation. The internal impedance ($R_i = 100 \Omega$) is put in series with the ideal voltage source as shown in Fig.1.29. This gives the equivalent voltage source representation of the given current source.

1.11. OHM'S LAW

This law states that the current flowing between any two points of a conductor (or circuit) is directly proportional to the potential difference across them, provided physical conditions (i.e. temperature etc.) remain the same.

Considering circuit shown in fig.1.30.

Mathematically ; $I \propto V$

$$\text{or } \frac{V}{I} = \text{Constant}$$

$$\text{or } \frac{V_1}{I_1} = \frac{V_2}{I_2} = \dots = \frac{V_n}{I_n} = \text{Constant}$$

In other words, the ratio of potential difference across any two points of a conductor to the current flowing between them is always constant, provided the physical conditions (i.e. temperature etc.) remain the same

This constant is known as resistance (R) of the conductor (or circuit)

$$\therefore \frac{V}{I} = R$$

$$\text{It can also be written as } V = IR \text{ or } I = \frac{V}{R}$$

Limitations of Ohm's law : Ohm's law cannot be applied to the circuits :

- (i) Consisting of electronic tubes or transistors because these elements are not bilateral.
- (ii) Consisting of non-linear elements such as electric arc etc.

Example 1.3. The specific resistance of platinum at 0°C is $10.5 \text{ micro - ohm - cm}$. What should be the length of platinum wire of diameter 0.0274 cm to have a resistance of 3 ohm at 0°C ?

Solution : Resistance of a wire at 0°C ;

$$R_0 = \rho_0 \frac{l}{a} \quad \text{or} \quad l = \frac{R_0 a}{\rho_0}$$

where,

$$R_0 = 3 \Omega ; \rho_0 = 10.5 \times 10^{-6} \Omega \text{ cm} = 10.5 \times 10^{-8} \Omega \text{ m}$$

$$a = \frac{\pi}{4} d^2 = \frac{\pi}{4} (0.0274)^2 \text{ cm}^2 = \frac{\pi}{4} (0.0274) \times 10^{-4} \text{ m}^2$$

$$\therefore l = \frac{3 \times \pi \times (0.0274)^2 \times 10^{-4}}{4 \times 10.5 \times 10^{-8}} = \mathbf{1.687 \text{ m (Ans.)}}$$

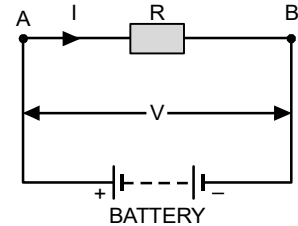


Fig.1.30: A resistor is connected across a battery

Example 1.4. A current of 0.5 A is passed through a coil of nichrome wire having a cross-sectional area of 0.01 cm^2 . If the resistivity of the nichrome is $108 \times 10^{-6}\text{ ohm-cm}$ and the p.d. across the ends of the coil is 54 volt , what is the length of the wire? What is the conductivity and conductance of the wire?

Solution : Resistance, $R = \rho \frac{l}{a}$

Where, $R = \frac{V}{I} = \frac{54}{0.5} = 108\ \Omega$; $a = 0.01\text{ cm}^2 = 0.01 \times 10^{-4}\text{ m}^2$

$\rho = 108 \times 10^{-6}\ \Omega\text{ cm} = 108 \times 10^{-8}\ \Omega\text{ m}$

$\therefore l = \frac{Ra}{\rho} = \frac{108 \times 0.01 \times 10^{-4}}{108 \times 10^{-8}} = 100\text{ m (Ans.)}$

Conductivity, $\sigma = \frac{I}{p} = \frac{1}{108 \times 10^{-8}} = 92.59 \times 10^4\text{ mho/m (Ans.)}$

Conductance, $G = \frac{I}{R} = \frac{1}{108} = 9.259 \times 10^{-3}\text{ mho (Ans.)}$

1.12. D.C. CIRCUITS

The closed path for the flow of direct current is called **d.c. circuit**.

A simple d.c. circuit is shown in fig.1.31. which contains a d.c. source (battery), a load (lamp), a switch, connecting leads and measuring instruments like ammeter and voltmeter.

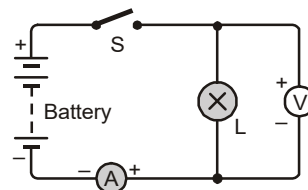


Fig.1.31: Simple dc circuit

1.13. SERIES CIRCUITS

A circuit in which number of resistors are connected such that same current flows through them is called *series circuit*.

Fig.1.32 shows a simple series circuit which carries three resistors R_1 , R_2 and R_3 connected in series across a supply voltage of V volt.

Current flowing through the circuit is I ampere.

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3$$

(As per Ohm's law)

If R is the effective resistance of the circuit, then

$$IR = IR_1 + IR_2 + IR_3 \quad \text{or} \quad R = R_1 + R_2 + R_3$$

i.e. Total resistance = Sum of the individual resistances.

This circuit is usually employed in marriages for decoration purposes.

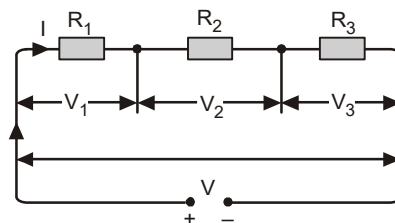


Fig.1.32: Three resistors connected in series.

1.14. PARALLEL CIRCUITS

A circuit in which number of resistors are connected such that different current flows through them but

potential difference across them is the same as shown in fig.1.33. Current flowing through the resistors R_1 , R_2 and R_3 is I_1 , I_2 and I_3 respectively, then;

The total current drawn by the circuit,

$$I = I_1 + I_2 + I_3 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad (\text{according to ohm's law})$$

If R is the effective resistance of the circuit, then

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad \text{or} \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

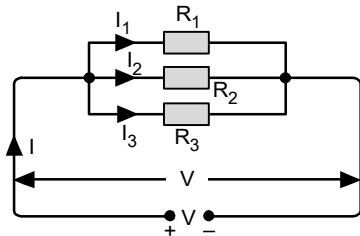


Fig.1.33: Three resistors connected in parallel

i.e. Reciprocal of effective resistance = sum of reciprocal of the individual resistances.

All domestic appliances are connected in parallel since these are operated at the same voltage and controlled independently.

1.15. SERIES – PARALLEL CIRCUITS

The circuit in which resistors are connected in series and parallel combination is called *series - parallel circuit*, as shown in fig.1.34.

Here, resistor R_2 and R_3 are connected in parallel, but their combination is connected in series with R_1 . Say effective value of R_2 and R_3 is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{R_2 + R_3}{R_2 R_3} \quad \text{or} \quad R_p = \frac{R_2 R_3}{R_2 + R_3}$$

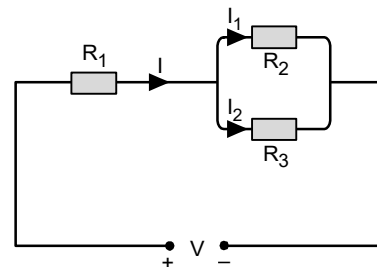


Fig.1.34: Series parallel circuit.

$$\text{Total or effective resistance of the circuit, } R = R_1 + R_p = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$\text{Alternately; total or effective resistance of the circuit, } R = R_1 + (R_2 \parallel R_3) = R_1 + \left(\frac{R_2 R_3}{R_2 + R_3} \right)$$

1.16. DIVISION OF CURRENT IN PARALLEL CIRCUITS

When two resistors having resistance R_1 and R_2 are connected in parallel across supply voltage of V volt, say the current flowing through each branch is I_1 and I_2 respectively.

According to ohm's law ;

$$I_1 R_1 = I_2 R_2 = IR = V$$

where R is total or effective resistance of the circuit and I is the total current.

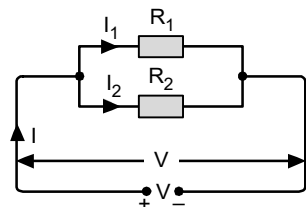


Fig.1.35: Two resistors connected in parallel

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Now,} \quad I_1 R_1 = I \frac{R_1 R_2}{R_1 + R_2} \quad \text{or} \quad I_1 = I \frac{R_2}{R_1 + R_2}$$

Similarly,
$$I_2 = I \frac{R_1}{R_1 + R_2}$$

The above equation shows that

Current in one branch = $\frac{\text{Resistance of other branch}}{\text{sum of resistance of two branches}} \times \text{total current}$

Example 1.5. A resistor R is connected in series with a parallel circuit comprising of two resistors having resistance of 6 and 4 ohm respectively. The total power dissipated in the circuit is 48 watt, applied voltage is 12V. Calculate the value of R .

Solution : Total power dissipated, $P = 48 \text{ W}$; Applied voltage, $V = 12 \text{ V}$

The circuit is shown in Fig.1.36.

Current supplied to the circuit,
$$I = \frac{P}{V} = \frac{48}{12} = 4 \text{ A}$$

Effective resistnace of the circuit,
$$R_{\text{eff}} = \frac{V}{I} = \frac{12}{4} = 3 \text{ ohm}$$

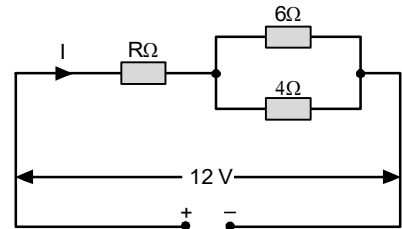


Fig.1.36: Circuit diagram

Now
$$R_{\text{eff}} = R + \left(\frac{6 \times 4}{6 + 4} \right)$$

Or
$$3 = R + 2.4 \text{ or } R = 3 - 2.4 = \mathbf{0.6 \text{ ohm (Ans.)}}$$

Example 1.6. Determine current I in the circuit shown in fig.1.37, all the resistors are given in ohm.

Solution : Simplified view of the circuit is shown in fig.1.38.

∴

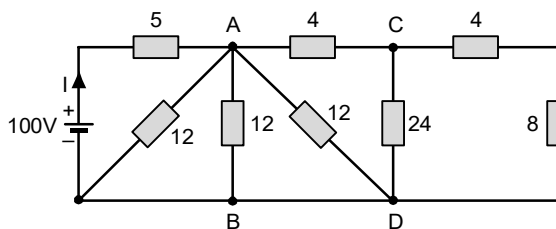


Fig.1.37: Given circuit

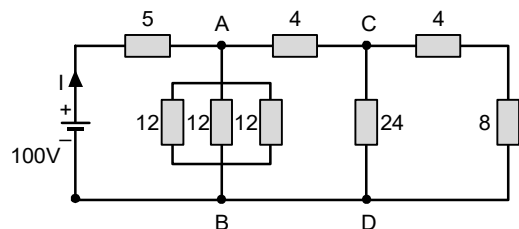


Fig.1.38: Simplified view of the given circuit

The effective resistance across the supply.

$$\begin{aligned} R &= [(\{ (4 + 8) \parallel 24 \} + 4) \parallel 12 \parallel 12 \parallel 12] + 5 \\ &= [\{ (12 \parallel 24) + 4 \} \parallel 12 \parallel 12 \parallel 12] + 5 = \left[\left(\frac{12 \times 24}{12 + 24} + 4 \right) \parallel 12 \parallel 12 \parallel 12 \right] + 5 \\ &= [(8 + 4) \parallel 12 \parallel 12 \parallel 12] + 5 = \left(\frac{12}{4} \right) + 5 = 3 + 5 = 8 \Omega \end{aligned}$$

$$\text{Current, } I = \frac{V}{R} = \frac{100}{8} = 12.5 \text{ A (Ans.)}$$

1.17. NETWORK TERMINOLOGY

Network theorems are applied to analyze the electrical network. While discussing these theorems one comes across various terms discussed below :

- 1. Electric Network :** The combination of various electric elements, connected in any manner, is called an *electric network*.
- 2. Electric circuit :** An *electric circuit* is a closed conducting path through which an electric current either flows or is intended to flow.
- 3. Parameters :** Various elements of an electric circuit are called its *parameters* such as resistors, inductors, capacitors etc.
- 4. Active network :** An electric network which contains one or more than one source of emf is called *active network*.
- 5. Passive network :** An electric network which does not contain any source of emf is called *passive network*.
- 6. Node :** A node is a point in the network where two or more circuit elements are joined. In fig.1.39, *A, B, C* and *D* are the nodes.
- 7. Junction :** A junction is a point in the network where three or more circuit elements are joined. In fact, it is a point where current is divided. In fig.1.39, *B* and *D* are junctions.
- 8. Branch :** The part of a network which lies between two junction points is called branch. In fig. 1.39. *D A B*, *B C D* and *B D* are the three branches.
- 9. Loop :** The closed path of a network is called a loop. In fig.1.39, *A B D A*, *B C D B* and *A B C D A* are the three loops.
- 10. Mesh :** The most elementary form of a loop which cannot be further divided is called a mesh. In fig.1.39, *A B D A* and *B C D B* are the two meshes but *A B C D A* is the loop.

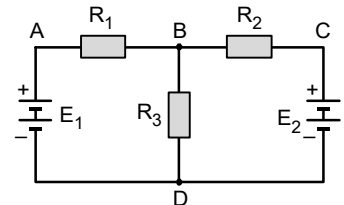


Fig.1.39: An electric network

1.18. KIRCHHOFF'S LAWS

Kirchhoff's First Law : It is also known as *Kirchhoff's Current Law (KCL)*.

It states that *The algebraic sum of all the currents meeting at a point or junction is zero.*

For algebraic sum, consider;

Incoming currents as +ve ; and Outgoing currents as - ve.

Applying Kirchhoff's current law to junction *O* in fig.1.40, we get,

$$I_1 + I_2 - I_3 + I_4 - I_5 = 0$$

$$\text{or} \quad I_1 + I_2 + I_4 = I_3 + I_5$$

i.e. Sum of incoming currents = sum of outgoing currents.

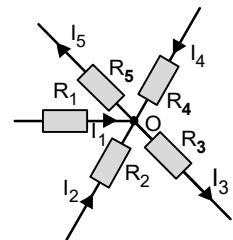


Fig.1.40: Five branches meeting at a junction

In other words,

At any junction of an electric network, the sum of incoming currents are equal to the sum of outgoing currents.

Kirchhoff's Second Law : It is also known as a *Kirchhoff's Voltage Law (KVL)* or *Kirchhoff's mesh law*. It states that

In a closed circuit or mesh, the algebraic sum of all the e.m.fs. plus the algebraic sum of all the voltage drops (i.e. product of current and resistances) is zero.

i.e. in a closed circuit or mesh,

algebraic sum of all the e.m.fs. + algebraic sum of all the voltage drops = 0

For algebraic sum, consider

A rise in potential as +ve ; and A fall in potential as -ve.

Consider a branch AB containing only one source of e.m.f. (E) as shown in fig.1.41(a). If this branch is traced from A to B , there is fall in potential, therefore, E is taken as negative (*i.e.* $-E$).

Similarly, if the branch is traced from A to B in fig.1.41(b), there is rise in potential and E will be taken as positive (*i.e.* $+E$), *i.e.*

- In fig.1.41 (b) from A to B , E is negative ($-E$);
- In fig.1.41(b), from A to B , E is positive ($+E$).

Note : Direction of flow of current is neither considered nor marked.

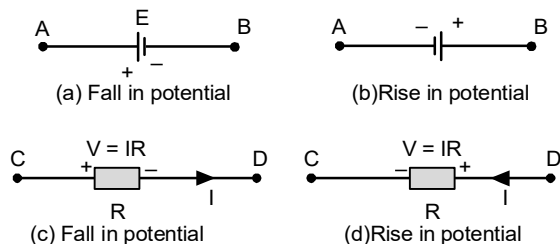


Fig.1.41: Algebraic signs for emf and voltage drop.

To determine sign for the voltage drop $V (= IR)$, consider a branch containing resistor of resistance R ohm in which current I ampere flows from C to D as shown in fig.1.41(c). Therefore, C is at higher potential w.r.t. terminal D .

Thus, tracing branch from C to D , V is negative (*i.e.* $-V$) as there is *fall in potential*. As we are moving in the direction of flow of current.

Similarly, while tracing branch C to D in fig.1.41(d), V is positive (*i.e.* $+V$) as there is *rise in potential* and we are moving opposite to the flow of current.

Note : Only the direction of flow of current determines the sign of V .

Illustration :

Consider a network shown in fig.1.42. In this circuit, we can apply *kVL* for the closed circuit $ABEFA$ and form an equation given below :

$$-R_1 (I_1 + I_2) - I_2 R_3 + E_1 = 0$$

Where $R_1 (I_1 + I_2)$ (voltage drop) is considered as negative, since we are tracing the circuit along the direction of flow of current.

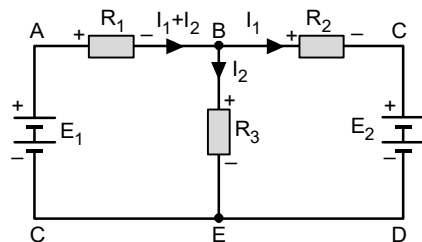


Fig.1.42: Given network

$I_2 R_3$ (voltage drop) is taken as negative as we are moving along the direction of flow of current.

E_1 (e.m.f. of battery) is taken as positive as we move from -ve to +ve terminal at the battery and there is a rise in potential (Note: The direction of flow of current is not to be considered).

Similarly, KVL can be applied to the other closed circuit $BCDEB$, we get, $-I_1 R_2 - E_2 + I_2 R_3 = 0$

1.19. SOLUTION OF NETWORK BY KIRCHHOFF'S LAWS

For solution of network, while applying Kirchhoff's laws, the following steps are taken:

- Name all the nodes and junctions as A, B, C, D, \dots
- Mark the assumed direction of flow of current in all the branches of the network according to KCL .
- Choose as many number of closed circuits, as the number of unknown quantities.
- For the chosen closed circuits frame the equations by applying KVL .
- Solve the equations and determine the unknown values.

Note: If the determined current carries the -ve sign, it shows that the actual direction of flow of current is opposite to that of the assumed direction of flow of current in the given branch.

Example 1.7. In the circuit shown in fig.1.43, calculate current and power in the 6 ohm resistor.

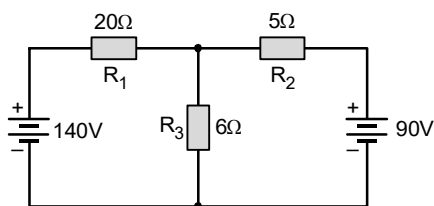


Fig.1.43: Given circuit

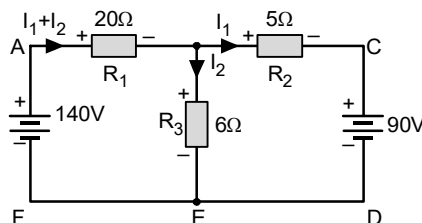


Fig.1.44: Circuit carrying current

Solution: The various junction points are marked in fig.1.44. According to Kirchhoff's first law, let the current flowing through various sections be as shown in fig.1.44.

Applying Kirchhoff's second law to mesh $ABEFA$, get,

$$-20(I_1 + I_2) - 6I_2 + 140 = 0 \quad \text{or} \quad 20I_1 + 26I_2 = 140$$

$$\text{or} \quad 10I_1 + 13I_2 = 70 \quad \dots\dots\dots(i)$$

Applying Kirchhoff's second law to mesh $BCDEB$, we get,

$$-5I_1 - 90 + 6I_2 = 0 \quad \text{or} \quad -5I_1 + 6I_2 = 90$$

$$\text{or} \quad -10I_1 + 12I_2 = 180 \quad \dots\dots\dots(ii)$$

Adding equation (i), and (ii), we get,

$$25I_2 = 250$$

$$I_2 = 10 \text{ A (Ans.)}$$

$$\text{Power in 6 ohm resistor} = I_2^2 R_3 = (10)^2 \times 6 = 600 \text{ W (Ans.)}$$

Example 1.8. Fig.1.45 shows two batteries connected in parallel each represented by an emf along with its internal resistance. A load resistance of $5\ \Omega$ is connected across the ends of the batteries. Calculate the current through each battery and the load.

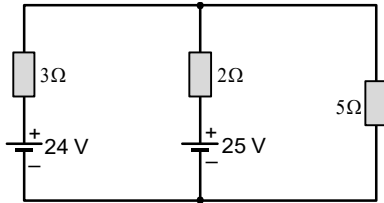


Fig.1.45: Given circuit.

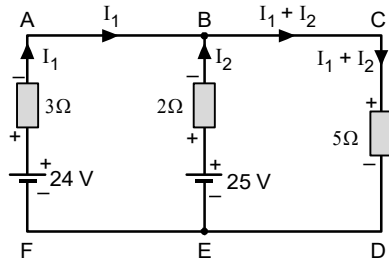


Fig.1.46: Circuit carrying current.

Solution : Assuming that the current flowing through various branches of the network is as marked in fig.1.46.

Applying *KVL* to mesh *ABEFA*, we get,

$$2 I_2 - 25 + 24 - 3 I_1 = 0$$

$$\text{or} \quad 2 I_2 - 3 I_1 = 25 - 24 \quad \text{or} \quad 2 I_2 - 3 I_1 = 1 \quad \dots\dots\dots(i)$$

Applying *KVL* to the mesh *BCDEB*, we get,

$$- 5 (I_1 + I_2) + 25 - 2 I_2 = 0$$

$$\text{or} \quad 2 I_2 + 5 (I_1 + I_2) = 25 \quad \text{or} \quad 7 I_2 + 5 I_1 = 25 \quad \dots\dots\dots(ii)$$

Multiplying equation (i) by 5, equation (ii) by 3 and adding, we get,

$$I_2 = \frac{80}{31} = 2.58 \text{ A (Ans.)}$$

Substituting the value of I_2 in equation (i),

$$I_1 = \frac{43}{31} = 1.387 \text{ A (Ans.)}$$

$$\text{Current through load, } I_L = I_1 + I_2 = \frac{43}{31} + \frac{80}{31} = \frac{123}{31} \text{ A} = 3.967 \text{ A (Ans.)}$$

Example 1.9. Solve the network shown in fig.1.47 for the current through 6 ohm resistor.

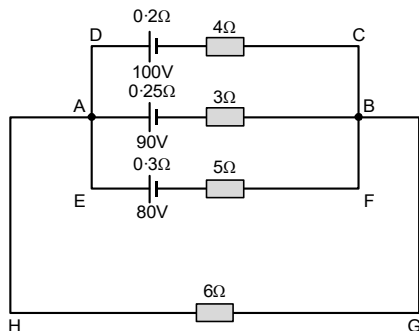


Fig.1.47: Given circuit

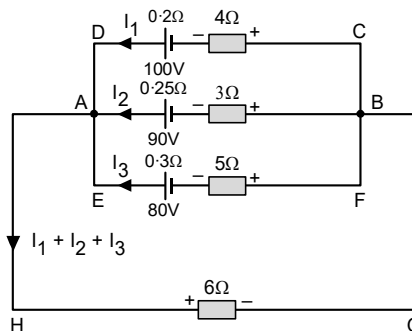


Fig.1.48: Circuit carrying current

Solution : Let the current flowing through various branches be as marked in fig.1.48.

Applying Kirchhoff's second law to the following closed circuits,

Circuit CDAHGB

$$-4I_1 - 0.2I_1 + 100 - 6(I_1 + I_2 + I_3) = 0$$

$$\text{or} \quad 10.2I_1 + 6I_2 + 6I_3 = 100 \quad \dots\dots\dots(i)$$

Circuit BAHGB

$$-3I_2 - 0.25I_2 + 90 - 6(I_1 + I_2 + I_3) = 0$$

$$\text{or} \quad 6I_1 + 9.25I_2 + 6I_3 = 90 \quad \dots\dots\dots(ii)$$

Circuit FEAHGBF

$$-5I_3 - 0.3I_3 + 80 - 6(I_1 + I_2 + I_3) = 0$$

$$\text{or} \quad 6I_1 + 6I_2 + 11.3I_3 = 80 \quad \dots\dots\dots(iii)$$

Subtracting (ii) from (i), we get,

$$4.2I_1 - 3.25I_2 = 10 \quad \dots\dots\dots(iv)$$

Solving (ii) and (iii), we get,

$$31.8I_1 + 68.525I_2 = 537 \quad \dots\dots\dots(v)$$

From equation (iv) and (v), we get,

$$391.51I_2 = 137.4$$

$$\therefore \quad I_2 = \frac{1937.4}{391.15} = 4.953 \text{ A}$$

Solving equation (v), we get, $I_1 = 6.21 \text{ A}$

Solving equation (iii), we get, $I_3 = 1.15 \text{ A}$

Current in 6 ohm resistor, $I = I_1 + I_2 + I_3$
 $= 6.21 + 4.953 + 1.15$
 $= 12.313 \text{ A (Ans.)}$

Example 1.10. In the circuit shown in fig.1.49 find the value of I_S for $I = 0$.

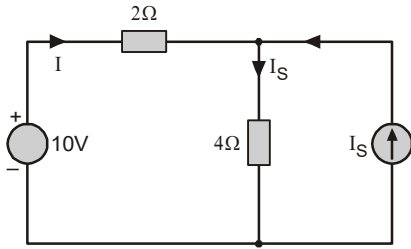


Fig.1.49: Given circuit

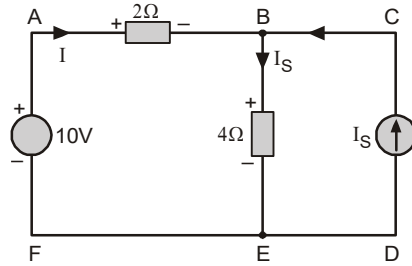


Fig.1.50: Circuit for solution.

Solution : Considering circuit shown in fig.1.50, applying *KCL* at junction *B*, we get,
Current through branch *BE* (i.e. $4\ \Omega$ resistor)

$$= I + I_S = 0 + I_S = I_S \quad (\because I = 0)$$

Applying *KVL* to mesh *ABEFA*, we get,

$$-2I - 4I_S + 10 = 0$$

or $2I + 4I_S = 10$

or $I_S = \frac{10}{4} = 2.5\text{ A (Ans.)} \quad (\because I = 0)$

Example 1.11. Formulate the Kirchhoff's voltage law equation for the circuit shown in fig.1.51. Determine the values of currents I_1 , I_2 and I_3 .

Solution : Applying *KVL* to closed circuit *efgd e*, we get,

$$-10 + 0.4I_2 - 1.5I_3 + 3(I_1 + I_2) = 0$$

$$3I_1 + 3.4I_2 - 1.5I_3 = 10 \quad \dots\dots(i)$$

Applying *KVL* to closed circuit *aedcba*, we get,

$$-I_1 - 3(I_1 + I_2) - 6(I_1 + I_2 + I_3) - 0.5I_1 + 12 = 0$$

$$-10.5I_1 - 9I_2 - 6I_3 + 12 = 0$$

$$10.5I_1 + 9I_2 + 6I_3 = 12 \quad \dots\dots(ii)$$

Applying *KVL* to closed circuit *dghcd*, we get,

$$1.5I_3 - 6 + 0.3(I_2 + I_3) + 6(I_1 + I_2 + I_3) = 0$$

$$6I_1 + 6.3I_2 + 7.8I_3 = 6 \quad \dots\dots(iii)$$

Solving equation (i), (ii) and (iii), we get,

$$I_1 = -1.242\text{ A (Ans.)}$$

$$I_2 = 3.537\text{ A (Ans.)}$$

$$I_3 = -1.1325\text{ A (Ans.)}$$

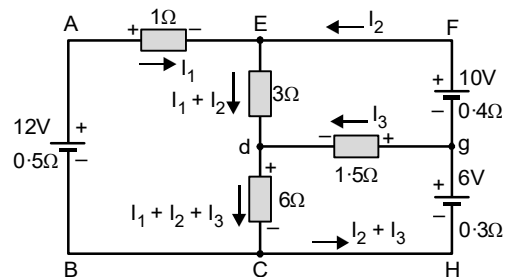


Fig.1.51: Given circuit.

The negative sign with current I_1 and I_3 shows that the actual flows of current is opposite to that of the direction marked in fig.1.51.

Example 1.12. Find the magnitude and direction of the currents in all branches of the circuit shown in fig.1.52, using Kirchhoff's laws. All resistances are in ohm.

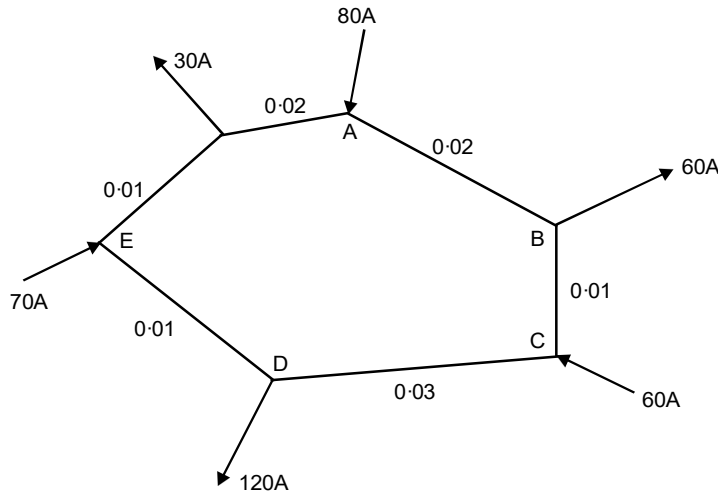


Fig.1.52: Given circuit

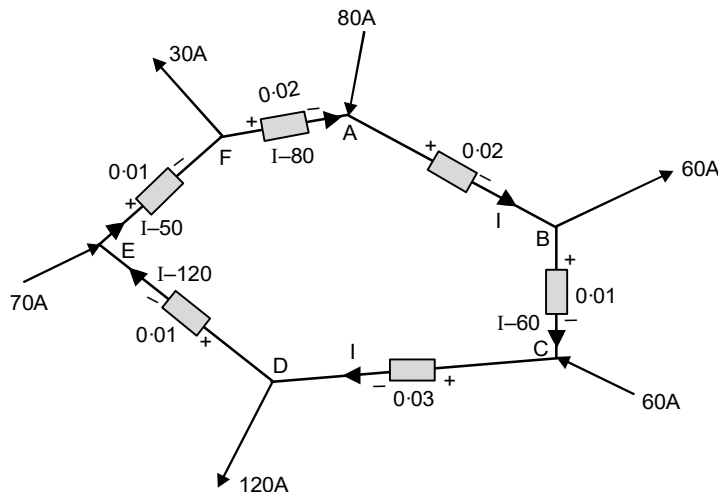


Fig.1.53: Circuit with assumed current.

Solution : Applying Kirchhoff's first law, let current flowing through various branches be as shown in fig.1.53.

Applying Kirchhoff's second law to a closed loop $ABCDEFA$, we get,

$$- 0.02 I - 0.01 (I - 60) - 0.03 I - 0.01 (I - 120) - 0.01 (I - 50) - 0.02 (I - 80) = 0$$

$$\text{or } 0.02 I + 0.01 I + 0.03 I + 0.01 I + 0.01 I + 0.02 I = 0.6 + 1.2 + 0.5 + 1.6$$

or $0.1 I = 3.9$ or $I = 39 \text{ A}$

Current in various branches is as under :

$$I_{AB} = + 39 \text{ A} \quad (\text{i.e. } A \text{ to } B)$$

$$I_{BC} = I - 60 = - 21 \text{ A} \quad (\text{i.e. } C \text{ to } B)$$

$$I_{CD} = I = 39 \text{ A} \quad (\text{i.e. } C \text{ to } D)$$

$$I_{DE} = I - 120 = - 81 \text{ A} \quad (\text{i.e. } E \text{ to } D)$$

$$I_{EF} = I - 50 = - 11 \text{ A} \quad (\text{i.e. } F \text{ to } E)$$

$$I_{FA} = I - 80 = - 41 \text{ A} \quad (\text{i.e. } A \text{ to } F)$$

Example 1.13. A Wheatstone bridge consists of $AB = 4 \text{ ohm}$, $BC = 3 \text{ ohm}$, $CD = 6 \text{ ohm}$ and $DA = 5 \text{ ohm}$. A 2 volt cell is connected between B and D and a galvanometer of 10 ohm resistance between A and C. Find the current through the galvanometer.

Solution : The circuit is shown in fig.1.54.

Applying Kirchhoff's first law at junction B, A & C, the current in various branches is marked.

Applying Kirchhoff's second law to various closed loops ;

Considering loop $BACB$, we get,

$$- 4I_1 - 10I_3 + 3I_2 = 0$$

$$\text{or} \quad 4I_1 - 3I_2 + 10I_3 = 0 \quad \dots(i)$$

Considering loop $ADCA$, we get,

$$- 5(I_1 - I_3) + 6(I_2 + I_3) + 10I_3 = 0$$

$$\text{or} \quad - 5I_1 + 5I_3 + 6I_2 + 6I_3 + 10I_3 = 0$$

$$\text{or} \quad 5I_1 - 6I_2 - 21I_3 = 0 \quad \dots(ii)$$

Considering loop $BADEB$, we get

$$- 4I_1 - 5(I_1 - I_3) + 2 = 0$$

$$\text{or} \quad - 4I_1 - 5I_1 + 5I_3 = -2$$

$$\text{or} \quad 9I_1 - 5I_3 = 2 \quad \dots(iii)$$

Multiplying equation (i) by 2 and subtracting from equation (ii), we get,

$$5I_1 - 6I_2 - 21I_3 = 0$$

$$8I_1 - 6I_2 + 20 I_3 = 0$$

$$- \quad + \quad -$$

$$- 3I_1 \quad - 41I_3 = 0$$

$$\therefore \quad I_1 = - \frac{41}{3} I_3$$

Substituting the value of I_1 in equation (iii), we get,

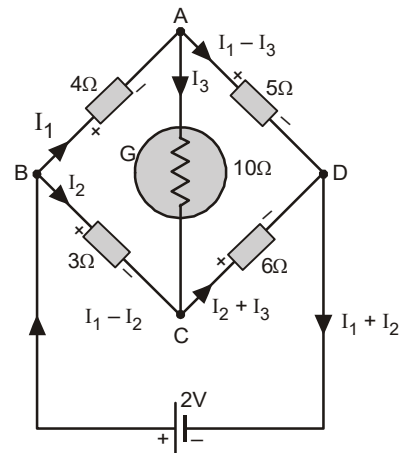


Fig.1.54: Circuit for bridge.

$$9\left(-\frac{41}{3}I_3\right) - 5I_3 = 2 \quad \text{or} \quad -123I_3 - 5I_3 = 2 \quad \text{or} \quad I_3 = \frac{-1}{64} \text{ A}$$

Current flowing through galvanometer is $1/64$ ampere from C to A.

Example 1.14. Determine the current I in 8 ohm resistance in the circuit shown in fig.1.55.

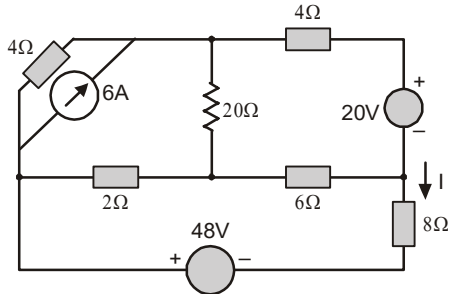


Fig.1.55: Given circuit.

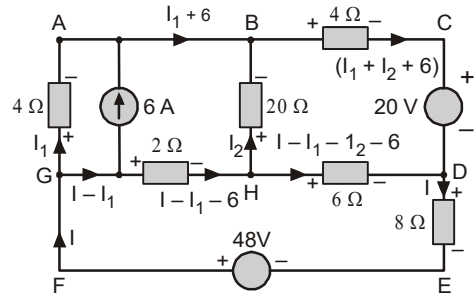


Fig.1.56: Circuit for solution.

Solution : A simplified circuit is shown in fig.1.56. Applying *KCL at various junctions*, different currents are marked in various sections.

Applying Kirchhoff's voltage law to

Loop $A B H G A$

$$20 I_2 + 2 (I - I_1 - 6) - 4 I_1 = 0 \quad \text{or} \quad 2I - 6I_1 + 20I_2 = 12$$

$$I - 3I_1 + 10I_2 = 6 \quad \dots(i)$$

Loop $B C D H B$

$$-4 (I_1 + I_2 + 6) - 20 + 6 (I - I_1 - I_2 - 6) - 20I_2 = 0$$

$$6I - 10I_1 - 30I_2 = 80 \quad \text{or} \quad 3I - 5I_1 - 15I_2 = 40 \quad \dots(ii)$$

Loop $G H D E F G$

$$-2 (I - I_1 - 6) - 6 (I - I_1 - I_2 - 6) - 8I + 48 = 0$$

$$16I - 8I_1 - 6I_2 = 96 \quad \text{or} \quad 8I - 4I_1 - 3I_2 = 48 \quad \dots(iii)$$

Eliminating, I_1 from equation (i) and (ii), we get,

$$4I - 95I_2 = 90 \quad \dots(iv)$$

Eliminating I_1 from equation (ii) and (iii), we get,

$$28I + 45I_2 = 80 \quad \dots(v)$$

Eliminating I_2 from equation (iv) and (v), we get,

$$568 I = 2330 \quad \text{or} \quad I = \frac{2330}{568} \text{ A}$$

\therefore Current in 8Ω resistor, $I = 4.1 \text{ A}$ (Ans.)

Alternatively

The three equation are :

$$I - 3I_1 + 10I_2 = 6$$

$$3I - 5I_1 - 15I_2 = 40$$

$$8I - 4I_1 - 3I_2 = 48$$

The three equation can be solved by the method of determinants *i.e.* by applying *Cramer's Rule*. The matrix from of the above equation is

$$\begin{pmatrix} 1 & -3 & 10 \\ 3 & -5 & -15 \\ 8 & -4 & -3 \end{pmatrix} \begin{pmatrix} I \\ I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 6 \\ 40 \\ 48 \end{pmatrix}$$

$$D_0 = \begin{vmatrix} 1 & -3 & 10 \\ 3 & -5 & -15 \\ 8 & -4 & -3 \end{vmatrix} = 1(15 - 60) + 3(-9 + 120) + 10(-12 + 40) = 568$$

$$D = \begin{vmatrix} 6 & -3 & 10 \\ 40 & -5 & -15 \\ 48 & -4 & -3 \end{vmatrix} = 6(15 - 60) + 3(-120 + 720) + 10(-160 + 240) = 2330$$

$$I = \frac{D}{D_0} = \frac{2330}{568} = 4.1 \text{ A (Ans.)}$$

PRACTICE EXERCISE

- Two batteries *A* and *B* are connected in parallel and a load of 5Ω is connected across their terminals. *A* has an emf of 6 V and an internal resistance of 1Ω and *B* has an emf of 4 V and an internal resistance of 0.5Ω . Use Kirchhoff's laws to determine the magnitude of currents and also the directions in each of the batteries. Also determine the pd across external resistance. (Ans. 1.625 A , -0.75 A , 0.875 A , 8.75 V)
- By using Kirchhoff's laws find the current in *XY* in the circuit shown in fig.1.57. (Ans. 40 A)

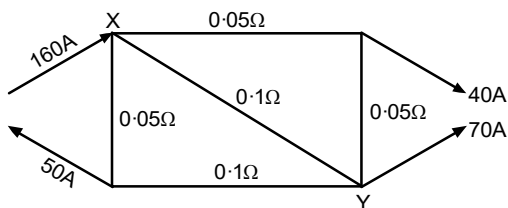


Fig.1.57: Given circuit

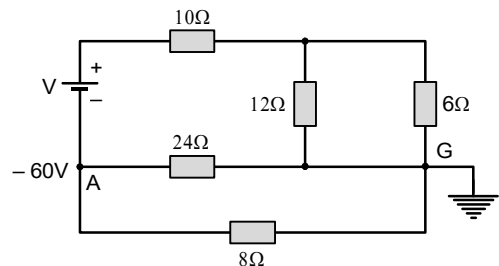


Fig.1.58: Given circuit

- In fig.1.58 the potential of point *A* = -60 V . Using Kirchhoff's laws find (a) value of *V* and (b) power dissipated by 8Ω resistance. (Ans. 200 V , 450 W)

4. Find the value of R and the current through it in the network shown in fig.1.59, when the current is zero in branch OA . (Ans. 6Ω , $0.5A$)

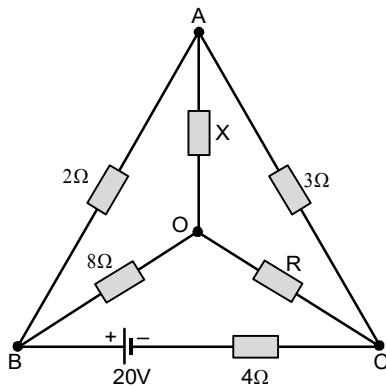


Fig.1.59: Given network

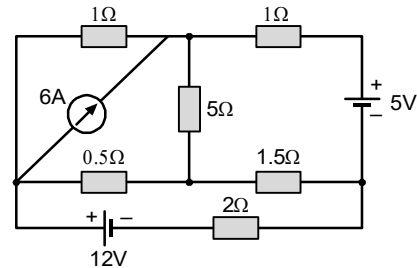


Fig.1.60: Given circuit

5. Determine the current in the $2\text{-}\Omega$ resistance of circuit shown in fig.1.60. (Ans. $4.1A$)
6. What is the difference of potential between X and Y in the network shown in fig.1.61. (Ans. $9.4V$)

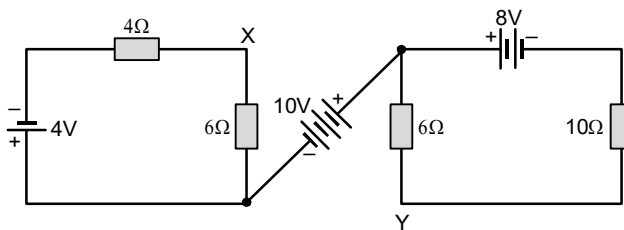


Fig. 1.61: Given network

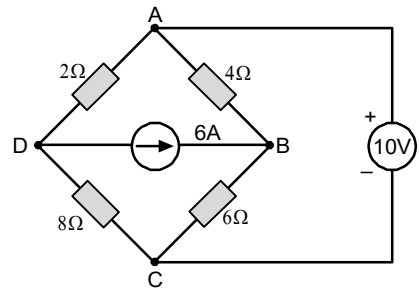


Fig.1.62: Given network

7. Find the total power delivered to the circuit by two sources in fig.1.62. (Ans. $164W$)

1.20. SUPERPOSITION THEOREM

This theorem is applicable to linear bilateral network having two or more than two sources.

According to this theorem, the current flowing through any section is the algebraic sum of all the currents which should flow in that section if each source of emf would be considered separately and other sources are replaced by their internal resistance (or impedance).

For instant, consider a circuit shown in fig.1.63. Let the current flowing through various branches be as marked in fig.1.63. According to superposition theorem.

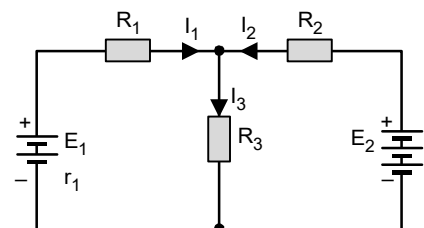


Fig.1.63: Given circuit

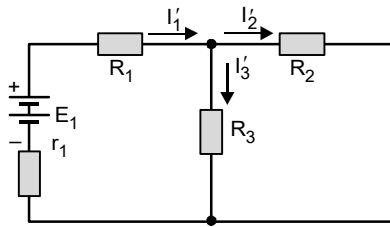


Fig.1.64: Considering source E_1 only

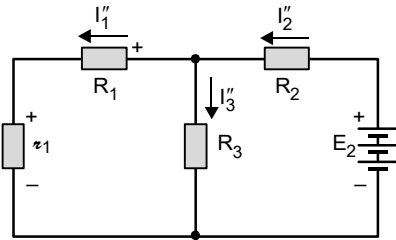


Fig.1.65: Considering source E_2 only

1. First, consider source E_1 only and replace the other source E_2 by its internal resistance. As its internal resistance is not given it is taken as zero (short circuit). Draw the circuit as shown in fig.1.64 and determine currents in various section as I_1' , I_2' and I_3' respectively.
2. Then consider the other source E_2 and replace the source E_1 by its internal resistance r_1 as shown in fig.1.65. Determine the currents in various sections as I_1'' , I_2'' and I_3'' respectively.

Actual flow of current in various sections ;

$$I_1 = I_1' - I_1'' ; I_2 = I_2' - I_2'' ; I_3 = I_3' + I_3''$$

Example 1.15. Find the current in different branches of the network shown in fig.1.66.

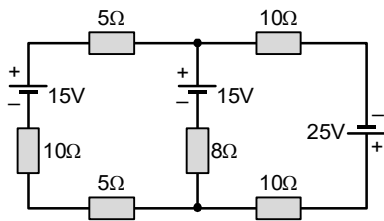


Fig.1.66: Given circuit.

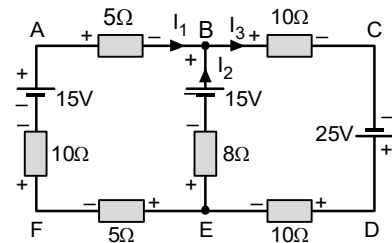


Fig.1.67: Circuit for solution.

Solution : Let the current flowing through different branches be as marked in fig.1.67.

According to superposition theorem, reducing the circuit as shown in fig.1.68.

$$\text{Total resistance} = 20 + \frac{8 \times 20}{28} = 25.714 \Omega$$

$$\text{Current supplied, } I_1' = \frac{15}{25.714} = 0.5833 \text{ A}$$

$$\text{Branch current } I_2' = 0.5833 \times \frac{20}{28} = 0.4167 \text{ A}$$

$$\text{Branch current } I_3' = 0.5833 \times \frac{8}{28} = 1.666 \text{ A}$$

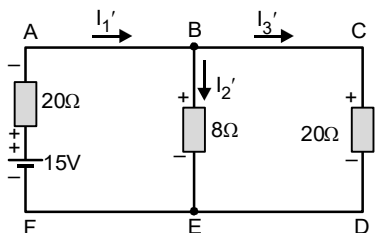


Fig.1.68: Considering one source only.

Now, reducing the circuit as shown in fig.1.69.

$$\text{Total resistance} = 8 + \frac{20 \times 20}{40} = 18\Omega$$

$$\text{Current supplied, } I_2'' = \frac{15}{18} = 0.8333 \text{ A}$$

$$\text{Branch current, } I_1'' = 0.8333 \times \frac{20}{40} = 0.4167 \text{ A}$$

$$\text{Branch current, } I_3'' = 0.8333 \times \frac{20}{40} = 0.4167 \text{ A}$$

Again, reducing the circuit as shown in fig.1.70.

$$\text{Total resistance} = 20 + \frac{20 \times 8}{28} = 25.714\Omega$$

$$\text{Current supplied, } I_3''' = \frac{25}{25.714} = 0.9722 \text{ A}$$

$$\text{Branch current, } I_1''' = 0.9722 \times \frac{8}{28} = 0.2778 \text{ A}$$

$$\text{Branch current, } I_2''' = 0.9722 \times \frac{20}{28} = 0.6944 \text{ A}$$

\therefore Actual flow of current in different branches ;

$$I_1 = I_1' - I_1'' + I_1''' = 0.5833 - 0.4167 + 0.2778 = \mathbf{0.4444 \text{ A (Ans.)}}$$

$$I_2 = -I_2' + I_2'' + I_2''' = -0.4167 + 0.8333 + 0.6944 = \mathbf{1.1111 \text{ A (Ans.)}}$$

$$I_3 = I_3' + I_3'' + I_3''' = 0.1666 + 0.4167 + 0.9722 = \mathbf{1.5555 \text{ A (Ans.)}}$$

Example 1.16. Find the current in the circuit given in fig.1.71.

(UPTU)

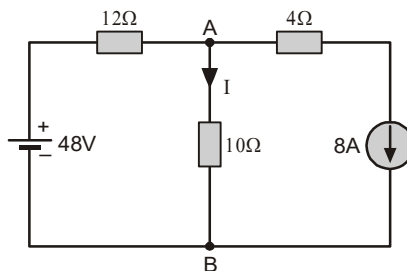


Fig.1.71: Given circuit

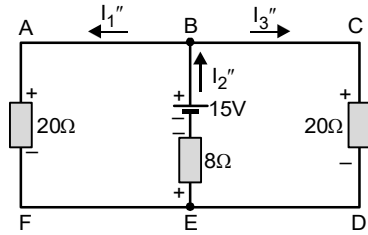


Fig.1.69: Considering second source only.

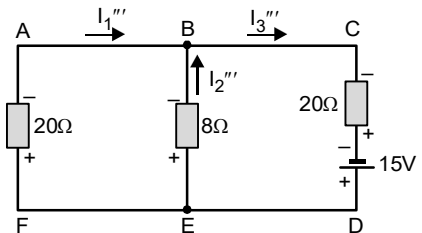


Fig.1.70: Considering third source only.

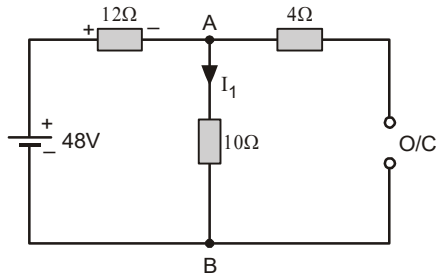


Fig.1.72: Considering voltage source only.

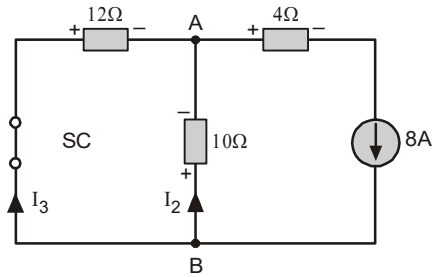


Fig.1.73: Considering current source only.

Solution : Applying superposition theorem

Case I : Considering 48 V source only and denoting 8 A source by its internal resistance *i.e.* open circuit as shown in Fig.1.72.

Current supplied by 48 V battery, $I_1 = \frac{48}{12+10} = 2.18\text{A}$ (from A to B)

Case II : Considering 8A current source only and replacing 48 V voltage battery by its internal resistance *i.e.* short circuit as shown in fig.1.73.

Current is divided in two paths ; current in 10 Ω resistor,

$$I_2 = \frac{12}{10+12} \times 8 = 4.36\text{A} \text{ (from B to A)}$$

∴ Resultant current flowing through 10 Ω resistor

i.e. $I = 2.18 - 4.36 = -2.18\text{ A (Ans.)}$ (from B to A)

Example 1.17. For the circuit of fig.1.74. find I using superposition theorem.

Solution : Replacing 128 V source by its internal resistance (*i.e.* short circuit), the circuit is reduced to a circuit shown in fig. 1.75.

Equivalent resistance,

$$\begin{aligned} R'_{eq} &= [\{ (R_4 \parallel R_5) + R_2 \} \parallel R_3] + R_1 \\ &= [\{ (8 \parallel 24) + 10 \} \parallel 40] + 10 \end{aligned}$$

$$= \left[\left\{ \frac{8 \times 24}{8 + 24} + 10 \right\} \parallel 40 \right] + 10 = \left[\frac{16 \times 40}{16 + 40} + 10 \right] = \frac{150}{7} \Omega$$

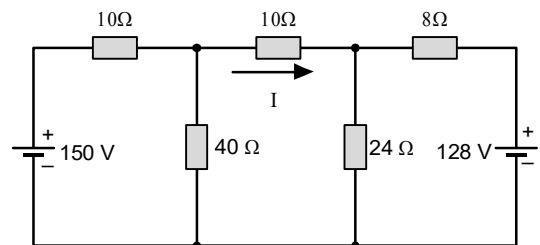


Fig.1.74 : Given circuit.

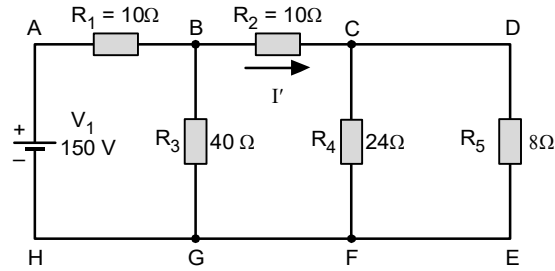


Fig.1.175: Circuit replacing the source of 128V.

$$\text{Current through branch } AB = \frac{V_1}{R'_{eq}} = \frac{150}{150/7} = 7\text{A}$$

$$\text{Current through branch } BC, I' = I_{AB} \times \frac{R_{BG}}{R_{BG} + R_{BF}} = 7 \times \frac{40}{40 + 16} = 5\text{A (from B to C)}$$

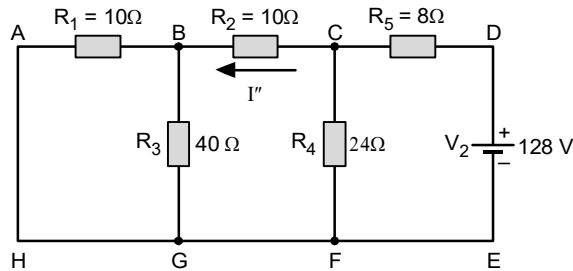


Fig.1.176: Circuit replacing the source of 150V.

Replacing 150 V source by its internal resistance (*i.e.* short circuit), the circuit is reduced to a circuit shown in fig.1.76.

$$\text{Equivalent resistance, } R''_{eq} = [\{ (R_1 \parallel R_3) + R_2 \} \parallel R_4] + R_5 = [\{ (10 \parallel 40) + 10 \} \parallel 24] + 8$$

$$= \left[\left\{ \frac{10 \times 40}{10 + 40} + 10 \right\} \parallel 24 \right] + 8 = \left[\frac{18 \times 24}{18 + 24} + 8 \right] = \frac{128}{7} \Omega$$

$$\text{Current through branch } DC = \frac{V_2}{R''_{eq}} = \frac{128}{128/7} = 7\text{A}$$

$$\text{Current through branch } CB, I'' = I_{DC} \times \frac{R_{CF}}{R_{CG} + R_{CF}} = 7 \times \frac{24}{18 + 24} = 4\text{A (from C to B)}$$

$$\text{Current, } I = I' - I'' = 5 - 4 = 1\text{ A (Ans.)}$$

PRACTICE EXERCISE

1. By using superposition theorem, find the current in resistance R shown in fig.1.77. $R_1 = 0.15 \Omega$, $R_2 = 0.12 \Omega$, $R = 3 \Omega$, $E_1 = 6.15 \text{ V}$, $E_2 = 6.45 \text{ V}$. Internal resistance of cells are negligible.

(Ans.2.06A)

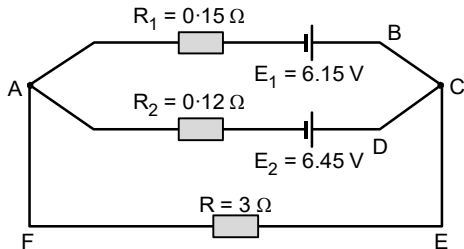


Fig. 1.77: Given network.

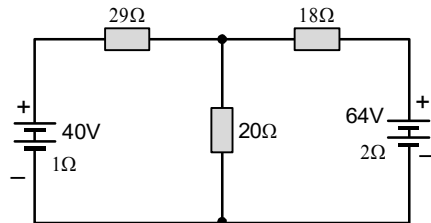


Fig.1.78: Given network

2. Determine the branch currents by superposition theorem in the network shown in fig.1.78.
(Ans.0.2A, 1.5A, 1.7A)
3. Determine current through 16Ω resistor in the following network (fig.1.79) using superposition theorem.
(Ans.1.2A from B to A)

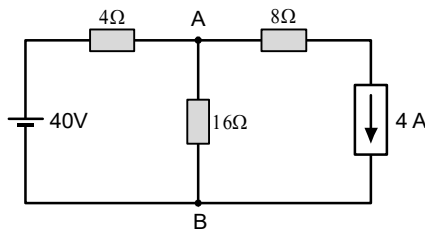


Fig.1.79: Given network

1.21. THEVENIN'S THEOREM

Thevenin's theorem states that :

The current flowing through a resistor connected across any two terminals of a network can be determined by converting the remaining network into a voltage source of emf, E_{th} and internal resistance, R_{th} .

Where, E_{th} = The open circuit voltage across the two terminals of the given branch, called Thevenin voltage.

R_{th} = The equivalent resistance of the network across the given terminals with all other sources replaced by their internal resistances, called Thevenin resistance.

For illustration, consider a circuit shown in fig.1.80. To determine the current through load resistance R_L , proceed with the following steps :

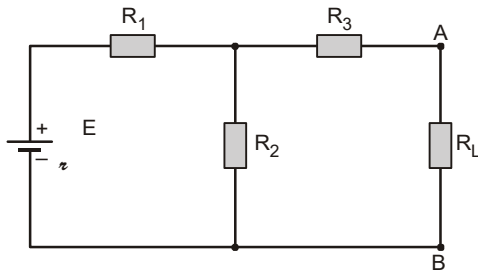
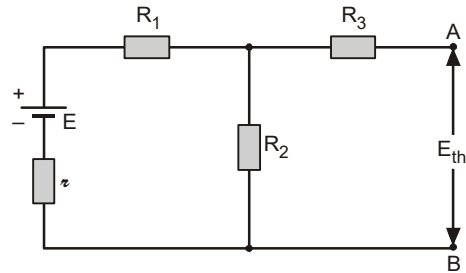


Fig.1.80: Given circuit.

Fig.1.81: Circuit to determine E_{th}

- Remove the resistance R_L in which current is to be determined, thus creating an open circuit between terminals A and B as shown in fig.1.81.
- Determine the open circuit voltage (Thevenin voltage E_{th}) between the terminals A and B i.e.,

$$\text{Voltage across } R_2 = I_2 R_2$$

$$E_{th} = \left(\frac{E}{r + R_1 + R_2} \right) R_2$$

- Replace the source (battery) by its internal resistance and determine the resistance R_{th} (Thevenin resistance) of the network as seen from the terminals A and B as shown in fig.1.82.

$$R_{th} = \frac{(r + R_1) R_2}{(r + R_1) + R_2} + R_3$$

- Replace the entire network by a single Thevenin voltage source having an e.m.f. E_{th} and internal resistance R_{th} as shown in fig.1.83.

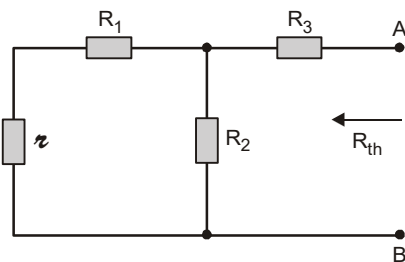
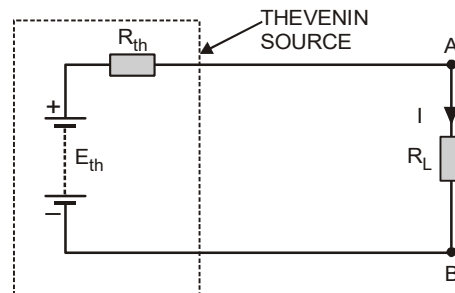
Fig.1.82: Circuit to determine R_{th} 

Fig.1.83: Thevenin circuit.

- Connect the load resistance R_L back to its terminals A and B from where it was removed.
- Determine the current flowing through the load resistance R_L by applying ohm's law i.e.

$$I = \frac{E_{th}}{R_{th} + R_L}$$

Example 1.18. Determine current through 12Ω resistor connected across terminals A - B in the electric circuit shown in fig.1.84 using Thevenin's Theorem.

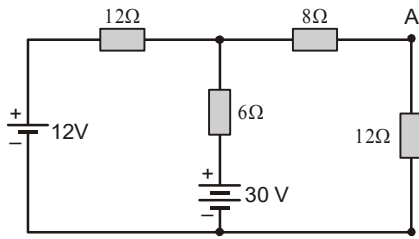


Fig.1.84: Given circuit.

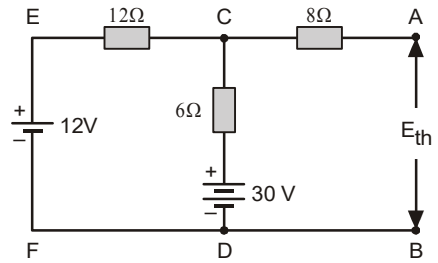


Fig.1.85: Circuit to determine E_{th}

Solution : To determine E_{th} , open the terminals A and B as shown in fig.1.85.

Current in the circuit $DCEFD$,

$$I = \frac{30 - 12}{12 + 6} = \frac{18}{18} = 1\text{A}$$

Open circuit voltage across the terminals AB , i.e.

$$E_{th} = 30 - 1 \times 6 = 24\text{ V}$$

Thevenin resistance R_{th} of the network when viewed through the terminals A and B with all voltage sources are being short circuited as shown in fig.1.86.

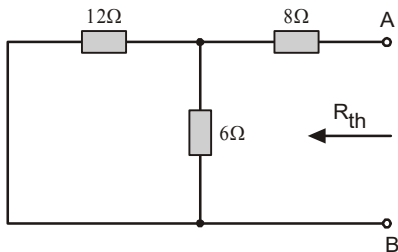


Fig.1.86: Circuit to determine R_{th}

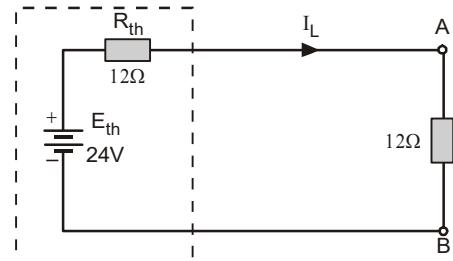


Fig.1.87: Thevenin circuit.

$$R_{th} = 8 + (6 \parallel 12) = 8 + \frac{6 \times 12}{6 + 12} = 12\ \Omega$$

The thevenin network is shown in fig.1.87.

Current through 12Ω resistor connected across terminal AB .

$$I_L = \frac{E_{th}}{R_{th} + R_L} = \frac{24}{12 + 12} = 1\text{ A (Ans.)}$$

Example 1.19. Find current I using thevenin's theorem in the circuit shown in fig.1.88.

Solution : To determine thevenin voltage or open circuit voltage across AB , remove 4Ω resistor connected across AB as shown in fig.1.89.

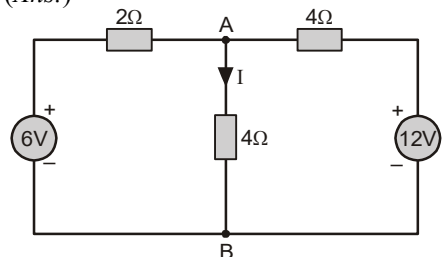


Fig.1.88: Given circuit.

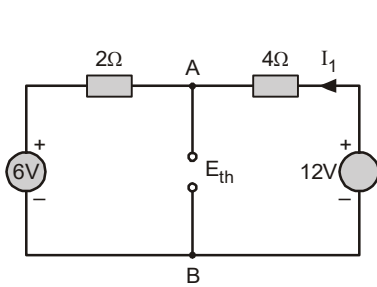


Fig.1.89: Circuit to determine E_{th} **Fig. 1.90:** Circuit to determine R_{th}

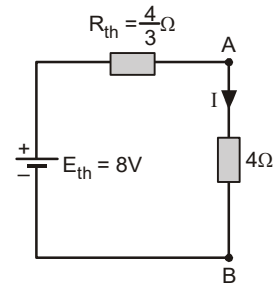
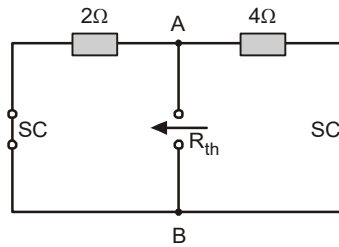


Fig.1.91: Thevenin circuit

$$I_1 = \frac{12 - 6}{2 + 4} = \frac{6}{6} = 1 \text{ A}$$

Open circuit voltage across AB i.e. thevenin voltage,

$$E_{th} = 12 - 4 \times 1 = 8 \text{ V}$$

To determine thevenin resistance looking into terminal AB , replace the voltage source by their internal resistance i.e. short circuit as shown in fig.1.90.

$$R_{th} = 2 \parallel 4 = \frac{2 \times 4}{2 + 4} = \frac{4}{3} \Omega$$

The thevenin equivalent circuit is shown in fig.1.91.

Current in 4Ω resistor connected across AB ,

$$I = \frac{E_{th}}{R_{th} + R_L} = \frac{8}{\frac{4}{3} + 4} = \frac{8}{\frac{16}{3}} = \frac{8}{16} \times 3 = 1.5 \text{ A (Ans.)}$$

Example 1.20. Find Thevenin's equivalent circuit at terminals BC of fig 1.92. Hence determine current through the resistor $R = 1\Omega$.

Solution : To determine thevenin equivalent resistance of given circuit with reference to terminals BC , replace voltage sources by their internal resistance as shown in fig.1.93.

$$R_{th} = [(11 + 1) \parallel 2] \parallel [(2 + 8) \parallel 4]$$

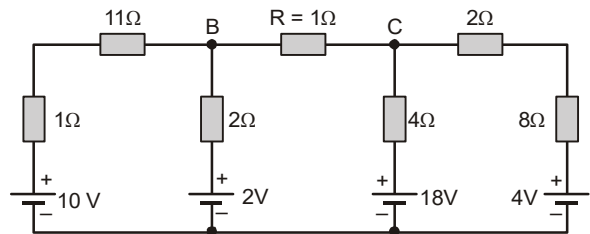
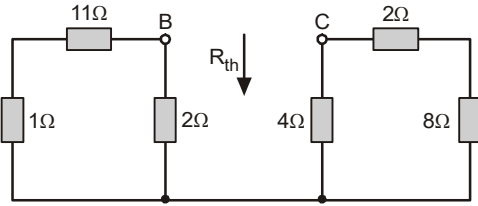
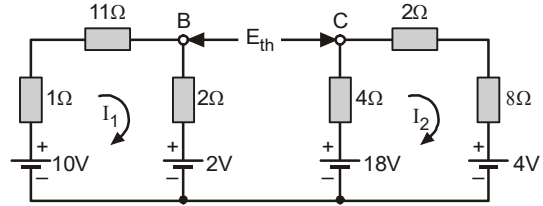


Fig.1.92: Given circuit

$$= \left[\frac{2 \times 12}{2 + 12} \right] \parallel \left[\frac{10 \times 4}{10 + 4} \right] = \left(\frac{12}{7} \right) \parallel \left(\frac{20}{7} \right) = \frac{15}{14} = 1.0714 \Omega$$

Fig.1.93: Circuit to determine R_{th} Fig.1.94: Circuit to determine E_{th}

To determine open circuit voltage across the terminals BC (i.e. thevenin voltage), redraw the circuit as shown in fig.1.94.

$$\text{Current in the loop of terminal } B, I_1 = \frac{10-2}{11+1+2} = \frac{8}{14} = \frac{4}{7} \text{ A}$$

$$\text{Voltage at point } B, V_B = 10 - \frac{4}{7}(1+11) = \frac{22}{7} \text{ V}$$

$$\text{Current in the loop of terminal } C, I_2 = \frac{18-4}{4+2+8} = \frac{14}{14} = 1 \text{ A}$$

$$\text{Voltage at point } C, V_C = 18 - 4 \times 1 = 14 \text{ V}$$

$$\text{Thevenin voltage, } E_{th} = V_{CB} = V_C - V_B = \left(14 - \frac{22}{7}\right) = \frac{76}{7} = 10.857 \text{ V}$$

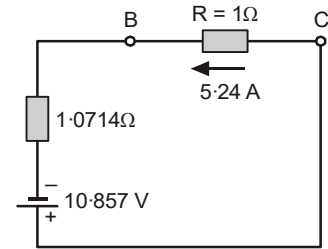


Fig.1.95: Thevenin circuit.

The Thevenin's equivalent circuit is shown in fig.1.95.

$$\text{Current through resistor } R \text{ of } 1 \Omega, I = \frac{E_{th}}{R_{th} + R} = \frac{10.857}{1.0714 + 1} = 5.24 \text{ A (Ans.)}$$

Example 1.21. A bridge network $ABCD$ is arranged as follows : resistance between terminal $A - B$; $B - C$; $C - D$; $D - A$ and $B - D$ are 10, 30, 15, 20 and 40 ohm respectively. A 2 volt battery of negligible internal resistance is connected between terminals A and C . Determine the value and direction of the current in 40 ohm resistor by applying Thevenin theorem.

Solution : The bridge circuit is shown in fig.1.96. To determine Thevenin voltage E_{th} , remove 40 ohm resistor. Then the circuit is reduced to as shown in fig.1.97.

$$\text{Current in branch } ABC, I_1 = \frac{2}{10+30} = 0.05 \text{ A}$$

$$\text{Current in branch } ADC, I_2 = \frac{2}{20+15} = 0.05714 \text{ A}$$

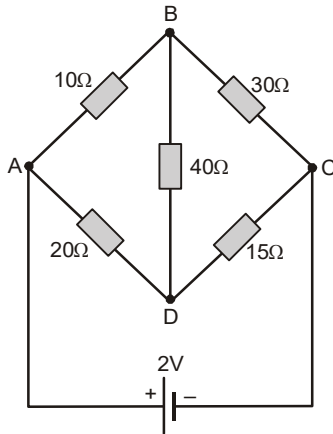


Fig.1.96: Given circuit as per data.


Voltage at point B , $V_B = 2 - 0.05 \times 10 = 1.5 \text{ V}$

Voltage at point D , $V_D = 2 - 0.05714 \times 20 = 0.857 \text{ V}$


Potential difference across terminal B and D i.e.

Thevenin voltage, $E_{th} = 1.5 - 0.857 = 0.643 \text{ V}$

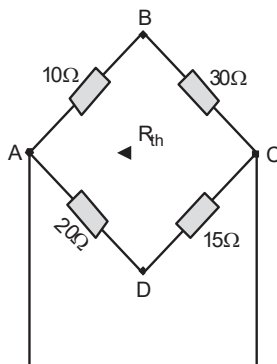To determine resistance R_{th} looking between terminals B and D , the source is replaced by its internal resistance (zero in this case) as shown in fig.1.98(a). The circuit is further simplified as shown in fig.1.98(b).



(a) Source is replaced

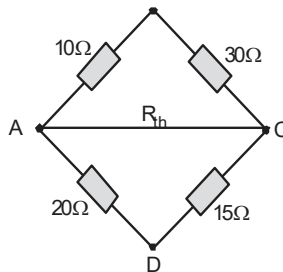

(b) Simplified circuit

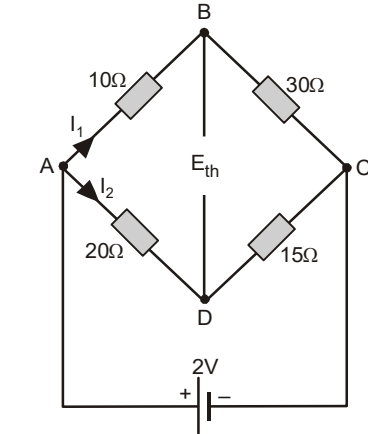


Fig.1.97: Circuit to determine E_{th}

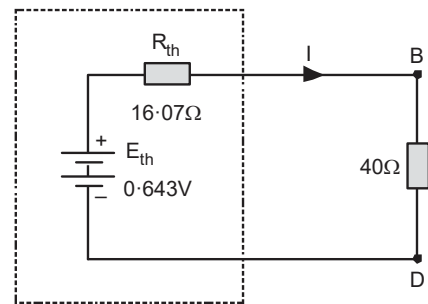


FIG.1.99: Thevenin circuit.

Fig.1.98: Circuit to determine R_{th}

Fig.1.99: Thevenin circuit.

A little thought will reveal that the resistance across terminal B and D i.e. Thevenin resistance,

$$R_{th} = \frac{10 \times 30}{10 + 30} + \frac{20 \times 15}{20 + 15} = 7.5 + 8.57 = 16.07 \Omega$$

Thevenised circuit is shown in fig.1.99.

$$\therefore \text{Current in } 40 \text{ ohm resistor. } I = \frac{0.643}{16.07 + 40} = 11.467 \text{ mA (Ans.)}$$

Example 1.22. State Thevenin's theorem and calculate current in a 1000Ω resistor connected between terminals A and B , as shown in fig.1.100.

Solution : To determine open circuit voltage across AB i.e. E_{th} , consider fig.1.101.

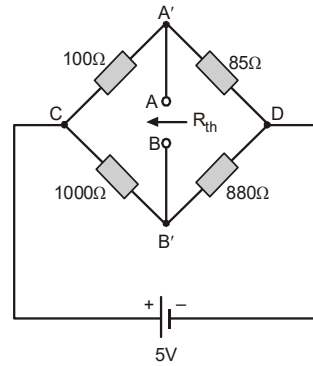
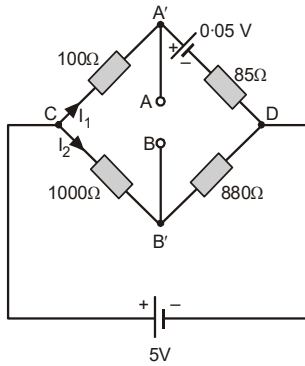
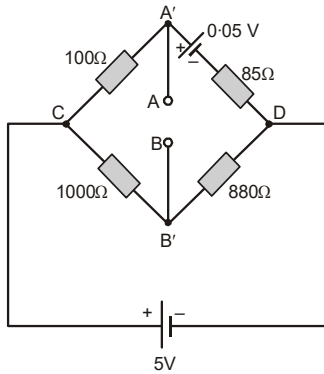


Fig.1.100: Given circuit. **Fig.1.101:** Circuit to determine E_{th} **Fig.1.102(a):** Circuit to determine R_{th}

$$\text{Current, } I_1 = \frac{5 - 0.05}{100 + 85} = \frac{4.95}{185} \text{ A}$$

$$\text{Potential at point A, } V_A = V_C - I_1 \times 100 = 5 - \frac{4.95}{185} \times 100 = 2.324 \text{ V}$$

$$\text{Current, } I_2 = \frac{5}{1000 + 880} = \frac{5}{1880} \text{ A}$$

$$\text{Potential at point B, } V_B = V_C - I_2 \times 1000 = 5 - \frac{5}{1880} \times 1000 = 2.340 \text{ V}$$

Terminal B is at higher potential than terminal A .

$$\text{Thevenin voltage, } E_{th} = V_{BA} = 2.340 - 2.324 = 0.016 \text{ V}$$

Replacing the batteries by their internal resistance (i.e. zero resistance), the network becomes as shown in fig.1.102(a). The network can further be simplified as shown in fig.1.102(b).

$$\begin{aligned} R_{th} &= R_{AB} = 100 \parallel 85 + 1000 \parallel 880 \\ &= \frac{100 \times 85}{100 + 85} + \frac{1000 \times 880}{1000 + 880} \end{aligned}$$

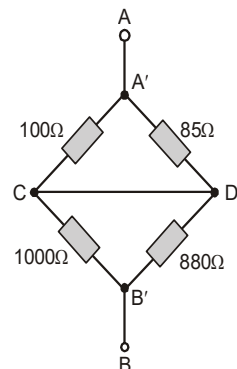


Fig.1.102(b): Simplified circuit.

$$= 45.946 + 468.085$$

$$= 514.031 \, \Omega$$

Current in $1000 \, \Omega$ resistor when connected across AB ,

$$I_L = \frac{E_{th}}{R_{th} + R_L} = \frac{0.016}{514.031 + 1000}$$

$$= \frac{0.016}{1514.031} = 10.6344 \, \mu\text{A} \text{ (Ans.)}$$

The current flows from terminal B to A .

Example 1.23. Find the thevenin's equivalent circuit for terminal pair AB of the network shown in fig.1.104.

Solution : For determining the Thevenin's equivalent resistance R_{th} of the circuit with reference to terminals AB the voltage source is short-circuited and current source is open-circuited, as shown in fig.1.105.

$$R_{th} = 6 + (15 \parallel 10) + 4 = 6 + \frac{15 \times 10}{15 + 10} + 4 = 16 \, \Omega$$

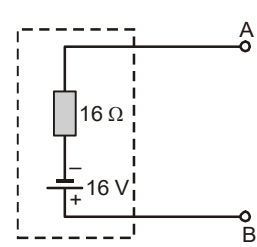
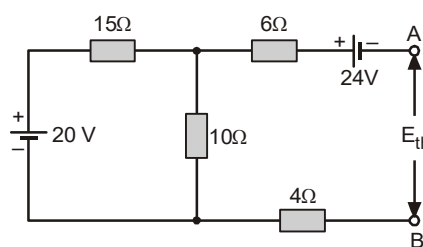
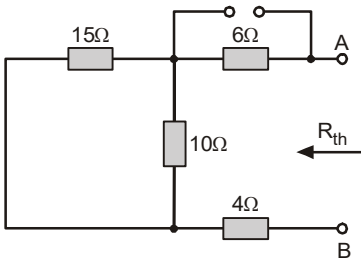


Fig.1.105: Circuit to determine R_{th} **Fig.1.106:** Circuit to determine E_{th} **Fig.1.107:** Thevenin equivalent

Converting current source of 4A connected across 6Ω resistor source into the equivalent voltage source, the circuit becomes as shown in fig.1.106.

Considering terminal A and B open circuited there is no current through resistor of $4 \, \Omega$ and $6 \, \Omega$ (hence no voltage drop occurs across them),

$$\text{Voltage across } 10 \, \Omega \text{ resistor} = \frac{20}{15 + 10} \times 10 = 8 \, \text{V}$$

$$\text{Thevenin voltage across } AB, E_{th} = 8 - 24 = -16 \, \text{V}$$

Thevenin's equivalent circuit is shown in fig.1.107.

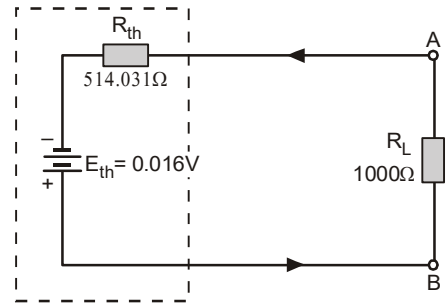


Fig.1.103: Thevenin circuit.

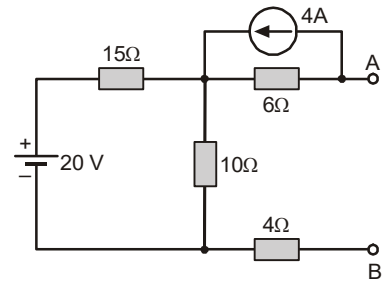


Fig.1.104: Given circuit.

PRACTICE EXERCISE

1. Find current I using thevenin's theorem in the circuit shown in fig.1.108

(Ans. 2.4A).

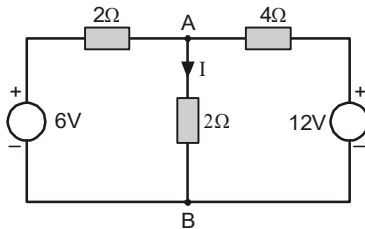


Fig.1.108: Given circuit

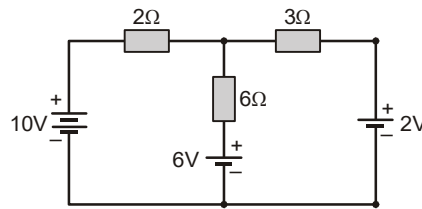


Fig.1.109: Given circuit

2. Using thevenin theorem find the current in 3Ω resistor in Fig.1.109. (Ans. 1.556A)
 3. Using Mesh equation method, find current in the resistance R_1 of the network shown in Fig.1.110. (Ans. 0.625A)
 4. By applying thevenin theorem, find the current in 15Ω resistor of the network shown in fig.1.111. (Ans. 3.5A)

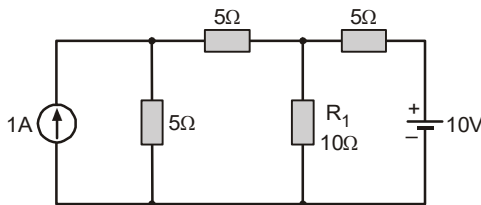


Fig.1.110: Given circuit

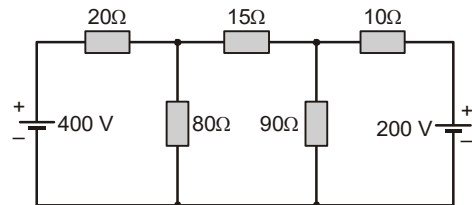


Fig.1.111: Given circuit

5. Find the thevenin's equivalent circuit for terminal pair AB of the network shown in fig.1.112. (Ans. $E_{th} = -6V$, $R_{th} = 9\Omega$)

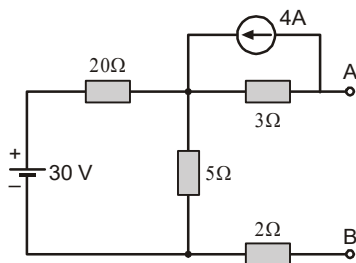


Fig.1.112: Given circuit

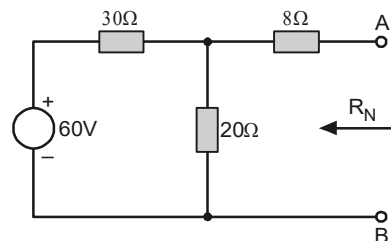


Fig.1.113: Given circuit

6. Draw the thevenin's equivalent circuit across AB, and determine current flowing through $12W$ resistor for the network shown in fig.1.113. (Ans. 4.533 A)

1.22. NORTON'S THEOREM

Norton's theorem states that :

The current flowing through a resistor connected across any two terminals of a network can be determined by converting the whole network into a current source having a current output of I_N in parallel with a resistance R_N .

Where, I_N = The short circuit current supplied by the source that would flow between the two selected terminals when these are short circuited, generally called Norton's current.

R_N = The equivalent resistance of the network across the two terminals with all other e.m.f. sources replaced by their internal resistances and current sources replaced by open circuit, generally called Norton's resistance.

Steps to determine Norton's equivalent circuit.

- Short circuit the terminals across which the load resistor is connected and calculate the current which would flow between them. This is the Norton current I_N .
- Redraw the network replacing each voltage source by a short circuit in series with its internal resistance if any and each current source by an open circuit in parallel with its internal resistance.
- Determine the resistance R_N of the network as seen from the network terminals. (Its value is the same as that of R_{th}).

1.23. CONVERSION OF THEVENIN'S EQUIVALENT INTO NORTON'S EQUIVALENT AND VICE-VERSA

A Thevenin's equivalent can be converted into its Norton's equivalent and vice-versa. According to statement, Norton's current source equals the current I_{SC} or I_N which flows across the terminals A and B when they are short circuited.

Hence
$$I_{SC} = \frac{E_{th}}{R_{th}} \quad \dots(i)$$

Like wise a Norton's circuit can be converted into its Thevenin's equivalent. The Thevenin's equivalent source V_{OC} or E_{th} is the voltage on open circuit and is given as

$$V_{OC} \text{ or } E_{th} = I_{SC} R_{th} \quad \dots(ii)$$

Each theorem is dual of the other.

Example 1.24. For the circuit shown in fig.1.114, obtain Norton current and equivalent resistance seen from 'AB'.

Solution : Equivalent resistance of the network with reference to terminals A and B , as shown in fig.1.115.

$$R_N = (30 \parallel 20) + 8 = \frac{30 \times 20}{30 + 20} + 8 = 12 + 8 = 20 \, \Omega \text{ (Ans.)}$$

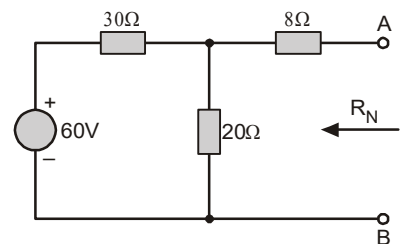


Fig.1.114: Given circuit.

The current supplied by 60 V source, when terminals A and B are short circuited as shown in fig.1.116.

$$I = \frac{60}{30 + (8 \parallel 20)} = \frac{60}{30 + \frac{8 \times 20}{8 + 20}} = \frac{42}{25} \text{ A}$$

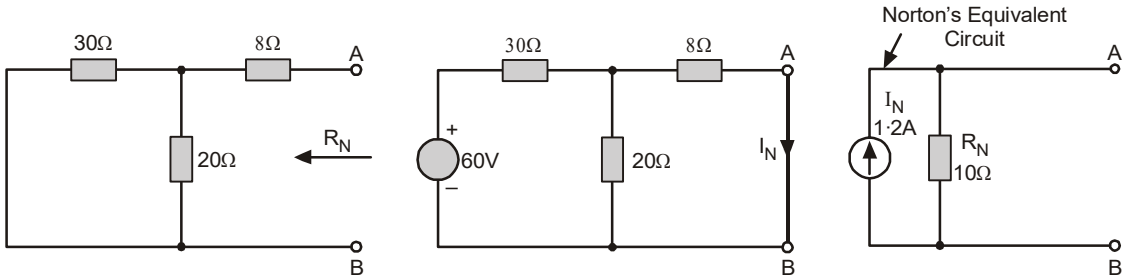


Fig.1.115: Circuit to determine R_N **Fig.1.116:** Circuit to determine I_N **Fig.1.117:** Norton's circuit.

Norton's current, I_N i.e., the current from terminal A to B when these are short circuited as shown in fig.1.117.

$$I_N = \frac{20}{20+8} \times I = \frac{20}{28} \times \frac{42}{25} = 1.2 \text{ A (Ans.)}$$

The Norton's equivalent circuit is shown in fig.1.117.

Example 1.25. Find the Norton's equivalent circuit, as seen by R_L in the circuit shown in fig.1.118.

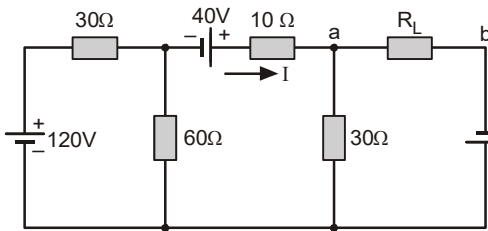


Fig.1.118: Given circuit.

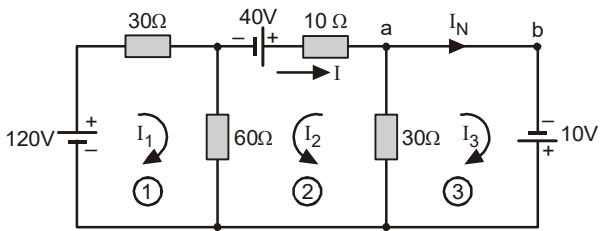


Fig.1.119: Circuit to determine I_N

Solution : Let the Norton's current be I_N , as shown in fig.1.119.

Applying *KVL* in Loop (1), we get,

$$30I_1 + 60(I_1 - I_2) = 120$$

$$\text{or} \quad 90I_1 - 60I_2 = 120$$

$$3I_1 - 2I_2 = 4 \quad \dots(i)$$

Applying *KVL* in Loop (2), we get,

$$60(I_2 - I_1) + 10I_2 + 30(I_2 - I_3) = 40$$

$$\text{or} \quad -60I_1 + 100I_2 - 30I_3 = 40$$

$$\dots(ii)$$

$$\text{or} \quad -6I_1 + 10I_2 - 3I_3 = 4$$

Applying *KVL* in Loop (3), we get,

$$30 (I_3 - I_2) = 10$$

$$\text{or} \quad -30I_2 + 30I_3 = 10 \quad \text{or} \quad -3I_2 + 3I_3 = 1 \quad \dots(iii)$$

Solving eqn. (ii) and (iii), we get,

$$-6I_1 + 10I_2 - 1 - 3I_2 = 4 \quad (\text{since } 3I_3 = 1 + 3I_2)$$

$$6I_1 + 7I_2 = 5 \quad \dots(iv)$$

Multiplying eqn. (i) by 2 and adding eqn. (iv), we get

$$I_2 = \frac{13}{3} \text{ A}$$

$$\text{from eqn. (iii),} \quad I_3 = \frac{1}{3} (1 + 3I_2) = \frac{1}{3} \left(1 + 3 \times \frac{13}{3} \right) = \frac{14}{3} \text{ A}$$

$$\therefore \quad \text{Norton's current } I_N = I_3 = \frac{14}{3} \text{ A}$$

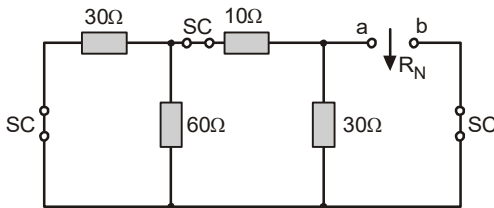


Fig.1.120: Circuit to determine R_N

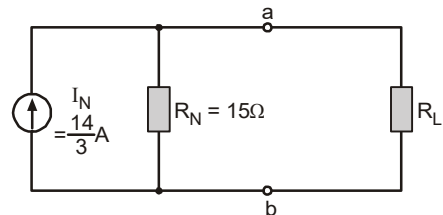


Fig.1.121: Norton's circuit

Considering fig.1.120.

Norton's Resistance R_N

$$R_N = [(30 \parallel 60) + 10] \parallel 30 = \left(\frac{30 \times 60}{30 + 60} + 10 \right) \parallel 30 = (20 + 10) \parallel 30 = \frac{30 \times 30}{30 + 30} = 15 \Omega$$

Norton's equivalent circuit is shown in fig.1.121.

Example 1.26. For the network shown in fig.1.122 draw a Norton's equivalent circuit and determine the current flowing through 15Ω resistor.

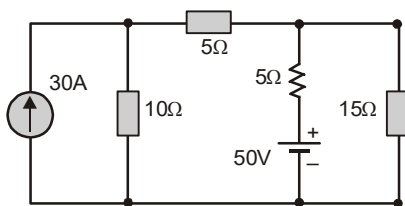


Fig.1.122: Given circuit

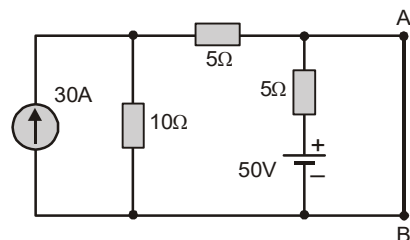


Fig.1.123: Circuit to determine I_N

Solution : To determine I_N , the 15Ω resistor is removed and terminals

A and B are short circuited as shown in fig.1.123. Since, there are two sources due to which current will flow between terminal A and B , therefore applying superposition theorem

$$I_N = I_1 + I_2$$

- (i) Considering only current source, the circuit will be reduced as shown in fig.1.124.

$$\text{Current } I_1 = 30 \times \frac{10}{10+5} = 20\text{A}$$

- (ii) Considering only voltage source, The circuit will be as shown in fig.1.125.

$$I_2 = \frac{50}{5} = 10\text{A}$$

According to superposition theorem :

$$\text{Norton current, } I_N = I_1 + I_2 = 20 + 10 = \mathbf{30\text{ A (Ans.)}}$$

Now replacing current source with open circuit and voltage source with short circuit, the circuit will reduce to as shown in fig.1.126.

Looking between the terminals A and B , the Norton resistance,

$$R_N = \frac{5 \times (5 + 10)}{5 + (5 + 10)} = \mathbf{3.75\Omega\text{ (Ans.)}}$$

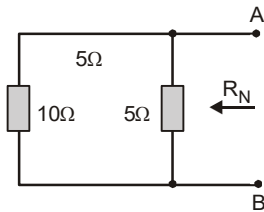


Fig.1.126: Circuit to determine R_N

The Norton's equivalent circuit is shown in fig.1.127.

Current flowing through 15Ω resistor,

$$I = 30 \times \frac{3.75}{3.75 + 15} = \mathbf{6\text{ A (Ans.)}}$$

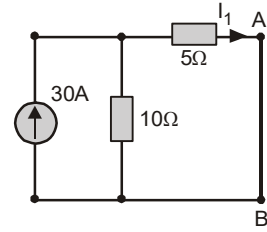


Fig.1.124: Considering only current source

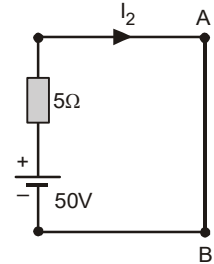


Fig.1.125: Considering only voltage source.

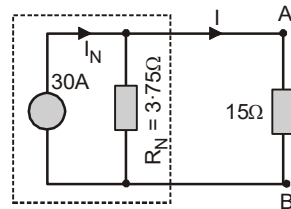


Fig.1.127: Norton's circuit.

PRACTICE EXERCISE

Solve all the problems mentioned in the previous exercise by using Norton's Theorem.

1.24. TIME DOMAIN ANALYSIS OF *RL* AND *RC* CIRCUITS

To analyse *RL* and *RC* circuits under time domain, the *RL* and *RC* circuits are opened and closed and their effects are analysed.

1.25. ANALYSIS OF *RL* CIRCUITS (*Closing and opening of *RL* circuit*)

A coil containing resistance $R \, \Omega$ and inductance L henry is shown in fig. 1.128. When the circuit is closed through switch S , the current increases gradually and takes some time to attain its final value. The reason for the delay is that when current increases to attain its final value, an e.m.f. (self-induced e.m.f.) is induced in the inductance of the coil which opposes the increase in current.

Let at any instant, the current in the circuit be i ampere and is increasing at the rate of di/dt . Then applied voltage.

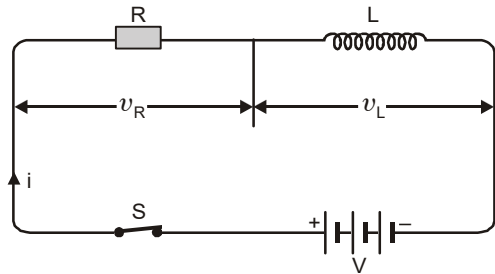


Fig.1.128: Closing of *RL* circuit

$$V = v_R + v_L = iR + L \frac{di}{dt} \left(v_L = e_L = L \frac{di}{dt} \right)$$

After some time, the current (i) obtains its final value (I) and rate of change of current (di/dt) becomes zero. Then

$$V = IR + 0 \text{ or } I = V/R.$$

Similarly, when an inductive circuit (or coil) is opened, the current does not attain its zero value instantaneously but it falls gradually.

Thus, the role of an inductance, in a d.c. circuit to delay the change (rise or fall) in current. Its behaviour is just analogous to inertia in mechanics. The delay in change of current, in either case, depends upon the value of R and L as explained in the next articles.

1.26. RISE OF CURRENT IN AN INDUCTIVE CIRCUIT

Consider an inductive circuit shown in fig. 1.128. At any instant, let the value of current be i ampere which is changing at the rate of di/dt , then

$$V = iR + L \frac{di}{dt}$$

$$\text{or} \quad (V - iR) = L \frac{di}{dt}$$

$$\text{or} \quad \frac{di}{(V - iR)} = \frac{dt}{L}$$

Multiplying both sides by $-R$ and then integrating, we get,

$$\int \frac{-R di}{(V - iR)} = -\frac{R}{L} \int dt$$

$$\text{or} \quad \log_e (V - i R) = -\frac{R}{L}t + K \quad \dots(i)$$

where K is a constant of integration whose value can be determined from the initial known conditions, i.e. at $t = 0$; $i = 0$. Substituting these values in the exp. (i), we get,

$$\log_e V = K$$

\therefore Expression (i) becomes ;

$$\log_e (V - i R) = -\frac{R}{L}t + \log_e V$$

$$\text{or} \quad \log_e \frac{V - i R}{V} = -\frac{R}{L}t$$

$$\text{or} \quad \frac{V - i R}{V} = e^{-Rt/L} \quad \text{or} \quad V - i R = V e^{-Rt/L}$$

$$\text{or} \quad i = \frac{V}{R} (1 - e^{-Rt/L})$$

Now, V/R represents the final value of the steady current I attained by the circuit.

$$\therefore \quad i = I (1 - e^{-Rt/L}) \quad \dots(ii)$$

$$\text{or} \quad i = I (1 - e^{-t/\lambda})$$

where λ is called time constant of the circuit.

Time constant

Expression (ii) shows the rise of current w.r.t. time t . The exponent of e is Rt/L . The quantity L/R must have the dimensions of time so that exponent of e (i.e. Rt/L) is a number.

The quantity L/R is called the *time constant* of the circuit and effects the rise of current in the circuit. It is represented by λ .

$$\therefore \quad \text{Time constant, } \lambda = L/R \text{ second}$$

If time interval, $t = \lambda$ (or L/R), then

$$i = I (1 - e^{-1}) = 0.632 I \quad (Rt/L = R \times L/R \times R = 1)$$

Hence, the time required for the current in an $R - L$ circuit, to reach 0.632 times of its steady value (I) while rising is called the **time constant** of the circuit.

1.27. DECAY OF CURRENT IN AN INDUCTIVE CIRCUIT

An inductive circuit containing resistance R and inductance L in series is shown in fig. 1.129. When switch is thrown to position 1, the current in the circuit starts rising and attains its final value $I (= V/R)$ after some time. If now, the switch is thrown to position 2, the current in the circuit does not cease at once but gradually reduces to zero.

Let at any instant (during decay), the current in the circuit be i ampere and is decreasing at the rate of di/dt , then

$$0 = iR + L \frac{di}{dt}$$

or
$$\frac{di}{i} = -\frac{R}{L} dt$$

Integrating both sides, we get,

$$\log_e i = -\frac{R}{L}t + K$$

...(i) **Fig.1.129:** Opening and short circuiting of RL circuit

where K is constant of integration whose value can be determined from the initial conditions, i.e. at $t = 0$; $i = I (= V/R)$. Substituting these values in exp. (i), we get,

$$\log_e I = 0 + K \text{ or } K = \log_e I$$

\therefore Expression (i) becomes ;

$$\log_e i = -\frac{R}{L}t + \log_e I$$

or
$$\log_e \frac{i}{I} = -\frac{R}{L}t \text{ or } \frac{i}{I} = e^{-Rt/L}$$

or
$$i = I e^{-Rt/L}$$

$$i = I e^{-t/\lambda}$$

...(ii)

where $\lambda (= L/R)$ is called time constant of the circuit.


Time constant

The quantity L/R is called the *time constant* of the circuit and affects the fall of current in the circuit. It is represented by λ .


\therefore Time constant, $\lambda = L/R$ second

$$i = I e^{-1} = 0.368 I$$

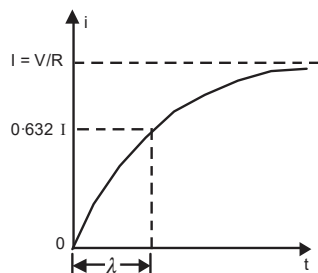Hence, the time required for the current, in an $R-L$ circuit, to reach 0.368 times of its steady value (I) while decaying is called the **time constant** of the circuit.



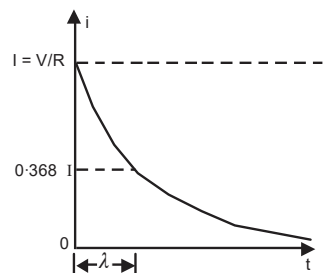(a) Graph between i and t when RL circuit is conned to dc source



(b) Graph between i and t when RL circuit is disconnected from source and short circuited

Fig. 1.130: Graph between current and time

Fig. 1.130 (a) shows a graph between current and time in an $R - L$ circuit, when it is connected across a d.c. source. The current rises in the circuit following exponential law. Whereas, fig.1.130 (b) shows a graph between current and time in an $R - L$ circuit, when it is short circuited after attaining its final steady value of current. The current decays in the circuit following exponential law.

Example 1.27. The resistance and inductance of a coil are 4Ω and 0.15 mH respectively. What potential difference exists at the terminals of the solenoid at the instant when the current is 1.5 A , but increasing at the rate of $10000 \text{ A per second}$?

Solution : Voltage across the solenoid, $E = IR + L \frac{di}{dt}$

where, $I = 1.5 \text{ A}$; $R = 4 \Omega$; $L = 0.5 \times 10^{-3} \text{ H}$; $di/dt = 10000 \text{ A/s}$;

$$\therefore E = 1.5 \times 4 + 0.15 \times 10^{-3} \times 10000 = 7.5 \text{ V (Ans.)}$$

Example 1.28. A coil having a resistance of 10Ω and inductance of 6 H is connected to a constant supply voltage of 100 V . Find (i) the rate of change of current at the instant of closing the switch ; (ii) final steady value ; (iii) time constant of the circuit and (iv) the time taken for the current to reach a value of 4 A .

Solution : We know that $V = iR + L \frac{di}{dt}$

(i) At the time of closing the switch, $i = 0$

$$\therefore 100 = 0 + 6 \frac{di}{dt} \quad \text{or} \quad \frac{di}{dt} = \frac{100}{6} = 16.67 \text{ A/s (Ans.)}$$

(ii) Final steady value, $I = V/R = 100/10 = 10 \text{ A (Ans.)}$

(iii) Time constant, $\lambda = L/R = 12/20 = 0.6 \text{ (Ans.)}$

(iv) Now, $i = I(1 - e^{-t/\lambda})$

$$\text{or} \quad 4 = 10(1 - e^{-t/0.6}) \quad \text{or} \quad 0.4 = 1 - e^{-t/0.6}$$

$$\text{or} \quad e^{-t/0.6} = 0.6 \quad \text{or} \quad e^{t/0.6} = 1/0.6 = 1.67$$

$$\text{or} \quad (t/0.6) \log_e e = \log_e 1.67 \quad \text{or} \quad t/0.6 = \log_e 1.67$$

$$\text{or} \quad t = 0.6 \times 0.5128 = 0.3077 \text{ s (Ans.)}$$

Example 1.29. Consider a series $R - L$ circuit connected to a battery source of 5 volt . If $R = 5 \text{ ohm}$ and $L = 5 \text{ henry}$, find the current $i(t)$ through the inductance. Find the voltage across resistance and inductance separately at the time of switching the supply and when sufficient time has elapsed after switching the source.

Solution : The current flowing through the circuit is given by the expression,

$$i(t) = \frac{V}{R} (1 - e^{-Rt/L})$$

where, $V = 5 \text{ V}$; $R = 5 \Omega$ and $L = 5 \text{ H}$.

$$\therefore i(t) = \frac{5}{5}(1 - e^{-t}) = 1 - e^{-t}$$

(i) At the time of switching, $t = 0$

$$\therefore i(t) = 1 - e^{-0} = 0$$

Now, $V = iR + L \frac{di}{dt}$

$$\therefore \text{Voltage across resistor, } iR = 0 \text{ V (Ans.)}$$

$$\text{Voltage across inductor, } L \frac{di}{dt} = 5 \text{ V (Ans.)}$$

(ii) When the sufficient time is elapsed i.e. $t \rightarrow \infty$

$$i(t) = 1 - e^{-\infty} = 1$$

$$\therefore \text{Voltage across resistor, } iR = 5 \text{ V (Ans.)}$$

$$\text{Voltage across inductor, } L \frac{di}{dt} = 0 \text{ V (Ans.)}$$

Example 1.30. Consider the series $R - L$ circuit connected to a battery and a switch as shown in fig. 1.131. Switch S_1 closes at $t = 2$ second ; switch S_2 closes at $t = 5$ second. (i) Find the current $i(t)$ in the resistance R ; (ii) Plot the current $i(t)$ for $0 \leq t \leq 10$ second to the scale. Assume R/L equal to 100.

Solution : When switch S_1 is closed and switch S_2 remains open the circuit becomes as shown in fig.1.132.

The switch is closed after 2 seconds, therefore upto 2 seconds no current flows (OA) through the circuit.

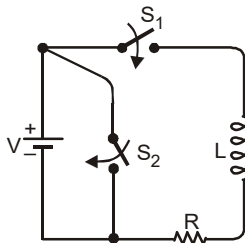


Fig.1.131: Given Circuit

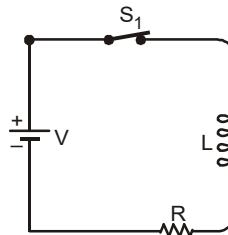


Fig. 1.132: When S_1 is closed and S_2 is opened

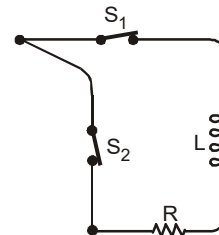


Fig. 1.133: When S_2 is closed and S_1 is opened

After 2 second, when switch S_1 is closed current starts rising exponentially (AB) given by the equation ;

$$i(t) = \frac{V}{R} (1 - e^{-Rt/L}) = \frac{V}{R} (1 - e^{-100t})$$

After $t = 5$ seconds, the switch S_2 is closed and the circuit becomes as shown in fig.1.133. The current starts decaying following the exponential law (BC) and is given by the equation ;

$$i(t) = \frac{V}{R} \left(e^{-Rt/L} \right) = \frac{V}{R} \left(e^{-100t} \right)$$

A graph between current and time is shown in fig.1.134.

Example 1.31. A coil having $L = 5 \text{ H}$ and $R = 10 \text{ } \Omega$ is connected to a constant 180 V supply source. How long does it take the voltage across the resistor to reach 90 V ?

Solution :

$$i = \frac{V}{R} \left(1 - e^{-t/\lambda} \right)$$

or

$$i R = V \left(1 - e^{-t/\lambda} \right)$$

where,

$$i R = 90 \text{ V} ; V = 180 \text{ V} ; \lambda = L/R = 5/10 = 0.5$$

$$\therefore 90 = 180 \left(1 - e^{-t/0.5} \right)$$

$$\text{or } 0.5 = 1 - e^{-t/0.5} \text{ or } e^{-t/0.5} = 0.5$$

$$\text{or } e^{t/0.5} = 1/0.5 \text{ or } (t/0.5) \log_e e = \log_e 2$$

$$\text{or } t = 0.5 \times 0.6931 = 0.3466 \text{ s (Ans.)}$$

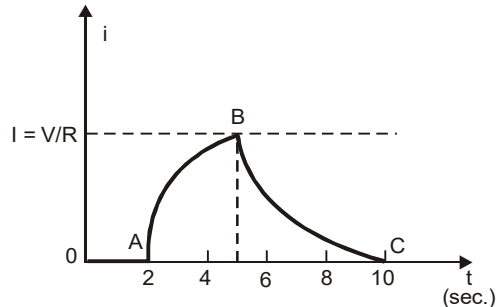


Fig.1.134 : Graph between i & t

PRACTICE EXERCISE

1. The resistance and inductance of a coil are $3 \text{ } \Omega$ and 0.1 mH respectively. What potential difference exists at the terminals of the solenoid at the instant when the current is 1 A , but increasing at the rate of $10000 \text{ A per second}$?
2. A coil having a resistance of $20 \text{ } \Omega$ and inductance of 12 H is connected to a constant supply voltage of 100 V . Find (i) the rate of change of current at the instant of closing the switch ; (ii) final steady value ; (iii) time constant of the circuit and (iv) the time taken for the current to reach a value of 4 A (Ans, 8.33 A/s , 5 A , 0.6 , 0.9656 s)
3. Consider a series $R - L$ circuit connected to a battery source of 1 volt . If $R = 1 \text{ ohm}$ and $L = 1 \text{ henry}$, find the current $i(t)$ through the inductance. Find the voltage across resistance and inductance separately at the time of switching the supply and when sufficient time has elapsed after switching the source. (Ans. $0V, 1V, 1V, 0V$)
4. Consider the series $R - L$ circuit connected to a battery and a switch as shown in fig. 1.131. Switch S_1 closes at $t = 1 \text{ second}$; switch S_2 closes at $t = 2.5 \text{ second}$. (i) Find the current $i(t)$ in the resistance R ; (ii) Plot the current $i(t)$ for $0 \leq t \leq 5 \text{ second}$ to the scale. Assume R/L equal to 100 .
5. A coil having $L = 6.4 \text{ H}$ and $R = 8 \text{ } \Omega$ is connected to a constant 200 V supply source. How long does it take the voltage across the resistor to reach 100 V ? (Ans. 0.5545 s)

1.28. ANALYSIS OF RC CIRCUITS (*Closing of RC circuit*)

In an RC circuit, when the circuit is closed, the capacitor is charged from a fixed value of d.c. supply. The rate of charging is controlled by the resistor connected in series with the capacitor.

Consider a capacitor of capacitance C farad connected in series with a resistor of R ohms, to be charged from a d.c. source of V volt. When the switch S is open the voltage across the capacitor is zero as shown in fig. 1.135. However, when the switch is closed, the charge on the capacitor starts rising and so does the potential difference across it.

At the switching instant : At the instant when switch is closed, the voltage built up across the capacitor is zero. Therefore, the entire voltage V is dropped across the resistor R and the charging current is maximum (say I_m).

$$\therefore \text{At the switching instant, current } I_m = \frac{V}{R} \quad \dots(i)$$

At any instant during charging : After closing the switch, the capacitor starts charging and the voltage across it increases gradually. This decreases the charging current. Let at any instant during charging,

v = p.d. across the capacitor

i = charging current

q = charge on the capacitor = Cv

According to Kirchhoff's second law,

Applied voltage = voltage across capacitor + voltage across resistor

$$V = v + iR \quad \dots(ii)$$

or

$$V = v + C \frac{dv}{dt} R \quad \left(\because i = \frac{dq}{dt} = \frac{d}{dt}(Cv) = C \frac{dv}{dt} \right)$$

or

$$V = v + CR \frac{dv}{dt}$$

or

$$-\frac{dv}{V-v} = -\frac{dt}{RC}$$

Integrating both sides w.r.t. ' t ' ;

$$\int -\frac{dv}{V-v} = \int -\frac{dt}{RC}$$

$$\log_e (V-v) = -\frac{t}{RC} + K \quad \dots(iii)$$

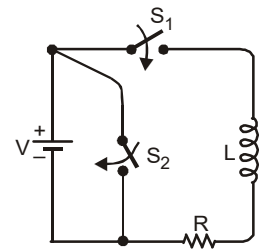


Fig. 1.135: Opening of RC Circuit

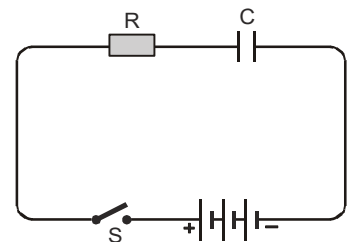


Fig.1.136: Closing of RC circuit.

where K is a constant of integration whose value can be determined from the initial conditions. At the instant of closing the switch S , $t = 0$; $v = 0$

\therefore Substituting these values in equation (iii), we get, $\log_e V = K$

Putting the value of $K = \log_e V$ in equation (iii), we get,

$$\log_e (V-v) = -\frac{t}{RC} + \log_e V$$

or

$$\log_e \frac{V-v}{V} = -\frac{t}{RC}$$

or
$$v = V(1 - e^{-t/RC})$$

The above expression shows the variation of voltage (v) developed across the capacitor w.r.t. time (t). It is represented graphically in fig.1.137.

The voltage across the capacitor is increasing following an * exponential law. The other quantities vary as under :

(i) *Variation of charge stored in the capacitor with time*

We know that $v = q/C$ and $V = Q/C$;

$$\therefore \frac{q}{C} = \frac{Q}{C} (1 - e^{-t/RC})$$

or
$$q = Q(1 - e^{-t/RC}) \quad \dots(v)$$

where q is the charge at any instant ' t ' and Q is the full charge on the capacitor.

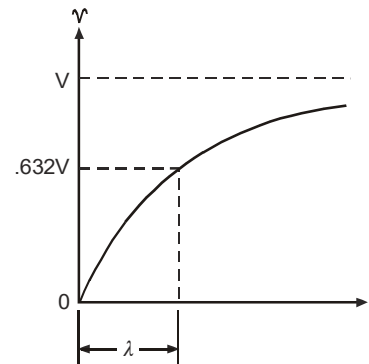


Fig.1.137: Graph between v and i when circuit is closed.

(ii) *Variation of charging with time*

From equation (ii), we have, $V - v = iR$

From equation (iv), we have, $V - v = V e^{-t/RC}$

$$\therefore i R = V e^{-t/RC}$$

or
$$i = \frac{V}{R} e^{-t/RC}$$

From equation (i) above, $I_m = \frac{V}{R}$

$$\therefore i = I_m e^{-t/RC} \quad \dots(iv)$$

where $I_m (= V/R)$ is the initial charging current.

This charging current decreases following the exponential law and is represented graphically in fig.1.138.

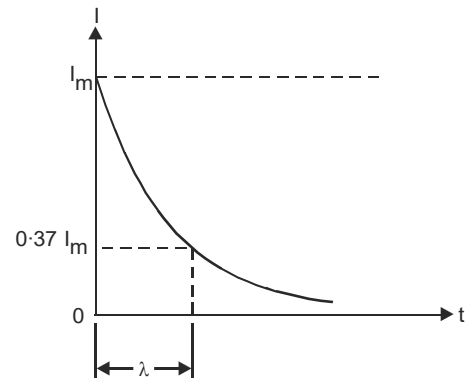


Fig.1.138: Graph between i and t when circuit is opened.

1.29. TIME CONSTANT

The rise of p.d. across the capacitor is given by the equation ;

$$v = V(1 - e^{-t/RC})$$

In this equation, the exponent of e is t/RC . The exponent of e must be a number, therefore, the quantity RC should have the ** dimensions of time. Hence, the quantity RC is called the *time constant* of the circuit and affects the charging (or discharging) time. It is generally represented by λ (or T or τ).

* A quantity is said to vary following exponential law, if it changes to half of its value in say t seconds and in the next t seconds the value changes to half of the new value and so on.

∴ Time constant, $\lambda = RC$ second.

The time constant will be in seconds if R and C are in ohm and farad respectively. The time constant λ affects the time period of the charging process of capacitor. The larger the time constant, the longer the charging (or discharging) period and *vice-versa*.

In fact, the time constant indicates the rate at which a capacitor is charged. It can be defined in the following ways :

(i) We have seen the expression in the previous article

$$V = v + CR \frac{dv}{dt}$$

At the instant of closing the switch S , $v = 0$

$$\therefore V = CR \frac{dv}{dt} \quad \text{or} \quad \frac{dv}{dt} = \frac{V}{CR}$$

$$\text{i.e. Rate of rise of voltage} = \frac{V}{CR}$$

If this rate of rise of voltage could continue the capacitor voltage will reach to final value V in time

$$= V \div V/RC = RC \text{ second i.e. time constant } \lambda$$

Hence, the time required for the capacitor voltage to rise to its final steady value (V volt) if it continued rising at its initial rate (i.e. V/RC) is called the **time constant** of the circuit.

(ii) If the time interval $t = RC$ (i.e. λ),

then

$$\begin{aligned} v &= V(1 - e^{-t/\lambda}) = V(1 - e^{-1}) \\ &= V\left(1 - \frac{1}{e}\right) = V\left(1 - \frac{1}{2.718}\right) = 0.632 V \end{aligned}$$

Hence, the time required for the capacitor voltage to rise to 0.632 of its final steady value is known as the **time constant** of the circuit. Refer fig.1.137.

(iii) If the time interval $t = RC$ (i.e. λ))

then

$$i = I_m e^{-t/\lambda} = I_m e^{-1} = I_m \times \frac{1}{e} = \frac{I_m}{2.718} = 0.37 I_m$$

Hence, the time required for the charging current to fall to 0.37 of its initial maximum value I_m ($= V/R$) is called the time constant of the circuit. Refer fig.1.138.

1.30. DISCHARGING OF A CAPACITOR

Consider a capacitor of C farad connected in series with a resistor of R ohm and a switch S . When the switch is open, the capacitor is charged to V volt and the current in the circuit is zero as shown in fig.1.139.

$$\text{** Units of } RC = \frac{\text{volt}}{\text{ampere}} \times \frac{\text{coulomb}}{\text{volt}} = \frac{\text{volt}}{\text{coulomb / sec}} \times \frac{\text{coulomb}}{\text{volt}} = \text{second.}$$

When the switch S is closed, the charge on the capacitor starts decreasing and so does the voltage across it.

Let at any instant during discharging ;

v = p.d. across the capacitor

i = discharging current

q = charge on the capacitor = Cv

According to Kirchhoff's second law, $0 = v + iR$

$$\text{or} \quad 0 = v + CR \frac{dv}{dt}$$

$$\text{or} \quad v = -CR \frac{dv}{dt}$$

$$\text{or} \quad \frac{dv}{v} = -\frac{dt}{RC}$$

Integrating both sides, we get

$$\int \frac{dv}{v} = -\frac{1}{RC} \int dt \therefore \log_e v = -\frac{t}{RC} + K \quad \dots(i)$$

where K is a constant of integration whose value can be determined from the initial conditions. At the instant of closing the switch S , $t = 0$; $v = V$.

\therefore Substituting these values in equation (i), we get,

$$\log_e V = K$$

Putting the value of $K = \log_e V$ in equation (i), we get,

$$\log_e v = -\frac{t}{RC} + \log_e V$$

$$\text{or} \quad \log_e \frac{v}{V} = -\frac{t}{RC}$$

$$\text{or} \quad \frac{v}{V} = e^{-t/RC}$$

$$\therefore v = V e^{-t/RC} \quad \dots(ii)$$

The above expression shows the variation of voltage (v) across the capacitor w.r.t. time (t) while discharging and is represented graphically in fig.1.140.

The other quantities vary as under :

(i) *Variations of charge on the capacitor with time*

$$\text{Since} \quad v = \frac{q}{C} \text{ and } V = \frac{Q}{C}$$

Substituting these values in equation (ii), we get,

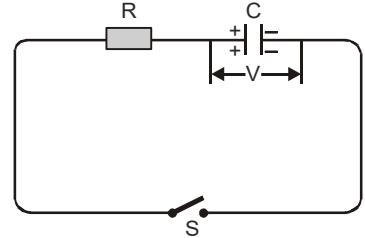


Fig.1.139: Charged capacitor with open switch without supply

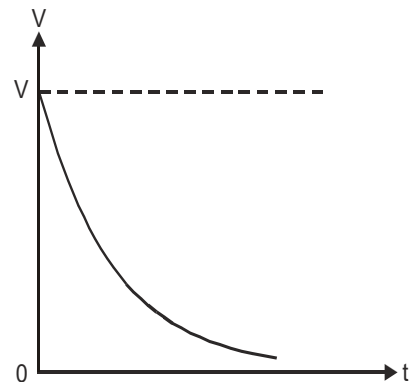


Fig.1.140: Graph between v and t during discharging of capacitor

$$\frac{q}{C} = \frac{Q}{C} e^{-t/RC}$$

or

$$q = Q e^{-t/RC}$$

(ii) Variation of discharging current with time

We know that

$$0 = v + iR$$

or

$$iR = -v$$

or

$$i = -\frac{V}{R} e^{-t/RC} = -I_m e^{-t/RC}$$

where

$$I_m = \frac{V}{R} = \text{initial current}$$

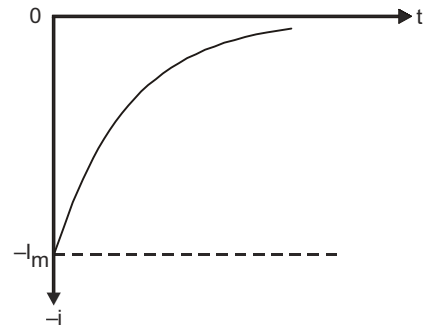


Fig.1.141: Graph between i and t during discharging of capacitor.

The variation of discharging current is shown graphically in fig.1.141.

Example 1.32. A capacitor is charged by a d.c. source through a resistor of 1.2 mega ohm. If in one second the p.d. across the capacitor reaches 75% of the final value, calculate the capacity of the capacitor.

Solution : Series resistance, $R = 1.2 \text{ M } \Omega = 1.2 \times 10^6 \Omega$; Time, $t = 1$ second

P.d. across capacitor, $v = \frac{75}{100}V = 0.75 V$

While charging, the p.d. across capacitor is given by the equation

$$v = V \left(1 - e^{-t/RC}\right)$$

$$0.75 V = V \left(1 - e^{-t/RC}\right) \quad \text{or} \quad 0.75 = \left(1 - e^{-t/RC}\right)$$

or

$$\log_e 0.25 = \frac{-t}{RC} \log_e e$$

or

$$-1.3863 = \frac{-1}{1.2 \times 10^6 C} \times 1 \quad \text{or} \quad C = \frac{1}{1.3863 \times 1.2 \times 10^6} = 0.6011 \mu\text{F} \text{ (Ans.)}$$

Example 1.33. The charge on a perfect capacitor of capacitance $2 \mu\text{F}$ falls to 60% of its value in 4 minutes, when the two plates of the capacitor are joined by an unknown resistance. What is the value of unknown resistance.

Solution : Capacitance of the capacitor, $C = 2 \mu\text{F} = 2 \times 10^{-6} \text{ F}$

Let the charge on the capacitor be Q coulomb when it is fully charged. This charge falls to q coulomb after 4 minutes.

$$\frac{q}{Q} = 60\% = 0.6$$

and

$$t = 4 \times 60 = 240 \text{ second}$$

while discharging through resistance of R ohm,

$$q = Q e^{-t/RC}$$

or $0.6 = e^{-240/R \times 2 \times 10^{-6}}$

or $\log_e 0.6 = \frac{240}{R \times 2 \times 10^{-6}}$

or $R = \frac{240}{0.5108 \times 10^{-6}} = 234.9 \times 10^6 \text{ ohm} = \mathbf{234.9 \text{ M } \Omega} \text{ (Ans.)}$

Example 1.34 A $16 \mu\text{F}$ capacitor is connected in series with a $1 \text{ M } \Omega$ resistor across a 240 V d.c. supply. Calculate (i) the time constant, (ii) the initial charging current, (iii) the time taken for the p.d. across the capacitor to grow to 168 V and (iv) the current and the p.d. across the capacitor in 4 second after it is connected to the supply.

Solution : Time constant, $\lambda = RC = 1 \times 10^6 \times 16 \times 10^{-6} = \mathbf{16 \text{ second}} \text{ (Ans.)}$

Initial charging current, $I_m = V/R = 240/1 \times 10^6 = \mathbf{240 \mu\text{A}} \text{ (Ans.)}$.

$$v = V (1 - e^{-t/RC})$$

$$168 = 240 (1 - e^{-t/16})$$

or $e^{-t/16} = 0.3 \quad \text{or} \quad e^{t/16} = 1/0.3 \quad \text{or} \quad e^{t/16} = 3.33$

or $(t/16) \log_e e = \log_e 3.33$

or $t = 16 \log_e 3.33 = 16 \times 1.203 = \mathbf{19.247 \text{ second}} \text{ (Ans.)}$

$$i = I_m e^{-t/RC} = 240 \times 10^{-6} e^{-4/16} = \mathbf{308.17 \mu\text{A}} \text{ (Ans.)}$$

Now, $v = 240 (1 - e^{-4/16}) = \mathbf{53.1 \text{ V}} \text{ (Ans.)}$

PRACTICE EXERCISE

1. A capacitor is charged by a d.c. source through a resistor of one mega ohm. If in one second the p.d. across the capacitor reaches 80% of the final value, calculate the capacity of the capacitor. (Ans. $0.6213 \mu\text{F}$)
2. The charge on a perfect capacitor of capacitance $1 \mu\text{F}$ falls to 50% of its value in 5 minutes, when the two plates of the capacitor are joined by an unknown resistance. What is the value of unknown resistance. (Ans. $432.9 \text{ M } \Omega$)
3. An $8 \mu\text{F}$ capacitor is connected in series with a $0.5 \text{ M } \Omega$ resistor across a 200 V d.c. supply. Calculate (i) the time constant, (ii) the initial charging current, (iii) the time taken for the p.d. across the capacitor to grow to 160 V and (iv) the current and the p.d. across the capacitor in 4 second after it is connected to the supply.

(Ans. 4 second , $400 \mu\text{A}$, 6.4376 second , $147.15 \mu\text{A}$, 126.424 V)

PROJECT


USE OF BREADBOARD

Please follow the instructions as per the video link given below:

<https://www.youtube.com/watch?v=6WReFkfrUIk&t=7s>

Project-1: Design and build a circuit to illuminate an LED using a 9V battery.

Step-1: Components required

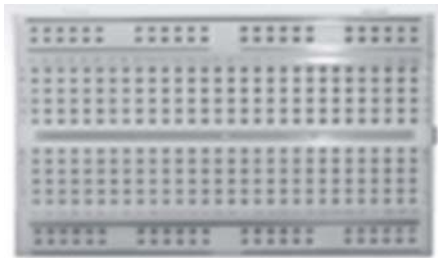

1. A small breadboard.



2. A 9V battery.



3. One LED of any colour.



4. A resistor of resistance ____ ohm ____ watt.

An LED operates at 2V and draws 20 mA, the larger leg is anode and shorter leg is cathode.

Colour codes: Black, Brown, Red, Orange, Yellow, Green, Blue, Violet, Grey, White; these colours represent the numeral value – 0, 1, 2, 3, 4, 5, 6, 7, 8 and 9 respectively.

From the left end of the resistor, first colour band represent a digit, second colour band represent a digit whereas third colour band represent a multiplier as power of 10.

The fourth band represents tolerance - silver band for 10% and gold colour for 5% tolerance. For 470 ohm resistor with 5% tolerance colour coding will be yellow, violet, black and gold.

Step-2: Selection of resistor



$$\text{Voltage across resistor, } V_R = V - V_{LED} = 9 - 2 = 7V$$

Current in the circuit, $I = VR/R$

Resistance of the resistor, $R = VR/I = 7V/20 \text{ mA} = 7/0.02 = 350 \text{ ohm}$

Considering safety of LED, a resistor of 470 ohm, 0.5 W be selected.

Step-3: Circuit diagram

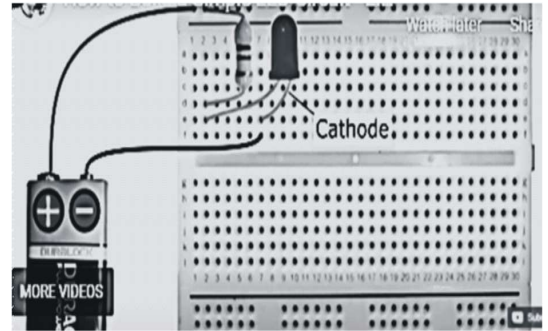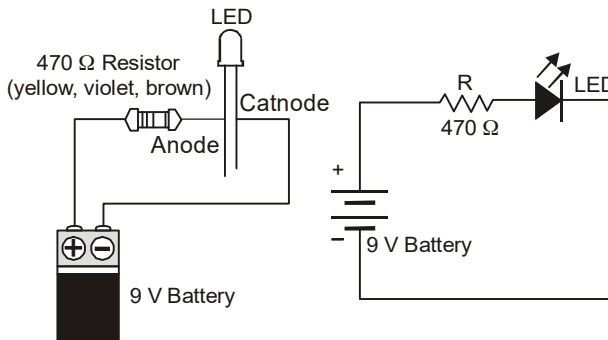

Circuit on breadboard

Project-2: Design and build a circuit to illuminate four LEDs connected in series, using a 9V battery.

Project-3: Design and build a circuit to illuminate four LEDs connected in parallel, using a 9V battery.

SUMMARY

1. *Circuit Elements:* In general, the circuit elements can be categorised as:
 1. Active and passive elements.
 2. Unilateral and bilateral elements.
 3. Linear and non-linear elements.
 4. Lumped and distributed elements.
2. *Resistors:* Resistor is a component, used to limit the amount of current or divide the voltage in an electronic circuit. The ability of a resistor to oppose the current is called resistance.
3. *Classification of resistors :* The resistors may be classified as fixed and variable resistors.
4. *Inductors :* A component that opposes the change of current in circuit is called an inductor. The ability of an inductor or coil due to which it opposes the change of current flowing through it is called its inductance.
5. *Classification Inductors :* Inductors can be classified broadly as fixed and variable inductors.
6. *Capacitors :* Two conducting plates separated by an insulating material (or dielectric) forms a capacitor. Capacitor has the ability to store electric charge. The capacity of a capacitor to store charge per unit potential difference is called its capacitance.
7. *Classification of capacitors :* The capacitors can also be classified broadly as fixed and variable capacitors.
8. *Voltage and current sources :* To deliver electrical energy to electrical/electronic circuits, a source is required. The source may be either a d.c. (direct current) source or an a.c. (alternating current) source.

9. *Constant voltage source* : An electrical source is called a constant voltage source if it supplies power at almost constant voltage to a load irrespective to its value.
10. *Constant Current source* : An electrical source is called a constant current source if it supplies power at almost constant current to a load irrespective to its value.
11. *Source transformation (Conversion of Voltage Source to Current Source and Vice-Versa)* : It has been seen that, the same electrical source behaves as a constant voltage source and as a constant current source.
12. *Ohm's law* : This law states that the current flowing between any two points of a conductor (or circuit) is directly proportional to the potential difference across them, provided physical conditions (i.e. temperature etc.) remain the same.
13. *D.C circuit* : The closed path for the flow of direct current is called d.c. circuit.
14. *Effective value of the resistance (R)*
 - (i) in series circuit ; $R = R_1 + R_2 + \dots + R_n$
 - (ii) in parallel circuit ; $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$
15. *Kirchhoff's laws* : *K C L* states that $\Sigma I = 0$ at a junction. *K V L* states that $\Sigma E + \Sigma IR = 0$ in a loop. While applying *KCL*, incoming currents are taken as +ve and outgoing currents as - ve.
16. *Superposition theorem* : In this method, If there are two or more than two sources, current is determined in the required branch by considering each source separately and then resultant value is determined by superimposing them.
17. *Thevenin's theorem* : According to this theorem, to determine current in a resistor, the resistor is removed and an open circuit voltage across the two terminals is determined called thevenin voltage E_{th} . Then, resistance of the whole network is determined across the terminals called Thevenin resistance R_{th} replacing all the voltage sources by their internal resistances, $I = E_{th}/(R_{th} + R_L)$.
18. *Norton's theorem* : It is similar to Thevenin's theorem but in this case, the network is reduced to a current source having a current output of I_N when the given terminals are short circuited in parallel with a resistance R_N similar to R_{th} . Then, $I = I_N R_N/(R_N + R_L)$.
19. Closing and opening of an inductive circuit : $V = iR + L \frac{di}{dt}$
 - (i) *Rise of current when circuit is closed* : at any instant.

$$i = I (1 - e^{-Rt/L}) \text{ where } I = V/R$$
 - (ii) *Decay of current when circuit is opened* : at any instant

$$i = I e^{-Rt/L} \text{ where } I = V/R$$
20. *Time constant* : $\lambda = L/R$ second

21. Charging of a capacitor

(i) Current at the switching instant, $I_m = \frac{V}{R}$

(ii) Voltage across capacitor at any instant, $v = V (1 - e^{-t/RC})$

(iii) Charge stored in the capacitor at any instant, $q = Q (1 - e^{-t/RC})$

(iv) Charging current at any instant, $i = I_m (1 - e^{-t/RC})$

22. Discharging of a capacitor

(i) Voltage across capacitor at any instant, $v = V e^{-t/RC}$.

(ii) Charge on the capacitor at any instant, $q = Q e^{-t/RC}$.

(iii) Discharge current at any instant, $i = -I_m e^{-t/RC}$.

SHORT ANSWER QUESTIONS

1. What do you mean by elements of an electric circuit?
2. How will you differentiate between active and passive elements?
3. How will you differentiate between unilateral and bilateral elements?
4. How will you differentiate between linear and non-linear elements?
5. How will you differentiate between lumped and distributed elements?
6. What are resistors? How will you classify them?
7. What are inductors? How will you classify them?
8. What are capacitors? How will you classify them?
9. What do you mean by constant voltage source?
10. How will you differentiate between ideal and real constant voltage source?
11. What do you mean by constant current source?
12. How will you differentiate between ideal and real constant current source?
13. State Ohm's law and give its limitations.
14. In series circuits, show that effective resistance is sum of the individual resistances.
15. In parallel circuits show that
16. How will you differentiate between node and function in an electric network?
17. How will you differentiate between loop and mesh in an electric network?
18. State Kirchhoff's current and voltage laws.
19. State superposition theorem.
20. State Thevenin's theorem.
21. State Norton's theorem.
22. How will you justify that the unit of L/R is second?
23. How will you justify that the unit of RC is second?

S No.	Question (In para)	Marks	CO	BL	PO
1.	What do you mean by elements of an electric circuit?	2	CO1	BL1	PO1
2.	How will you differentiate between active and passive elements?	2	CO1	BL2	PO1
3.	How will you differentiate between unilateral and bilateral elements?	2	CO1	BL2	PO1
4.	How will you differentiate between linear and non-linear elements?	2	CO1	BL2	PO1
5.	How will you differentiate between lumped and distributed elements?	2	CO1	BL2	PO1
6.	What are resistors? How will you classify them?	2	CO1	BL3	PO2
7.	What are inductors? How will you classify them?	2	CO1	BL3	PO2
8.	What are capacitors? How will you classify them?	2	CO1	BL3	PO2
9.	What do you mean by constant voltage source?	2	CO1	BL2	PO1
10.	How will you differentiate between ideal and real constant voltage source?	2	CO1	BL2	PO1
11.	What do you mean by constant current source?	2	CO1	BL2	PO1
12.	How will you differentiate between ideal and real constant current source?	2	CO1	BL2	PO1
13.	State Ohm's law and give its limitations.	2	CO1	BL2	PO1
14.	In series circuits, show that effective resistance is sum of the individual resistances.	2	CO1	BL3	PO2
15.	In parallel circuits show that $\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$	2	CO1	BL3	PO2
16.	How will you differentiate between node and function in an electric network?	2	CO1	BL3	PO2
17.	How will you differentiate between loop and mesh in an electric network?	2	CO1	BL3	PO2
18.	State Kirchhoff's current and voltage laws.	2	CO1	BL1	PO1
19.	State superposition theorem.	2	CO1	BL1	PO1
20.	State Thevenin's theorem.	2	CO1	BL1	PO1
21.	State Norton's theorem.	2	CO1	BL1	PO1
22.	How will you justify that the unit of L/R is second?	5	CO1	BL4	PO3
23.	How will you justify that the unit of RC is second?	5	CO1	BL4	PO3

NUMERICAL FOR PRACTICE

- There are two wires A and B of the same material. A is 10 times longer than B and has twice the cross-section as that of B . If the resistance of A is one ohm, what is the resistance of B ?
(Ans. $1/5$ ohm)
- Calculate the resistance between the points X and Y in network shown in fig. 1.142. All the resistors are given in ohms.
(Ans. 4 ohm)

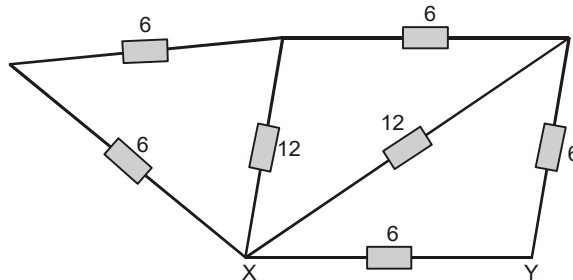


Fig. 1.142

- A resistance of $15\ \Omega$ is connected in series with two resistances each of $30\ \Omega$ arranged in parallel. What resistance must be connected across the parallel combination that the total current taken shall be 3 A with 75 V applied.
(Ans. 30 ohm)
- A letter A is constructed of a uniform wire of resistance 3 ohm per cm. The sides of the letter are 20 cm long and the cross piece is 10 cm long while the apex angle is 60° . Find the resistance of the letter between the two ends of the legs.
(Ans. 80 Ω)
- Two batteries A and B connected in parallel and load of $5\ \Omega$ is connected across their terminals. A has an e.m.f. of 6 V and an internal resistance of $1\ \Omega$; B has an e.m.f. of 4V and an internal resistance of $0.5\ \Omega$. Using Kirchhoff's laws determine the value and direction of flow of current in each battery and in the external resistance. Also determine the potential difference across the external resistance.
(Ans. 1.625 A charging ; 0.75 A discharging ; 0.875 A ; 4.375 V)
- A wheatstone bridge $ABCD$ is arranged as follows :
Resistance between $A - B$, $B - C$, $C - D$, $D - A$ and $B - D$ are 20, 4, 16, 8 and 10 ohm respectively. A 200 V supply is connected between terminals A and C . Determine the currents in branches AB and AD of the circuit and total current taken from the supply.
(Ans. 7.44 A; 11.905 A ; 19.345 A)
- In the circuit shown in fig.1.143, determine the current supplied by the d.c. generator of 280V.
(Ans. 4 A)
- By using Kirchhoff's laws, determine current in XY in the circuit shown in fig. 1.144.
(Ans. 40 A)
- Using superposition theorem, find the current in all the branches of the circuit shown in fig.1.145.
(Ans. 4.4915 A, 2.2881 A, 2.2084 A)

10. Using superposition theorem, determine potential difference across 60Ω resistor in the network shown in fig. 1.146. (Ans. 87.3 V)

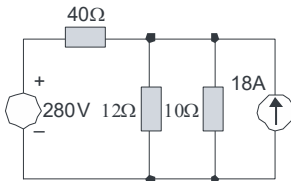


FIG. 1.143

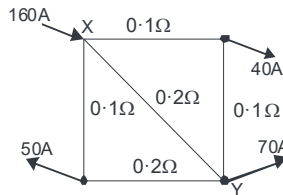


FIG. 1.144

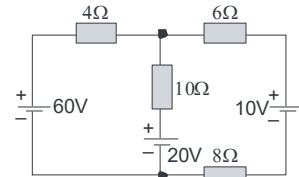


FIG. 1.145

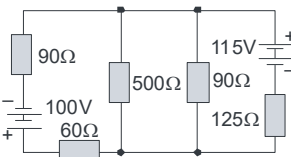


FIG. 1.146

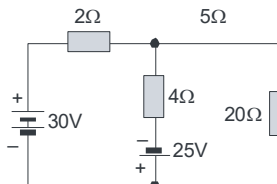


FIG. 1.147

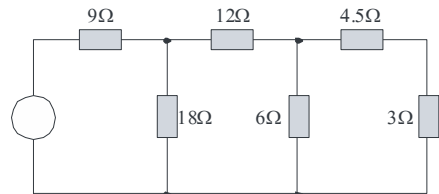


FIG. 1.148

11. Using Thevenin's theorem, determine the current in 20 ohm resistor of the network shown in fig. 1.147. (Ans. 0.433 A)
12. Using Thevenin's theorem, determine the current in 3 ohm resistor in the network shown in fig. 1.148. What will be the value of current if this resistance is replaced by 15 ohm resistor? (Ans. $2\text{ A}, 1\text{ A}$)
13. Using Norton's theorem, determine current in 60Ω resistor of the network shown in fig. 1.146. (Ans. 0.433 A)
14. Using Norton's theorem, determine current in 3Ω resistor of the network shown in fig. 1.148. (Ans. 2 A)
15. The resistance and inductance of a coil are 5Ω and 0.15 m H respectively. What potential difference exists at the terminals of the solenoid at the instant when the current is 3 A but increasing at the rate of 10^5 A/s . (Ans. 30 V)
16. The resistance and inductance of an inductive coil are 5Ω and 20 H respectively. At the instant of closing the supply, the current increases at the rate of 4 A/s . Calculate (i) the applied voltage (ii) the rate of growth of current when the current is 5 A (iii) the time taken to reach 10 A after closing the circuit and (iv) the time taken to reach 10 A while decaying after reaching the maximum value. (Ans. $80\text{ V}; 2.75\text{ A/s}; 3.923\text{ s}; 1.88\text{ s}$)
17. A $2\mu\text{F}$ capacitor is connected, by closing switch, to a supply of 100 V through a 1 M ohm series resistance. Calculate (i) the time constants (ii) initial charging current, (iii) the initial rate of rise of p.d. across capacitor, (iv) voltage across the capacitor 6 second after the switch has been closed and (v) the time taken for the capacitor to be fully charged.

(Ans. $25; 100\mu\text{ A}; 50\text{ V/s}; 95.1\text{ V}; 10\text{ s}$)

18. A capacitor is charged from d.c. source through a resistance of 2 mega – ohm. If it takes 0.5 seconds for the charge to reach 75% of its initial value, what is the capacitance of the capacitor.
(Ans. $18 \times 10^{-4} F$)
19. A resistance R and a $2 \mu F$ capacitor are connected in series across a 200 V d.c. supply. Across the capacitor is connected a neon lamp that strikes at 120 V. Calculate the value of R to make the lamp strike 5 seconds after switch is closed.
(Ans. $2.73 M \Omega$)

MULTI-CHOICE QUESTIONS

- If the length of a conductor or wire is doubled and its diameter is also doubled, then its resistance will
 - increase to four times
 - decrease to half
 - increase to two times
 - remain the same
- A man has three resistances, each of value $1/3$ ohm. What is the value of minimum resistance which he can obtain by combining them?
 - 1 ohm
 - 3 ohm
 - $1/3$ ohm
 - $1/9$ ohm
- Kirchhoff's first law states that at a junction in an electric network
 - The algebraic sum of all the currents is zero.
 - The algebraic sum of all the emfs is zero.
 - The algebraic sum of all the voltage drops is zero
 - The algebraic sum of all the forces is zero.
- If n identical resistors are connected in series, their total value is K ohm. What will be their effective value if they are now connected in parallel ?
 - K/n
 - K^2/n
 - K/n^2
 - n^2/K
- A parallel arrangement of 3 ohm and 6 ohm resistors is placed in series with an 8 ohm resistor. If p.d. of 60 V is connected across the whole circuit, the current in the three-ohm resistor is 6A
 - 6A
 - 4A
 - 2A
 - 5A
- A voltage source is considered to be an ideal one if its internal resistance is
 - almost equal to zero
 - between 100 to 1000 ohm
 - between 1000 to 9000 ohm
 - almost equal to infinity
- In an inductive coil, the delay in change of current depends upon the value of its
 - Resistance
 - Inductance
 - Capacitance
 - Earth
- A voltage divider and its Thevenin's equivalent circuit is shown in the fig.1.149. What will be the value of E_{th} and R_{th}

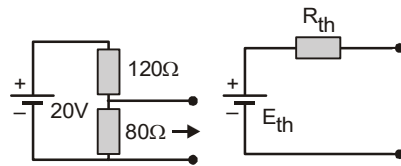


Fig. 1.149

- (A) 8V, 48 Ω (B) 4V, 48 Ω (C) 4V, 24 Ω (D) 8V, 24 Ω

9. In the circuit shown in the fig.1.150, the power consumed in the resistor connected across A– B is

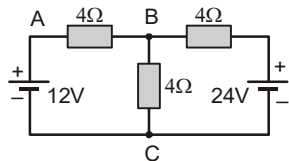


Fig. 1.150

- (A) 32 W (B) 0W (C) 16 W (D) 64 W

S No.	Question (In para)	Marks	CO	BL	PO
1.	If the length of a conductor or wire is doubled and its diameter is also doubled, then its resistance will (A) increase to four times (B) decrease to half (C) increase to two times (D) remain the same	1	CO1	BL3	PO1
2.	A man has three resistances, each of value $1/3$ ohm. What is the value of minimum resistance which he can obtain by combining them? (A) 1 ohm (B) 3 ohm (C) $1/3$ ohm (D) $1/9$ ohm	1	CO1	BL3	PO1
3.	Kirchhoff's first law states that at a junction in an electric network (A) The algebraic sum of all the currents is zero. (B) The algebraic sum of all the emfs is zero. (C) The algebraic sum of all the voltage drops is zero (D) The algebraic sum of all the forces is zero.	1	CO1	BL1	PO1
4.	If n identical resistors are connected in series, their total value is K ohm. What will be their effective value if they are now connected in parallel? (A) K/n (B) K^2/n (C) K/n^2 (D) n^2/K	1	CO1	BL1	PO1

<p>5. A parallel arrangement of 3 ohm and 6 ohm resistors is placed in series with an 8 ohm resistor. If p.d. of 60 V is connected across the whole circuit, the current in the three-ohm resistor is 6A</p> <p>(A) 6A (B) 4A (C) 2A (D) 5A</p>	1	CO1	BL5	PO1
<p>6. A voltage sources is considered to be an ideal one if its internal resistance is</p> <p>(A) almost equal to zero (B) between 100 to 1000 ohm (C) between 1000 to 9000 ohm (D) almost equal to infinity</p>	1	CO1	BL2	PO2
<p>7. In an inductive coil, the delay in change of current depends upon the value of its</p> <p>(A) Resistance (B) Inductance (C) Capacitance (D) Earth</p>	1	CO1	BL2	PO3
<p>8. A voltage divider and its Thevenin's equivalent circuit is shown in the fig.1.151. What will be the value of E_{th} and R_{th}</p> <p>(A) 8V, 48 W (B) 4V, 48 W (C) 4V, 24 W (D) 8V, 24 W</p> <div data-bbox="217 1028 623 1183"> </div> <p style="text-align: center;">Fig. 1.151</p>	1	CO1	BL6	PO4
<p>9. In the circuit shown in the fig.1.152, the power consumed in the resistor connected across A—B is</p> <p>(A) 32 W (B) 0 W (C) 16 W (D) 64 W</p> <div data-bbox="189 1392 482 1547"> </div> <p style="text-align: center;">Fig. 1.152</p>	1	CO1	BL6	PO4

TEST QUESTIONS

1. What are the various electric circuit elements? How will you distinguish between.
(i) linear and non-linear elements (ii) Active and passive elements.
2. Giving examples, explain what do you mean by
(i) Fixed and variable resistors. (ii) Fixed and variable capacitors
3. Explain, what do you mean by real voltage and current sources.
4. State and explain Ohm's law. Give its limitations.
5. Show that :
(i) in series circuit, the effective value of resistance ; $R = R_1 + R_2 + \dots + R_n$.
(ii) in parallel circuit, the reciprocal of the effective value of resistance, is equal to the sum of the reciprocal of individual resistances.
6. Distinguish between
(i) Node and junction ; (ii) loop and mesh
7. State and explain Kirchhoff's current and voltage law.
8. While applying Kirchhoff's voltage law to a loop, how signs are applied to the e.m.f. and voltage drop?
9. State and explain superposition theorem how is it applied for solving a network?
10. State Thevenin's theorem, illustrate the application of the theorem with reference to an appropriate electric network.
11. State and explain Norton's theorem. Show that this theorem is just the converse of Thevenin's theorem.
12. When a d.c. supply is connected to an inductive circuit and the circuit is closed, prove that current in the circuit at any instant is given by the relation
$$i = \frac{V}{R} \left(1 - e^{-Rt/L}\right)$$
13. A d.c. voltage V is applied across a circuit consisting of resistance R ohms in series with a capacitance C farads. Derive expression for variation of voltage across C with time.
14. A condenser and a resistor are connected in series with a d.c. source. Find the charge on the condenser at a time ' t ' after switching the circuit and hence determine the rate of growth of charge?
15. A condenser and a resistor are connected in series with a d.c. source of V volt. Derive an expression for the voltage across the capacitor after ' t ' second when the capacitor is discharged.

S No.	Question (In para)	Marks	CO	BL	PO
1.	What are the various electric circuit elements? How will you distinguish between. (i) linear and non-linear elements (ii) Active and passive elements.	5	CO1	BL2	PO1
2.	By giving examples, explain what do you mean by (i) Fixed and variable resistors. (ii) Fixed and variable capacitors	5	CO1	BL2	PO1
3.	Explain, what do you mean by real voltage and current sources.	5	CO1	BL2	PO1
4.	State and explain Ohm's law. Give its limitations.	5	CO1	BL3	PO2
5.	Show that : (i) in series circuit, the effective value of resistance. $R = R_1 + R_2 + \dots + R_n$. (ii) in parallel circuit, the reciprocal of the effective value of resistance, is equal to the sum of the reciprocal of individual resistances.	8	CO1	BL3	PO2
6.	Distinguish between (i) Node and junction ; (ii) loop and mesh	5	CO1	BL4	PO2
7.	State and explain Kirchhoff's current and voltage law.	8	CO1	BL3	PO2
8.	While applying Kirchhoff's voltage law to a loop, how signs are applied to the e.m.f. and voltage drop?	8	CO1	BL5	PO4
9.	State and explain superposition theorem how is it applied for solving a network?	10	CO1	BL5	PO4
10.	State Thevenin's theorem, illustrate the application of the theorem with reference to an appropriate electric network.	10	CO1	BL5	PO4
11.	State and explain Norton's theorem. Show that this theorem is just the converse of Thevenin's theorem.	10	CO1	BL5	PO4
12.	When a d.c. supply is connected to an inductive circuit and the circuit is closed, prove that current in the circuit at any instant is given by the relation, $I =$	10	CO1	BL6	PO4
13.	A d.c. voltage V is applied across a circuit consisting of resistance R ohms in series with a capacitance C farads. Derive expression for variation of voltage across C with time.	10	CO1	BL6	PO5
14.	A condenser and a resistor are connected in series across a d.c. source. Find the charge on the				

	condenser at a time 't' after switching the circuit and hence determine the rate of growth of charge?	10	CO1	BL6	PO5
15.	A condenser and a resistor are connected in series with a d.c. source of V volt. Derive an expression for the voltage across the capacitor after 't' second when the capacitor is discharged.	10	CO1	BL6	PO5

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												

ANSWERS TO MULTI-CHOICE QUESTIONS

Multi-Choice questions :

- | | | | | |
|--------|--------|--------|--------|--------|
| 1. (B) | 2. (D) | 3. (A) | 4. (C) | 5. (B) |
| 6. (A) | 7. (B) | 8. (A) | 9. (C) | |



LABORATORY WORK

NECESSITY

To bridge the gap between theory and practice, it is very important to perform various experiments in the laboratories. The following points show the importance of laboratory work.

1. By performing various experiments in the laboratory, the students can understand the subject matter more effectively.
2. Experiments have more deep rooted effects on the developing brain of the students.
3. By performing experiments, students become more confident to handle various instruments and devices.
4. In the laboratories, students can see the actual parts of various machines and equipment. This improves their working knowledge.
5. Ultimately, experimentation in the Laboratories built-up self confidence in the students to work in different industries/works/departments.

TOOLS NEEDED:

The following are some essential tools which should be kept by each students while working in Electrical Laboratories: (i) Test pin (ii) Screw drivers (7.5 cm & 20 cm) (iii) Cutter (with sleeves) (iv) Plier (with sleeves) etc.

IMPORTANT POINTS:

The following important points must be kept in mind while performing various experiments in the laboratory:

1. First of all, the students should study the general layout/ setup of the laboratory.
2. Before starting the experiment, one should check the protective and switching devices of relevant machines / equipment.
3. Connecting leads of proper sizes (with thimbles at both ends) should be used.
4. For every experiment before energizing, the connections must be got checked by the teacher in-charge.
5. The measuring instruments of proper range should be selected for correct results.
6. The instruments and apparatus should be carefully handled to prevent any damage.
7. Every student must be familiar with the use of three basic instruments viz voltmeter, ammeter and wattmeter.

Voltmeter: it is always connected across the terminals (parallel) where voltage is to be measured.

Ammeter: it is always connected in series with the circuit in which current is to be measured.

Wattmeter: it has two coils, one current coil marked M-L is connected in series and the other potential coil marked V1 – V2 is connected in parallel.

PRECAUTIONS TO BE OBSERVED:

The following are some of the important precautions to be observed while performing various experiments in electrical laboratory.

1. Never touch the bare conductors or terminals while performing experiments without switching off the supply.
2. Always wear shoes with rubber sole while performing experiments.
3. Always check that the connections are tight otherwise sparking may occur.

Experiment:

Basic safety precautions. Introduction and use of measuring instruments – voltmeter, ammeter, multi-meter, oscilloscope. Real-life resistors, capacitors and inductors.

Objective: To make the students aware of

1. Basic safety precautions.
2. The use of measuring instruments – voltmeter, ammeter, multi-meter, oscilloscope.
3. Real-life resistors, capacitors and inductors.

1. Basic safety precautions

1. Find out the location of electrical panels of workplace so that power can be quickly shut down in the event of a fire or electrical accident.
2. Always maintain a minimum 1 metre clearance around the electrical panels at all times to permit ready and safe operation and maintenance of equipment.
3. Never overload circuits or wires, overloading causes overheating of wires which can cause arcing or fire.
4. Inspect all electrical equipment before use to ensure that chords and plugs are in good condition not worn, twisted, abraded or missing ground points.
5. Ensure that all electrical outlets have a grounded connection requiring a three-pronged plug. All electrical equipment should have three-pronged grounded plugs.
6. While working on electrical equipment, ensure that power has been disconnected.
7. Before working on electrical equipment, ensure that all extension cords used are carefully placed and visible (not subject to any danger).
8. Ensure that extension cords are of adequate size to carry the current. The failure may lead to electric fire.
9. Always keep flammable materials away from electrical equipment.
10. Keep all the electrical equipment away from wet locations. Never handle electrical equipment when hands, feet or body are wet.
11. If an electrical fire happens, leave the area and pull the nearest fire alarm. Do not use water on an electrical fire. If it is safe and possible to reach the panel, shutdown the main power source.
12. If a person gets an electric shock, do not touch the equipment, cord or person. Evaluate the situation, if safe shut down the main power source and call the fire department to treat the injured person.

2. The use of measuring instruments – voltmeter, ammeter, multi-meter, oscilloscope.

Voltmeter

Voltmeter is a device/instrument which is used to measure potential difference across the load or between any two points in a circuit. Voltmeter is always connected across (in parallel with) the load or across the network. Based on circuit conditions, it carries some current. If this current is large, it disturbs the circuit conditions.

To minimise the effect of voltmeter on the circuit conditions, the resistance of voltmeter is made very high so that it carries a small amount of current. Hence the resistance of a voltmeter is always kept very high. The pictorial view of a dc and an ac voltmeter is shown in fig. P1.1(a) and (b) respectively.



Fig. P1.1(a) DC Voltmeter



Fig. P1.1(b) AC Voltmeter

Ammeter

Ammeter is a device/instrument which is used to measure electric current flowing through the load or in a circuit or its branch. Ammeter is always connected in series with the load or a circuit or its branch in which current is to be measured. Accordingly, it carries the same current as that of the load or circuit. If this instrument is having high resistance, there will be more voltage drop across the instrument, this will definitely disturb the circuit conditions.

To minimise the effect of ammeter on the circuit conditions, the resistance of ammeter is kept very low so that the voltage drop across it be kept low. Hence the resistance of an ammeter is always kept very low. The pictorial view of a dc and an ac ammeter is shown in fig. P1.2(a) and (b) respectively.



Fig. P1.2(a) DC Ammeter



Fig. P1.2(b) AC Ammeter

Multi-meter

Multi-meter is a device/instrument which is used to measure resistance of a resistor, potential difference (both dc and ac) across two terminals and current (dc and ac both) flowing through any circuit or its branch. The pictorial view of an analogue and a digital multi-meter is shown in fig. P1.3(a) and (b) respectively.



Fig. P1.3(a) Analog Multi-meter



Fig. P1.3(b) Digital Multi-meter

Cathode Ray Oscilloscope (CRO)

Cathode Ray Oscilloscope (CRO) is a device/instrument which is used for drawing and calibrating graph of voltage versus time very quickly and conveniently. This instrument is obviously useful for the design and repair of circuits in which voltages and currents are changing with time. The heart of the oscilloscope is a cathode ray tube (CRT). The pictorial view of a CRO is shown in fig. P1.4.

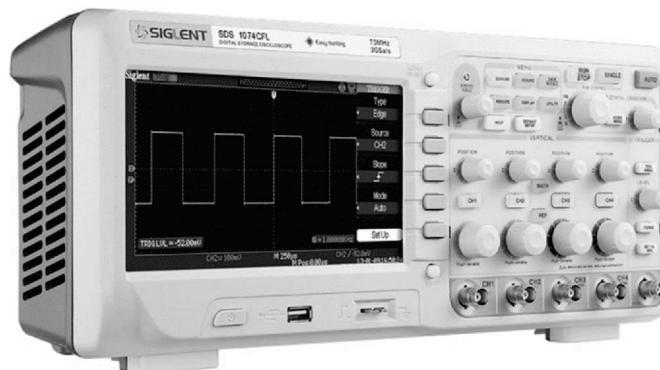


Fig. P1.4 CRO (Cathode Ray Oscilloscope)

Inductor

Inductor is a solenoid i.e. when a length of wire is wound in the form of a coil it obtains the properties of a basic inductor. It is a circuit element which opposes the change of current. The property of a coil due to which it opposes the change of current (ac current) is called inductance. The unit of inductance is henry (H). The pictorial view of a general inductor is shown in fig. P1.5(a) whereas its symbol is shown in fig. P1.5(b).



Fig. P1.5(a) Inductor

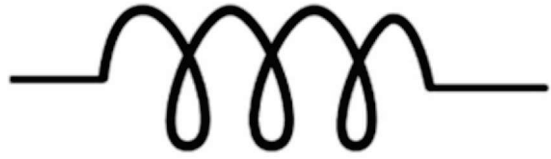


Fig. P1.5(b) Symbol of an Inductor

Capacitor

Two conducting surfaces separated by a dielectric medium or insulator form a capacitor. Capacitors may be classified on the basis of dielectric medium used in the capacitor or the shape of its plates. It has the ability to store electric charge. Capacitance of a capacitor is measured in farad (F). The pictorial view of various types of capacitors is shown in fig. P1.6(a) whereas, symbol of fixed and variable capacitor is shown in fig. P1.6(b& c) respectively.

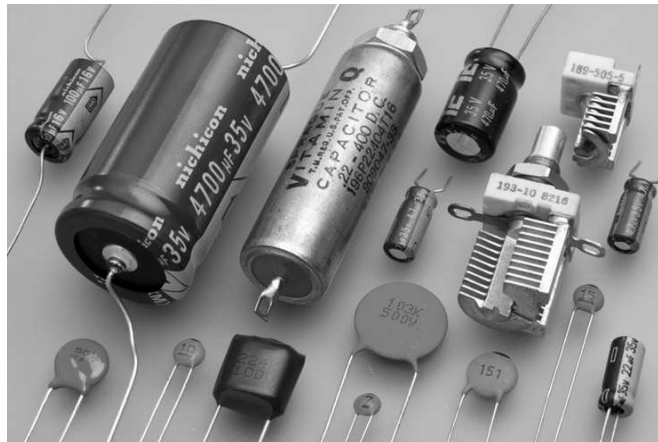


Fig. P1.6(a) Various types of capacitors

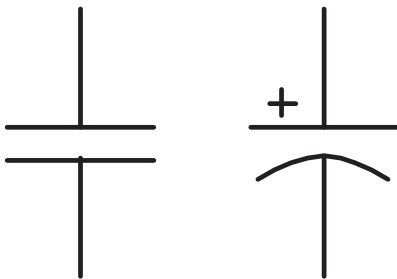


Fig. P1.6(b) Symbol of fixed capacitors

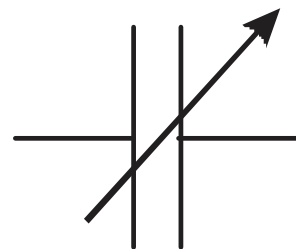


Fig. P1.6(c) Symbol of variable capacitors

Resistor

Resistor is a circuit element which restricts the flow of current. It is used to limit the current in a circuit or in any branch. It is also used to control voltages in various sections of the networks. A resistor is represented by a letter R or r. The resistance of a resistor is measured in ohm (Ω). Small resistors used in electronic circuits are having colour bands on its body to represent its value. A resistor is shown in fig.P1.7(a), fig. P1.7(b) shows the symbol of fixed resistor, whereas fig. P1.7(c) shows the symbol of a variable resistor.




Fig. P1.7(a) Resistor



Fig. P1.7(b) Symbol of fixed resistor



Fig. P1.7(c) Symbol of fixed resistor

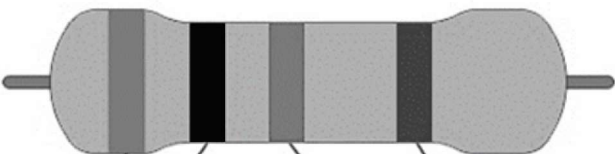

	1 st digit	2 nd digit	3 rd digit	multiply	tolerance	TCR (ppm/K)
Black	0	0	0	1	1% (F)	100
Brown	1	1	1	10	2% (G)	50
Red	2	2	2	100		15
Orange	3	3	3	1K		25
Yellow	4	4	4	10K		
Green	5	5	5	100K	0.5% (D)	
Blue	6	6	6	1M	0.25% (C)	10
Violet	7	7	7	10M	0.1% (B)	5
Gray	8	8	8	100M	0.05% (A)	
White	9	9	9	1G		
Gold				0.1	5% (J)	
Silver				0.01	10% (K)	
None					20% (M)	

Fig. P1.7(d) Colour coding of resistors

2 AC Circuits

RATIONALE

The use of d.c. is limited to a few applications *e.g.* electroplating, charging of batteries, electric traction, electronic circuits etc. For large scale power generation, transmission, distribution and utilisation, a.c. system is invariably adopted. In a.c. system, voltage acting in the circuit changes polarity and magnitude at regular interval of time and hence the current.

Alternating supply is invariably used for domestic and industrial applications. *The path for the flow of alternating current is called an a.c. circuit.* In d.c. circuits, the opposition to the flow of current is only resistance of the circuit. Whereas, in a.c. circuits, the opposition to the flow of current is due to resistance (R), inductive reactance ($X_L = 2\pi fL$) and capacitive reactance ($X_C = 1/2 \pi fC$) of the circuit. In a.c. circuits frequency plays an important role.

Although single-phase system is employed for the operation of almost all the domestic and commercial appliances *e.g.* lamps, fans, electric irons, refrigerators, TV sets, washing machines, exhaust fans, computers etc. But it has its own limitations in the field of generation, transmission, distribution and industrial applications. Due to this it has been replaced by poly-phase system.

In this chapter, we shall confine our attention to ac supply system, ac circuits and their practical utility in the field of engineering.

UNIT OUTCOMES

U2-O1: Unit-2 Learning Outcome-1

To know about ac systems, terms used in this system and the elements employed in ac circuits.

U2-O2: Unit-2 Learning Outcome-2

Phasor representation of alternating quantities with different combinations of circuit elements.

U2-O3: Unit-2 Learning Outcome-3

To analyse various series and parallel combination ac electric networks.

U2-O4: Unit-2 Learning Outcome-4

To analyse polyphase systems and circuits.

UNIT SPECIFICS

- Basic idea about alternating current and alternating voltage. How is it different to d.c.?
- Importance of sinusoidal alternating voltage and current waveform
- Terms used in a.c. such as frequency, time period, cycle, wave form, instantaneous, average, rms and peak values.
- Vector representation of a.c. quantities, phase and phase difference.
- Rectangular and polar quantities, addition, subtraction, multiplication and division of vector quantities.
- Behaviour of resistor, inductor and capacitor when connected across ac supply.
- LC Series and Parallel circuit.
- Importance of power factor and its effects on the power system?
- Series and parallel resonant circuit and their applications,
- Three-phase system and its advantages.
- Star and delta connections and how line and phase voltages are related?

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES






Unit II Outcomes	EXPECTED MAPPING WITH COURSE OUTCOMES (1-weak Correlation; 2-Medium correlation; 3-Strong Correlation)		
	CO-1	CO-2	CO-3
U2-O1	3	--	--
U2-O2	3	--	--
U2-O3	3	--	--
U2-O4	3	--	--

Interesting facts

- The power plant was built in 1882 by Thomas Edison. He built his Pearl Street Power Station which provided electricity to 85 buildings. In the beginning, people were so scared of electricity that they would not let their children to go near lights.
- In India, the 1st hydroelectric power plant, Sidrapong hydroelectric power plant, is located in the Darjeeling district of West Bengal. It was established in 10 November 1897 with a capacity of 130 kW (2 units each of 65kW).
- You might be wondering to see birds sitting on high voltage electric wires and yet not getting electrocuted. It is because both of their feet are on the same line leading to an incomplete circuit. If any other part of their body would touch another line or iron frame of the tower/pole, they would feel the jolt (electric shock that may lead to death).

Video Resource

Videos Links for circuit

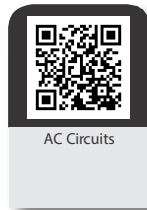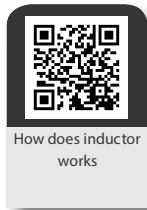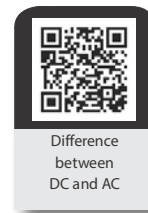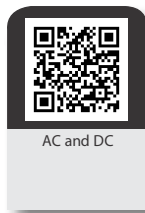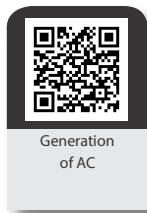

2.1. ALTERNATING VOLTAGE AND CERRENT

A voltage that changes its polarity and magnitude at regular intervals of time is called an *alternating voltage*.

When an alternating voltage source is connected across a load resistor R , as shown in fig.2.1, the current flows through it in one direction and then in opposite direction when the polarity is reversed.

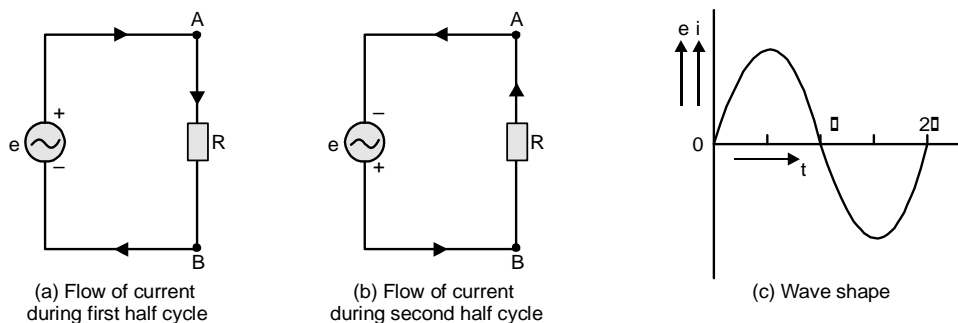


Fig. 2.1: Alternating voltage and current.

Fig.2.1 (c) shows the wave shape of the source voltage (representing the variation of voltage w.r.t. time) and current flowing through the circuit (*i.e.* load resistor R).

Wave form : The graph representing the manner in which an alternating voltage or current changes w.r.t. time is known as *wave-form* or *wave-shape*. While plotting a graph, usually the instantaneous values of the alternating quantities are taken along *y-axis* and time along *x-axis*. The alternating voltage or current may vary in different manner, as shown in fig.2.2, accordingly their wave shapes are named in different ways such as irregular wave ; triangular wave ; square wave ; periodic wave ; saw-tooth wave ; sine wave etc.

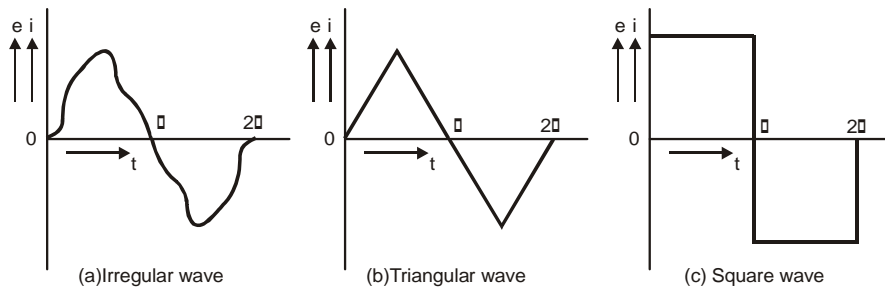


Fig.2.2: Wave shape of ac quantities (i)

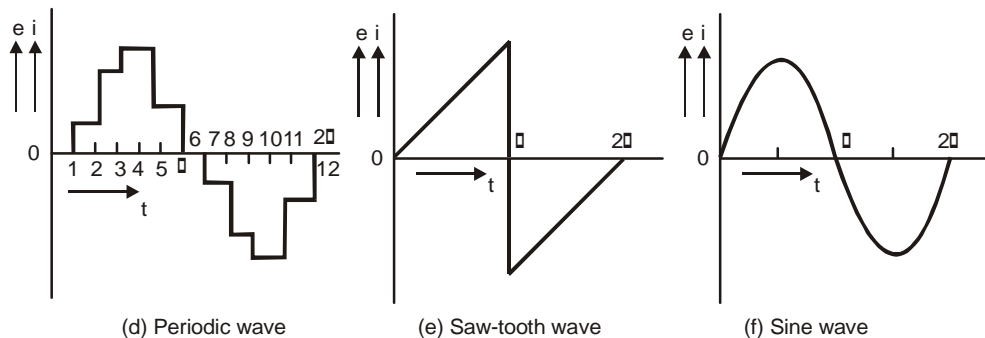


Fig.2.2: Wave shape of ac quantities

2.2. ADVANTEGES OF AC SYSTEM OVER DC SYSTEM

- (i) The alternating voltage can be stepped up and stepped down efficiently by means of transformer. To transmit huge power over a long distance, the voltages are stepped up (upto 400 kV) for economical reasons at the generating stations. Whereas, they are stepped down to a very low level (400/230 V) for utilisation of electrical energy from safety point of view.
- (ii) The *a.c.* motors (*i.e.* induction motors) are cheaper in cost, simple in construction, more efficient and robust as compared to *d.c.* motors.
- (iii) The switchgear (*e.g.* switches, circuit breakers etc.) for *a.c.* system is simpler than *d.c.* system. Thus, *a.c.* system is universally adopted for generation, transmission, distribution and utilisation of electrical energy.

2.3. DIFFERENCE BETWEEN AC AND DC

AC current	DC current
1. Alternating current reverses periodically and its magnitude changes.	1. Direct current flows only in one direction and remains unaltered.
2. Amplitude and polarities are varying continuously.	2. Amplitude and polarities are fixed.
3. It has a particular frequency.	3. It is independent of frequency.

<p>4. <i>AC</i> can be generated at higher voltages.</p> <p>5. In case of <i>ac</i>, the cost of generation is less.</p> <p>6. Alternating voltage can be increased (stepped up) or decreased (stepped down) easily with the help of a transformer.</p> <p>7. <i>AC</i> motors are of less cost, more robust and durable.</p> <p>8. The maintenance cost of <i>ac</i> equipment and appliances is less.</p> <p>9. <i>AC</i> cannot be used directly for electroplating</p> <p>10. The speed of <i>ac</i> motors cannot be controlled easily.</p>	<p>4. <i>DC</i> cannot be generated at high voltages because of commutation difficulties.</p> <p>5. In case of <i>dc</i>, the cost of generation is more.</p> <p>6. Direction voltage cannot be increased or decreased easily.</p> <p>7. <i>DC</i> motors are costly and less durable.</p> <p>8. The maintenance cost of <i>dc</i> equipment and appliances is more.</p> <p>9. Only <i>dc</i> can be used directly for electroplating.</p> <p>10. The speed control of <i>dc</i> motor is very easy and economical.</p>
--	---

2.4. SINUSOIDAL ALTERNATING QUANTITY

An alternating quantity (*i.e.* voltage or current) which varies according to sine of angle θ ($\theta = \omega t$) is known as *sinusoidal alternating quantity*. Its wave shape is shown in fig.2.2 (f). For generation of electric power, sinusoidal voltages and currents are selected all over the world due to the following reasons :

- (i) The sinusoidal voltages and currents cause low iron and copper losses in a.c. rotating machines and transformers. This improves the efficiency of a.c. machines.
- (ii) The sinusoidal voltages and currents offer less interference to nearby communication system (telephone lines etc.)
- (iii) They produce least disturbance in the electrical circuits.

Whenever the word '*alternating voltage or current*' is used in this text, it means sinusoidal alternating voltage or current unless stated otherwise.

2.5. GENERATION OF ALTERNATING VOLTAGE AND CURRENT

An alternating voltage can be generated either (i) by rotating a coil in a uniform magnetic field at constant speed as shown in fig.2.3 or

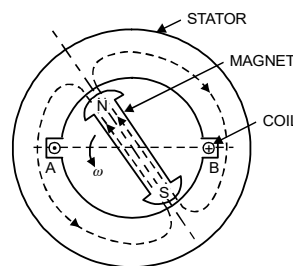
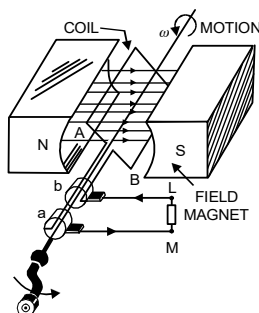


Fig. 2.3: Coil rotating in the stationary magnetic field. **Fig. 2.4:** Field rotating in the stationary coil.

(ii) by rotating a uniform magnetic field within a stationary coil at a constant speed as shown in fig. 2.4. The first method is generally applied in small a.c. generators, whereas, second method is applied in large a.c. generators due to economical considerations. In both the cases, magnetic field is cut by the conductors (or coil sides) and an e.m.f. is induced in them. The direction and magnitude of the induced e.m.f. in the conductors depend upon the position of the conductors as explained below :

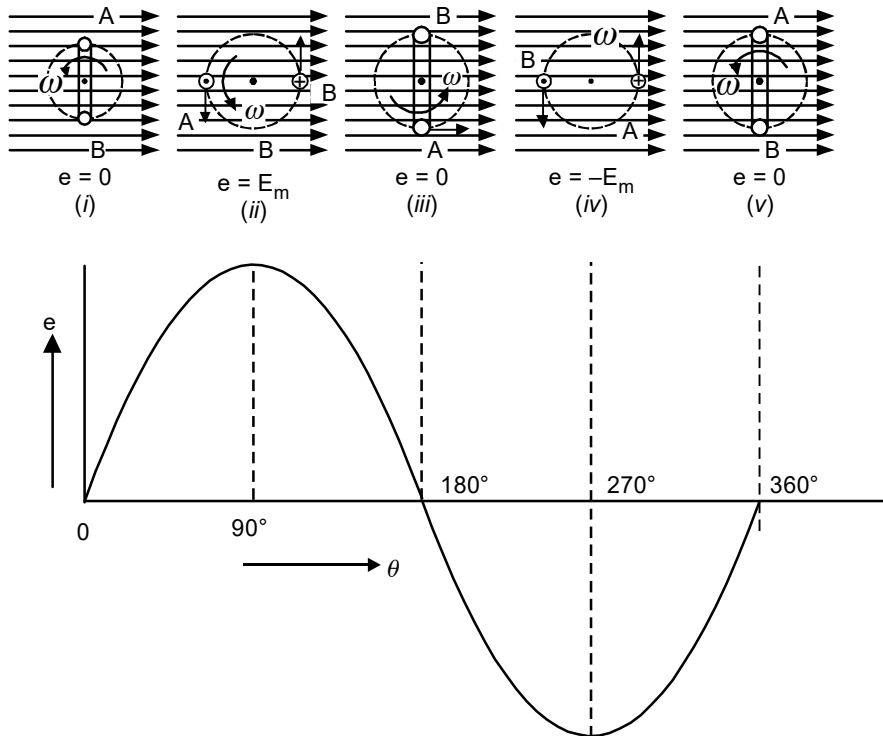


Fig. 2.5: EMF induced in a coil at various instants

For simplicity, consider a coil placed in a uniform magnetic field to which a load (LM) is connected through brushes and slip rings as shown in fig.2.3. When it is rotated in anticlockwise direction at a constant angular velocity of ω radians per second, an e.m.f. is induced in the coil sides. The cross-sectional view of the coil and its different positions at different instants are shown in fig.2.5.

The magnitude of induced e.m.f. depends upon the rate at which the flux is cut by the conductors. At (i), (iii) and (v) instants, induced e.m.f. in the conductor A and B is zero as they are moving parallel to the magnetic lines of force and the rate of flux cut is zero. Whereas, the magnitude of e.m.f. induced in the conductor A and B is maximum at instant (ii) and (iv) as the conductors are moving perpendicular to the magnetic lines of force and the rate of flux cut is maximum.

The direction of e.m.f. induced in the conductors is determined by applying *Fleming's right hand rule*. At instant (ii), the direction of e.m.f. induced in conductor A is outward whereas, at instant (iv), the direction of induced e.m.f. in the conductor A is inward (i.e. the direction of induced e.m.f. at this instant is opposite to that of the direction of induced e.m.f. at instant (ii)).

The wave shape of the e.m.f. induced in the coil is also shown in fig.2.5.

2.6. EQUATION OF ALTERNATING E.M.F. AND CURRENT

Consider a coil having N turns rotating in a uniform magnetic field of density B Wb/m² in the counter-clockwise direction at an angular velocity of ω radians per second as shown in fig.2.6.

At the instant, as shown in fig.2.6 (b) maximum flux ϕ_m is linking with the coil. After t seconds, the coil is rotated through an angle $\theta = \omega t$ radians. The component of flux linking with the coil at this instant is $\phi_m \cos \omega t$. Whereas, the other component $\phi_m \sin \omega t$ is parallel to the plane of the coil.

According to Faraday's laws of electromagnetic induction, the magnitude of e.m.f. induced in the coil at this instant *i.e.*

Instantaneous value of e.m.f. induced in the coil,

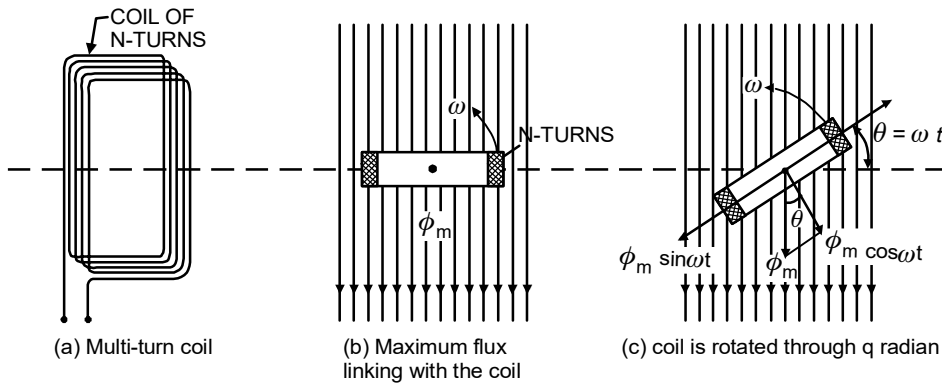


Fig. 2.6: EMF developed in a rotating coil

$$e = -N \frac{d\phi}{dt} \quad (\text{--ve sign indicates that in effect the induced e.m.f. is opposite to the very cause which produces it})$$

$$\text{or} \quad e = -N \frac{d}{dt} \phi_m \cos \omega t \quad (\because \phi = \phi_m \cos \omega t)$$

$$\text{or} \quad e = -N \phi_m (-\omega \sin \omega t)$$

$$\text{or} \quad e = \omega N \phi_m \sin \omega t \quad \dots(i)$$

The value of induced e.m.f. will be maximum when angle θ

or $\omega t = 90^\circ$ (*i.e.* $\sin \omega t = 1$)

$$\therefore E_m = \omega N \phi_m \quad \dots(ii)$$

Putting this value in equation (i), we get,

$$e = E_m \sin \omega t = E_m \sin \theta$$

From the above equation it is clear that the magnitude of the induced e.m.f. varies according to sine of angle θ . The wave shape of the induced e.m.f. is shown in fig. 2.7. This wave form is called sinusoidal wave.

If this voltage is applied across resistor, an alternating current will flow through it varying sinusoidally *i.e.* following a sine law and its wave shape will be same as shown in fig.2.7.

This alternating current is given by the equation :

$$i = I_m \sin \omega t = I_m \sin \theta$$

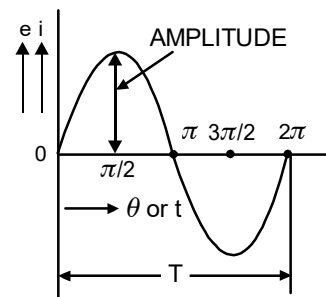


Fig.2.7: Wave shape of induced emf

2.7. IMPORTANT TERMS

An alternating voltage or current changes its magnitude and direction at regular intervals of time. A sinusoidal voltage or current varies as a sine function of time t or angle $\theta (= \omega t)$. The following important terms are generally used in alternating quantities :

- (i) **Wave form** : The shape of the curve obtained by plotting the instantaneous values of alternating quantity (voltage or current) along y -axis and time or angle ($\theta = \omega t$) along x -axis is called *wave form* or *wave shape*. Fig.2.7 shows the waveform of an alternating quantity varying sinusoidally. The graphical representation of an alternating quantity is called its *wave form*.
- (ii) **Instantaneous value** : The value of an alternating quantity *i.e.* voltage or current at any instant is called its *instantaneous value* and is represented by e or i respectively.
- (iii) **Cycle** : When an alternating quantity goes through a complete set of +ve and -ve values or goes through 360 electrical degrees, it is said to have completed one *cycle*.
- (iv) **Alternation** : One half cycle is called *alternation*. An alternation spans 180 electrical degrees.
- (v) **Time period** : The time taken in seconds to complete one cycle by an alternating quantity is called *time period*. It is generally denoted by T .
- (vi) **Frequency** : The number of cycles made per second by an alternating quantity is called *frequency*. It is measured in cycles per second (c/s) or hertz (Hz) and is denoted by f .
- (vii) **Amplitude** : The maximum value (positive or negative) attained by an alternating quantity in one cycle is called its *amplitude* or *peak value* or *maximum value*. The maximum value of voltage and current is generally denoted by E_m (or V_m) and I_m respectively.

2.8. IMPORTANT RELATIONS

Some of the terms used in a.c. terminology have definite relations among themselves as given below :

- (i) **Relation between frequency and time period** : Consider an alternating quantity having a frequency of f c/s. Then

Time taken to complete f cycle = 1 s

Time taken to complete 1 cycle = $1/f$ second

Hence time period, $T = 1/f$ second or $f = 1/T$ c/s

- (ii) **Relation between frequency and angular velocity** : Consider an alternating quantity having a frequency of f c/s.

Angular distance covered in one cycle = 2π radian

\therefore Angular distance covered per second in f cycles = 2π radian

Hence, $\omega = 2\pi f$ radian/s

2.9. VALUES OF ALTERNATING VOLTAGE AND CURRENT

The voltage and current in d.c. system are constant so that there is no problem of specifying their magnitudes. Whereas, in a.c. system, the alternating voltage and current vary from instant to instant. So the question arises how to express the magnitude of alternating voltage and current. The following three ways are adopted to express the magnitude of these quantities :

- (i) Peak Value.
- (ii) Average value or Mean value.
- (iii) Effective value or R.M.S. value.

The r.m.s. value of an alternating quantity (voltage or current) represents the real magnitude. Whereas, the peak and average values are important in some of the engineering applications.

2.10. PEAK VALUE

The maximum value attained by an alternating quantity during one cycle is called is *peak value*. This is also called *maximum value* or *crest value* or *amplitude*. A sinusoidal alternating quantity obtains its maximum value at 90° as shown in fig. 2.7. The peak of an alternating voltage and current is represented by E_m and I_m . The knowledge of peak value is important in case of testing dielectric strength of insulating materials.

2.11. AVERAGE VALUE

The arithmetic average of all the instantaneous values considered of an alternating quantity (current or voltage) over one cycle is called average value.

In case of symmetrical waves (like sinusoidal current or voltage wave) the +ve half is exactly equal to the -ve half, therefore, the average value over a complete cycle is zero. Since work is being done by the current in the +ve as well as in -ve half cycle, therefore, average value is determined regardless of signs. Hence, to determine average value of alternating quantities having symmetrical waves, only (+ve half) cycle is considered.

Divide the +ve half cycle into n number of equal parts as shown in fig. 2.8. Let $i_1, i_2, i_3 \dots i_n$ be the mid-ordinates.

Average value of current, I_{av} = mean of mid-ordinates.

$$= \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

$$= \frac{\text{Area of alternation}}{\text{base}}$$

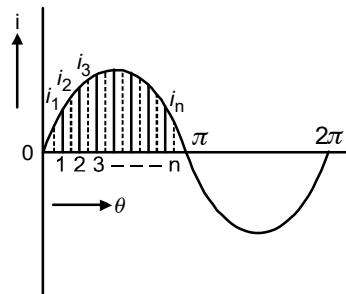


Fig.2.8: Considering half cycle of an alternating quantity for a symmetrical wave

2.12. AVERAGE VALUE OF SINUSOIDAL CURRENT

The alternating current varying sinusoidally, as shown in fig. 2.9, is given by the equation :

$$i = I_m \sin \theta$$

Consider an elementary strip of thickness $d\theta$ in the +ve half cycle, i be its mid-ordinate. Then

$$\text{Area of strip} = i d\theta$$

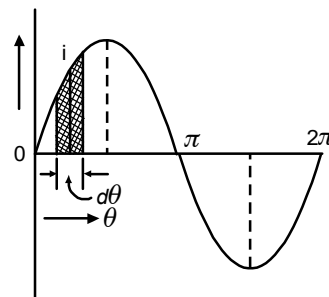


Fig.2.9: Sinusoidal alternating current

$$\begin{aligned}\text{Area of half cycle} &= \int_0^{\pi} i d\theta = \int_0^{\pi} I_m \sin \theta d\theta \\ &= I_m (-\cos \theta)_0^{\pi} = I_m (-(\cos \pi - \cos 0)) = I_m [-(-1 - 1)] = 2 I_m\end{aligned}$$

Base = 0 to $\pi = \pi - 0 = \pi$

$$\therefore \text{Average value, } I_{av} = \frac{\text{Area of alternation}}{\text{base}} = \frac{2 I_m}{\pi} = \frac{I_m}{\pi/2} = 0.637 I_m$$

2.13. EFFECTIVE OR R.M.S. VALUE

That steady current which when flows through a resistor of known resistance for a given time produces the same amount of heat as produced by the alternating current when flows through the same resistor for the same time is called **effective or r.m.s. value** of the alternating current.

Let i be the alternating current flowing through a resistor of resistance R for time t seconds which produces the same amount of heat energy as produced by I_{eff} (a direct current). The base of one

alternation is divided into n equal parts, as shown in fig. 2.10, so that interval is of $\frac{t}{n}$ second. Let $i_1, i_2, i_3, \dots, i_n$ be the mid-ordinate.

Then heat energy produced in the

First interval = $i_1^2 R t / n$ joule

Second interval = $i_2^2 R t / n$ joule

Third interval = $i_3^2 R t / n$ joule

n th interval = $i_n^2 R t / n$ joule

$$\text{Total heat produced} = Rt \left(\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n} \right) \text{ joule} \quad \dots(i)$$

Since I_{eff} is considered as the effective value of this current.

$$\text{Then total heat energy produced by this current} = I_{eff}^2 R t \text{ joule} \quad \dots(ii)$$

Equating equation (i) and (ii), we get,

$$I_{eff}^2 R t = Rt \left(\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n} \right)$$

$$\text{or } I_{eff} = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}} = \sqrt{\text{mean of squares of instantaneous values}}$$

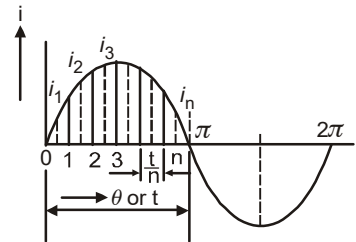


Fig.2.10: Wave shape of an alternating current

or I_{eff} = Square root of mean of squares of instantaneous values
 = root-mean-square (*r.m.s.*) value

It is the actual value of an alternating quantity which tells us the energy transfer capability of an a.c. source. For example, if we say that 5A alternating current is flowing through a circuit, it means the *r.m.s.* value of alternating current which flows through the circuit is 5A. It transfers the same amount of energy as is transferred by 5A d.c.

The ammeters and voltmeters record the *r.m.s.* values of alternating currents and voltages respectively. The domestic single-phase a.c. supply is 230 V, 50 Hz. Where 230 V is the *r.m.s.* value of alternating voltage.

2.14. R.M.S. VALUE OF SINUSOIDAL CURRENT

An alternating current varying sinusoidally is given by the equation ;

$$i = I_m \sin \theta$$

To determine the r.m.s. value, the squared wave of the alternating current is drawn as shown in fig. 2.11.

Considering an elementary strip of thickness $d\theta$ in the first half cycle of the squared wave. Let i^2 be its mid-ordinate. Then

$$\text{Area of strip} = i^2 d\theta$$

Area of first half cycle of squared wave

$$\begin{aligned} &= \int_0^{\pi} i^2 d\theta = \int_0^{\pi} (I_m \sin \theta)^2 d\theta \\ &= I_m^2 \int_0^{\pi} \sin^2 \theta d\theta = I_m^2 \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta \\ &= \frac{I_m^2}{2} \int_0^{\pi} (1 - \cos 2\theta) d\theta = \frac{I_m^2}{2} \left(\theta - \frac{\sin 2\theta}{2} \right)_0^{\pi} \\ &= \frac{I_m^2}{2} \left((\pi - 0) - \frac{\sin 2\pi - \sin 0}{2} \right) \\ &= \frac{I_m^2}{2} [(\pi - 0) - (0 - 0)] = \frac{\pi I_m^2}{2} \end{aligned}$$

Base = 0 to $\pi = \pi - 0 = \pi$

Effective or r.m.s. value,

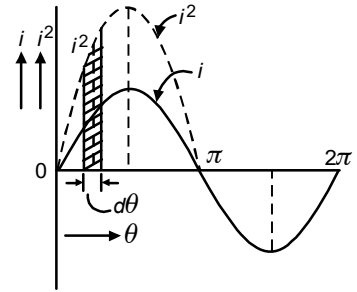


Fig.2.11: Squared wave of a sinusoidal alternating current

$$I_{r.m.s.} = \sqrt{\frac{\text{Area of first half of squared wave}}{\text{base}}} = \sqrt{\frac{\pi I_m^2}{2\pi}} = \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

Usually r.m.s. value of alternating current is simply represented by I instead of $I_{r.m.s.}$. Similarly, r.m.s. value of alternating voltage is represented by E or V .

2.15. FORM FACTOR AND PEAK FACTOR

There exists a definite relation among the average value, r.m.s. value and peak value of an alternating quantity. The relationship is expressed by the two factors namely, form factor and peak factor.

(i) **Form factor :** The ratio of r.m.s. value to average value of an alternating quantity is called *form factor*.

$$\text{Mathematically, Form factor} = \frac{I_{r.m.s.}}{I_{av}} \text{ or } \frac{E_{r.m.s.}}{E_{av}}$$

For the current varying sinusoidally ;

$$\text{Form factor} = \frac{I_{r.m.s.}}{I_{av}} = \frac{I_m/\sqrt{2}}{2I_m/\pi} = \frac{\pi I_m}{2\sqrt{2} I_m} = 1.11$$

(ii) **Peak factor :** The ratio of maximum value to r.m.s. value of an alternating quantity is called *peak factor*.

$$\text{Mathematically, Peak factor} = \frac{I_m}{I_{r.m.s.}} \text{ or } \frac{E_m}{E_{r.m.s.}}$$

For current varying sinusoidally :

$$\text{Peak factor} = \frac{I_m}{I_{r.m.s.}} = \frac{I_m}{I_m/\sqrt{2}} = \sqrt{2} = 1.4142$$

Example 2.1. An alternating voltage is given by $v = 282.8 \sin 377t$. Find

- (i) Frequency
- (ii) r.m.s. value
- (iii) average value
- (iv) the instantaneous value of voltage when 't' is 3 m sec.
- (v) the time taken for the voltage to reach 200V for the first time after passing through zero value.

Solution : (i) Given that, $v = 282.8 \sin 377 t$

Comparing above equation with

$$v = V_{in} \sin \omega t$$

$$\omega = 377 \text{ rad/sec.}$$

$$\therefore \text{Frequency, } f = \frac{377}{2\pi} = \frac{377}{2 \times 3.14} = 60 \text{ Hz (Ans.)}$$

(ii) RMS value of the voltage, $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{282.8}{\sqrt{2}} = \mathbf{200\text{ V}}$ (Ans.)

(iii) Average value, $V_{av} = \frac{2V_m}{\pi} = \frac{2 \times 282.8}{\pi} = \mathbf{180\text{ V}}$ (Ans.)

(iv) $v = 282.8 \sin 377 t$. At $t = 3\text{ ms} = 3 \times 10^{-3}\text{ s}$


$v = 282.8 \sin 377 \times 3 \times 10^{-3} = \mathbf{255.9\text{ V}}$ (Ans.)

(v) $v = 282.8 \sin 377 t$ or $200 = 282.8 \sin 377 t$

or $t = \frac{1}{377} \sin^{-1} \left(\frac{200}{282.8} \right) = 2.08 \times 10^{-3}\text{ s} = \mathbf{2.08\text{ ms}}$ (Ans.)

Example 2.2. Find the rms value, average value and form factor of the voltage waveform shown in fig.2.12.

Solution : Average value of voltage over one cycle
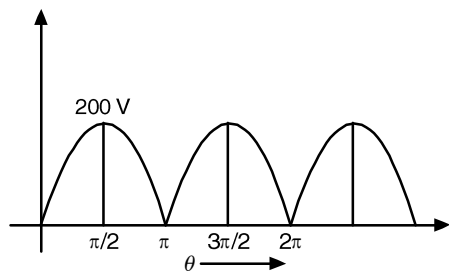
$$\begin{aligned} &= \frac{2 \int_0^{\pi} V_m \sin \theta d\theta}{2\pi} = \frac{V_m}{\pi} \int_0^{\pi} \sin \theta d\theta \\ &= \frac{2V_m}{\pi} = \frac{2}{\pi} \times 200 = \mathbf{127.32\text{ V}} \text{ (Ans.)} \end{aligned}$$


RMS value of voltage over one cycle

Fig.2.12: Full-wave rectified wave

$$\begin{aligned} &= \sqrt{\frac{2 \int_0^{\pi} V_m^2 \sin^2 \theta d\theta}{2\pi}} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} 2 \sin^2 \theta d\theta} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta} \\ &= \sqrt{\frac{V_m^2}{2\pi} \times \pi} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = \mathbf{141.42\text{ V}} \text{ (Ans.)} \end{aligned}$$

Form factor = $\frac{\text{RMS value}}{\text{Average value}} = \frac{141.42}{127.32} = \mathbf{1.11}$ (Ans.)

Example 2.3. Find the average and rms values of the current, $i(t) = 10 + 10 \sin 314t$.

Solution : The wave diagram of given current $i(t) = 10 + 10 \sin 314t$ is shown in fig.2.13.

Average value of the given current,

$$\begin{aligned}
 I_{av} &= I_{dc} + I_{av} \text{ of ac component.} \\
 &= 10 + \frac{2 I_m}{\pi} = 10 + \frac{2 \times 10}{\pi} \\
 &= 10 + 6.366 = \mathbf{16.366 \text{ A (Ans.)}}
 \end{aligned}$$

RMS value of the given current

$$\begin{aligned}
 I_{rms} &= I_{dc} + I_{rms} \text{ of ac component} \\
 &= 10 + \frac{I_m}{\sqrt{2}} = 10 + \frac{10}{\sqrt{2}} \\
 &= 10 + 7.071 = \mathbf{17.071 \text{ A (Ans.)}}
 \end{aligned}$$

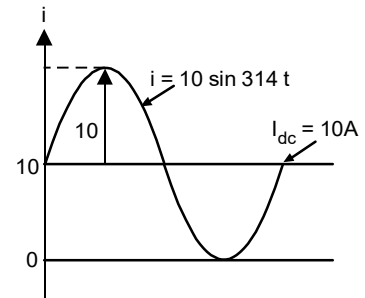


Fig.2.13: Wave diagram

Example 2.4. Calculate the average value, r.m.s. value, form factor and peak factor of a periodic current wave having values for equal time interval changing suddenly from one value to next : 0, 30, 45, 60, 90, 60, 45, 30, 0, -30, -45, -60 etc. ampere. What would be the average and the r.m.s. value of a sine wave having the same peak value ?

Solution : The periodic wave form of the alternating current is shown in fig.2.14.

Average value of current,

$$\begin{aligned}
 I_{av} &= \frac{i_1 + i_2 + \dots + i_n}{n} \text{ (where } n = 8 \text{)} \\
 &= \frac{0 + 30 + 45 + 60 + 90 + 60 + 45 + 30}{8} \\
 &= \mathbf{45 \text{ A (Ans.)}}
 \end{aligned}$$

R.M.S. value of current,

$$\begin{aligned}
 I_{r.m.s.} &= \sqrt{\frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}} = \sqrt{\frac{0^2 + (30)^2 + (45)^2 + (60)^2 + (90)^2 + (60)^2 + (45)^2 + (30)^2}{8}} \\
 &= \sqrt{\frac{21150}{8}} = \mathbf{51.42 \text{ A (Ans.)}}
 \end{aligned}$$

$$\text{Form factor} = \frac{I_{r.m.s.}}{I_{av}} = \frac{51.42}{45} = \mathbf{1.1427 \text{ (Ans.)}}$$

$$\text{Peak factor} = \frac{I_m}{I_{r.m.s.}} = \frac{90}{51.42} = \mathbf{1.75 \text{ (Ans.)}}$$

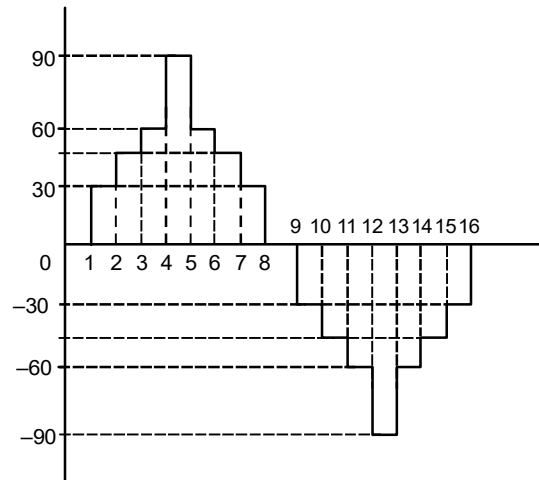


Fig.2.14: Wave shape of periodic current

Average value of sinusoidal a.c. having peak value of 90 A ;

$$I_{av} = 0.637 I_m = 0.637 \times 90 = 57.33 \text{ A (Ans.)}$$

R.M.S. value,

$$I_{r.m.s.} = \frac{I_m}{\sqrt{2}} = \frac{90}{\sqrt{2}} = 63.64 \text{ A (Ans.)}$$

PRACTICE EXERCISE

1. An alternating voltage is given by $v = 141.4 \sin 314t$. Find
 - (i) Frequency
 - (ii) r.m.s. value
 - (iii) average value
 - (iv) the instantaneous value of voltage when 't' is 3 m sec.
 - (v) the time taken for the voltage to reach 200V for the first time after passing through zero value.
(Ans, 50Hz, 100V, 90V, 114.4V, 2.5ms)
2. Find the rms value, average value and form factor of a rectified sinusoidal ac voltage having maximum value of 100V. (Ans, 63.66V, 70.71V, 1.11)
3. Find the average and rms values of the current, $I(t) = 15 + 15 \sin 314t$ (Ans, 24.55A, 25.6A).
4. Calculate the average value, r.m.s. value, form factor and peak factor of a periodic current wave having values for equal time interval changing suddenly from one value to next : 0, 20, 45, 50, 80, 50, 45, 20, 0, -20, -45, -50 etc. ampere. What would be the average and the r.m.s. value of a sine wave having the same peak value ?
(Ans, 38.75A, 45.07A, 1.163, 1.775, 50.96A, 56.56A)

2.16. PHASOR REPRESENTATION OF SINUSOIDAL QUANTITY

It has been seen that an alternating quantity (varying sinusoidally) can be represented in the form of wave and equation. The wave form shows the graphical representation, whereas, the equation represents the mathematical expression of the instantaneous value of an alternating quantity.

The same alternating quantity can also be represented by a line of definite length (representing its maximum value) rotating in counter-clockwise direction at a constant velocity (ω radians/second). Such a rotating line is called a *phasor*.

Thus, an alternating quantity can be represented by a phasor which shows its magnitude and direction at that instant.

For instant, consider an alternating quantity (current) represented by the equation $i = I_m \sin \omega t$. Take a line OA to represent the maximum value of current I_m to scale. Imagine this line is rotating in counter-clockwise direction at an angular velocity of ω radian/s about point O . After t seconds the line is rotated through an angle θ ($\theta = \omega t$), from its horizontal position as shown in fig.2.15. The projection of line OA on the Y -axis is OB .

$$\begin{aligned} OB &= OA \sin \theta = I_m \sin \omega t \\ &= i \text{ (the value of current at that instant)} \end{aligned}$$

Hence, the projection of the phasor OA on the Y -axis (i.e. OB) at any instant gives the value of current at that instant.

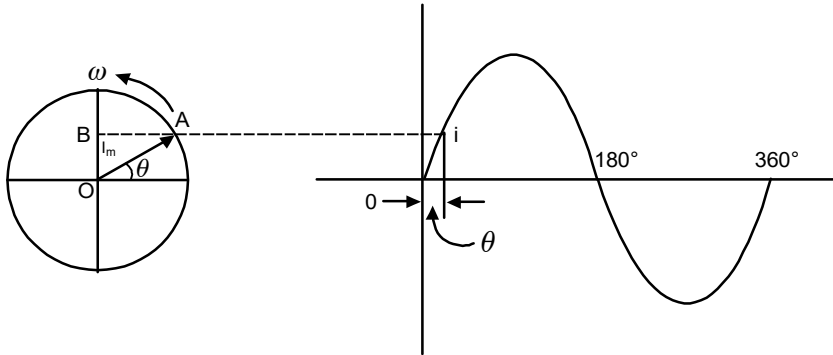


Fig. 2.15: Plotting of sine wave

Thus, a sinusoidal alternating quantity is represented by a phasor (vector) of length to scale equal to its maximum value rotated through an angle θ with the axis of reference (*i.e.* X -axis).

The phasor representation of an alternating quantity enables us to understand its magnitude and position on the axis. The alternating quantities can be added and subtracted with a fair degree of ease by representing them vectorially (phasor diagram).

2.17. PHASE AND PHASE DIFFERENCE

The phase of an alternating quantity (current or voltage) at an instant is defined as the fractional part of a cycle through which the quantity has advanced from a selected origin (see fig.2.16). In actual practice, we are more concerned with the phase difference between the two alternating quantities rather than their *absolute phase*.

The two alternating quantities having same frequency, when attain their zero value at different instants, the quantities are said to have a phase difference. This angle between zero points (and are becoming positive) of two alternating quantities is called *angle of phase difference*.

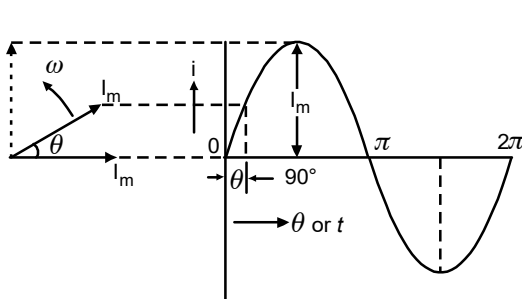


Fig.2.16: Phasor and wave diagram (single quantity)

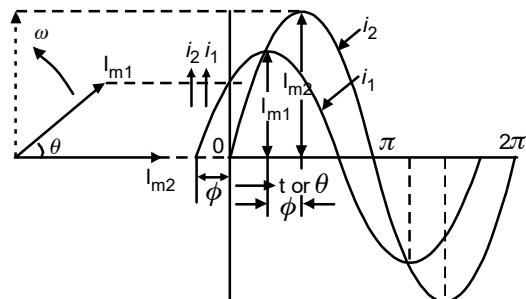


Fig.2.17: Phasor and wave diagram (two quantities)

In fig. 2.17, two alternating currents of magnitude I_{m1} and I_{m2} are shown vectorially. Both the vectors are rotating at same angular velocity of ω radian per second. The zero values are obtained by the two currents at different instants. Therefore, they are said to have a phase difference of angle ϕ .

In other words, **the phase difference may be defined as the angular displacement between the maximum positive value of the two alternating quantities having the same frequency.**

The quantity which attains its +ve maximum value prior to the other is called a *leading* quantity, whereas, the quantity which attains its +ve maximum value after the other is called a *lagging* quantity. In this case current I_{m1} is leading current w.r.t. I_{m2} or in other words current I_{m2} is the lagging current w.r.t. I_{m1} .

2.18. ADDITION AND SUBTRACTION OF ALTERNATING QUANTITIES

In a.c. circuits, sometimes it is required to add or subtract the alternating quantities. In such cases, we proceed as follows :

Addition of alternating quantities

The given alternating quantities are represented as phasors and then they are added in the same manner as forces are added. Only phasors of the similar quantities are added *i.e.* either all the currents are added or all the voltages are added. Voltages and currents are never added with each other. For addition, the following method is most suitable and simple:

Method of components : In this method each phasor is resolved into horizontal and vertical components. The horizontal components are added algebraically to obtain the resultant horizontal component I_{XX} . Similarly, vertical components are summed up algebraically to obtain the resultant vertical component I_{YY} .

Consider an a.c. parallel circuit consisting of three branches each carrying a current of i_1 , i_2 and i_3 respectively as shown in fig. 2.18. Let the three currents be represented by ;

$$i_1 = I_{m1} \sin (\omega t + \theta_1) ;$$

$$i_2 = I_{m2} \sin \omega t$$

and

$$i_3 = I_{m3} \sin (\omega t - \theta_2)$$

The maximum values of the three currents I_{m1} , I_{m2} and I_{m3} are represented by the phasors as shown in fig.2.19(a).

Resolving the components horizontally and vertically.

Algebraic sum of horizontal components ;

$$I_{XX} = I_{m1} \cos \theta_1 + I_{m2} + I_{m3} \cos \theta_2$$

Algebraic sum of vertical components ;

$$I_{YY} = I_{m1} \sin \theta_1 + 0 - I_{m3} \sin \theta_2$$

Maximum value of resultant components ;

$$I_{mr} = \sqrt{(I_{XX})^2 + (I_{YY})^2}$$

If ϕ is the phase difference (leading) between resultant current and horizontal axis as shown in fig. 2.19(b). Then

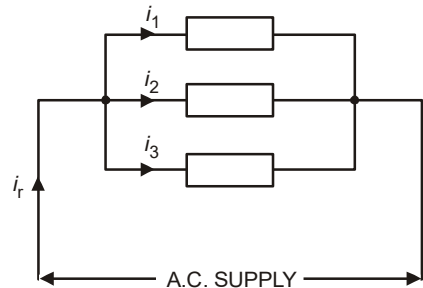
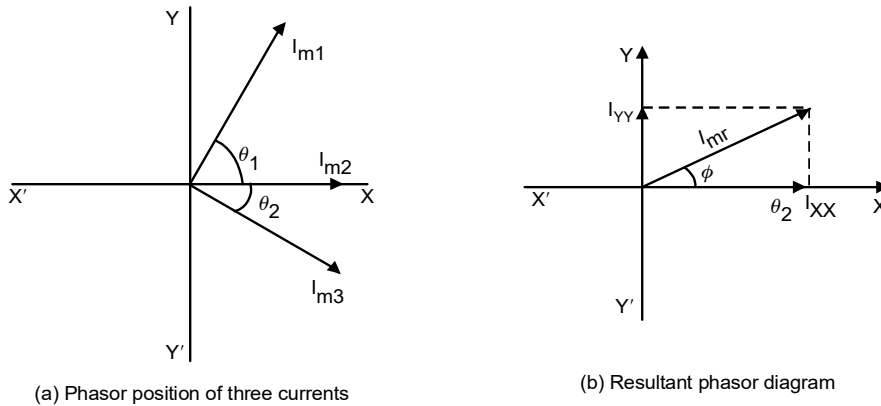


Fig.2.18: Circuit diagram

**Fig.2.19:** Phasor diagram.

$$\phi = \tan^{-1} \frac{I_{YY}}{I_{XX}}$$

The instantaneous value of the resultant current is given by the relation ;

$$i_r = I_{mr} \sin (\omega t + \phi)$$

However, if I_{YY} comes out to be negative, the angle of phase difference will be lagging (*i.e.* $-\phi$). Then the instantaneous value of the resultant current will be given by the relation

$$i_r = I_{mr} \sin (\omega t - \phi)$$

Subtraction of alternating quantities

The methods explained above (*i.e.* parallelogram method and method of components) are also applied for the subtraction of an alternating quantity. The only difference is that in this case, the phasor of the alternating quantity which is to be subtracted is reversed or represented 180° out of phase. Then it is added with the other alternating quantity (or quantities) as usual.

Example 2.5. Draw a phasor diagram showing the following voltages.

$$v_1 = 100 \sin 500 t ;$$

$$v_2 = 200 \sin (500 t + \pi/3)$$

$$v_3 = -50 \cos 500 t ;$$

$$v_4 = 150 \sin (500 t - \pi/4)$$

Find RMS value of resultant voltage.

Solution : $v_1 = 100 \sin 500 t$


$$v_2 = 200 \sin \left(500 t + \frac{\pi}{3} \right)$$

$$v_3 = -50 \cos 500 t$$

$$= -50 \sin \left(\frac{\pi}{2} - 500 t \right)$$

$$= 50 \sin (500 t - \pi/2)$$

$$v_4 = 150 \sin (500 t - \pi/4)$$

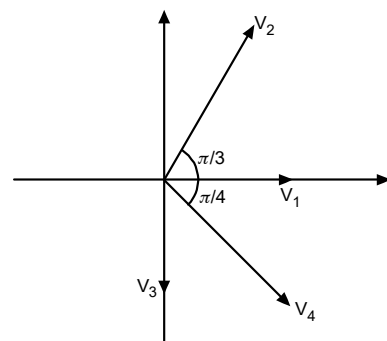**Fig.2.20:** Phasor representation of three voltages

All the four voltages are shown vectorially in fig.2.20.

Resolving the phasors in horizontal axis ;

$$\begin{aligned} V_{xx} &= V_1 \cos 0 + V_2 \cos \frac{\pi}{3} + V_3 \cos \frac{\pi}{2} + V_4 \cos \frac{\pi}{4} \\ &= 100 \times 1 + 200 \times 0.5 + 50 \times 0 + 150 \times 0.707 = 306.05 \text{ V} \end{aligned}$$

Resolving the phasors in vertical axis ;

$$\begin{aligned} V_{yy} &= V_1 \sin 0 + V_2 \sin \frac{\pi}{3} - V_3 \sin \frac{\pi}{2} - V_4 \sin \frac{\pi}{4} \\ &= 100 \times 0 + 200 \times 0.866 - 50 \times 1 - 150 \times 0.707 = 17.15 \text{ V} \end{aligned}$$

Maximum value of resultant voltage ;

$$V_{mr} = \sqrt{V_{xx}^2 + V_{yy}^2} = \sqrt{(306.05)^2 + (17.15)^2} = 306.53 \text{ V}$$

$$\text{RMS value of resultant voltage, } V_{rms(r)} = \frac{V_{mr}}{\sqrt{2}} = \frac{306.53}{\sqrt{2}} = \mathbf{216.75 \text{ V (Ans.)}}$$

2.19. A.C. CIRCUIT CONTAINING ONLY RESISTANCE (R)

The circuit containing a pure resistance (R) ohm is shown in fig.2.21.

The alternating voltage applied across the circuit is given by the equation ;

$$v = V_m \sin \omega t$$

The instantaneous value of current flowing through the resistor will be ;

$$i = \frac{v}{R} = \frac{V_m}{R} \sin \omega t \quad \dots(ii)$$

The value of current will be maximum when

$$\omega t = 90^\circ \text{ or } \sin \omega t = 1$$

$$I_m = V_m / R$$

Substituting this value in equation (ii), we get,

$$i = I_m \sin \omega t \quad \dots(iii)$$

Phase angle : The equation (i) and (iii), clearly show that there is no phase difference between applied voltage and current flowing through the circuit i.e. phase angle between voltage and current is zero. The phasor diagram and wave diagram is shown in fig.2.22 (a) and 2.22 (b) respectively.

Hence, in an a.c. circuit containing pure resistance,

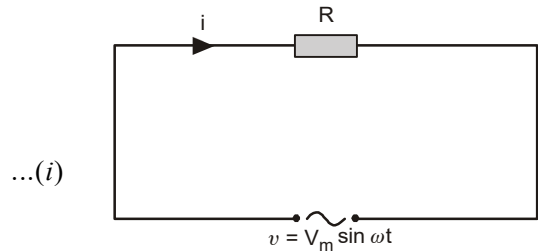


Fig.2.21: Circuit containing only resistance

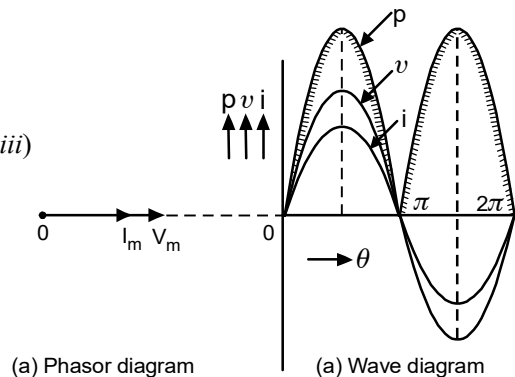


Fig.2.22: Phasor and Wave diagram

current is in phase with the voltage.

Power

Instantaneous power, $p = vi = (V_m \sin \omega t) (I_m \sin \omega t)$

$$= \frac{V_m I_m}{2} 2 \sin^2 \omega t$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} (1 - \cos 2 \omega t) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} - \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos 2 \omega t$$

Average power consumed in the circuit over a complete cycle.

$$P = \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} - \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos 2 \omega t$$

$$\text{or} \quad P = V_{r.m.s.} I_{r.m.s.} - \text{zero} \quad \text{or} \quad P = VI$$

Power curve : Fig.2.22. (b) shows the power curve for a pure resistive circuit. Points on the power curve are obtained from the product of the corresponding instantaneous values of voltage and current.

2.20. A.C. CIRCUIT CONTAINING PURE INDUCTANCE (L)

The circuit containing a pure inductance of L henry is shown in fig.2.23.

The alternating voltage applied across the circuit is given by the equation ;

$$v = V_m \sin \omega t \quad \dots(i)$$

As a result, an alternating current i flows through the inductance which induces an e.m.f. in it, given by the relation;

$$e = -L \frac{di}{dt}$$

This induced e.m.f. is equal and opposite to the applied voltage.

$$\therefore v = -e = -\left(-L \frac{di}{dt}\right)$$

$$\text{or} \quad V_m \sin \omega t = L \frac{di}{dt} \quad \text{or} \quad di = \frac{V_m}{L} \sin \omega t dt$$

Integrating both sides,

$$\int di = \int \frac{V_m}{L} \sin \omega t dt \quad \text{or} \quad i = \frac{V_m}{\omega L} (-\cos \omega t)$$

$$\text{or} \quad i = \frac{V_m}{\omega L} \sin (\omega t - \pi/2) = \frac{V_m}{X_L} \sin (\omega t - \pi/2) \quad \dots(ii)$$

where $X_L = \omega L$ is the opposition offered to the flow of alternating current by a pure inductance and is called **inductive reactance**.

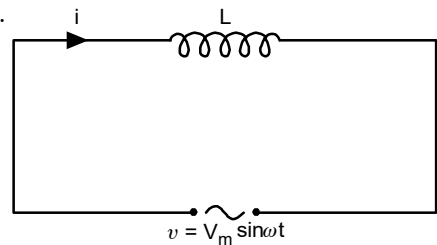


Fig.2.23: Circuit containing pure inductance

The value of current will be maximum when $\sin(\omega t - \pi/2) = 1$ i.e. $I_m = \frac{V_m}{X_L}$

$$\therefore i = I_m \sin(\omega t - \pi/2) \quad \dots(iii)$$

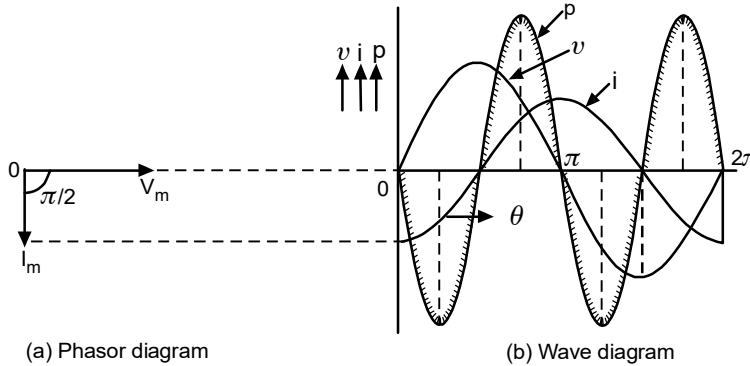


Fig. 2.24: Phasor and Wave diagram

Phase angle : The equation (i) and (iii), clearly show current flowing through a pure inductive circuit lags behind the applied voltage v by 90° . The phasor diagram is shown in fig. 2.24 (a) and 2.24 (b) respectively.

Hence, in an a.c. circuit containing pure inductance, **current lags behind the voltage by 90° .**

Power : Instantaneous power, $p = vi = V_m \sin \omega t \times I_m \sin(\omega t - \pi/2)$

$$\begin{aligned} &= V_m I_m \sin \omega t \cos \omega t = \frac{V_m I_m}{2} 2 \sin \omega t \cos \omega t \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \sin 2 \omega t \end{aligned}$$

Average power consumed in the circuit over a complete cycle,

$$P = \text{average} \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \sin 2 \omega t = \text{zero}$$

Hence, average power consumed in a pure inductive circuit is **zero**.

Power curve : The power curve for a pure inductive circuit is shown in fig. 3.4 (b). It is very clear that average power in a half cycle (one alternation) is zero, as the negative and positive loop area under power curve is the same.

It is interesting to note that during the first quarter cycle, what so ever power (or energy) is supplied by the source to the inductance (or coil) is stored in the magnetic field set-up around it. However, in the next quarter cycle, the magnetic field collapses and the power (or energy) stored in the field is returned to the source. This process is repeated in each and every alternation. Hence, no power or energy is consumed in this circuit.

2.21. A.C. CIRCUIT CONTAINING PURE CAPACITANCE (C)

The circuit containing a pure capacitor of capacitance C farad is shown in fig.2.25.

The alternating voltage applied across the circuit is given by the equation ;

$$v = V_m \sin \omega t \quad \dots(i)$$

Charge on the capacitor at any instant,

$$q = C v$$

Current flowing through the circuit,

$$i = \frac{d}{dt} q = \frac{d}{dt} (C v)$$

$$\text{or} \quad i = \frac{d}{dt} C V_m \sin \omega t = C V_m \frac{d}{dt} \sin \omega t$$

$$\text{or} \quad i = \omega C V_m \cos \omega t = \frac{V_m}{1/\omega C} \sin (\omega t + \pi/2) = \frac{V_m}{X_C} \sin (\omega t + \pi/2) \quad \dots(ii)$$

where $X_C = 1/\omega C$ is the opposition offered to the flow of alternating current by a pure capacitor and is called *capacitive reactance*.

The value of current will be maximum when $\sin (\omega t + \pi/2) = 1$

$$\text{i.e.} \quad I_m = V_m/X_C$$

Substituting this value in equation (ii), we get,

$$i = I_m \sin (\omega t + \pi/2) \quad \dots(iii)$$

Phase angle : The equation (i) and (iii), clearly show that current flowing through pure capacitive circuit leads the applied voltage by 90° . The phasor diagram and wave diagram is shown in fig.2.26 (a) and 2.26 (b) respectively.

Hence, in an a.c. circuit containing pure capacitance **current leads the voltage by 90°** .

Power : Instantaneous power, $p = v i = V_m \sin \omega t \times I_m \sin (\omega t + \pi/2)$

$$= V_m I_m \sin \omega t \cos \omega t = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \sin 2 \omega t$$

or Average power over a complete cycle,

$$P = \text{zero}$$

Hence, average power consumed in a pure capacitive circuit is **zero**.

Power curve : The power curve for a pure capacitive circuit is shown in fig. 2.26 (b). It is very clear from the curve that average power in a half cycle (one alternation) is zero since the positive and negative loop area under power curve is the same.

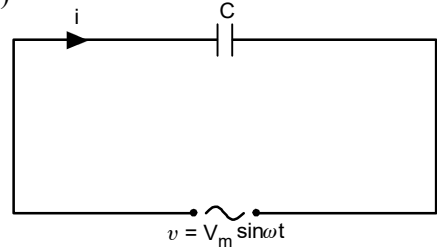


Fig.2.25: Circuit containing pure capacitance

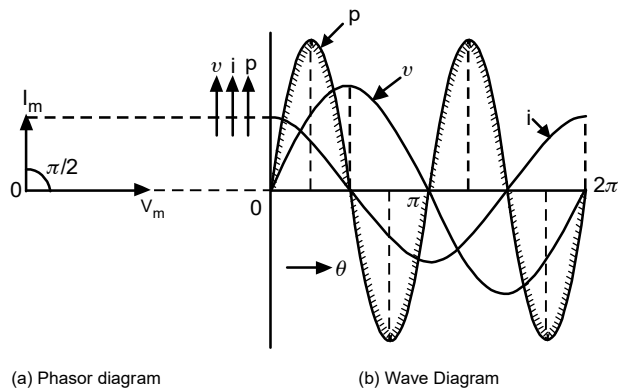


Fig. 2.26: Phasor and wave diagram

It is interesting to note that, during the first quarter cycle, what so ever power (or energy) is supplied by the source to the capacitor is stored in the electric field set-up between the capacitor plates. In the next quarter cycle, the electric field collapses and the power (or energy) stored in the field is returned to the source. This process is repeated in each alternation. **Hence, no power is consumed by this circuit.**

Example 2.6. An a.c. circuit consists of a pure resistance of 8 ohm and is connected across an a.c. supply of 240 V, 50 Hz. Calculate (i) current ; (ii) power consumed and (iii) write down the equation for voltage and current.

Solution : (i) Current in the circuit, $I = \frac{V}{R} = \frac{240}{8} = 30 \text{ A (Ans.)}$

(ii) Power consumed, $P = VI = 240 \times 30 = 7200 \text{ W (Ans.)}$

(iii) Maximum value of applied voltage, $V_m = \sqrt{2} V = \sqrt{2} \times 240 = 339.4 \text{ V}$

Maximum value of current, $I_m = \sqrt{2} \times 30 = 42.42 \text{ A}$

Angular velocity, $\omega = 2 \pi f = 2 \pi \times 50 = 314.16 \text{ rad/s}$

Equation for applied voltage ;

$$v = V_m \sin \omega t = 339.4 \sin 314.16 t \text{ (Ans.)}$$

As in a pure resistive circuit, voltage and current are in phase with each other, therefore, current is given by the equation ;

$$i = I_m \sin \omega t = 42.42 \sin 314.16 t \text{ (Ans.)}$$

Example 2.7. An inductive coil having negligible resistance and 0.1 henry inductance is connected across 230 V, 50 Hz supply. Find (i) the inductive reactance (ii) r.m.s. value of current (iii) power and (iv) equations for voltage and current.

Solution : Inductive reactance, $X_L = 2 \pi L = 2 \pi \times 50 \times 0.1 = 31.416 \Omega \text{ (Ans.)}$

Current, $I = 230/X_L = 200/31.416 = 7.32 \text{ A (Ans.)}$

Power, $P = \text{Zero (Ans.)}$

Now, $V_m = \sqrt{2} V = \sqrt{2} \times 230 = 325.27 \text{ V ;}$

$$I_m = \sqrt{2} I = \sqrt{2} \times 7.32 = 10.35 \text{ A}$$

and

$$\omega = 2 \pi f = 314 \text{ rad/s}$$

\therefore

$$v = V_m \sin \omega t = \mathbf{325.27 \sin 314 t \text{ (Ans.)}}$$

In pure inductive circuit, current lags behind voltage by $\pi/2$ radian.

\therefore

$$i = I_m \sin (\omega t - \pi/2) = \mathbf{10.35 \sin (314 t - \pi/2) \text{ (Ans.)}}$$

Example 2.8. A capacitor has a capacitance of 50 microfarad. Find its capacitive reactance for frequencies of 25 and 50 Hz. Find in each case the current if the supply voltage is 400 V.

Solution : Capacitance of the capacitor, $C = 50 \times 10^{-6} \text{ F}$

Supply voltage, $V = 400 \text{ V}$

When supply frequency, $f_1 = 25 \text{ Hz}$

$$\text{Capacitive reactance, } X_{C1} = \frac{1}{\omega_1 C} = \frac{1}{2\pi f_1 C} = \frac{1}{2\pi \times 25 \times 50 \times 10^{-6}} = \mathbf{127.32 \Omega \text{ (Ans.)}}$$

$$\text{Current in the circuit, } I_1 = \frac{V}{X_{C1}} = \frac{400}{127.32} = \mathbf{3.14 \text{ A (Ans.)}}$$

When supply frequency, $f_2 = 50 \text{ Hz}$

$$\text{Capacitive reactance, } X_{C2} = \frac{1}{\omega_2 C} = \frac{1}{2\pi f_2 C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = \mathbf{63.66 \Omega \text{ (Ans.)}}$$

$$\text{Current in the circuit, } I_2 = \frac{V}{X_{C2}} = \frac{400}{63.66} = \mathbf{6.28 \text{ A (Ans.)}}$$

PRACTICE EXERCISE

1. An a.c. circuit consists of a pure resistance of 16 ohm and is connected across an a.c. supply of 230 V, 50 Hz. Calculate (i) current ; (ii) power consumed and (iii) write down the equation for voltage and current.
(Ans, 23 A, 5290 W ; 325.27 Sin 314.16 t ; 32.53 sin 314.16 t)
2. An inductive coil having negligible resistance and 0.1 henry inductance is connected across 200 V, 50 Hz supply. Find (i) the inductive reactance (ii) r.m.s. value of current (iii) power and (iv) equations for voltage and current.
(Ans, 31.416 Ω ; 6.366 A ; 0 W, 282.84 sin 314 t, 9 sin (314t- $\pi/2$)
3. A capacitor has a capacitance of 30 microfarad. Find its capacitive reactance for frequencies of 25 and 50 Hz. Find in each case the current if the supply voltage is 440 V.
(Ans, 212.2 Ω , 2.073 A ; 106.1 Ω ; 4.146 A)

2.22. A.C. SERIES CIRCUITS

An ac circuit may have combination of resistance, inductance and capacitance. In actual practice, a.c. circuits contain two or more than two such components connected in series or parallel. A series circuit is a circuit in which each component carries the same current. An a.c. series circuit may be ;

- (i) $R - L$ series circuit (ii) $R - C$ series circuit (iii) $R - L - C$ series circuit.

2.23. R – L SERIES CIRCUIT

An R - L series circuit contains resistance (R) and inductance (L) connected in series as shown in fig 2.27

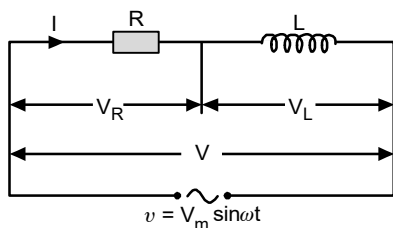


Fig. 2.27: R-L series circuit

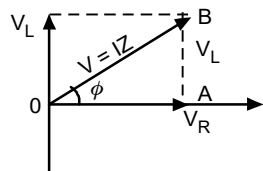


Fig.2.28: Phasor diagram

Its phasor diagram is shown in fig. 2.28. To draw the phasor diagram, current I (r.m.s. value) is taken as the reference vector. Voltage drop in resistance $V_R (= IR)$ is taken in phase with current vector, whereas, voltage drop in inductive reactance $V_L (= IX_L)$ is taken 90° ahead of the current vector (since current lags behind the voltage by 90° in pure inductive circuit). The vector sum of these two voltages (drops) is equal to the applied voltage V (r.m.s. value).

Now, $V_R = IR$ and $V_L = IX_L$ (where $X_L = 2 \pi f L$)

In right angle triangle OAB

$$V = \sqrt{(V_R)^2 + (V_L)^2} = \sqrt{(IR)^2 + (IX_L)^2} = I \sqrt{R^2 + X_L^2}$$

or
$$I = \frac{V}{\sqrt{R^2 + X_L^2}} = \frac{V}{Z}$$

where $Z = \sqrt{R^2 + X_L^2}$ is the total opposition offered to the flow of alternating current by an $R - L$ series circuit and is called *impedance* of the circuit. It is measured in ohm.

Phase angle : From the phasor diagram shown in fig.2.28, it is clear that current, in this circuit, lags behind the applied voltage by an angle ϕ , called *phase angle*.

From phasor diagram ; $\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R}$ or $\phi = \tan^{-1} X_L/R$

Power : If the alternating voltage applied across the circuit is given by the equation.

$$v = V_m \sin \omega t$$

Then,
$$i = I_m \sin (\omega t - \phi)$$

\therefore Instantaneous power, $p = v i$

$$\begin{aligned}
 &= V_m \sin \omega t \cdot I_m \sin (\omega t - \phi) = \frac{V_m I_m}{2} 2 \sin \omega t \sin (\omega t - \phi) \\
 &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} [\cos \phi - \cos (2 \omega t - \phi)] \\
 &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi - \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos (2 \omega t - \phi)
 \end{aligned}$$

Average power consumed in the circuit over a complete cycle,

$$P = \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi - \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos (2 \omega t - \phi)$$

or
$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi - \text{zero} = V_{r.m.s.} I_{r.m.s.} \cos \phi = VI \cos \phi$$

where $\cos \phi$ is called *power factor* of the circuit.

From phasor diagram ; $\cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z}$

Thus, **power factor** is defined as the cosine of the angle between voltage and current in an a.c. circuit. It may also be defined as the ratio of resistance to impedance of an a.c. circuit.

Alternatively : Power, $P = VI \cos \phi = IZ \cdot I \cdot \frac{R}{Z} = I^2 R$

This shows that power is actually consumed in resistance only ; inductance does not consume any power.

Power curve : The phasor diagram and wave diagram for voltage and current are shown in fig.2.29 (a) and 2.29 (b) respectively where applied voltage ($v = V_m \sin \omega t$) is taken as reference quantity. The power curve for $R - L$ series circuit is also shown in fig. 2.29 (b). The points on the power curve are obtained from the product of the corresponding instantaneous values of voltage and current. It is clear that power is negative between angle 0 and ϕ and between 180° and $(180 + \phi)$. During rest of the cycle the power is positive. Since the area under the positive loops is greater than that under the negative loops, the net power over a complete cycle is positive. Hence, a definite quantity of power is utilised or consumed by this circuit.

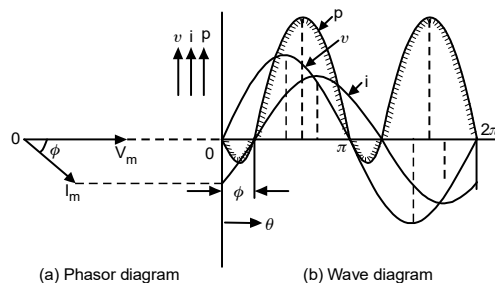


Fig. 2.29: Phasor and wave diagram.

2.24. IMPEDANCE TRIANGLE

The simplified phasor diagram of $R - L$ series circuit is shown in fig. 2.30. When each side of this phasor diagram is divided by a common factor I , we get another right angled triangle, as shown in fig. 2.31, whose sides represent R , X_L and Z . Such a triangle is known as *impedance triangle*.

Thus, a right angled triangle whose base represents circuit resistance, perpendicular represents circuit reactance and hypotenuse represents circuit impedance is called an **impedance triangle**.

The concept of impedance triangle is useful since it enables us to calculate :

(i) the impedance of the circuit,

$$Z = \sqrt{R^2 + X^2}$$

(ii) the power factor of the circuit,

$$\cos \phi = R/Z$$

(iii) phase angle, $\phi = \tan^{-1} X_L/R$.

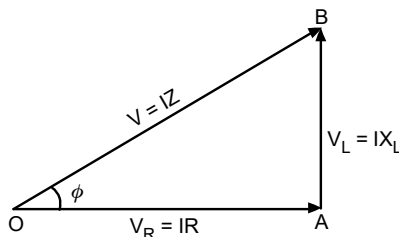


Fig.2.30: Voltage triangle for an R - L series circuit

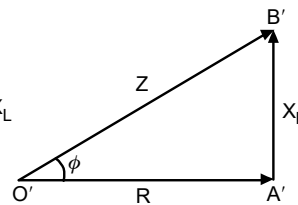


Fig.2.31: Impedance triangle

2.25. TRUE POWER AND REACTIVE POWER

The power which is actually consumed or utilised in an a.c. circuit is called *true power* or *active power* or *real power*. We have seen that power is consumed only in resistance. A pure inductor and a pure capacitor do not consume any power, since in a half cycle what so ever power is received from the source by these components the same is returned to the source. This power which flows back and forth (*i.e.* in both directions in the circuit) or reacts upon itself is called *reactive power*. It does not do any useful work in the circuit. It has been seen that in pure resistive circuit current is in phase with the applied voltage, whereas, in pure inductive and capacitive circuit, current is 90° out of phase. Thus, it is concluded that the current in phase with the voltage produces true or active power, whereas, the current 90° out of the phase with the voltage contributes to reactive power. Hence,

True power = voltage \times current in phase with voltage

Reactive power = voltage \times current 90° out of phase with voltage.

The phasor diagram for an inductive circuit is shown in fig. 2.32. where current I lags behind the voltage V by an angle ϕ° . The current I can be resolved into two rectangular components *i.e.* (i) $I \cos \phi$, in phase with voltage V and (ii) $I \sin \phi$, which is 90° out of phase with voltage V .

\therefore True power, $P = V \times I \cos \phi = VI \cos \phi$ watt

Reactive power, $P_r = V \times I \sin \phi = VI \sin \phi$ VAR

Apparent power, $P_a = V \times I = VI$ VA

The bigger units of true power, reactive power and apparent power are kW (or MW), $kVAR$ (or $MVAR$) and kVA (or MVA) respectively.

Active component of current : The current component

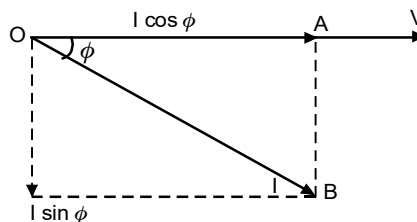


Fig.2.32: Active and reactive component of current

which is in phase with circuit voltage (*i.e.* $I \cos \phi$) and contributes to active or true power of the circuit is called *active component* or *wattfull component* or *in-phase component* of current.

Reactive component of current : The current component which is in quadrature (or 90° out of phase) to circuit voltage (*i.e.* $I \sin \phi$) and contributes to reactive power of the circuit is called *reactive component* of current.

Power triangle : When each component of current, in fig. 2.32, is multiplied by voltage V , a power triangle is obtained as shown in fig. 2.33. This right angled triangle indicates the relation among true power, reactive power and apparent power.

In the above discussion, the following points are worth noting :

- (i) When an active component of current is multiplied with circuit voltage, it results in active or true power. It is this power which produces torque in motors, heat in heaters, light in lamps etc. wattmeters indicate this power.
- (ii) When the reactive component of current is multiplied with circuit voltage, it results in reactive power. It is this power which merely flows back and forth without doing any work. This power determines the power factor of the circuit.
- (iii) When the circuit current is multiplied with circuit voltage, it results in apparent power. It is so called because it appears that product of voltage and current is power. But in a.c. circuits (except pure resistive circuit) there is usually phase difference between voltage and current so that VI does not give real power. To avoid confusion, it is measured in volt-ampere.
- (iv) From power triangle shown in fig. 2.33, the power factor may also be determined by taking ratio of true power to apparent power, *i.e.* power factor, $\cos \phi = \text{true power/apparent power}$.

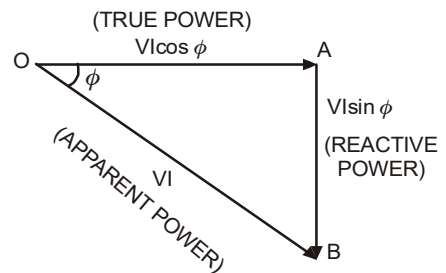


Fig.2.33: Power triangle

2.26. POWER FACTOR AND ITS IMPORTANCE

In a.c. circuits, the power factor may be expressed as :

$$p.f. = \cos \phi = R/Z = \text{true power/ apparent power}$$

In case of pure resistive circuit, current is in phase with circuit voltage *i.e.* $\phi = 0$. Therefore, power factor of the circuit, $\cos \phi = 1$. Whereas, in case of pure inductive or capacitive circuit, current is 90° out of phase with circuit voltage *i.e.* $\phi = 90^\circ$. Therefore, power factor of the circuit $\cos \phi = 0$. For circuits having resistance-inductance ; resistance-capacitance or resistance-inductance and capacitance, the power factor lies between 0 and 1. *It may be noted that the value of p.f. can never be more than one.*

Usually, the word *lagging* or *leading* is attached with the numerical value of p.f. to signify whether the current lags or leads the voltage. In inductive circuits, current always lags behind the voltage and their power factors are mentioned as lagging p.f. Whereas, for capacitive circuits, the power factor is mentioned as leading p.f. since in these cases current always leads the voltage vector.

Importance of power factor

The power factor of an a.c. circuit plays an important role in the power system. Since power of an a.c. circuit is given by the relation;

$$P = VI \cos \phi \text{ or } I = \frac{P}{V \cos \phi}$$

From the above relation, it is clear that for fixed power at constant voltage, the current drawn by the circuit increases with decrease in p.f.

Thus at low p.f., a.c. circuits draw more current from their mains and results in the following disadvantages :

1. **Greater conductor size :** At low p.f., the conductors are to carry more current for the same power therefore, they require larger area of cross-section.
2. **Poor efficiency :** At low power factors, the conductors have to carry larger current which increases copper losses ($I^2 R$) and results in poor efficiency.
3. **Larger voltage drop :** At lower power factors, the conductors have to carry larger current which increases voltage drop (IR) in the system and results in poor regulation.
4. **Larger kVA rating of equipment :** The kVA rating of electrical machines and equipment connected in the power system such as alternators, transformers, switch gears etc. will be more at lower power factors since it is inversely proportional to power factor (*i.e.* $\text{kVA} = \text{kW} / \cos \phi$).

To improve the power factor of an a.c. circuit a **capacitor** is connected across the circuit *i.e.* parallel to the circuit.

2.27. Q-FACTOR OF A COIL

Reciprocal of power factor of a coil is known as its *Q-factor*. It is also called quality factor or figure of merit of the coil.

$$\text{Mathematically, } Q\text{-factor} = \frac{1}{p.f.} = \frac{1}{\cos \phi} = \frac{Z}{R}$$

If the value of R is very small in comparison to its inductive reactance X_L then,

$$Q\text{-factor} = \frac{X_L}{R} = \frac{\omega L}{R}$$

$$\text{Also, } Q = 2\pi \times \frac{\text{maximum energy stored}}{\text{energy dissipated per cycle}}$$

Example 2.9. A coil having a resistance of 15Ω and an inductance of 63.66 mH is connected across a 250 V , 50 Hz supply. Calculate (i) the reactance and impedance of the coil, (ii) the current, (iii) the phase difference between current and the applied voltage and (iv) the power factor. Draw also the phasor diagram showing voltage and current.

Solution : The circuit is shown in fig.2.34.

(i) Reactance, $X_L = 2\pi fL = 2\pi \times 50 \times 63.66 \times 10^{-3} = 20 \Omega$ (Ans.)

Impedance, $Z = \sqrt{R^2 + X_L^2} = \sqrt{(15)^2 + (20)^2} = 25 \Omega$ (Ans.)

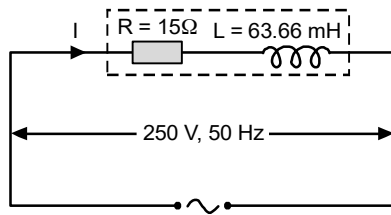


Fig. 2.34: Circuit diagram

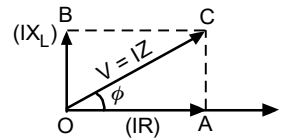


Fig.2.35: Phasor diagram

(ii) Current, $I = \frac{V}{Z} = \frac{250}{25} = 10 \text{ A}$ (Ans.)

(iii) Phase difference, $\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{20}{15} = \tan^{-1} 1.333 = 53.13^\circ$ (Ans.)

(iv) Power factor, $\cos \phi = 0.6$ lag (Ans.)

The phasor diagram for the circuit is shown in fig. 2.35.

Example 2.10. A coil connected to 50 V d.c. supply, draws 5 A and the same coil when connected to 50 V, a.c. voltage of frequency 50 Hz draws 2.5A. Calculate the parameters of the coil and power factor.

Solution : Let the resistance and inductance of the coil be R ohm and L henry respectively.

When coil is connected to d.c. supply, the opposition is only resistance of the coil,

\therefore Resistance of the coil, $R = \frac{V_{d.c.}}{I_{d.c.}} = \frac{50}{5} = 10\Omega$ (Ans.)

When coil is connected across a.c. supply of 50 V, 50 Hz, the opposition is impedance of the coil,

\therefore Impedance of the coil, $Z = \frac{V_{ac}}{I_{ac}} = \frac{50}{2.5} = 20 \Omega$

$$\text{Now, } Z = \sqrt{R^2 + X_L^2} \quad \text{or} \quad Z^2 = R^2 + X_L^2$$

or $X_L = \sqrt{Z^2 - R^2} = \sqrt{(20)^2 - (10)^2} = \sqrt{300}$

and $L = \frac{X_L}{2\pi f} = \frac{\sqrt{300}}{2\pi \times 50} = 55.13 \text{ mH}$ (Ans.)

\therefore Parameters are $R = 10 \Omega$ and $L = 55.13 \text{ mH}$

Power factor, $\cos \phi = \frac{R}{Z} = \frac{10}{20} = 0.5$ lagging (Ans.)

Example 2.11. A coil when connected to 230 V d.c. supply dissipates 2645 watt of power. When connected across 230 V a.c. supply of frequency 50 Hz., it dissipates 1058 watt of power. Calculate the value of resistance and inductance of the coil.

Solution : When d.c. is applied across the coil, the opposition is only resistance of the coil,

$$\therefore R = \frac{V_{dc}^2}{P_{dc}} = \frac{(230)^2}{2645} = 20 \, \Omega \text{ (Ans.)}$$

When a.c. is applied across the coil ;

$$P_{ac} = I_{ac}^2 R \text{ or } I_{ac} = \sqrt{P_{ac}/R} = \sqrt{1058/20} = 7.273 \text{ A}$$

$$\text{Impedance, } Z = \frac{V_{ac}}{I_{ac}} = \frac{230}{7.273} = 31.623 \, \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{(31.623)^2 - (20)^2} = 24.495 \, \Omega$$

$$\text{Inductance, } L = \frac{X_L}{2\pi f} = \frac{24.495}{2\pi \times 50} = 0.078 \text{ H (Ans.)}$$

Example 2.12. The voltage and current through a circuit element are

$$v = 100 \sin (314 t + 55^\circ) \text{ volt}$$

$$i = 10 \sin (314 t + 325^\circ) \text{ ampere}$$

Find the value of power drawn by the element.

Solution : Given

$$v = 100 \sin (314 t + 55^\circ) \text{ V}$$

$$i = 10 \sin (314 t + 325^\circ) \text{ A}$$

or

$$i = 10 \sin (314 t - 35^\circ) \text{ A}$$

Now their phasor representation is shown in fig. 2.36

\therefore Phase difference between voltage and current is 90° .

Now power drawn by the circuit, $P = VI \cos \phi$

$$= \frac{100}{\sqrt{2}} \times \frac{10}{\sqrt{2}} \times \cos 90^\circ$$

$$= \frac{1000}{2} \times 0^\circ = 0 \text{ W (Ans.)}$$

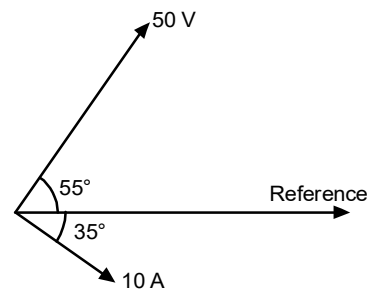


Fig.2.36: Phasor diagram

which indicates that element is pure inductive.

Example 2.13. A coil of resistance 1.5 ohm and impedance 6 ohm is placed in series with a second coil of resistance 2 ohm. When a voltage of 230 V, 50 Hz is applied to the circuit, the current flowing through the circuit is 7 A. Find the inductance of the second coil.

Solution : The circuit is shown fig. 2.37.

Impedance of whole circuit,

$$Z = V/I = 230/7 = 32.86 \, \Omega$$

Resistance of whole circuit,

$$R = R_1 + R_2 = 1.5 + 2 = 3.5 \, \Omega$$

Inductive reactance,

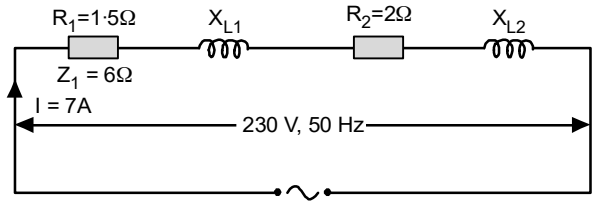


Fig.2.37: Circuit as per given data

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{(32.86)^2 - (3.5)^2} = 32.67 \, \Omega$$

Inductive reactance of I coil, $X_{L1} = \sqrt{Z_1^2 - R_1^2} = \sqrt{(6)^2 - (1.5)^2} = 5.81 \, \Omega$

Inductive reactance of II coil, $X_{L2} = X_L - X_{L1} = 32.67 - 5.81 = 26.86 \, \Omega$

∴ Inductance, $L_2 = X_{L2}/2\pi f = 26.86/2\pi \times 50 = 85.5 \, \text{m H (Ans.)}$

PRACTICE EXERCISE

1. A coil having a resistance of $12 \, \Omega$ and an inductance of $0.1 \, \text{H}$ is connected across a $100 \, \text{V}$, $50 \, \text{Hz}$ supply. Calculate (i) the reactance and impedance of the coil, (ii) the current, (iii) the phase difference between current and the applied voltage and (iv) the power factor. Draw also the phasor diagram showing voltage and current.

(Ans, $31.416 \, \Omega$; $33.63 \, \Omega$; $2.97 \, \text{A}$; 69.1° ; $0.3568 \, \text{lag}$)

2. A coil connected to $100 \, \text{V d.c.}$ supply draws $10 \, \text{A}$ and the same coil when connected to $100 \, \text{V, a.c.}$ voltage of frequency $50 \, \text{Hz}$ draws $5 \, \text{A}$. Calculate the parameters of the coil and power factor.

(Ans, $10 \, \Omega$; $55.13 \, \text{mH}$; $0.5 \, \text{lagging}$)

3. A coil when connected to $230 \, \text{V d.c.}$ supply dissipates $2000 \, \text{W}$ of power. When connected across $230 \, \text{V a.c.}$ supply of frequency $50 \, \text{Hz}$, it dissipates $800 \, \text{W}$ of power. Calculate the value of resistance and inductance of the coil.

(Ans, $20 \, \Omega$, $0.078 \, \text{H}$)

4. The voltage and current through a circuit element are

$$v = 50 \sin(314t + 70^\circ) \, \text{volt}$$

$$i = 10 \sin(314t + 340^\circ) \, \text{ampere}$$

Find the value of power drawn by the element.

(Ans. $0 \, \text{W}$)

5. A voltage $e = 200 \sin 100\pi t$ is applied to a coil having $R = 200 \, \text{ohm}$ and $L = 638 \, \text{millihenry}$. Find the expression for the current and also determine the power taken by the coil.

(Ans. $0.706 \sin(100\pi t - 45.06^\circ)$ $50 \, \text{W}$)

6. A non-inductive resistance of $10 \, \text{ohm}$ is connected in series with an inductive coil across $200 \, \text{V}$, $50 \, \text{Hz}$ ac supply. The current drawn by the series combination is $10 \, \text{ampere}$. The resistance of the coil is $2 \, \text{ohm}$. Determine (i) inductance of the coil (ii) Power factor (iii) voltage across the coil.

(Ans. $50.93 \, \text{mH}$; $0.6 \, \text{lag}$, $161.24 \, \text{V}$)

7. An inductive load is connected in series with a non-inductive resistance of $8 \, \text{ohms}$. The combination is connected across an a.c. supply of $100 \, \text{volt}$, $50 \, \text{Hz}$. A voltmeter connected

across the non-inductive resistor and then across the inductive load gives the reading of 64 volt and 48 volt respectively. Calculate the following :

- (i) impedance of the load ;
- (ii) Impedance of the combination ;
- (iii) Power absorbed by the load ;
- (iv) Power absorbed by the resistor ;
- (v) Total power taken from the supply ;
- (vi) Power factor of the load ;
- (vii) Power factor of the whole circuit.

(Ans. 6 ohm; 12.5 Ω ; 0.586 lag; 225 W; 512 W; 737 W; 0.586 lag; 0.92 lag)

8. An arc lamp (which may be regarded as being non-inductive) takes 10 A at 50 V. Calculate the impedance of choke of 1ohm resistance to be placed in series with it in order that it may be operated at 200 V, 50 Hz supply. Find also the total power used and the power factor.

(Ans. 19.105 Ω ; 0.3 lag; 600 W)

2.28. R – C SERIES CIRCUIT

A circuit that contains a pure resistance R ohm connected in series with a pure capacitor of capacitance C farad is known as $R - C$ series circuit.

An $R - C$ series circuit and its phasor diagram is shown in fig.2.38 and 2.39 respectively. To draw, the phasor diagram, current I (r.m.s. value) is taken as the reference vector. Voltage drop in

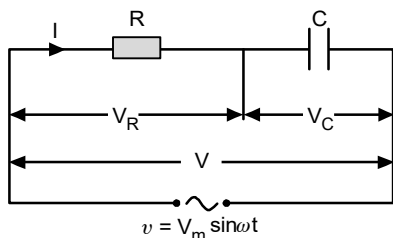


Fig. 2.38: R-C series circuit

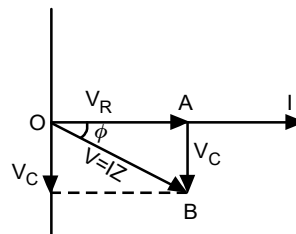


Fig. 2.39: Phasor diagram

resistance $V_R (= IR)$ is taken in phase with current vector, whereas, voltage drop in capacitive reactance $V_C (= IX_C)$ is taken 90° behind the current vector (since current leads the voltage by 90° in pure capacitive circuit). The vector sum of these two voltage drops is equal to the applied voltage V (r.m.s. value).

Now $V_R = IR$ and $V_C = IX_C$ (where $X_C = 1/2 \pi f C$)

In right angled triangle OAB

$$V = \sqrt{(V_R)^2 + (V_C)^2} = \sqrt{(IR)^2 + (IX_C)^2} = I \sqrt{R^2 + X_C^2}$$

or
$$I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{Z}$$

where $Z = \sqrt{R^2 + X_C^2}$ is the total opposition offered to the flow of alternating current by an $R - C$ series circuit and is called *impedance* of the circuit. It is measured in ohm.

Phase angle : From the phasor diagram it is clear that current in this circuit leads the applied voltage by an angle ϕ called *phase angle*.

From the phasor diagram shown in fig.2.38 ;

$$\tan \phi = \frac{V_C}{V_R} = \frac{IX_C}{IR} = \frac{X_C}{R} \quad \text{or} \quad \phi = \tan^{-1} X_C/R$$

Power : If the alternating voltage applied across the circuit is given by the equation :

$$v = V_m \sin \omega t \quad \dots(i)$$

$$\text{Then,} \quad i = I_m \sin (\omega t + \phi) \quad \dots(ii)$$

\therefore Instantaneous power,

$$\begin{aligned} p = vi &= V_m \sin \omega t I_m \sin (\omega t + \phi) = \frac{V_m I_m}{2} 2 \sin (\omega t + \phi) \sin \omega t \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} [\cos \phi - \cos(2\omega t + \phi)] = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi + \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(2\omega t + \phi) \end{aligned}$$

Average power consumed in the circuit over a complete cycle,

$$P = \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi - \text{average of } \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(2\omega t + \phi)$$

$$\text{or} \quad P = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi - \text{zero} = V_{r.m.s.} I_{r.m.s.} \cos \phi = VI \cos \phi$$


where $\cos \phi$ is called *power factor* of the circuit.

From phasor diagram

$$\cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z} \text{ same as in } R-L \text{ series circuit.}$$

Alternatively ; Power,
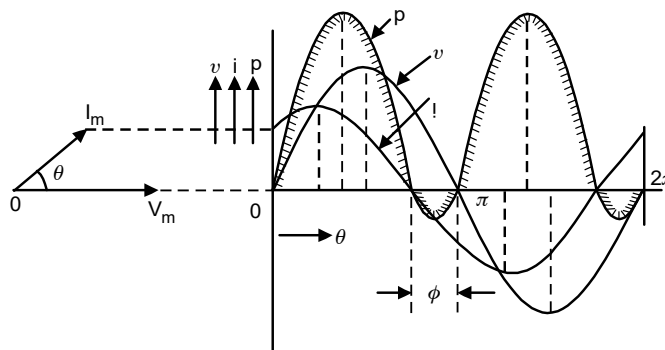
$$P = VI \cos \phi = IZ \cdot I \cdot \frac{R}{Z} = I^2 R$$



(a) Phasor diagram

(b) Wave diagram

Fig. 2.40: Phasor and wave diagram

This shows that power is actually consumed in resistance only ; capacitor does not consume any power.

Power curve : The phasor diagram and wave diagram for voltage and current are shown in fig.2.40 (a) and 2.40 (b) respectively, where applied voltage ($v = V_m \sin \omega t$) is taken as reference quantity. The power curve for $R - C$ circuit is also shown in 2.40 (b). The points on the power curve are obtained from the product of the corresponding instantaneous values of voltage and current. It is clear that power is negative between angle $(180^\circ - \phi)$ and 180° and between $(360^\circ - \phi)$ and 360° . During rest of the cycle, the power is positive. Since the area under the positive loops is greater than that under the negative loops, the net power over a complete cycle is positive. Hence, a definite quantity of power is utilised or consumed by this circuit.

Impedance triangle

When each side of the simplified phasor diagram shown in fig. 2.41 is divided by a common factor I , we get another right angled triangle (shown in fig. 2.42 known as *impedance triangle*).

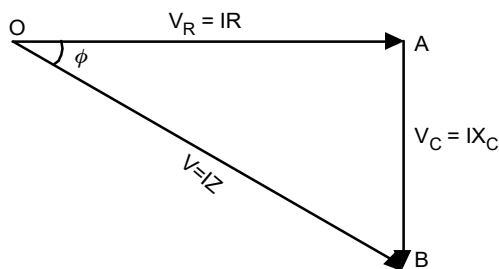


Fig. 2.41: Voltage Triangle

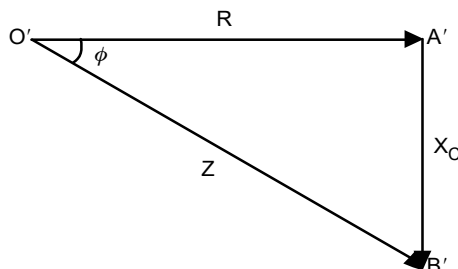


Fig. 2.42: Impedance triangle

Example 2.14. A resistance of 20 ohm and capacitor of 212.2 μF capacitance are connected in series across a 250 V, 50 Hz supply. Calculate (i) impedance of the circuit ; (ii) current ; (iii) power factor and phase angle ; (iv) power consumed in the circuit.

Solution : The circuit is shown in fig. 2.43.

$$\text{Impedance, } Z = \sqrt{R^2 + X_C^2}$$

$$\begin{aligned} \text{where, } X_C &= 1/2 \pi f C = 1/2 \pi \times 50 \times 212.2 \times 10^{-6} \\ &= 15 \Omega ; \\ R &= 20 \Omega \end{aligned}$$

$$(i) \quad \therefore Z = \sqrt{(20)^2 + (15)^2} = 25 \Omega \text{ (Ans.)}$$

$$(ii) \text{ Current, } I = \frac{V}{Z} = \frac{250}{25} = 10 \text{ A (Ans.)}$$

$$(iii) \text{ Power factor, } \cos \phi = \frac{R}{Z} = \frac{20}{25} = 0.8 \text{ leading (Ans.)}$$

$$\text{Phase angle, } \phi = \cos^{-1} 0.8 = 36.87^\circ \text{ (Ans.)}$$

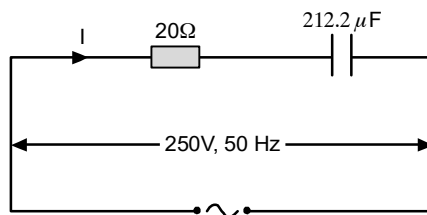


Fig.2.43: Circuit diagram

(iv) Power, $P = VI \cos \phi = 250 \times 10 \times 0.8 = \mathbf{2000\ W}$ (Ans.)

Example 2.15. A 110 V, 100 W lamp is to be operated on 220 V, 50 Hz supply mains. In order that lamp should operate in correct voltage. Calculate value of :

(i) non inductive resistance

(ii) pure inductance

(iii) pure capacitance

Ans. Lamp's rating : 110 V, 100 W

Supply voltage, $V_S = 220\ V$ and Frequency, $f = 50\ Hz$

$$\text{Resistance of the lamp, } R_L = \frac{(110)^2}{100} = 121\ \Omega$$

$$\text{Operating current, } I = \frac{100}{110} = 0.9091\ A$$

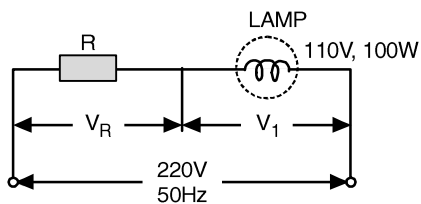


Fig. 2.44: Resistance in series

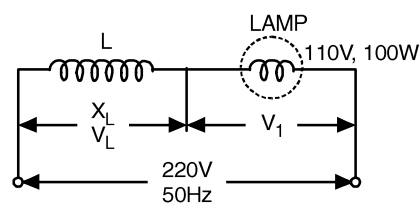


Fig. 2.45: Pure inductance in series

(i) For operating the lamp using non-inductive resistance, as shown in fig. 2.44.

Let the value of resistance be $R\ \Omega$.

$$\therefore I(R + R_L) = V$$

$$\text{or } R + R_L = \frac{220}{0.9091} = 242\ \text{ohm}$$

$$\text{or } R = 242 - R_L = 242 - 121 = \mathbf{121\ \Omega} \text{ (Ans.)}$$

(ii) For operating the lamp using pure inductance as shown in Fig. 2.45.

Let the value of inductance be L henry and $X_L = 2\pi fL$,

$$\therefore IZ = V \quad \text{or} \quad \frac{V}{I} = \frac{220}{0.9091} = 242\ \Omega$$

$$\text{or } \sqrt{R_L^2 + X_L^2} = 242$$

$$R_L^2 + X_L^2 = (242)^2 \quad \text{or} \quad X_L^2 = 242^2 - 121^2$$

$$\text{or } X_L = \sqrt{242^2 - 121^2} = 209.58\ \Omega$$

$$\text{or } 2\pi fL = 209.58 \quad \text{or} \quad L = \frac{209.58}{2\pi \times 50} = \mathbf{0.667\ H} \text{ (Ans.)}$$

(iii) For operating the lamp using pure capacitor, as shown in fig. 2.46.

Let C be the capacitance of the capacitor.

$$X_C = \frac{1}{2\pi fC}$$

And $IZ = V$ or $Z = \frac{V}{I} = \frac{220}{0.9091} = 242 \Omega$

$$\sqrt{R_L^2 + X_C^2} = Z \quad \text{or} \quad R_L^2 + X_C^2 = Z^2$$

or $X_C = \sqrt{Z^2 - R_L^2} = \sqrt{(242)^2 + (121)^2} = 209.58 \Omega$

or $\frac{1}{2\pi fC} = X_C$ or $C = \frac{1}{2\pi \times 50 \times 209.58} = 15.188 \mu\text{F}$ (Ans)

Example 2.16. A 400 Hz generator has an induced e.m.f. of 100 V and an internal impedance $(5 + j0)$ ohm. If it supplies an impedance consisting of a 40 ohm capacitive reactance in series with 10 ohm resistance, what is the magnitude of the current passing through it? Determine also the voltage at the terminals of the generator.

Solution : Simple circuit is shown in fig.2.47.

Total impedance of the circuit.

$$\begin{aligned} Z_T &= \sqrt{(R_i + R)^2 + (X_C)^2} \\ &= \sqrt{(5 + 10)^2 + (40)^2} = 42.72 \Omega \end{aligned}$$

Circuit current, $I = V/Z = 100/42.72 = 2.341 \text{ A}$ (Ans.)

Load impedance, $Z_L = \sqrt{R^2 + X_C^2} = \sqrt{(10)^2 + (40)^2} = 41.231 \Omega$

Terminal voltage, $V_L = IZ_L = 2.341 \times 41.231 = 96.52 \text{ V}$ (Ans.)

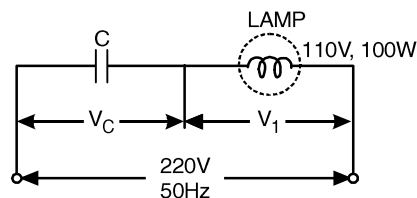


Fig.2.46: Pure capacitor in series

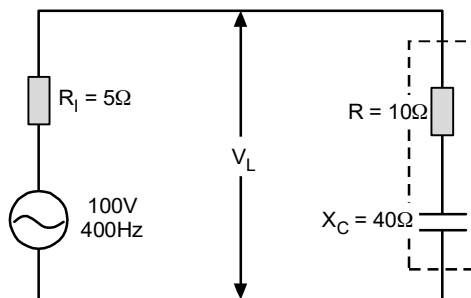


Fig.2.47: Circuit diagram

PRACTICE EXERCISE

1. A resistance of 15 ohm and capacitor of 150 μF capacitance are connected in series across a 230 V, 50 Hz supply. Calculate (i) impedance of the circuit ; (ii) current ; (iii) power factor and phase angle ; (iv) power consumed in the circuit.

(Ans, 25.987 Ω ; 8.85 A; 0.577 leading, 54.75° ; 1174.9 W)

2. A 120 V, 60 W lamp is to be operated on 220 V, 50 Hz supply mains. In order that lamp should operate in correct voltage. Calculate value of : (i) non inductive resistance, (ii) pure inductance, (iii) Pure capacitance

(Ans, 200 Ω ; 1.174 H; 8.63 μF Ω)

3. A voltage of 125 V at 50 Hz is applied across a non inductive resistor connected in series with a condenser. The current in the circuit is 2.2 A. The power loss in the resistor is 96.8 W and that in the condenser is negligible. Calculate the resistance and the capacitance.

(Ans, 20 ohm; 53.18 ohm; 59.85 μ F)

4. A resistor R in series with a capacitor C is connected to a 50 Hz, 240 V supply. Find the value of C so that R absorbs, 300 W at 100 V.

(Ans, 43.77 μ F)

2.29. R – L – C SERIES CIRCUIT

A circuit that contains a pure resistance of R ohm, a pure inductance of L henry and a pure capacitor of capacitance C farad ; all connected in series is known as $R - L - C$ series circuit.

An $R - L - C$ series circuit is shown in fig.2.48.

Here $X_L = 2 \pi f L$ and $X_C = 1/2 \pi f C$

When a resulting current I (r.m.s. value) flows through the circuit, the voltage across each component will be

$V_R = IR$ i.e. voltage across R in phase with I ;

$V_L = IX_L$ i.e. voltage across L leads I by 90° ;

$V_C = IX_C$ i.e. voltage across C lags I by 90° ;

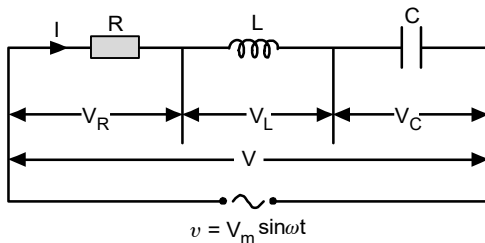


Fig. 2.48: Circuit diagram

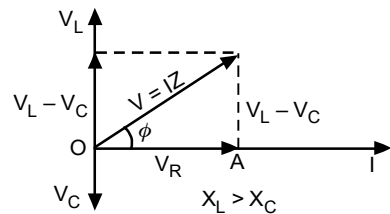


Fig.2.49: Phasor diagram

The phasor diagram is shown in fig.2.49 where current is taken as the reference phasor. Since voltage across inductance V_L leads the current vector I by 90° and voltage across capacitance V_C lags the current vector I by 90° , they act opposite to each other. If $V_L > V_C$, in effect, the circuit behaves as an inductive circuit but when $V_L < V_C$, the circuit behaves as a capacitive circuit. Here, the phasor diagram is drawn for an inductive circuit (i.e. when $V_L > V_C$).

$$V = \sqrt{(V_R)^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

or
$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

or
$$I = \frac{V}{\sqrt{(R)^2 + (X_L - X_C)^2}} = \frac{V}{Z}$$

where $Z = \sqrt{R^2 + (X_L - X_C)^2}$ is the total opposition offered to the flow of alternating current by an $R - L - C$ series circuit and is called *impedance* of the circuit.

Phase angle : From phasor diagram : $\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$

or
$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

Power : Average power, $P = VI \cos \phi = I^2 R$

Power, factor, $\cos \phi = \frac{V_R}{V} = \frac{R}{Z}$

If the alternating voltage applied across the circuit is given by the equation

$$v = V_m \sin \omega t$$

the circuit current is represented by the equation as per the constants or parameters explained below :

Three cases of $R - L - C$ series circuit

- (i) When $X_L > X_C$, the phase angle ϕ is positive. In effect, the circuit behaves as an $R - L$ series circuit. The circuit current lags behind the applied voltage and p.f. is lagging. The current is given by the equation.

$$i = I_m \sin (\omega t - \phi)$$

- (ii) When $X_L < X_C$, the phase angle ϕ is negative. In effect, the circuit behaves as an $R - C$ series circuit. The circuit current leads the applied voltage and p.f. is leading. The current is given by the equation.

$$i = I_m \sin (\omega t + \phi)$$

- (iii) When $X_L = X_C$, the phase angle ϕ is zero. In effect, the circuit behaves like a pure resistive circuit. The circuit current is in phase with applied voltage and p.f. is unity. The current is given by the equation.

$$i = I_m \sin \omega t$$

Impedance triangle

Fig. 2.50 shows the impedance triangle of the circuit when $X_L > X_C$, whereas, fig. 2.51 shows the impedance triangle of the circuit when $X_L < X_C$.

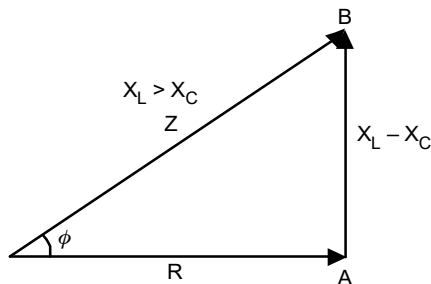


Fig. 2.50: Impedance triangle $X_L > X_C$

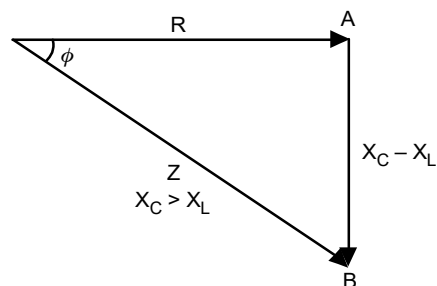


Fig. 2.51: Impedance triangle $X_L < X_C$

2.30. SERIES RESONANCE

In an $R-L-C$ series circuit, when circuit current is in phase with the applied voltage, the circuit is said to be in series resonance. This condition is obtained in an $R-L-C$ circuit, shown in fig.2.52,

when $X_L = X_C$ (or $X_L - X_C = 0$)

At resonance ; $X_L - X_C = 0$ or $X_L = X_C$

$$\text{Impedance, } Z_r = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\text{Current, } I_r = \frac{V}{Z_r} = \frac{V}{R}$$

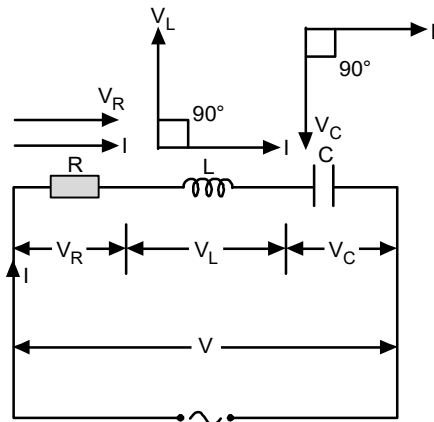


Fig. 2.52: Resonant circuit $X_L = X_C$

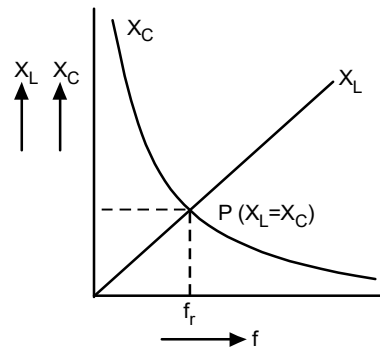


Fig.2.53: Graph for X_L and X_C

Since, at resonance, the opposition to the flow of current is only resistance (R) of the circuit, the circuit draws *maximum current* under this conditions.

Resonant frequency : The value of $X_L (= 2 \pi f L)$ and $X_C (= 1/2 \pi f C)$ can be changed by changing the supply frequency. When frequency increases, the value of X_L , increases, whereas, the value of X_C decreases, and *vice-versa*. Thus to obtain series resonance, the frequency is adjusted to f_r so that $X_L = X_C$ the condition at point P shown in fig.2.53.

\therefore At series resonance, $X_L = X_C$

$$2 \pi f_r L = \frac{1}{2 \pi f_r C} \quad \text{or} \quad f_r = \frac{1}{2 \pi \sqrt{LC}}$$

where f_r is the *resonant frequency* in Hz when L and C are measured in henry and farad respectively.

Effects of series resonance

The following are the main effects of series resonance :

- (i) At resonance $X_L = X_C$, therefore, the impedance of the circuit is minimum and is reduced to the resistance of the circuit only, *i.e.*

$$Z_r = R$$

(ii) Since, impedance is minimum, the circuit current is maximum at resonance, *i.e.*

$$I_r = V/Z_r = V/R$$

(iii) Power taken by the circuit is maximum, as I_r is maximum, *i.e.*

$$P_r = I_r^2 R$$

(iv) As the current drawn by the circuit, at resonance, is very large (maximum), the voltage drop across L (*i.e.* $V_L = IX_L = I \times 2\pi f_r L$) and C (*i.e.* $V_C = IX_C = I \times 1/2\pi f_r C$) are also very large.

In power system, at resonance, the excessive voltage built up across the inductive and capacitive components (such as circuit breakers, reactors, etc.) may cause damage. Therefore, series resonance should be avoided in power system. However, in some of the electronic devices (such as antenna circuit of radio and TV receiver, tuning circuits etc.), the principle of series resonance is used to increase the signal voltage and current at a desired frequency (f_r).

*Since a series resonant circuit has the capability to draw heavy current and power from the mains, it is often regarded as **acceptor circuit**.*

2.31. RESONANCE CURVE

The curve obtained by plotting a graph between current and frequency is known as resonance curve. A resonance curve of a typical $R - L - C$ series circuit is shown in fig.2.54. It may be noted that current reaches its maximum value at the resonant frequency (f_r), falling off rapidly on either side of that point. It is because when the value of frequency is lower than resonance frequency, $X_C > X_L$ and when the value of frequency is higher than f_r , $X_C < X_L$. In both the cases, impedance of the circuit increases ($Z > Z_r$) and the value of current decreases.

Note that resistance of the circuit also plays its own role. Smaller the resistance, the greater the current at resonance.

Bandwidth : The range of frequency over which circuit current is equal to or more than 70.7% of maximum value (*i.e.* I_r , current at resonance) is known as the *bandwidth* of a series resonant circuit.

Fig.2.55 shows a resonance curve of a typical $R - L - C$ circuit where the circuit current is equal to or greater than 70.7% of maximum current (*i.e.* $I_r = V/R$) between frequency range f_1 to f_2 .

$$\therefore \text{Bandwidth, } BW = f_2 - f_1$$

Here, the frequency f_1 is called the *lower cut-off frequency* and the frequency f_2 is called the *upper cut-off frequency*. The bandwidth represents the frequency range at which the circuit offers low impedance to circuit current.

The following points may be noted here :

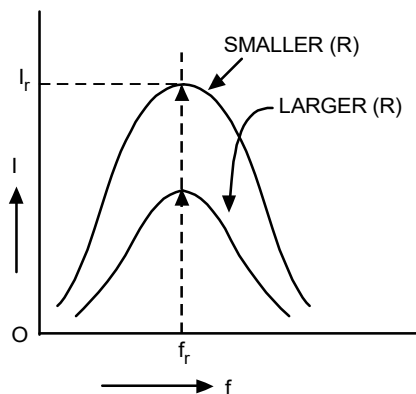


Fig.2.54: Resonance curve

- (i) If the resonant frequency is not located at the centre of upper and lower cut-off frequency, then

$$f_r = \sqrt{f_1 f_2}$$

- (ii) When the resonant frequency is located sufficiently near to the centre of the two cut-off frequencies and Q of the circuit is ≥ 10 , then

$$f_1 = f_r - \frac{BW}{2} \text{ and } f_2 = f_r + \frac{BW}{2}$$

Selectivity : From the resonance curve, it is clear that for smaller resistance the resonance curve is sharp and flat for the larger resistance. A sharper resonance curve provides smaller band of frequencies to give reasonable response and hence provides better selectivity. It also shows that selectivity is reciprocal of bandwidth.

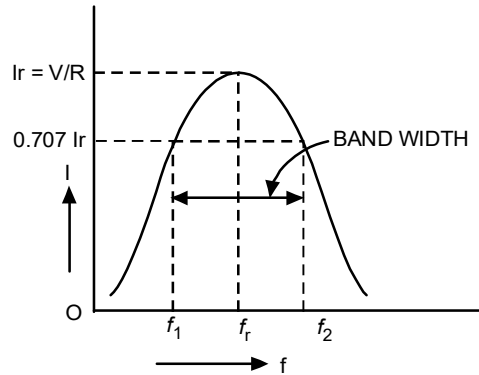


Fig.2.55: Resonance curve showing band width.

2.32 Q-FACTOR OF SERIES RESONANT CIRCUIT

We have seen that at series resonance, the circuit draws largest current from the mains, this produces a heavy voltage across L or C . The factor by which the *p.d.* across L or C rises to that of the applied voltage is called the *Q-factor* of the series resonant circuit.

$$\therefore \quad Q\text{-factor} = \frac{\text{Voltage across } L \text{ or } C}{\text{Applied voltage}} = \frac{I_r X_L}{I_r R} = \frac{X_L}{R} = \frac{\omega_r L}{R}$$

$$\text{where, } \omega_r = 2\pi f_r = 2\pi \frac{1}{2\pi \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\therefore \quad Q\text{-factor} = \frac{L}{R} \times \frac{1}{\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

The value of Q -factor depends entirely upon the design of coil (*i.e.* $R - L$ which is a part of $R - L - C$ circuit).

Example 2.17. A coil resistance 10Ω and inductance 111.4 mH is connected in series with a capacitor of $159.16 \mu\text{F}$ across a 200 V , 50 Hz supply. Calculate (a) inductive reactance (b) capacitive reactance (c) impedance (d) current (e) voltage across coil and capacitor.

Solution : The circuit is shown in fig.2.56.

Where, $R = 10 \Omega$; $L = 111.4 \text{ mH}$; $C = 159.16 \mu\text{F} = 159.16 \times 10^{-6} \text{ F}$; $V = 200 \text{ V}$; $f = 50 \text{ Hz}$

(a) Inductive reactance, $X_L = 2\pi fL = 2\pi \times 50 \times 111.14 \times 10^{-3} = 35 \Omega$ (Ans.)

$$\begin{aligned}
 (b) \text{ Capacitive reactance, } X_C &= \frac{1}{2\pi f C} \\
 &= \frac{1}{2\pi \times 50 \times 159.16 \times 10^{-6}} \\
 &= \mathbf{20 \, \Omega \text{ (Ans.)}}
 \end{aligned}$$

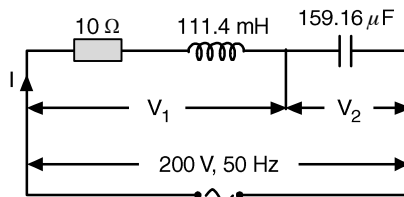


Fig. 2.56: Circuit as per data given

$$\begin{aligned}
 (c) \text{ Impedance, } Z &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{10^2 + (35 - 20)^2} \\
 &= \mathbf{25 \, \Omega \text{ (Ans.)}}
 \end{aligned}$$

$$(d) \text{ Current, } I = \frac{V}{Z} = \frac{200}{25} = \mathbf{8 \, A \text{ (Ans.)}}$$

$$\begin{aligned}
 (e) \text{ Voltage across coil, } V_1 &= I Z_{\text{COIL}} = I \sqrt{R^2 + X_L^2} \\
 &= 8 \sqrt{10^2 + 35^2} = \mathbf{291.2 \, V \text{ (Ans.)}}
 \end{aligned}$$

$$\text{Voltage across capacitor, } V_2 = I X_C = 8 \times 20 = \mathbf{160 \, V \text{ (Ans.)}}$$

Example 2.18. Find applied voltage and power loss in the circuit shown in fig. 2.57.

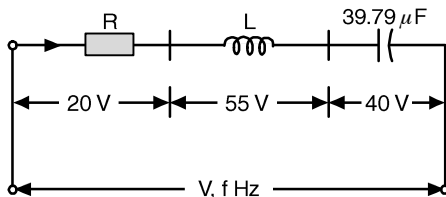


Fig. 2.57: Given Ccircuit

$$\text{Solution : Here, } C = 39.79 \, \mu\text{F} ; X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 39.79 \times 10^{-6}} = 80 \, \Omega$$

$$\text{Applied voltage, } V = \sqrt{20^2 + (55 - 40)^2} = \mathbf{25 \, V \text{ (Ans.)}}$$

$$\text{Current, } I = \frac{V_C}{X_C} = \frac{40}{80} = 0.5 \text{ A}$$

$$\text{Power loss, } P = V_R \times I = 20 \times 0.5 = \mathbf{10 \, \text{watt} \text{ (Ans.)}}$$

Example 2.19. A coil of resistance $12 \, \Omega$ and inductance $0.051 \, \text{H}$, a non-inductive resistance of $20 \, \Omega$ resistance and a loss-free $212.2 \, \mu\text{F}$ capacitor are connected across a $240 \, \text{V}$, $50 \, \text{Hz}$ sinusoidal supply, Calculate (i) the current and (ii) the power factor of the circuit.

Solution : The circuit is shown in fig.2.58.

$$\text{Here, } R_1 = 12 \, \Omega ; L = 0.051 \, \text{H} ; R_2 = 20 \, \Omega ;$$

$$C = 212.2 \, \mu\text{F} = 212.2 \times 10^{-6} \, \text{F} ; V = 240 \, \text{V} ; f = 50 \, \text{Hz}$$

$$\text{Resistance of the whole circuit, } R = R_1 + R_2$$

$$= 12 + 20 = 32 \, \Omega$$

$$\text{Inductive reactance, } X_L = 2 \pi f L$$

$$= 2 \pi \times 50 \times 0.051$$

$$= 16 \, \Omega$$

$$\text{Capacitive reactance, } X_C = \frac{1}{2 \pi f C}$$

$$= \frac{1}{2 \pi \times 50 \times 212.2 \times 10^{-6}} = 15 \, \Omega$$

$$\text{Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{32^2 + (16 - 15)^2} = 32.016 \, \Omega$$

$$(i) \quad \text{Circuit current, } I = \frac{V}{Z} = \frac{240}{32.016} = 7.496 \, \text{A (Ans.)}$$

$$(ii) \quad \text{Power factor of the circuit, } \cos \phi = \frac{R}{Z} = \frac{32}{32.016} = 0.9995 \, \text{(lagging) (Ans.)}$$

(since $X_L > X_C$)

Example 2.20. A series R-L-C circuit consisting of a resistance of $20 \, \Omega$, inductance $0.2 \, \text{H}$ and capacitance of $150 \, \mu\text{F}$ is connected across a $230 \, \text{V}$, $50 \, \text{Hz}$ source. Calculate (i) the impedance (ii) the current (iii) the magnitude and nature of the power factor (iv) the frequency of supply to be adjusted to make power factor unity.

Solution : The circuit is shown in fig.2.59

$$\text{Here, } R = 20 \, \Omega ; L = 0.2 \, \text{H} ; C = 150 \, \mu\text{F} = 150 \times 10^{-6} \, \text{F}$$

$$\text{Inductive, reactance, } X_L = 2 \pi f L = 2 \pi \times 50 \times 0.2 = 62.83 \, \Omega$$

$$\text{Capacitance reactance, } X_C = \frac{1}{2 \pi f C} = \frac{1}{2 \pi \times 50 \times 150 \times 10^{-6}} = 21.22 \, \Omega$$

$$(i) \text{ Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{20^2 + (62.83 - 21.22)^2}$$

$$= 46.17 \, \Omega \, \text{(Ans.)}$$

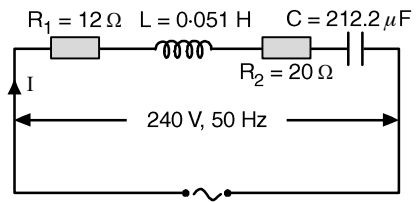


Fig.2.58: Circuit as per data

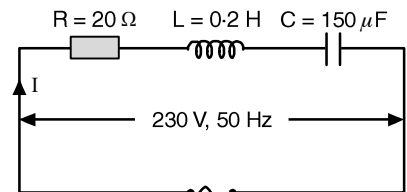


Fig. 2.59: Circuit diagram

$$(ii) \text{ Circuit current, } I = \frac{V}{Z} = \frac{230}{46.17} = 4.98 \text{ A (Ans.)}$$

$$(iii) \text{ Power factor} = \cos \phi = \frac{R}{Z} = \frac{20}{46.167} = 0.433 \text{ (Ans.)}$$

The power factor, is **lagging** because inductive reactance is more than capacitive reactance *i.e.* the circuit behaves as an inductive circuit.

Power factor will be unity when

$$X_L = X_C \quad \text{or} \quad 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\text{or} \quad f_r = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} = \frac{1}{2\pi \sqrt{0.2 \times 150 \times 10^{-6}}} = 29.06 \text{ Hz (Ans.)}$$

Example 2.21. An inductive coil takes 10 A and dissipates 1500 W when connected to a 250 V, 25 Hz supply. Calculate the following, (i) the impedance ; (ii) the effective resistance ; (iii) the reactance ; (iv) the value of the capacitance required to be connected in series with coil to make the power factor of the circuit unity ; and (vi) what is now the current taken by the coil ? Also draw the phasor diagram of the two cases.

Solution : The circuit is shown in fig.2.60.

Power dissipated in the coil, $I^2 R = 1500 \text{ W}$

\therefore Resistance of the coil, $R = 1500/(10)^2 = 15 \Omega \text{ (Ans.)}$

Impedance of the coil, $Z = V/I = 250/10 = 25 \Omega \text{ (Ans.)}$

Inductive reactance of the coil, $X_L = \sqrt{Z^2 - R^2} = \sqrt{(25)^2 - (15)^2}$
 $= 20 \Omega \text{ (Ans.)}$

Power factor, $\cos \phi = R/Z = 15/25 = 0.6 \text{ lag (Ans.)}$

The p.f. of the circuit will be unity when, $X_C = X_L$

or $1/2\pi f C = 20$

or $C = \frac{1}{2\pi \times 25 \times 20} = 159.2 \mu\text{F (Ans.)}$



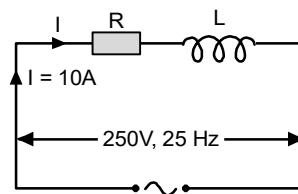


Fig. 2.60: Circuit diagram

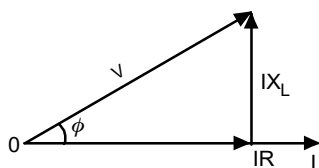

(a)

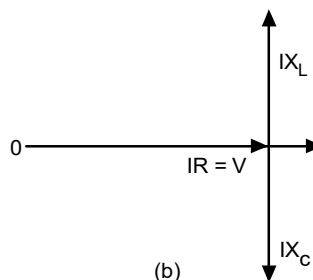

(b)

Fig.2.61: Phasor diagram

Now, current, $I = \frac{V}{R} = \frac{250}{15} = \mathbf{16.67 \text{ A}}$ (Ans.)

The phasor diagram for the two cases is drawn in fig. 2.61 (a) and (b) respectively.

Example 2.22 A choke coil is connected series with a $100 \mu\text{F}$ capacitor. With a constant supply voltage of 250 V , it is found that the circuit takes its maximum current of 50 A when the supply frequency is 100 Hz . Determine (i) resistance and inductance of the choke coil ; (ii) voltage across the capacitor and (iii) Q -factor of the circuit.

Solution : At resonance ; Current, $I_r = V/R$

or $R = V/I_r = 250/50 = \mathbf{5 \Omega}$ (Ans.)

Also $2 \pi f_r L = 1/2 \pi f_r C$

or $L = \frac{1}{(2\pi f_r)^2 C} = \frac{1}{(2\pi \times 100)^2 \times 100 \times 10^{-6}} = \mathbf{25.33 \text{ mH}}$ (Ans.)

Voltage across capacitor,

$$V_C = I_r X_C = 50 \times 1/2 \pi \times 100 \times 100 \times 10^{-6} = \mathbf{795.8 \text{ V}}$$
 (Ans.)

$$Q\text{-factor} = \frac{V_L}{V_R} = \frac{X_L}{R} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 100 \times 25.33 \times 10^{-3}}{5} = \mathbf{3.183}$$
 (Ans.)

Example 2.23. A series resonant circuit has a Q -factor of 150 ; an inductance of 0.1 H and a capacitance of $0.1 \mu\text{F}$. Calculate the band width of the circuit.

Solution : At resonance, frequency

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 0.1 \times 10^{-6}}} = \frac{10^4}{2\pi} \text{ Hz}$$

Now, $Q = \frac{f_r}{BW}$

\therefore Bandwidth, $BW = \frac{f_r}{Q} = \frac{10^4}{2\pi \times 150} = \mathbf{10.61 \text{ Hz}}$ (Ans.)

$$Q\text{-factor} = V_C/V = 397.88/250 = \mathbf{1.59}$$
 (Ans.)

Example 2.24. A coil of resistance 40Ω and inductance 0.75 H are in a series circuit with a capacitor C . The resonant frequency is 60 Hz . If supply is 250 V , 50 Hz find

(i) line current, (ii) power factor, (iii) power consumed.

Solution : Here, $R = 40 \Omega$; $L = 0.75 \text{ H}$; $f_r = 60 \text{ Hz}$; $V = 250 \text{ V}$; $f = 50 \text{ Hz}$.



Fig. 2.62: Circuits with given data

$$\text{At resonance, } X_L = X_C \quad \text{or} \quad 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\text{or} \quad C = \frac{1}{(2\pi f_r)^2 L} = \frac{1}{(2\pi \times 60)^2 \times 0.75} = 9.38 \mu\text{F}$$

$$\text{At 50 Hz, } X_L = 2\pi f L = 2\pi \times 50 \times 0.75 = 235.6 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 9.38 \times 10^{-6}} = 339.35 \Omega$$

$$\text{Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(40)^2 + (235.6 - 339.35)^2} = 111.2 \Omega$$

$$(i) \text{ Line current, } I = \frac{V}{Z} = \frac{250}{111.2} = \mathbf{2.248 \text{ A (Ans.)}}$$

$$(ii) \text{ Power factor, } \cos \phi = \frac{R}{Z} = \frac{40}{111.2} = \mathbf{0.36 \text{ leading (Ans.)}}$$

$$(iii) \text{ Power consumed, } P = VI \cos \phi = 250 \times 2.248 \times 0.36 = \mathbf{202.32 \text{ W (Ans.)}}$$

PRACTICE EXERCISE

1. A coil of resistance 8Ω and inductance 0.12 henry is connected in series with a condenser of capacitance 140 microfarad across a 230 volt, 50 Hz supply. Determine :
 (i) Impedance of the entire circuit, (ii) Current flowing through the condenser,
 (iii) Power factor of the circuit, (iv) Voltage across the condenser.
 (Ans. 17Ω ; 13.53 A ; 0.471 (lagging); 307.7 V)
2. A coil of resistance 10 ohms and inductance 0.1 H is connected in series with a condenser of capacitance 150 micro-farad across a 200 V , 50 Hz supply. Determine (i) impedance ; (ii) current ; (iii) power factor ; (iv) voltage across the coil ; (v) voltage across the condenser.
 (Ans. 14.28Ω ; 14 A ; 0.7 lag; 461.57 V ; 297.08 V)
3. A series R - L - C circuit with $R = 10\Omega$; $L = 0.02 \text{ H}$, $C = 2 \mu\text{F}$ is connected to 100 V variable frequency source. Find the frequency for which the current is maximum. (Ans. 795.77 Hz)
4. Determine the parameters of an $R - L - C$ series circuit that will resonate at 1000 Hz , has a bandwidth of 100 Hz and draws 16 W from a 200 V generator operating at the resonant frequency of the circuit. (Ans. 2500Ω ; 3.98 H , $6.3 \times 10^{-6}\text{F}$)
5. A 10 mH coil is connected in series with a loss free capacitor to a variable frequency source of 20 V . The current in the circuit has maximum value of 0.2 A at a frequency of 100 kHz . Calculate :
 (i) the value of capacitance ; (ii) the Q factor of the coil ; (iii) the half power frequencies.
 (Ans. 253.3 pF ; 62.8 ; 99.204 kHz ; 100.796 kHz)

2.33. A.C. PARALLEL CIRCUITS

The a.c. circuits in which number of branches are connected in such a manner so that voltage across each branch is the same but current flowing through them is different, are called *a.c. parallel circuits*. The parallel circuits are used more frequently in a.c. system because of the following reasons :

- (i) Almost all the electrical appliances (or devices) of different ratings are operated at the same supply voltage and are connected in parallel.
- (ii) Each device is required to be operated independently (with a switch) without disturbing the operation of other devices. Hence, connected in parallel.

2.34. METHODS OF SOLVING PARALLEL A.C. CIRCUITS


In parallel circuits, number of branches are connected in parallel. Each branch, generally, contains number of components like resistance, inductance and capacitance forming series circuits. Therefore each branch is analysed separately as a series circuit and then the effects of separate branches are combined together. While carrying out circuit calculations, the magnitudes and phase angles of voltages and currents are taken into account. The following methods may be applied for solving a.c. parallel circuits.

- (i) Phasor (or vector) method.
- (ii) Admittance method.
- (iii) Method of phasor algebra (or symbolic method or J-method).

The method to be applied for the solution, depends upon the conditions of the problem. However, in general, the method which yields quick results is applied.

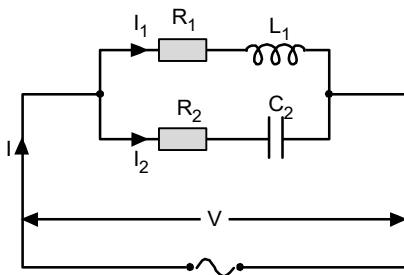2.35. PHASOR (OR VECTOR) METHOD

To solve parallel a.c. circuits by this method, proceeds as follows :



Fig; 2.63: Parallel ac circuit

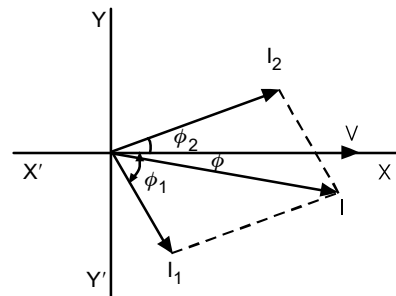


Fig. 2.64: Phasor diagram

Step I : Draw the circuit as per the given problem as shown in fig. 2.63. (Here, for illustration, we have considered two branches connected in parallel. One branch contains resistance and inductance in series, whereas second branch contains resistance and capacitance in series. The supply voltage is V volts).

Step II : Find the impedance of each branch of the circuit separately, *i.e.*

$$Z_1 = \sqrt{R_1^2 + X_{L1}^2} \text{ where } X_{L1} = 2 \pi f L_1$$

$$Z_2 = \sqrt{R_2^2 + X_{C2}^2} \text{ where } X_{C2} = 1/2 \pi f C_2$$

Step III : Determine the magnitude of current and phase angle with the voltage in each branch.

$$I_1 = \frac{V}{Z_1} ; \phi_1 = \tan^{-1} \frac{X_{L1}}{R_1} \text{ (lagging) [for inductive branch]}$$

$$I_2 = \frac{V}{Z_2} ; \phi_2 = \tan^{-1} \frac{X_{C2}}{R_2} \text{ (lagging) [for capacitive branch]}$$

Step IV : Draw the phasor diagram taking voltage as the reference phasor. Represent the branch currents on it as shown in fig. 2.64.

Step V : Find the phasor sum of branch currents by the method of components.

$$I_{XX} = I_1 \cos \phi_1 + I_2 \cos \phi_2$$

$$I_{YY} = -I_1 \sin \phi_1 + I_2 \sin \phi_2 \text{ (negative)}$$

$$I = \sqrt{(I_{XX})^2 + (I_{YY})^2}$$

Step VI : Find the phase angle ϕ between the total current I and circuit voltage V .

$$\phi = \tan^{-1} \frac{I_{YY}}{I_{XX}} \text{ lagging (since, } I_{YY} \text{ is negative)}$$

Power factor of the circuit = $\cos \phi$ (lagging)

or Power factor = $\frac{I_{XX}}{I}$ (lagging)

Example 2.25. The circuits A and B are connected in parallel to a 250 V, 50 Hz supply. Circuit A consists of resistance 15 ohm in series with an inductive reactance of 15 ohm and circuit B consists of resistance 30 ohm in series with a capacitive reactance of 15 ohm. Determine (i) the current drawn by each circuit ; (ii) total current drawn from the mains.

Solution : The circuit is shown in fig.2.65.

$$\text{Impedance, } Z_1 = \sqrt{R_1^2 + X_{L1}^2} = \sqrt{(15)^2 + (15)^2} = 21.21 \Omega$$

$$\text{Impedance, } Z_2 = \sqrt{R_2^2 + X_{C2}^2} = \sqrt{(30)^2 + (15)^2} = 33.54 \Omega$$

$$\text{Current, } I_1 = \frac{V}{Z_1} = \frac{250}{21.21} = 11.78 \text{ A (Ans.)}$$

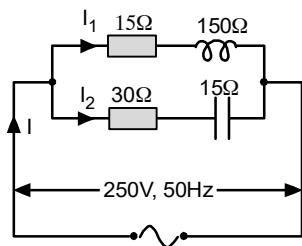


Fig. 2.65: Circuit diagram

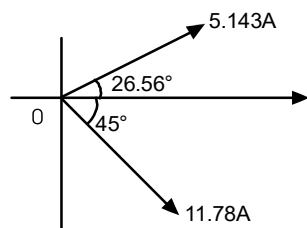


Fig. 2.66: Phasor diagram

$$\text{Current, } I_2 = \frac{V}{Z_2} = \frac{250}{33.54} = 7.45 \text{ A (Ans.)}$$

$$\text{Phase angle, } \phi_1 = \tan^{-1} \frac{X_{L1}}{R_1} = \tan^{-1} \frac{15}{15} = 45^\circ \text{ lag}$$

$$\text{Phase angle, } \phi_2 = \tan^{-1} \frac{X_{C2}}{R_2} = \tan^{-1} \frac{15}{30} = 26.56^\circ \text{ leading}$$

The phasor diagram representing voltage as reference phasor is shown in fig. 2.66.

Resolving the currents horizontally and vertically, we get,

$$I_{XX} = I_1 \cos \phi_1 + I_2 \cos \phi_2 = 11.78 \cos 45^\circ + 7.45 \times \cos 26.56^\circ = 15 \text{ A}$$

$$I_{YY} = -I_1 \sin \phi_1 + I_2 \sin \phi_2$$

$$= -11.78 \times \sin 45^\circ + 7.45 \sin 26.56^\circ = -5 \text{ A}$$

$$\text{Current drawn from the mains, } I = \sqrt{I_{XX}^2 + I_{YY}^2} = \sqrt{(15)^2 + (5)^2} = 15.81 \text{ A (Ans.)}$$

Example 2.26. A coil of resistance 30 ohm and inductance 0.1 H is connected in parallel with a non-inductive resistance of 40 ohm. Find (i) current in each branch of the circuit, (ii) total current supplied, (iii) phase angle and p.f. of combination when a voltage of 200 volt at 50 Hz is applied (iv) power consumed in the circuit.

Solution : The circuit is shown in fig.2.67.

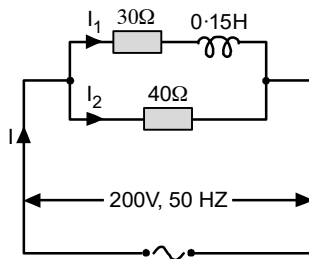


Fig. 2.67: Circuit diagram

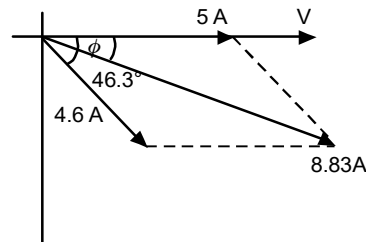


Fig. 2.68: Phasor diagram

Applied voltage, $V = 200 \text{ V}$; Supply frequency, $f = 50 \text{ Hz}$

Branch I

$$R_2 = 30 \Omega ; X_{L1} = 2 \pi f L_1 = 2 \pi \times 50 \times 0.1 = 31.4 \Omega$$

$$\text{Impedance, } Z_1 = \sqrt{R_1^2 + X_L^2} = \sqrt{(30)^2 + (31.4)^2} = 43.43 \text{ ohm}$$

$$\text{Current in the coil, } I_1 = \frac{V}{Z_1} = \frac{200}{43.43} = 4.6 \text{ A (Ans.)}$$

$$\text{Phase angle, } \phi_1 = \tan^{-1} \frac{X_{L1}}{R_1} = \tan^{-1} \frac{31.4}{30} = 46.3^\circ \text{ lagging}$$

Branch II

Resistance, $R_2 = 40 \text{ ohm}$

Branch current, $I_2 = \frac{V}{R_2} = \frac{200}{40} = 5 \text{ A (Ans.)}$

Phase angle, $\phi_2 = 0$ (I_2 is in phase with V)

The two currents are shown vectorially in fig. 2.68. Resolving the currents horizontally and vertically,

$$I_{XX} = I_2 + I_1 \cos \phi_1 = 5 + 4.6 \cos 46.3^\circ = 5 + 4.6 \times 0.691 = 8.18 \text{ A}$$

$$I_{YY} = 0 - I_1 \sin \phi_1 = 0 - 4.6 \sin 46.3^\circ = -4.6 \times 0.723 = -3.33 \text{ A}$$

Total current supplied, $I = \sqrt{I_{XX}^2 + I_{YY}^2} = \sqrt{(8.18)^2 + (-3.33)^2} = 8.83 \text{ A (Ans.)}$

Phase angle, $\phi = \tan^{-1} \frac{I_{YY}}{I_{XX}} = \tan^{-1} \left(\frac{-3.33}{8.18} \right) = -22.126^\circ \text{ (Ans.)}$

Power factor of the circuit, $\cos \phi = \cos (-22.126^\circ) = 0.9264 \text{ (lagging) (Ans.)}$

Power, $P = VI \cos \phi = 200 \times 8.83 \times 0.9264 = 1635.7 \text{ W (Ans.)}$

Example 2.27. A single phase motor takes 30 A at a pf of 0.6 lagging from 230 V, 50 Hz supply. What value of capacitance must a shunt capacitor have to raise the overall power factor to 0.9?

Solution : Active component of current drawn by motor, $I_a = I \cos \phi_1 = 50 \times 0.6 = 30 \text{ A}$

Initial power factor, $\cos \phi_1 = 0.6$ lagging

$$\tan \phi_1 = \tan \cos^{-1} 0.6 = 1.333$$

Improved power factor, $\cos \phi_2 = 0.9$ lagging

$$\tan \phi_2 = \tan \cos^{-1} 0.9 = 0.4843$$

Let C be the capacitance of capacitor connected across the motor as shown in fig. 2.69

The reactive current drawn by capacitor,

$$I_C = I_{r_1} - I_{r_2} = I_a \tan \phi_1 - I_a \tan \phi_2$$

$$I_C = I_a (\tan \phi_1 - \tan \phi_2) = 30 (1.333 - 0.4843) = 25.47 \text{ A}$$

The value of capacitance required, $C = \frac{I_C}{2\pi f V} = \frac{25.47}{2\pi \times 50 \times 250} = 324.3 \text{ } \mu\text{F (Ans.)}$

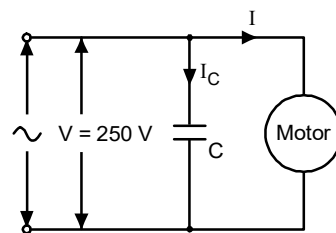


Fig.2.69: Circuit diagram

PRACTICE EXERCISE

1. A coil of resistance 15 ohm and inductance 0.05 H is connected in parallel with a non-inductive resistance of 20 ohm. Find (i) current in each branch of the circuit, (ii) total current supplied,

(iii) phase angle and p.f. of combination when a voltage of 200 volt at 50 Hz is applied (iv) power consumed in the circuit.

(Ans. 9.2 A; 10 A; 17.656 A; -22.126° ; 0.9264 (lagging); 3271.3 W)

2. A series ac circuit has a resistance of $15\ \Omega$ and inductive reactance of $10\ \Omega$. Calculate the value of capacitor which is connected across this series combination so that system has unity power factor. The frequency of ac supply is 50 Hz. (Ans. $97.94\ \mu\text{F}$)
3. The circuits A and B are connected in parallel to a 230 V, 50 Hz supply. Circuit A consists of resistance 20 ohm in series with an inductive reactance of 20 ohms and circuit B consists of resistance 40 ohm in series with a capacitive reactance of 20 ohm. Determine (i) the current drawn by each circuit ; (ii) total current drawn from the mains. (Ans. 8.13 A; 5.143 A; 10.91 A)
4. A single phase motor takes 5 A current at 230 V, 50 Hz supply at a p.f. 0.707 lagging. It is required to improve the p.f. of the motor to 0.9 by connecting a capacitor in parallel with it. Determine the capacitance of capacitor. (Ans. 25.23 mF)
5. A single phase motor takes 50 A at a pf of 0.6 lagging from 250 V, 50 Hz supply. What value of capacitance must a shunt capacitor have to raise the overall power factor to 0.9 ?

(Ans. 324.3 mF)

2.36. PARALLEL RESONANCE

An a.c. circuit containing an inductor and capacitor in parallel is said to be in parallel resonance when the circuit current is in phase with the applied voltage. Consider an inductor of L henry having some resistance R ohm connected in parallel with a capacitor of capacitance C farad across a supply voltage of V volt as shown in fig.2.70. The phasor diagram of the circuit is shown in fig.2.71.

The circuit current I_r will only be in phase with the supply voltage when

$$I_C = I_L \sin \phi_L$$

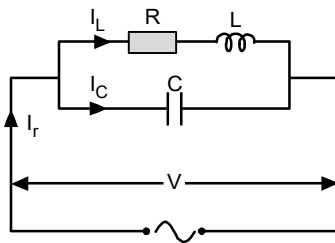


Fig. 2.70: Parallel resonance circuit

Since, at resonance the reactive component of current is suppressed, the circuit draws *minimum current* under this condition.

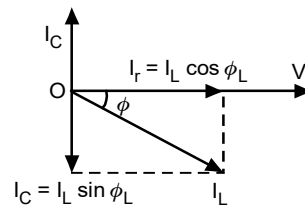


Fig. 2.71: Phasor diagram

Resonant frequency

The value of $X_L (= 2 \pi f L)$ and $X_C (= 1/2 \pi f C)$ can be changed by changing the supply frequency. When frequency increases, the value of X_L and consequently the value of Z_L increases. This decreases the magnitude of current I_L which also lags behind the voltage V by a progressively greater angle. On the other hand, the value of X_C decreases and consequently the value of I_C increases. At some frequency f_r (called resonance frequency), $I_C = I_L \sin \phi_L$ and resonance occurs.

∴ At parallel resonance, $I_C = I_L \sin \phi_L$

$$\text{where, } I_L = \frac{V}{Z_L} ; \sin \phi_L = \frac{X_L}{Z_L} \text{ and } I_C = \frac{V}{X_C} \quad \therefore \frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L} \quad \text{or } X_L X_C = Z_L^2$$

$$\text{or } \frac{\omega L}{\omega C} = Z_L^2 = (R^2 + X_L^2) \quad \dots(i)$$

$$\text{or } \frac{L}{C} = R^2 + (2 \pi f_r L)^2 \quad \text{or } 2 \pi f_r L = \sqrt{\frac{L}{C} - R^2}$$

$$\text{or } f_r = \frac{1}{2 \pi L} \sqrt{\frac{L}{C} - R^2} = \frac{1}{2 \pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \dots(ii)$$

If R is very small as compared to L , then

$$\text{Resonance frequency, } f_r = \frac{1}{2 \pi \sqrt{LC}}$$

Effect of parallel resonance

At parallel resonance ; Line current, $I_r = I_L \cos \phi$

$$\text{or } \frac{V}{Z_r} = \frac{V}{Z_L} \times \frac{R}{Z_L} \quad \text{or } \frac{1}{Z_r} = \frac{R}{Z_L^2}$$

$$\text{or } \frac{1}{Z_r} = \frac{R}{L/C} = \frac{CR}{L} \quad (\text{since } Z_L^2 = L/C \text{ from exp. i.)}$$

∴ Circuit impedance, $Z_r = L/CR$

It shows that

- (i) Circuit impedance $Z_r (= L/CR)$ is a pure resistive because there is no frequency terms present. If the value of L , R and C is in henry, ohm and farad then the value of Z_r is in ohm.
- (ii) The value of Z_r is very high because the ratio L/C is very large at parallel resonance.
- (iii) The value of circuit current $I_r (= V/Z_r)$ is very small, as shown in fig.2.72, because the value of Z_r is very high.
- (iv) The current flowing through the capacitor and coil is much greater than the line current because the impedance of each branch is quite low than circuit impedance Z_r .

*Since a parallel resonant circuit can draw a very small current and power from the mains, it is often regarded as **rejected circuit**.*

Resonance curve : A current-frequency curve for a typical parallel resonant circuit is shown in fig.2.72. The value of line current $I_r (= V/Z_r)$ is minimum at resonance.

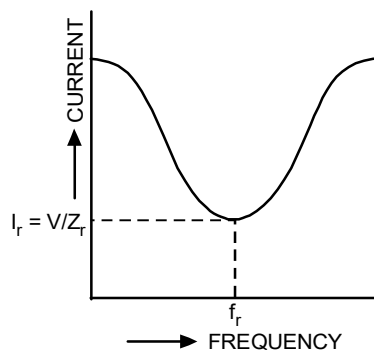


Fig. 2.72: Curve between f and I

2.37. Q-FACTOR OF A PARALLEL RESONANT CIRCUIT

We have seen that at parallel resonance, the current circulating between the two branches is many times greater than the line current drawn from the mains. This current simplification produced by the resonance is called the *Q-factor* of the parallel resonant circuit.

$$\therefore Q\text{-factor} = \frac{\text{Current circulating between } L \text{ and } C}{\text{Line current}} = \frac{I_C}{I_r}$$

$$\text{Now, } I_C = V/X_C = 2\pi f_r CV \text{ and } I_r = \frac{V}{L/CR}$$

$$\therefore Q\text{-factor} = \frac{2\pi f_r CV}{V} \times \frac{L}{CR} = \frac{2\pi f_r L}{R} \quad \dots \text{same as for series circuit}$$

$$\text{or } Q\text{-factor} = \frac{2\pi L}{R} \cdot \frac{1}{2\pi\sqrt{LC}} \quad \left(\because f_r = \frac{1}{2\pi\sqrt{LC}} \text{ neglecting } R \right)$$

$$\text{or } Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \text{or} \quad Q\text{-factor} = \sqrt{\frac{L}{C}} \text{ (neglecting } R)$$

The value of Q -factor is same as for series resonance.

2.38. COMPARISON OF SERIES AND PARALLEL RESONANT CIRCUITS

The comparison of series and parallel resonant circuit is given below :

S.No.	Particulars	Series Circuit	Parallel Circuit
1.	Impedance,	Minimum i.e. $Z_r = R$	Maximum i.e. $Z_r = L/CR$
2.	Current	Maximum i.e. $I_r = V/R$	Minimum i.e. $I_r = V/Z_r$
3.	Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
4.	Power factor	Unity	Unity
5.	Q -factor	X_L/R	X_L/R
6.	Amplification	It amplifies voltage	It amplifies current

Example 2.28. A parallel circuit consists of a coil having 25Ω resistance and 300 mH inductance in parallel with a capacitor of capacitance $4 \mu\text{F}$. Determine (i) the resonant frequency (ii) dynamic impedance of the circuit and (iii) Q -factor of the circuit at resonance.

$$\text{Solution : (i) Resonant frequency, } f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{or } f_r = \frac{1}{2\pi} \sqrt{\frac{1}{0.3 \times 4 \times 10^{-6}} - \frac{(25)^2}{(0.3)^2}} = \mathbf{144.68 \text{ Hz (Ans.)}}$$

$$\text{(ii) Dynamic impedance, } Z_r = \frac{L}{CR} = \frac{0.3}{4 \times 10^{-6} \times 25} = \mathbf{3000 \Omega \text{ (Ans.)}}$$

$$\text{(iii) } Q\text{-factor} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 145.27 \times 0.3}{25} = \mathbf{10.953 \text{ (Ans.)}}$$

Example 2.29. A coil of 15Ω resistance and 0.1 H inductance is connected in parallel with a capacitor of $15\text{ }\mu\text{F}$. Calculate the frequency at which the circuit will act as a non-inductive resistance of $R\text{ ohm}$. Find also the value of R , input current at resonant frequency and the ratio of the circulating current to the supply current at resonant frequency. The applied voltage is 100 V (rms) .

Solution : Capacitance, $C = 10\text{ }\mu\text{F} = 10 \times 10^{-6}\text{ F}$; $R = 10\text{ }\Omega$; $L = 0.1\text{ H}$; $V = 100\text{ V}$
The circuit will act as a resistive circuit at resonant frequency, *i.e.*

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \frac{1}{2\pi} \sqrt{\frac{1}{0.1 \times 15 \times 10^{-6}} - \frac{(10)^2}{(0.1)^2}} = \mathbf{127.74\text{ Hz (Ans.)}$$

$$\text{Dynamic resistance (or impedance)} = \frac{L}{CR} = \frac{0.1}{15 \times 10^{-6} \times 15} = \mathbf{444.44\text{ }\Omega (Ans.)}$$

$$\text{Input current at resonant frequency, } I = \frac{V}{L/CR} = \frac{100}{444.44} = \mathbf{0.225\text{ A (Ans.)}$$

The ratio of circulating current to line current at resonant frequency,

$$\frac{I_C}{I} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 127.74 \times 0.1}{15} = \mathbf{5.35 (Ans.)}$$

Example 2.30. An inductive circuit of resistance 2Ω and inductance 0.01 H is connected to a $250\text{ V, } 50\text{ Hz}$ supply. What value of capacitance is required to be placed in parallel with it to produce resonance ?

Solution : Here, $R = 2\text{ }\Omega$; $L = 0.014\text{ H}$; $V = 250\text{ V}$; $f = 50\text{ Hz}$

$$\text{Inductive reactance, } X_L = 2\pi fL = 2\pi \times 50 \times 0.01 = 3.14\text{ }\Omega$$

$$\text{Impedance, } Z = \sqrt{R^2 + X_L^2} = \sqrt{(2)^2 + (3.14)^2} = \mathbf{3.72\text{ }\Omega}$$

$$\text{At resonance, } Z = \sqrt{\frac{L}{C}}$$

$$\text{or } C = \frac{L}{Z^2} = \frac{0.01}{(3.72)^2} = \mathbf{722.6\text{ }\mu\text{F (Ans.)}$$

2.39. POLY-PHASE SYSTEM

Poly means many (more than one) and *phase* means windings or circuits, each of them having a single alternating voltage of the same magnitude and frequency. Hence, a polyphase system is essentially a combination of two or more than two voltages having same magnitude and frequency but displaced from one another by equal electrical angle. This angular displacement between the adjacent voltages is called phase difference and depends upon the number of phases.

$$\text{Phase difference} = \frac{360\text{ electrical degrees}}{\text{Number of phases}}$$

For three-phase system phase difference $= \frac{360^\circ}{3} = 120^\circ$ electrical.

*Thus, an a.c. system having a group of (two or more than two) equal voltages of same frequency arranged to have equal phase difference between them is called a **polyphase system**.*

2.40. ADVANTAGES OF 3-PHASE SYSTEM OVER 1-PHASE SYSTEM

1. **Constant power** : In single phase circuits, the power delivered is pulsating, whereas, in poly-phase system, power delivered is almost constant when the loads are balanced.
2. **Higher rating** : The rating (output) of a 3-phase machine is nearly 1.5 times the rating (output) of a single-phase machine of the same size.
3. **Power transmission economics** : To transmit the same amount of power over a fixed distance at a given voltage, 3-phase system requires only 75% of the weight of conducting material as required by single-phase system.
4. **Superiority of 3-phase induction motors** : The 3-phase induction motors are considered to be superior because of the following reasons :
 - (i) Three-phase induction motors are self starting, whereas 1-phase induction motors have no starting torque without auxiliary means.
 - (ii) Three-phase induction motors have higher power factor and efficiency than that of single-phase induction motors.

2.41. GENERATION OF 3-PHASE E.M.F.S.

In a 3-phase system, there are three equal voltages (or e.m.fs.) of the same frequency having a phase difference of 120° . These voltages can be produced by a three-phase, a.c. generator having three identical windings (or phases) displaced 120° electrical apart. When these windings are rotated in a stationary magnetic field [see fig. 2.73 (a)] or when these windings are kept stationary and the magnetic field is rotated [see fig. 2.73 (b)], an e.m.fs. is induced in each winding or phase. These e.m.fs. are of same magnitude and frequency but are displaced from one another by 120° electrical.

Consider three identical coils $a_1 a_2$, $b_1 b_2$ and $c_1 c_2$ mounted as shown in fig. 2.73 (a and b). Here, a_1 , b_1 and c_1 are the start terminals, whereas, a_2 , b_2 and c_2 are the finish terminals of the three coils. It may be noted that a phase difference of 120° electrical is maintained between the corresponding start terminals a_1 , b_1 and c_1 . Let the three coils mounted on the same axis be rotated (or the magnetic field system be rotated keeping coils stationary) in anticlockwise direction at ω radians/second, as shown in fig. 2.73 (a) and 2.73 (b) respectively. Three e.m.fs. are induced in the three coils respectively. Their magnitude and direction, at this instant, are as mentioned below :

- (i) The e.m.f. induced in coil $a_1 a_2$ is zero (consider start terminal a_1) and is increasing in the positive direction as shown by wave $e_{a_1 a_2}$ in fig. 2.73 (c).

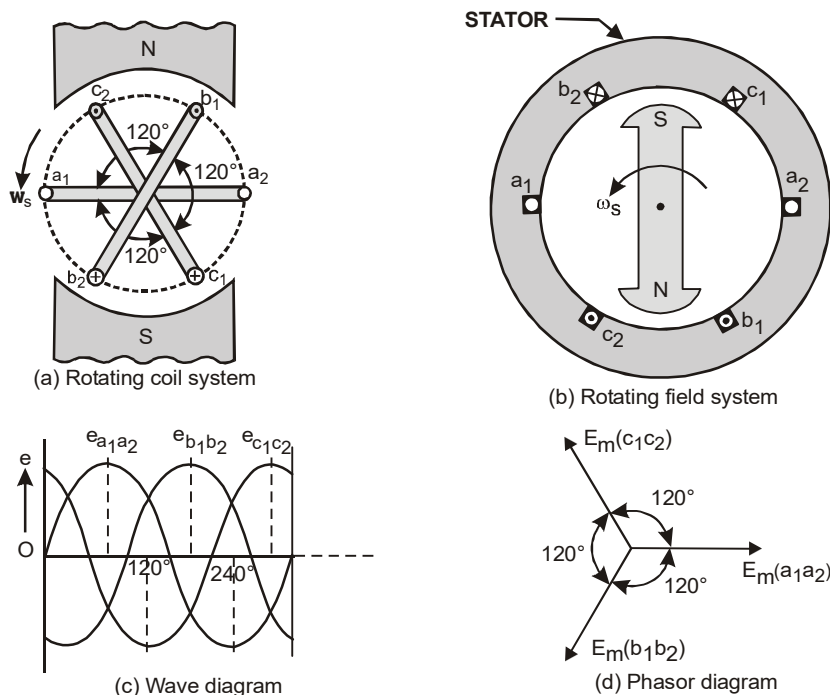


Fig. 2.73: Generation of 3-phase emfs

- (ii) The coil b_1b_2 is 120° (electrical) behind the coil a_1a_2 . The e.m.f. induced in this coil is negative and is becoming maximum negative (consider start terminal b_1) as shown by the e_{b1b2} in fig.2.73 (c).
- (iii) The coil c_1c_2 is 120° (electrical) behind b_1b_2 or 240° (electrical) behind a_1a_2 . The e.m.f. induced in this coil is positive and is decreasing (consider start terminal c_1) as shown by wave e_{c1c2} in fig.2.73 (c).

Phasor diagram

The e.m.fs. induced in three coils are of the same magnitude and frequency but are displaced by 120° (electrical) from each other as shown by phasor diagram in fig. 2.73 (d). These can be represented by the equations ;

$$e_{a1a2} = E_m \sin \omega t ;$$

$$e_{b1b2} = E_m \sin (\omega t - 2 \pi / 3)$$

$$e_{c1c2} = E_m \sin (\omega t - 4 \pi / 3) = E_m \sin (\omega t - 240^\circ)$$

2.42. NAMING THE PHASES

The three phases may be named out by numbers (1, 2 and 3) ; by letters (a , b and c) or by colours (*Red*, *Yellow* and *Blue* i.e. *R Y B*). In India they are named by *R Y B* i.e. red, yellow and blue.

2.43. PHASE SEQUENCE

In a three phase system, there are three voltages having same magnitude and frequency displaced by an angle of 120° electrical. They are attaining their positive maximum value in a particular order.

*The order in which the voltages (or e.m.fs.) in the three phases attain their maximum positive value is called the **phase sequence**.*

In the above article, the e.m.fs. in the three phases attain their positive maximum value in the order of a_1a_2 , b_1b_2 , c_1c_2 , therefore, the phase sequence is a, b, c . However, if the coils, or phases are being named out as R, Y, B in place of a, b, c respectively, then the phase sequence will be RYB .

The sequence RYB (or YBR or BRY) is considered as positive phase sequence, whereas, the RBV (or BYR or YRB) is considered as negative phase sequence.

The sequence knowledge of phase sequence is essential in the following important applications :

- (i) The direction of rotation of 3-phase induction motors depends upon the phase sequence of 3-phase supply. To reverse the direction of rotation, the phase sequence of the supply given to the motor has to be changed.
- (ii) The parallel operation of 3-phase alternators and transformers is only possible if phase sequence is known.

2.44. INTERCONNECTION OF THREE-PHASES

In a 3-phase a.c. generator, there are three windings. Each winding has two terminals (start and finish). If a separate load is connected across each phase winding as shown in fig.2.74, then each phase

supplies an independent load through a pair of leads (wires). Thus, six wires will be required in this case to connect the load to generator. This will make the whole system complicated and expensive.

In order to reduce the number of the conductors, the three phase windings of the a.c. generator are suitably inter-connected. The following are the two universally adopted methods of inter-connecting the three phases :

1. Star or wye (Y) connection ; 2. Mesh or delta (Δ) connection.

2.45. STAR OR WYE (Y) CONNECTION

In star or wye (Y) connections, the similar ends (either start or finish) of the three windings are connected to a common point called star or neutral point. The three line conductors are run from the remaining three free terminals called line conductors. Ordinarily only three wires are carried to the external circuit giving 3-phase, 3-wire star connected system. However, sometimes a fourth wire is carried from the star point to the external circuit, called neutral wire, giving 3-phase, 4-wire star connected system.

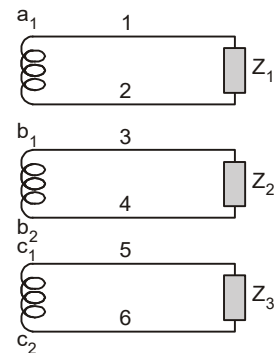


Fig. 2.74: Three coils representing three phases loaded separately.

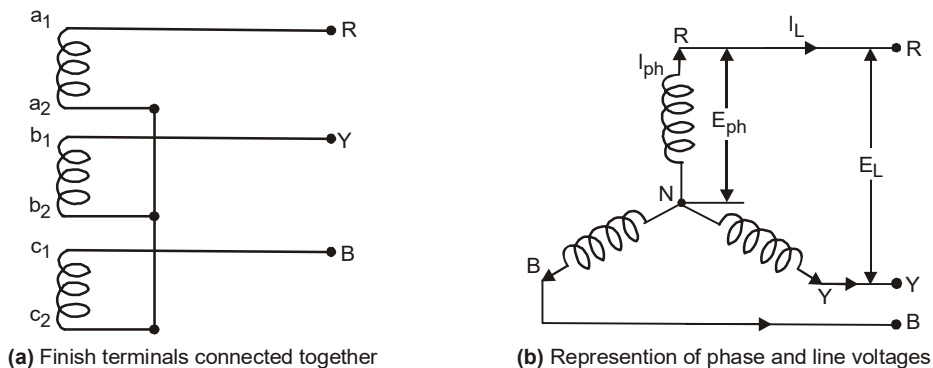


Fig. 2.75: Star connections

As shown in fig.2.75, the finish terminals a_2 , b_2 and c_2 of the three windings are connected to form a star or neutral point. From the remaining three free terminals three conductors are run, named R , Y and B . The current flowing through each phase is called phase current I_{ph} and current flowing through each line conductor is called line current I_L . Similarly, voltage across each phase is called phase voltage (E_{ph}) and voltage across two line conductors is called line voltage (E_L).

Relation between phase voltage and line voltage

The connections are shown in fig.2.76 (a). Since the system is balanced, the three voltages E_{NR} , E_{NY} and E_{NB} are equal in magnitude but displaced from one another by 120° electrical. Their phasor are shown in fig. 2.76 (b). The arrow heads on e.m.fs. and currents indicate the positive direction and not their actual direction at any instant.

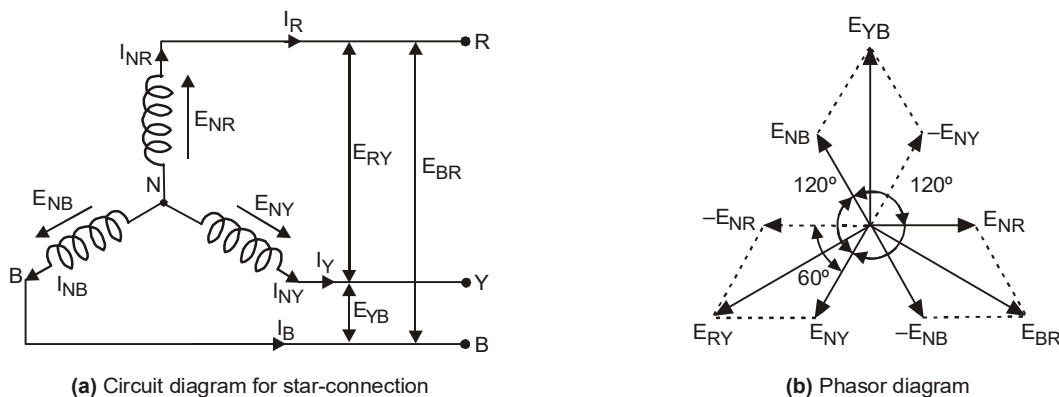


Fig. 2.76: Relation between line and phase voltages in star connections

Now, $E_{NR} = E_{NY} = E_{NB} = E_{ph}$ (in magnitude)

It may be seen that between any two lines, there are two phase voltages.

Tracing the loop $N R Y N$, we get $\overline{E_{NR}} + \overline{E_{RY}} - \overline{E_{NY}} = 0$

or $\overline{E_{RY}} = \overline{E_{NY}} - \overline{E_{NR}}$ (vector difference)

To find the vector sum of E_{NY} and $-E_{NR}$, reverse the vector E_{NR} and add it vectorially with E_{NY} as shown in fig. 2.76(b).

$$\therefore E_{RY} = \sqrt{E_{NY}^2 + E_{NR}^2 + 2 E_{NY} E_{NR} \cos 60^\circ}$$

$$\text{or } E_L = \sqrt{E_{ph}^2 + E_{ph}^2 + 2 E_{ph} E_{ph} \times 0.5} = \sqrt{3 E_{ph}^2} = \sqrt{3} E_{ph} \quad (\text{in magnitude})$$

$$\text{Similarly, } \overline{E_{YB}} = \overline{E_{NB}} - \overline{E_{NY}} \text{ or } E_L = \sqrt{3} E_{ph} = \overline{E_{NR}} - \overline{E_{NB}} \text{ or } E_L = \sqrt{3} E_{ph}$$

Hence, in star connections ; *Line voltage* = $\sqrt{3} \times \text{Phase voltage}$

Relation between phase current and line current

From fig.2.76(a), it is clear that same current flows through phase winding as well as the line conductor since line conductor is just connected in series with the phase winding.

$$\therefore I_R = I_{NR} ; I_Y = I_{NY} \text{ and } I_B = I_{NB}$$

where, $I_{NR} = I_{NY} = I_{NB} = I_{ph}$ (phase current) and $I_R = I_Y = I_B = I_L$ (line current)

Hence, in star connections ; *Line current* = *Phase current*

2.46. MESH OR DELTA (D) CONNECTION

In delta (Δ) or mesh connections, the finish terminal of one winding is connected to start terminal of the other winding and so on which forms a closed circuit. The three line conductors are run from three junctions of the mesh called line conductors, as shown in fig.2.77.

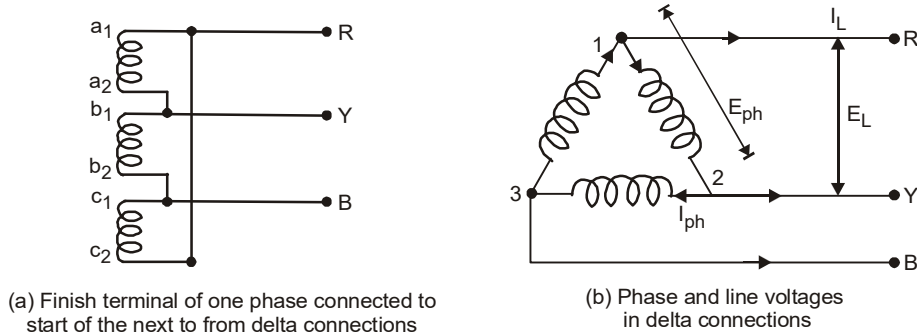


Fig. 2.77: Delta connection

To obtain delta connection a_2 is connected with b_1 , b_2 is connected with c_1 and c_2 is connected with a_1 as shown in fig. 2.77 (a). The three conductors R, Y and B are run from the three junctions called line conductors. The current flowing through each phase is called phase current (I_{ph}) and the current flowing through each line conductor is called line current (I_L) as shown in fig.2.77(b). Similarly, voltage across each phase is called phase voltage (E_{ph}) and voltage across two line conductors is called line voltage (E_L).

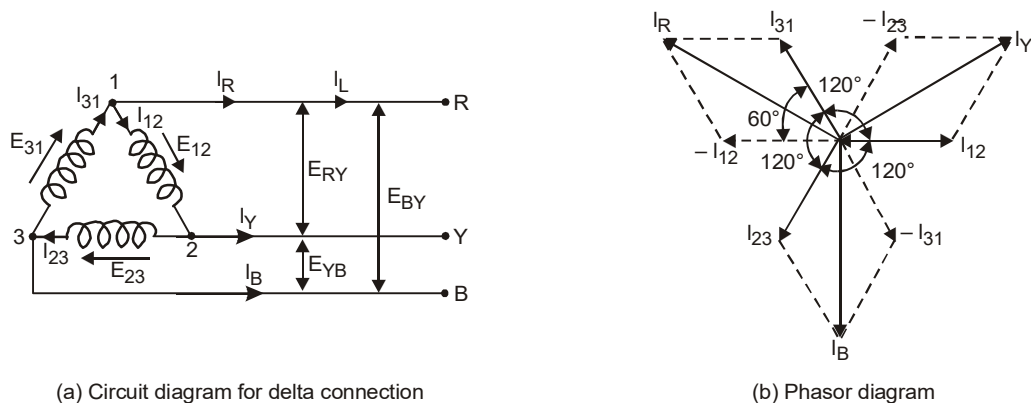


Fig. 2.78: Relation between line and phase currents in delta connection

Relation between phase voltage and line voltage

From fig. 2.78 (a), it is clear that voltage across terminals 1 and 2 is the same as across terminals R and Y.

$\therefore E_{12} = E_{RY}$; similarly $E_{23} = E_{YB}$ and $E_{31} = E_{BR}$

where $E_{12} = E_{23} = E_{31} = E_{ph}$ (phase voltage) and $E_{RY} = E_{YB} = E_{BR} = E_L$ (line voltage)

Hence, in delta connection; *Line voltage = Phase voltage.*

Relation between phase current and line current

Since the system is balanced, therefore, the three phase currents I_{12} , I_{23} and I_{31} are equal in magnitude but displaced from one another by 120° electrical. Their phasors are shown in fig.2.78 (b).

Thus $I_{12} = I_{23} = I_{31} = I_{ph}$ (in magnitude)

In fig. 2.78 (a), it may be seen that current is divided at every junction 1, 2 and 3.

Applying Kirchhoff's first law at junction 1 ;

Incoming currents = outgoing currents

$$\overline{I_{31}} = \overline{I_R} + \overline{I_{12}} \quad \text{or} \quad \overline{I_R} = \overline{I_{31}} - \overline{I_{12}} \quad (\text{vector difference})$$

To find the vector sum of I_{31} and $-I_{12}$, reverse the vector I_{12} and add it vectorially with I_{31} as shown in fig. 2.78 (b).

$$\therefore I_R = \sqrt{I_{12}^2 + I_{12}^2 + 2I_{31} I_{12} \cos 60^\circ} = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph} I_{ph} \times 0.5} \quad (\because I_R = I_L)$$

$$\text{or} \quad I_L = \sqrt{3 I_{ph}^2} = \sqrt{3} I_{ph} \quad (\text{in magnitude})$$

$$\text{Similarly, } \overline{I_Y} = \overline{I_{12}} - \overline{I_{23}} \quad \text{or} \quad I_L = \sqrt{3} I_{ph}$$

$$\text{and} \quad \overline{I_B} = \overline{I_{23}} - \overline{I_{31}} \quad \text{or} \quad I_L = \sqrt{3} I_{ph}$$

2.47. CONNECTIONS OF 3-PHASE LOADS

Similar to 3-phase supply, the three-phase loads may also be connected in

(i) Star or (ii) Delta

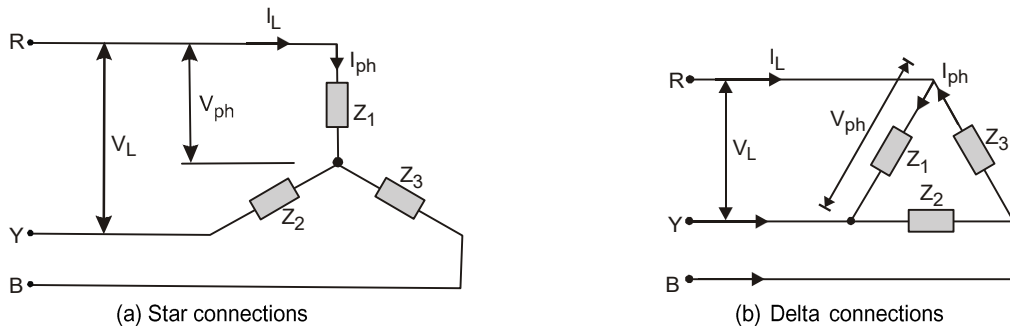


Fig. 2.79: Three-phase load, connected in star and delta

The 3-phase loads connected in star and delta are shown in fig. 2.79 (a) and (b) respectively.

The 3-phase loads may be balanced or unbalanced. If the three loads (impedances) Z_1 , Z_2 and Z_3 are having same magnitude and phase angle, then the 3-phase load is said to be a balanced load. Under such connections, all the phase or line currents and all the phase or line voltages are equal in magnitude.

Throughout this book, balanced 3-phase system will be considered unless stated otherwise.

2.48. POWER IN 3-PHASE CIRCUITS

Power in single-phase system or circuit is given by the relation ;

$$P = VI \cos \phi, \text{ where, } V = \text{voltage of single-phase i.e. } V_{ph}$$

$$I = \text{current of single-phase i.e. } I_{ph} \text{ and}$$

$$\cos \phi = \text{power factor of the circuit}$$

In 3-phase circuits (balanced load), the power is just the sum of powers in three phases,

$$\text{i.e., } P = 3 V_{ph} I_{ph} \cos \phi.$$

In star-connections

$$P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi \text{ (since } V_{ph} = V_L / \sqrt{3} \text{ and } I_{ph} = I_L)$$

$$\text{or } P = \sqrt{3} V_L I_L \cos \phi$$

In delta-connections

$$P = 3 V_L \frac{I_L}{\sqrt{3}} \cos \phi \text{ (since } V_{ph} = V_L \text{ and } I_{ph} = I_L / \sqrt{3})$$

$$\text{or } P = \sqrt{3} V_L I_L \cos \phi$$

Thus, the total power in a 3-phase balanced load, irrespective of connections (star or delta), is given by the relation $\sqrt{3} V_L I_L \cos \phi$. Its units are kW or W (watt).

$$\text{Apparent power, } P_a = \sqrt{3} V_L I_L$$

Its units are kVA or VA (volt-ampere)

$$\text{Reactive power, } P_r = \sqrt{3} V_L I_L \sin \phi$$

(volt-ampere-reactive).

Its units are kVAR or VAR

Example 2.31. Three resistors each of $200\ \Omega$ are connected in star across 400 V , 3-phase supply. Calculate the line current, phase current and power taken from the source. What will be the same values if the resistors are connected in delta?

Solution : When the resistors are connected in star as shown in fig.2.80.

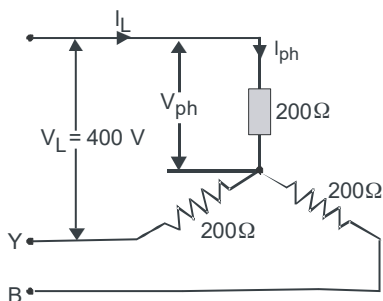


Fig.2.80: Star connections

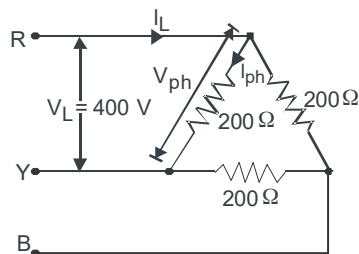


Fig. 2.81: Delta connections

Phase voltage, $V_{ph} = V_L / \sqrt{3} = 400 / \sqrt{3} = 231\text{ V}$

Phase current, $I_{ph} = V_{ph} / Z_{ph} = 231 / 200 = \mathbf{1.155\text{ A (Ans.)}}$

Line current, $I_L = I_{ph} = \mathbf{1.155\text{ A (Ans.)}}$

Power drawn, $P = 3 I_{ph}^2 R_{ph} = 3 \times (1.155)^2 \times 200 = \mathbf{800\text{ W (Ans.)}}$

When the resistor are connected in delta as shown in fig.2.81.

$V_{ph} = V_L = 400\text{ V}$

$I_{ph} = V_{ph} / Z_{ph} = 400 / 200 = \mathbf{2\text{ A (Ans.)}}$

$I_L = \sqrt{3} \times 2 = \mathbf{3.464\text{ A (Ans.)}}$

Power drawn, $P = 3 I_{ph}^2 R_{ph} = 3 \times (2)^2 \times 200 = \mathbf{2400\text{ W (Ans.)}}$

Example 2.32. Three similar coils each having a resistance of 6 ohm and an inductance of 0.0255 H in are connected in star across a , three phase, 400 V , 50 Hz supply. Calculate the line current, power factor, power in kW , kVA and kVAR .

Solution : The connection are shown in fig.2.82.

Here, $R = 6\ \Omega$, $L = 0.0255\text{ H}$, $f = 50\text{ Hz}$

$X_L = 2\pi fL = 2\pi \times 50 \times 0.0255 = 8\ \Omega$

Line voltage, $V_L = 400\text{ V}$

Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231\text{ V}$

$Z_{ph} = \sqrt{R^2 + X_L^2} = \sqrt{6^2 + 8^2} = 10\ \Omega$

Phase current, $I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{231}{10} = 23.1\text{ A}$

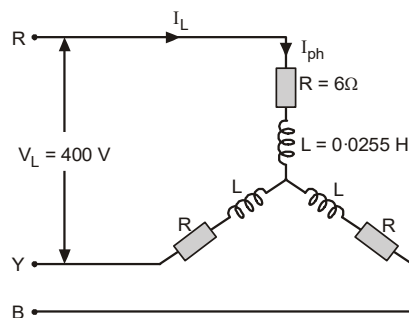


Fig. 2.82: Star connections

Line current, $I_L = I_{ph} = 23.1 \text{ A (Ans.)}$

Power factor, $\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{6}{10} = 0.6 \text{ lagging (Ans.)}$

Power input, $P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 23.1 \times 0.6 = 9600 \text{ W} = 9.6 \text{ kW (Ans.)}$

Power in KVA = $\frac{kW}{\cos \theta} = \frac{9.6}{0.6} = 16 \text{ (Ans.)}$

Power in kVAR = $\text{kVA} \times \sin \phi = \text{kVA} \times \sin \cos^{-1} \phi = 16 \times 0.8 = 12.8 \text{ (Ans.)}$

Example 2.33. A 3-phase star connected balanced load is connected across a 3-phase 400V, 50Hz supply. The line current is 20 A and the power consumed by the load is 12 kW. Calculate the, phase current, power factor resistance and inductance of the load.

Solution : The connection are shown in fig.2.83.

Here, $P = 12 \text{ kW} = 12000 \text{ W}$;

$V_L = 400 \text{ V}$; $f = 50 \text{ Hz}$; $I_L = 20 \text{ A}$

Phase voltage, $V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$

Phase current, $I_{ph} = I_L = 20 \text{ A (Ans.)}$

Phase impedance, $Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{231}{20} = 11.55 \Omega$

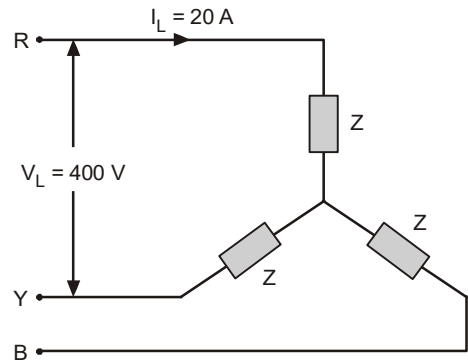


Fig. 2.83: Star connected balanced load

In 3-phase balanced load,

Power $P = \sqrt{3} V_L I_L \cos \phi$

\therefore Power factor, $\cos \phi = \frac{P}{\sqrt{3} V_L I_L} = \frac{12000}{\sqrt{3} \times 400 \times 20}$
 $= 0.866 \text{ (Ans.)}$

Resistance, $R = Z \cos \phi = 11.55 \times 0.866 = 10 \Omega \text{ (Ans.)}$

Inductive reactance, $X_L = \sqrt{Z_{ph}^2 - R^2} = \sqrt{(11.55)^2 - (10)^2} = 5.78 \Omega$

Inductance, $L = \frac{X_L}{2\pi f} = \frac{5.78}{2\pi \times 50} = 0.0184 \text{ H (Ans.)}$

Example 2.34. A 3-phase balanced delta connected load is connected to a 3-phase, 400 V, 50 Hz supply. It draws a line current of 17.32 A at 0.866 power factor lagging. Determine resistance and inductance of each branch. Also determine the power drawn by the load.

Solution : The connection are shown in fig.2.84.

Line voltage, $V_L = 400 \text{ V}$, $f = 50 \text{ Hz}$

Line current, $I_L = 17.32$ A, power factor, $\cos \phi = 0.866$ (lag).

$$\text{Phase current, } I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{17.32}{\sqrt{3}} = 10 \text{ A}$$

$$\cos \phi = 0.866$$

$$\phi = \cos^{-1} (0.866)$$

$$= 30^\circ$$

$$\text{Phase voltage, } V_{ph} = V_L = 400 \text{ V}$$

$$\text{Impedance of each branch, } Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{10} = 40 \Omega$$

$$\text{Power factor, } \cos \phi = \frac{R_{ph}}{Z_{ph}}$$

$$\text{Resistance of each branch, } R_{ph} = Z_{ph} \cos \phi = 40 \times 0.866 = \mathbf{34.64 \Omega} \text{ (Ans.)}$$

$$\text{Inductive reactance, } X_{ph} = \sqrt{Z_{ph}^2 - R_{ph}^2} = \sqrt{(40)^2 - (34.64)^2} = 20 \Omega$$

$$\text{Inductance, } L = \frac{X_{ph}}{2\pi f} = \frac{20}{2\pi \times 50} = \mathbf{63.66 \text{ mH}} \text{ (Ans.)}$$

$$\text{Power drawn, } P = 3V_{ph} I_{ph} \cos \phi = 3 \times 400 \times 10 \times 0.866 = \mathbf{10392 \text{ W}} \text{ (Ans.)}$$

$$\text{Power factor of the load, } \cos \phi = \frac{R}{Z} = \frac{15}{19.58} = 0.7661 \text{ lagging}$$

$$\begin{aligned} \text{Power absorbed in each phase, } P_{ph} &= V_{ph} I_{ph} \cos \phi \\ &= 200 \times 10.215 \times 0.7661 = \mathbf{1565 \text{ W}} \text{ (Ans.)} \end{aligned}$$

$$\text{Total power absorbed, } P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 200 \times 17.69 \times 0.7661 = \mathbf{4695 \text{ W}} \text{ (Ans.)}$$

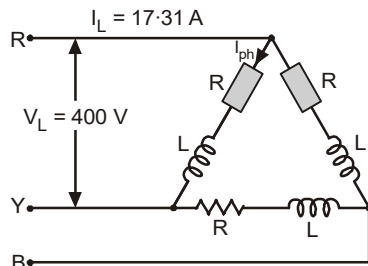




Fig. 2.84: Delta connected load

PRACTICE EXERCISE

- Three 100Ω resistors are connected first in star and then in delta across 415 V , 3-phase supply. Calculate the line and phase currents in each case and also the power taken from the source.
(Ans: 1.155 A; 800 W; 2 A; 3.464 A; 2400 W)
- Three similar coils each having a resistance of 8 ohm and an inductance of 0.0191 H in series in each phase is connected across a 400 V , three phase, 50 Hz supply. Calculate the line current, power input, kVA and kVAR taken by the load.
(Ans: 23.1 A ; 0.6 lagging; 9.6 kW; 16; 12.8)
- A 3-phase, 400 V supply is connected to a 3-phase star connected balanced load. The line current is 20 A and the power consumed by the load is 12 kW . Calculate the impedance of the load, phase current and power factor.
(Ans: 20 A; 0.866; 10Ω ; 0.0184 H)

4. A 3-phase balanced delta connected load is connected to a 3-phase, 400 V, 50 Hz supply. It draws a line current of 34.64 A at 0.8 power factor lagging. Determine resistance and inductance of each branch. Also determine the power drawn by each phase.
(Ans: 34.64 Ω ; 63.66 mH; 10392 W; 1565 W; 4695 W)
5. A 3- ϕ , 3-wire, Y-connected system has 150 V between phase to phase. Each phase has $Z = 5 \angle -30^\circ$. Find current in each phase and total power drawn from the mains. Draw the phasor diagram.
(Ans: 17.32 A; 3897 W)
6. Three similar coils each having a resistance of 15 ohm and an inductance of 0.04 henry are connected in star to a 3-phase 50 Hz supply, 200 volts between lines. Calculate the line current. If they are now connected in delta, calculate the phase current, line current and the total power absorbed in each phase.
(Ans: 5.9 A; 17.69 A; 1565 W; 4695 W)

PROJECT

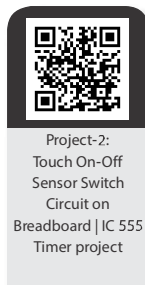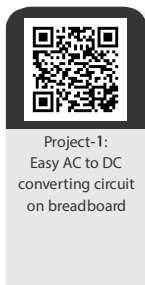

SUMMARY

1. *Alternating voltage* : A voltage that changes its polarity and magnitude at regular intervals of time is called an *alternating voltage*.
2. *Sinusoidal alternating quantity* : An alternating quantity that varies according to sine of angle θ is known as sinusoidal alternating quantity.
3. *Equation of an alternating quantity* :

$$e = E_m \sin \theta = E_m \sin \omega t ; i = I_m \sin \theta = I_m \sin \omega t$$
4. *Wave form* : The shape of the curve obtained by plotting the instantaneous values along y-axis and time or angle $\theta (= \omega t)$ along x-axis is called wave form or wave shape.
5. *Cycle* : When an alternating quantity goes through a complete set of +ve and -ve value or goes through 360 electrical degrees, it is said to have completed a cycle.
6. *Alternation* : One half of cycle is called an alternation.
7. *Time period (T)* : Time taken to complete one cycle in second is called time period.

8. *Frequency (f)* : The number of cycles made per second by an alternating quantity is called its frequency. It is measured in c/s or Hz (Hertz).
9. *Relations* : $f = 1/T$ and $\omega = 2 \pi f$
10. *Instantaneous value (v or i)* : The value of an alternating quantity at any instant is called its instantaneous value.
11. *Amplitude (V_m or I_m)* : The maximum value obtained by an alternating quantity during a cycle is called its amplitude or maximum value or peak value or crest value.
12. *Average value (V_{av} or I_{av})* : The arithmetic average of all the instantaneous values considered of an alternating quantity over one cycle is called its *average value*.

$$I_{av} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

For sinusoidal current, $I_{av} = 2 I_m / \pi = 0.637 I_m$.

13. *Effective or r.m.s. value ($V_{r.m.s.}$ or $I_{r.m.s.}$)* : That steady current which when flows through a resistor of known resistance for a given time produces the same amount of heat as produced by the alternating current when flows through the same resistor for the same time is called effective or r.m.s. value of the alternating current.

$$I_{r.m.s.} = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}}$$

For sinusoidal current, $I_{r.m.s.} = I_m / \sqrt{2} = 0.707 I_m$.

14. *Form factor* : $I_{r.m.s.} / I_{av}$; For sinusoidal quantities, its value is 1.11.
15. *Peak factor* : $I_m / I_{r.m.s.}$; For sinusoidal quantities, its value is 1.414.
16. *Phase* : The phase of an alternating quantity at an instant is defined as the fractional part of a cycle through which the quantity has advanced from a selected origin. It has less importance, in practice.
17. *Phase difference* : The angular displacement between the maximum positive values of two alternating quantities having the same frequency is called the phase difference between them.

Mathematically ; If $i_1 = I_{m1} \sin \omega t$ the $i_2 = I_{m2} \sin (\omega t \pm \phi)$

18. *Leading quantity* : An alternating quantity that attains its +ve maximum value prior to the other is called leading quantity.
19. *Lagging quantity* : An alternating quantity that attains its +ve maximum value after the other is called lagging quantity.
20. *A.C. Circuit* : The path for the flow of alternating current is called a.c. circuit.
21. *Pure resistive circuit* : Circuit contains pure resistance.

$$v = V_m \sin \omega t ; i = I_m \sin \omega t ; I_m = V_m / R ; P = VI ; p.f. = 1 ;$$

Current is in phase with voltage vector.

22. *Pure inductive circuit* : Circuit contains pure inductance.

$v = V_m \sin \omega t$; $i = I_m \sin (\omega t - \pi/2)$; $I_m = V_m/X_L$; $X_L = 2 \pi f L$; $P = 0$; $p.f. = 0$ lag ; Current lags behind voltage vector of 90° (i.e. $\pi/2$)

23. *Pure capacitive circuit* : Circuit contains pure capacitance.

$v = V_m \sin \omega t$; $i = I_m \sin (\omega t + \pi/2)$; $I_m = V_m/X_C$; $X_C = 1/2 \pi f C$; $P = 0$; $p.f. = 0$ lead ; Current leads the voltage vector by 90° (i.e. $\pi/2$).

24. *R—L series circuit* : Circuit contains resistance and inductance in series. It is generally called inductive circuit. $v = V_m \sin \omega t$; $i = I_m \sin (\omega t - \phi)$; $\phi = \tan^{-1} X_L/R$; $I_m = V_m/Z$; $Z = \sqrt{R^2 + X_L^2}$; $P = VI \cos \phi = I^2 R$; $p.f. = \cos \phi = R/Z$ lag ;

25. *Power triangle* : The three components of a right angled power triangle are :

(i) *True power* : It is the base or horizontal component of the power triangle which represents the actual or true power consumed in an a.c. circuit.

$P = VI \cos \phi$; unit of true power is watt (W), kilowatt (kW) or megawatts (MW)

(ii) *Reactive power* : It is the perpendicular or vertical component of the power triangle which represents reactive power of the circuit. This is the power which reacts in circuit, in fact, it is that power which is supplied by the source in a quarter cycle and the same is fed back in the next quarter cycle.

$P_r = VI \sin \phi$; units of reactive power are volt-ampere-reactive (VAR), kVAR or MVAR.

(iii) *Apparent power* : It is the hypotenuse of the power triangle. It is the power which looks to be consumed in the circuit but actually it is not so.

$P_a = VI$; units of apparent power are volt-ampere (VA), kVA or MVA.

26. *Power factor and its importance* : $p.f. = \cos \phi = R/Z = \text{true power/apparent power}$

Ill-effects of poor p.f. (i) greater conductor size, (ii) poor efficiency, (iii) poor voltage regulation and (iv) larger kVA rating of equipment.

27. *R—C series circuit* : Circuit contains resistance and capacitance in series. It is generally called capacitive circuit. $v = V_m \sin \omega t$; $i = I_m \sin (\omega t + \phi)$; $\phi = \tan^{-1} X_C/R$; $I_m = V_m/Z$; $Z = \sqrt{R^2 + X_C^2}$; $P = VI \cos \phi = I^2 R$; $P.f. = \cos \phi = R/Z$ leading ;

28. *R—L—C series circuit* : Circuit contains resistance, inductance and capacitance in series. This circuit behaves as under :

(i) When $X_L > X_C$inductive circuit.....p.f. lagging0 to 1

(ii) When $X_L < X_C$capacitive circuit.....p.f. leading0 to 1

(iii) When $X_L = X_C$resistive circuit.....p.f. unity....1 only.

29. *Series resonance* : An $R - L - C$ circuit is said to be in series resonance, when

$$X_L = X_C ; Z_r = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\text{Resonance frequency, } f_r = 1/2 \pi \sqrt{LC}$$

$$\text{Current is maximum i.e. } I_r = V/Z_r = V/R$$

$$Q\text{-factor} = 2 \pi f_r L/R = \frac{1}{R} \sqrt{\frac{L}{C}}$$

30. *A.C. Parallel Circuit* : An a.c. circuit in which number of branches (each branch contains number of component in series) are connected in parallel is called an a.c. parallel circuit.

31. *Method of solving parallel a.c. circuits* : The following methods are used :

(i) Phasor or vector method (ii) Admittance method (iii) Symbolic or j-method

Phasor or vector method : The magnitude and direction of the currents flowing through various branches is determined are represented as phasors. The phasors are resolved to determine the resultant.

32. *Parallel resonance* : A parallel circuit, containing inductor and capacitor in parallel, is said to be in parallel resonance when circuit current is in phase with the applied voltage, i.e.

$$I_C = I_L \sin \phi ; \text{Resonance frequency, } f_r = \frac{1}{2 \pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{If } R \text{ is very small and neglected, } f_r = \frac{1}{2 \pi \sqrt{LC}}$$

$$\text{Current is minimum, i.e., } I_r = V/Z_r ; Q\text{-factor} = 2 \pi f_r L/R = \frac{1}{R} \sqrt{\frac{L}{C}}$$

33. *Polyphase system* : An a.c. system having a group of (two or more than two) equal voltages of same frequency arranged to have equal phase difference between them (adjacent e.m.fs.) is called *polyphase system*.

34. *Advantage of 3-phase system* : Constant power ; higher rating (1.5 times), economy in power transmission ; superiority of 3-phase induction motor etc.

35. *Generation of 3-phase e.m.fs.* : $e_{a1a2} = E_m \sin \omega t$; $e_{b1b2} = E_m \sin (\omega t - 120^\circ)$; $e_{c1c2} = E_m \sin (\omega t - 240^\circ)$

36. *Interconnection of three-phases* : (i) Star-connection : $E_L = \sqrt{3} E_{ph}$; $I_L = I_{ph}$

$$(ii) \text{Delta-connection : } E_L = E_{ph} ; I_L = \sqrt{3} I_{ph}$$

$$\text{Power, } P = \sqrt{3} V_L I_L \cos \phi = 3 V_{ph} I_{ph} \cos \phi$$

SHORT ANSWER QUESTIONS

1. What do you understand by alternating current ?
2. What is difference between ac and dc ?
3. What is meant by instantaneous value ?
4. What is meant by peak value of an alternating quantity ?
5. What are scalar and vector quantities ?
6. What do you mean by phase ?
7. What is an in-phase condition ?
8. What is an out of phase condition ?
9. List the various factors governing the emf generation ?
10. Define average value of an alternating quantity.
11. What is *RMS* value of an alternating quantity ?
12. Why are alternating voltages and currents expressed in *RMS* values instead of average values ?
13. Define form factor.
14. Define peak factor of an alternating quantity.
15. What is significance of form factor ?
16. What is the significance of peak factor ?
17. Differentiate between form factor and peak factor.
18. How will you calculate average value for symmetrical waves ?
19. What is a phasor ?
20. What is the significance of the phasor representation of an alternating quantity ?
21. What is meant by phase difference ?
22. What are leading and lagging quantities ?
23. What is an *A.C.* circuit ?
24. What are the differences between *DC* circuit and *AC* circuit
25. What is the phase difference between voltage and current in a resistor ?
26. What is the average power in a resistor ?
27. What is the phase difference between current and voltage in an inductor (pure inductance ?
28. Define inductive reactance.

29. What is the value of average power in an inductor ?
30. What is the phase difference between voltage and current in a capacitor ?
31. Define capacitive reactance.
32. What is the value of average power in a capacitor.
33. What is a series RL circuit ?
34. What is the impedance of RL series circuit ?
35. What is apparent power of an AC circuit ?
36. What is real power of an A.C. circuit ?
37. What is power factor ?
38. What is reactive power of an $a.c.$ circuit ?
39. What is active component of an $a.c.$ current ?
40. What is a reactive component of an $a.c.$ current ?
41. What do you understand by RC series circuit ?
42. What is the impedance of RC series circuit ?
43. What is meant by RLC series circuit ?
44. What is the impedance of RLC series circuit ?
45. What is parallel ac circuit ?
46. What is mean by resonance circuit ?
47. What happens when RLC series circuit is at resonance ?
48. How does series resonance result in voltage amplification ?
49. The Q of a coil is 20 what does it mean ?
50. What are important points to be noted for a parallel circuit when it is at resonance ?
51. At parallel resonance why impedance of the circuit is pure resistance ?
52. Three-phase system is preferred over single-phase system, why ?
53. The knowledge of phase sequence is very important in industries and power system, why ?
54. In star connections the voltage between the two line terminals is not double to that of phase voltage but it is $\sqrt{3}$ times, why ?
55. What do you understand by the following terms :
(i) Three phase balanced supply, (ii) Three phase balanced load, (iii) Three phase unbalanced supply, (iv) Three phase unbalanced load, (v) Single phasing.
56. Write down the advantages of 3-phase system over single phase.
57. What are the two ways of connecting a 3-phase system ? Draw their phasor diagrams and write down the relationship between phase and line voltages and currents for these systems.

58. Show that the total power in a 3-phase balanced load is $P = \sqrt{3} V I \cos \phi$ where V is the rms line voltage, I is the rms line current and ϕ is the phase angle between phase voltage and phase current.
59. Compare 3-phase star and delta-connected systems

S No.	Question (In para)	Marks	CO	BL	PO
1.	What do you understand by alternating current ?	2	CO1	BL2	PO2

NUMERICAL FOR PRACTICE

- A current is given by $i = 45.34 \sin 377 t$, find (i) maximum value of current ; (ii) r.m.s. value of current ; (iii) frequency of current ; (iv) radians through which its phasor has advanced after 0.01 second ; (v) number of degrees in (iv) and (vi) value of current at instant mentioned in part (iv).
(Ans. 45.34 A ; 32 A ; 60 Hz ; 3.77 rad. ; 216° ; -26.6 A)
- An alternating voltage is given as $v = 200 \sin 314 t$ determine its (i) maximum value ; (ii) effective value ; (iv) form factor ; (v) value of voltage after 0.0025 second taking reckoning time from the instant when voltage is zero and becoming positive ; (vi) time after which voltage attains 200 V for the first time.
(Ans. 200 V ; 141.42 V ; 50 Hz ; 1.11 ; 141.42 V ; 1.67 ms)
- A sinusoidal voltage of 50 Hz has a maximum value of $100\sqrt{2}$ V. At what time measured from a positive maximum value will the instantaneous voltage be 70.7 V ?
(Ans. 3.33 ms)
- Calculate the r.m.s. value of a periodic voltage having the following values for equal intervals changing suddenly from one value to the next : 0, 10, 30, 60, 30, 10, 0, -10, -30, -60, -30, -10 etc.
(Ans. 30.55 V)
- For a full wave rectified alternating current, determine (i) average value ; (ii) r.m.s. value ; (iii) form factor and (iv) peak factor. (Ans. $0.637 I_m$; $0.707 I_m$; 1.11 ; 1.4142)
- Represent the following alternating currents as phasors on the same axes and determine phase angle of all other currents with I_1 : $i_1 = 15 \sin (\omega t + \pi/3)$; $i_2 = 16 \cos (\omega t - \pi/6)$; $i_3 = 20 \cos (\omega t - \pi/3)$; $i_4 = 10 \sin (\omega t - \pi/6)$. (Ans. 60° ; 30° ; 90°)
- An e.m.f. $e_1 = 50 \sin \omega t$ and the other $e_2 = 30 \sin (\omega t - \pi/6)$ act together in the same circuit. Find the resultant e.m.f. (Ans. $77.45 \sin (\omega t + 11.17^\circ)$)

8. A 230 V water heater operating for 3 hours daily on a.c. mains is found to give 250 k calorie per hour, the efficiency of heater system being 90%. Determine (i) the r.m.s. and the maximum value of current ; (ii) resistance of the heater ; (iii) also write down the equations for voltage and current when the supply frequency is 50 Hz.
(Ans. 1.41 A ; 1.993 A ; $163.1\ \Omega$; $v = 325.27 \sin 314\ t$; $i = 1.993 \sin 314\ t$)
9. An inductive coil has negligible resistance and inductance of 0.1 henry. It is connected across a 220 V, 50 Hz supply. Find the current and power. Also write down the expression for instantaneous value of applied voltage and current.
(Ans. 7 A ; zero ; $v = 311 \sin 314\ t$, $i = 9.9 \sin (314\ t - \pi/2)$)
10. A capacitor has a capacitance of 30 microfarad. Find its capacitive reactance for frequency of 25 and 50 Hz. Find in each case the current if the supply voltage is 400 V.
(Ans. $212.2\ \Omega$; $106.1\ \Omega$; 2.073 A ; 4.146 A)
11. A coil having a resistance of $7\ \Omega$ and an inductance of 31.8 m H is connected to 230 V, 50 Hz supply. Calculate (i) the circuit current, (ii) phase angle, (iii) power factor and (iv) power consumed.
(Ans. 18.85 A ; 55° lag ; 0.573 lag ; 2484.24 W)
12. A voltage $e = 200 \sin 100\ \pi t$ is applied to a coil having $R = 200\text{ ohm}$ and $L = 638\text{ millihenry}$. Find the expression for the current and also determine the power taken by the coil.
(Ans. $0.706 \sin (314\ t - 45.06^\circ)$; 50 W)
13. A 100 V, 60 W lamp is to be operated at 220 V, 50 Hz mains. What (i) pure resistance (ii) pure inductance or (iii) pure capacitance should be, placed in series with the lamp, which enable it to run without being damaged ? Which method would be preferred and why ?
(Ans. $200\ \Omega$; 1.038 H ; $9.75\ \mu\text{F}$)
14. Two coils are connected in series having resistance and inductive reactance 5 and 6 ohm, 3 and 7 ohm respectively. A sinusoidal voltage of 200 V, 50 Hz is applied across the combination. Calculate (i) current, power factor and power absorbed in the whole circuit ; (ii) voltage drop across each coil ; (iii) power factor and power absorbed in each coil.
(Ans. 13.1 A , 0.5241 lag , 1373 W ; 102.3 V , 99.77 V ; 0.64 lag , 858 W , 0.394 lag , 515 W)
15. A voltage of 125 V at 50 Hz is applied across a non-inductive resistor connected in series with a condenser. The current in the circuit is 2.2 A. The power loss in the resistor is 96.8 W and that in the condenser is negligible. Calculate the resistance and the capacitance.
(Ans. $20\ \Omega$; $59.85\ \mu\text{F}$)
16. An a.c. circuit having a resistance of 10 ohm, an inductance of 0.2 henry and a capacitance of $100\ \mu\text{F}$ in series, is connected across a single-phase 110V, 50 Hz supply. Calculate the following for this circuit. (i) Resultant reactance ; (ii) Impedance ; (iii) Current ; (iv) Voltages across R , L and C ; (v) Phase difference between the current and supply voltage ; (vi) Draw the phasor diagram of the circuit.
(Ans. 31 ohm ; 32.573 ohm ; 3.377 A , 33.77 V , 212.18 V , 107.49 V ; 72.12°)
17. A coil of resistance $100\ \Omega$ and inductance $100\ \mu\text{H}$ is connected in series with a 100 pF capacitor. The circuit is connected to a 50 V variable frequency supply. Calculate (i) the resonant frequency ; (ii) current at resonance ; (iii) voltage across L and C at resonance and (iv) Q -factor of the circuit. (Ans. $1.59 \times 10^6\text{ Hz}$; 0.5 A ; 500 V ; 500 V ; 10)

18. A capacitor of capacitance C farads is connected in series with a coil having $75\ \Omega$ resistance and 12 henry inductance. Calculate the value of C when the circuit is connected across 220 V, 60 Hz supply. (Ans. $0.587\ \mu F$)
19. Determine the parameter of an $R - L - C$ series circuit that will resonate at 10000 Hz, has a bandwidth of 1000 Hz and draws 15.3 W from a 200 V generator operating at the resonant frequency of the circuit. (Ans. $2.614\ \text{ohm}$, $416\ \text{m H}$, $609\ \text{p F}$)
20. A coil of resistance $15\ \text{ohm}$ and inductance 0.05 henry is connected in parallel with a non-inductive resistor of $20\ \text{ohm}$. Find (i) the current in each branch of the circuit, (ii) the total current supplied, and (iii) the phase angle of the combination, when a voltage of 230 volt at 50 hertz is applied across the circuit. Draw the relevant phasor diagram. (Ans. $10.59\ \text{A}$, $11.5\ \text{A}$; $20.31\ \text{A}$; 22.14° lagging)
21. Two coils are connected in parallel across a 200 V, 50 Hz supply. At the supply frequency, their impedances are 6 and $10\ \text{ohm}$ respectively and their resistances are 2 and $3\ \text{ohm}$ respectively, calculate : (i) The current in each coil ; (ii) the total current ; (iii) The total power. (Ans. $33.33\ \text{A}$; $20\ \text{A}$; $53.3\ \text{A}$; $3421.6\ \text{W}$)
22. A single phase motor draws $10\ \text{A}$ at $230\ \text{V}$ at a power factor of 0.8 lagging. Calculate the value of the capacitor which when connected across the terminals of the motor will bring the line current in phase with the voltage. Frequency of supply may be assumed as 50 Hz. (Ans. $166\ \mu F$)
23. A parallel circuit consists of a $2.5\ \mu F$ capacitor and a coil whose resistance and inductance are $15\ \Omega$ and $260\ \text{m H}$ respectively. Determine (i) the resonant frequency ; (ii) Q of the coil and (iii) dynamic impedance of the circuit. (Ans. $197\ \text{Hz}$, 21.45 , $6933.33\ \Omega$)
24. A coil has a resistance of $500\ \Omega$ and inductance of $350\ \mu H$. Find the capacitance of a capacitor which when connected in parallel with the coil, will produce resonance with a supply frequency of 10^6 Hz. If a second capacitor of capacitance $30\ \text{p F}$ is connected in parallel with the first capacitor, find the frequency at which resonance will occur. (Ans. $68.8\ \text{p F}$, $0.825\ \text{M Hz}$)
25. Three similar coils each having a resistance of $15\ \text{ohm}$ and an inductance of 0.04 henry are connected in star to a 3-phase, 50 Hz supply, 200 volt between lines. Calculate the line current. If they are now connected in delta, calculate the phase current, line current and the total power absorbed in each phase. (Ans. $5.9\ \text{A}$, $10.215\ \text{A}$, $17.69\ \text{A}$, $1565\ \text{W}$, $4695\ \text{W}$)
26. Three identical impedances are connected in delta to a 3-phase, $400\ \text{V}$, 50 Hz supply. The line current is $34.65\ \text{A}$ and total power taken from supply is $14.14\ \text{kW}$. Calculate the value of resistance and inductance of each phase. (Ans. $11.78\ \Omega$, $51.45\ \text{mH}$)
27. Three inductive coils each of inductances $50\ \text{mH}$ are connected in star to a 3-phase, $200\ \text{V}$, 50 Hz system. Calculate the inductance of each coil, which when connected in delta to the same supply, will taken the same line current. (Ans. $150\ \text{mH}$)
28. Three $100\ \text{ohm}$ non-inductive resistances are connected in (i) star (ii) delta across a $400\ \text{V}$, 50 Hz supply. Calculate the power taken from the supply in each case. In the event of one of the resistance getting opened what would be the value of the total power taken from the supply in each case. (Ans. $1600\ \text{W}$, $4800\ \text{W}$; $800\ \text{W}$, $3200\ \text{W}$)

29. Show that the power consumption, when three identical impedances are connected in delta across a balanced 3-phase supply is three times that when the same impedances are connected in star across the same 3-phase supply.
30. A 400 V, 3-phase system is connected to a balanced star load with the load impedance in each phase as $40 \angle 60^\circ$ ohm. Find (i) the line and phase currents and (ii) draw phasor diagram showing line voltages, line currents and phase currents.

(Ans. $5.775 A$; $5.775 A$)

Fill the following table yourself

S No.	Question (In para)	Marks	CO	BL	PO

MULTI-CHOICE QUESTIONS

- The r.m.s. value of an alternating current is given by steady current which when flowing through a given circuit for a given time produces
 - more heat than produced by a.c. when flowing through the same circuit
 - the same amount of heat as produced by a.c. when flowing through the same circuit.
 - less heat than produced by a.c. when flowing through the same circuit.
 - 144 joule.
- The average value of sinusoidal current is given by the relation
 - $I_m/\sqrt{2}$
 - $0.707 I_m$
 - $2 I_m/\pi$
 - none of above.
- In case of an unsymmetrical alternating quantity, the average value must always be taken over
 - the half cycle
 - the quarter cycle
 - the whole cycle
 - any fraction of the cycle.
- The r.m.s. value of sinusoidal alternating current is given by the relation
 - $I_m/\sqrt{2}$
 - $0.637 I_m$
 - $2 I_m/\pi$
 - $I_m/2$
- The amplitude factor of sinusoidal current is
 - 1.11
 - 1.414
 - 0.707
 - 0.637

6. *The r.m.s. value is a fraction of maximum value of sinusoidal current, the value of the fraction is*
 (A) $1/\sqrt{2}$ (B) 0.637 (C) $\sqrt{2}$ (D) none of above.
7. *The r.m.s. value of an a.c. signal is 10 volt. The peak to peak value will be*
 (A) 6.37 V (B) 14.14 V (C) 141 V (D) 28.28 V
8. *A wave completes one cycle in 10μ seconds, its frequency will be*
 (A) 0.1 M Hz (B) 100,000 Hz (C) 100 k Hz (D) All of these.
9. *An alternating quantity which attains its positive maximum value prior to the other is called the*
 (A) in phase quantity (B) lagging quantity (C) leading quantity (D) none of above.
10. *If the effective value of the sinusoidal voltage is 222 volt. Its average value will be*
 (A) 200 V (B) 246.42 V (C) 313.02 V (D) none of above
11. *The inductive reactance is measured in ohm because it*
 (A) Opposes the alternating current
 (B) Helps the alternating current
 (C) is the product of frequency and inductance
 (D) has a back e.m.f.
12. *In an R-L series circuit, if $R = X_L$, the phase difference between ac voltage and current will be*
 (A) 0° (B) 30° (C) 45° (D) 90°
13. *If an a.c. voltage is applied across a capacitor, the alternating current flows through the circuit because*
 (A) of high peak value of voltage. (B) capacitor offers low opposition
 (C) electrons can pass through capacitor (D) capacitor charges and discharges according to the supply frequency.
14. *As frequencies increases, the value of capacitive reactance*
 (A) increases (B) decreases
 (C) remains the same (D) First decreases then increases
15. *In a pure inductive a.c. circuit :*
 (A) voltage leads the current vector by 90°
 (B) current lags the voltage vector by 90°
 (C) current is in phase with voltage vector.
 (D) both a and b
16. *In an a.c. circuit, the true expression for apparent power is*
 (A) $V_{av} I_{av}$ (B) $VI \cos \phi$ (C) $V_{r.m.s.} I_{r.m.s.}$ (D) $VI \sin \phi$

17. *If the frequency of power supply offered to a pure capacitive circuit is doubled,*
 (A) the current will also be doubled
 (B) the current will reduce to half
 (C) the opposition to current decreases to half
 (D) both *a* and *b*
18. *The power factor of a series resonance circuit is*
 (A) zero (B) 0.5 lagging (C) unity (D) 0.5 leading
19. *The current in a parallel resonance circuit will be*
 (A) zero (B) infinity (C) very small (D) very large
20. *An R—L—C series circuit contains resistance 25 Ω , inductance 8 m H and capacitance of 80 μ F, the p.f. of the circuit will be*
 (A) unity (B) zero (C) lagging (D) leading
21. *For the same rating, the size of 3-phase machine to that of 1-phase machine will be*
 (A) more (B) less (C) same (D) none of the above.
22. *To transmit the same amount of power over a particular distance at a given voltage, the amount of conducting material required in a 3-phase system to that of 1-phase system will be*
 (A) 1.5 times (B) 0.5 times (C) $\sqrt{3}$ times (D) 0.75 times
23. *The phase sequence of a 3-phase system is RYB. The same phase sequence can be represented as*
 (A) RBY (B) BYR (C) YBR (D) YRB
24. *In a balanced 3-phase, star-connected system, the phase difference between phase voltages and their respective line voltages are*
 (A) 30° (B) 60° (C) 120° (D) 45°
25. *In a balanced 3-phase, star-connected system, the relation between phase voltage (V_{ph}) and line voltage (V_L) is*
 (A) $V_{ph} = \sqrt{3} V_L$ (B) $V_{ph} = 0.577 V_L$ (C) $V_{ph} = V_L \sqrt{2}$ (D) none of above
26. *A 3-phase load is said to be a balanced load, if all the three phases have the same*
 (A) impedance (B) power factor (C) both *a* and *b* (D) none of above
27. *Three 100 ohm resistors are connected in star across a 400 V, 3-phase supply, if one of the resistors is disconnected, then the line current will be*
 (A) 2 A (B) 4 A (C) $4/\sqrt{3}$ A (D) $4\sqrt{3}$ A
28. *Three 50 ohm resistors are connected in delta across a 400 V, 3-phase supply, if one of the resistor is disconnected, then the phase current will be*
 (A) $8/\sqrt{3}$ A (B) $8 \times \sqrt{3}$ A (C) 8 A (D) $4\sqrt{3}$ A

29. In a 3-phase, balanced load, the power consumed is given by the relation
 (A) $\sqrt{3} V_L I_L \cos \phi$ (B) $3 V_{ph} I_{ph} \cos \phi$ (C) both a and b (D) none of the above
30. When three 10 ohm resistors are connected in star across a 400 V, 3-phase supply, each resistor must have a power rating.
 (A) 5290 W (B) 2300 W (C) 4000 W (D) 4600 W
31. Three delta connected resistors absorb 30 kW when connected to a 400 V, 3-phase supply. When they are connected in star across the same supply the power absorbed will be
 (A) 60 kW (B) 90 kW (C) 20 kW (D) 10 kW
32. Three identical resistances, each of 15Ω , are connected in star across a 400 V, 3-phase supply. The value of resistance the each phase of the equivalent delta-connected load would be
 (A) 5Ω (B) 45Ω (C) 30Ω (D) 7.5Ω

Fill the following table yourself

S No.	Question (In para)	Marks	CO	BL	PO

TEST QUESTIONS

1. Explain how a sinusoidal e.m.f. is generated.
2. Derive an expression for the instantaneous value of alternating voltage varying sinusoidally.
3. Explain the terms amplitude, cycle, time period, frequency and phase difference as applied to alternating wave forms.
4. Define r.m.s. value and average value of an alternating quantity.
5. Show that the r.m.s. value of a sinusoidal a.c. voltage of amplitude V_m is $V_m/\sqrt{2}$.
6. Derive the expression for average and r.m.s. value of a sinusoidally varying quantity.
7. Show that the form factor of the sinusoidal wave form is 1.11.
8. Derive the values of form factor and peak factor of a sinusoidally varying quantity.
9. Explain how sinusoidal quantities can be represented by vectors.
10. Explain the component method for addition of alternating quantities.

11. Distinguish between
 - (i) Time period and frequency
 - (ii) Cycle and alternation
 - (iii) Peak factor and form factor
 - (iv) Average and *rms* value of an alternating current.
12. Explain why the phasor of current across an inductor lags its voltage by 90° and the phasor of current across a capacitor leads its voltage by 90° .
13. Determine phase angle relationship between alternating voltage and current in a purely inductive and a purely capacitance circuit under steady state condition.
14. Explain with mathematical expression that power consumed in a pure inductance is zero.
15. Explain with mathematical expression that power consumed in a pure capacitance is zero.
16. Show that power consumed in a pure resistive circuit is not constant but it is fluctuating.
17. Develop the expression for the power consumed in an ac single-phase *R-L* series circuit.
18. What do you mean by 'watt-less current'.
19. What do you understand by real power, reactive power and apparent power ?
20. What is power factor ? Discuss its practical importance.
21. Explain how capacitor is used to improve the pf.
22. What is power factor in *R—L—C* series circuit ; when $X_L > X_C$, $X_L < X_C$, $X_L = X_C$?
23. Define *Q*-factor for the series resonant circuit and express it in terms of the circuit parameters.
24. If the voltage of *R*-phase is represented by $v_R = V_m \sin \omega t$, write down similar expression for the voltage of *Y*-phase and *B*-phase. The phase sequence being *RBV*.
25. What are the advantages of 3-phase system over 1-phase system ?
26. What do you understand by 3-phase power supply ? Describe star and delta-connections by showing line voltages and phase voltages, line currents and phase currents.
27. Derive the relation between phase and line voltages and currents for a balanced 3-phase star-connected system.

Or

For star connected system in a 3-phase circuit prove that $V_L = \sqrt{3} V_{ph}$ and $I_L = I_{ph}$.

Or

Derive the relationship between the line and phase voltages of an alternator.

28. Write down the relationship between line voltage and line current with phase voltage and phase current in star-connected and delta-connected circuits.
29. Derive expression for power in 3-phase star and delta connections.
30. Obtain the line and phase relationships for voltages and currents for a delta-connected 3-phase power system. Also obtain the expression of total power and per phase power.
31. Develop an expression for the total power in a balanced 3-phase load.
32. Describe the basic features of a balanced 3-phase system.
33. Show that power consumption, when three identical impedances are connected in delta across a balanced 3-phase supply, is three times that when the same impedances are connected in star across the same 3-phase supply.

Fill the following table yourself

S No.	Question (In para)	Marks	CO	BL	PO

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												

ANSWERS TO MULTI-CHOICE QUESTIONS

Multi-choice questions :

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (B) | 2. (C) | 3. (C) | 4. (A) | 5. (B) |
| 6. (A) | 7. (D) | 8. (D) | 9. (C) | 10. (A) |
| 11. (A) | 12. (C) | 13. (D) | 14. (B) | 15. (D) |
| 16. (C) | 17. (D) | 18. (C) | 19. (C) | 20. (D) |
| 21. (B) | 22. (D) | 23. (C) | 24. (A) | 25. (B) |
| 26. (C) | 27. (A) | 28. (C) | 29. (C) | 30. (A) |
| 31. (D) | 32. (B) | | | |



Experiment: No 2

Measuring the steady-state and transient time-response of R-L, R-C, and R-L-C circuits to a step change in voltage (transient may be observed on a storage oscilloscope). Sinusoidal steady state response of R-L, and R-C circuits – impedance calculation and verification. Observation of phase differences between current and voltage. Resonance in R-L-C circuits.

To analyse the ac circuits, we can perform the following experiments:

1. To find voltage – current relationship in an R-L series circuit and to determine power factor of the circuit.
2. To verify series and parallel resonance in AC circuits.

Objective:

1. After performing the experiment, one understands the relation between alternating current and voltage in ac circuits. He also becomes familiar with p.f. in ac circuits.
2. To make the students familiar with RLC-series and parallel resonance.

Apparatus/Instruments/Components required:

- (i) Single-phase 230V ac supply.
- (ii) One switch S.
- (iii) One choke coil (say choke of a fluorescent tube).
- (iv) A single-phase autotransformer or variac.
- (v) One ac ammeter of range
- (vi) One wattmeter of range
- (vii) One ac voltmeters of range
- (viii) One power factor meter.
- (ix) Connecting leads etc.

Additional Apparatus/Instruments/Components required:

- (x) Signal generator to supply variable frequency to the circuit.
- (xi) An electrolytic capacitor (ac capacitor).
- (xii) A variable resistance R_h (Rheostat).

Circuit Diagram:

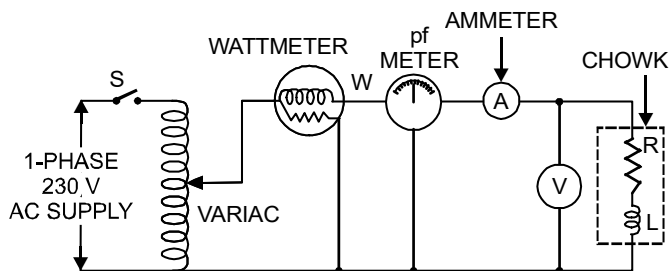


Fig.P2.1: Circuit to determine relation between V and I in R-L series circuit

Theory: Wattmeter reading = W ; Voltmeter reading = V

Ammeter reading = I ; P.f. meter reading = K

$$\text{Calculated } p.f. = \frac{W}{VI}$$

Plot a curve between V and I from the readings recorded.

Procedure:

To perform the experiment, proceed as follows:

- (i) Make the connections as per the circuit diagram shown in fig. P2.1.
- (ii) Get the connections checked by the teacher in-charge.
- (iii) Bring the variac at lowest point and switch ON the switch S .
- (iv) Increase the voltage through variac in steps and take the readings of voltmeter, ammeter, wattmeter and p.f. meter.
- (v) Plot the curve between voltage and current.
- (vi) Dismantle the circuit.

Observation Table:

S No.	Calculations				Observations
	Voltmeter reading (V) in volt	Ammeter reading (I) in ampere	Wattmeter reading (W) in Watt	p.f. meter reading (K)	Calculated $P.f. = W/VI$
1.					
2.					
3.					

Result:

1. Current increases when voltage increases. It can be shown graphically by plotting a curve between V and I .
2. Calculated p.f., it comes out to be the same as measured.
3. Observe the wave shapes at various terminals of the circuit with the help of CRO.

Circuit Diagram for RLC series resonance

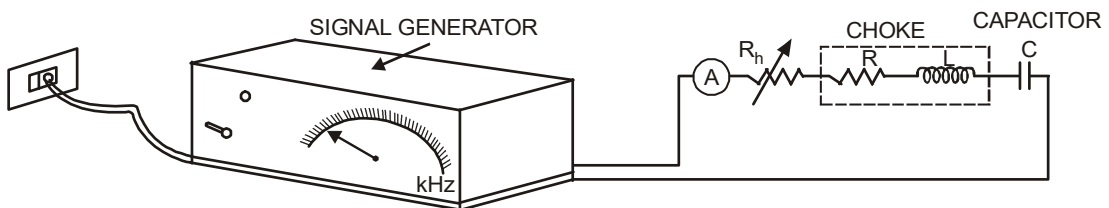


Fig. P2.2: Circuit to determine resonance in R-L-C series circuit

Theory: At resonance, $X_L = X_C$

At resonance, ; $2\pi f_r L = \frac{I}{2\pi f_r C}$ $f_r = \frac{1}{2\pi\sqrt{LC}}$

then impedance, $Z_T = R$

Current is maximum at resonance in RLC series circuit.

In RLC parallel circuits, the current will be minimum at resonance.

Procedure:

To perform this experiment, proceed as follows:

1. Make the connections as per the circuit diagram shown in fig. P2.2.
2. Get the connections checked by the teacher in-charge.
3. Bring the needle of signal generator to minimum (zero) frequency.
4. Switch-ON the supply to the signal generator.
5. Increase the frequency supplied to the circuit gradually and record the ammeter readings in the observation table.
6. Note the value of frequency on the signal generator against maximum current; It represents the resonance frequency.
7. Switch-OFF the supply bring the needle of signal generator to zero, change the value of R_h and repeat the steps 4, 5 and 6.
8. Switch-OFF the supply and change the connections as shown Fig. P2.3.
9. Repeat the experiment, by changing the frequency get minimum value of current.
10. Record the readings in the above table for parallel ac circuits.

Circuit Diagram for Parallel resonance:

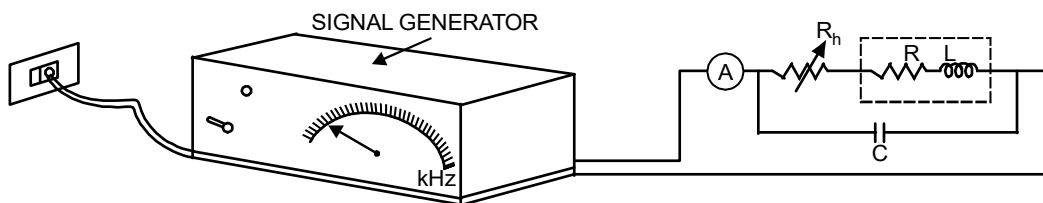


Fig. P2.3: Circuit to determine resonance in R-L-C parallel circuit

Observation Table:

SNo.	Rheostat set for R_{h1}		Rheostat set for R_{h2}		Rheostat set for R_{h3}	
	Reading of signal generator (f)	Reading of signal Ammeter (I)	Reading of signal generator (f)	Reading of signal Ammeter (I)	Reading of signal generator (f)	Reading of signal Ammeter (I)
For Series resonance circuit						
1.						
2.						
For Parallel resonance circuit						
1.						
2.						

Result:

In all the three settings, the value of resonance frequency comes out to be the same because resonance frequency is independent of circuit resistance.

Viva:

1. What do you mean by impedance of an ac circuit?
2. What do understand by resonant ac series circuit?
3. What do understand by resonant ac parallel circuit?

3

Transformers

RATIONALE

The operation of all the electrical machines such as transformers, *d.c.* machines, synchronous machines, induction motors etc. rely upon their magnetic circuits. The closed path followed by the magnetic lines of force is called a *magnetic circuit*. The operation of all the electrical devices and machines depend upon the magnetism produced by their magnetic circuits. Therefore, to obtain the required characteristics of these devices, their magnetic circuits have to be designed carefully.

Transformer is a major electrical machine or device which is used in the power system. At generating stations, it is used to step-up the voltage for economical reasons whereas, it is used to step-down the voltage at receiving stations for safety reasons (for utilisation of electrical energy voltage is reduced to 220 volt)

In this chapter, we shall focus our attention on magnetic materials, transformer and its working.

UNIT OUTCOMES

U3-O1: Unit-3 Learning Outcome-1

To know about the magnetic effect of electric current and its applications.

U3-O2: Unit-3 Learning Outcome-2

To understand how electric power is transferred from one circuit to the other.

U3-O3: Unit-3 Learning Outcome-3

To analyse the effect of load power factor on the working of transformer.

U3-O4: Unit-3 Learning Outcome-4

To analyse losses and efficiency of a transformer.

U3-O5: Unit-3 Learning Outcome-5

To know about autotransformers and 3-phase transformers.

UNIT SPECIFIC

- Study of magnetic materials and significance of B-H curve.
- Basic idea about a single-phase transformer and its construction.
- Principle of operation of transformer.
- Transformer equivalent circuit.

- Major losses which occur in transformer and voltage regulation of a transformer.
- Study of an auto-transformer.
- Basic idea about 3-phase transformers.

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES




Unit-II Outcome	EXPECTED MAPPING WITH COURSE OUTCOMES (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)		
	CO-1	CO-2	CO-3
U3-O1	1	3	--
U3-O2	1	3	--
U3-O3	1	3	--
U3-O4	1	3	--
U3-O5	--	3	--

Interesting facts

- In a typical microwave, more energy is used to power its digital clock than it uses to heat the food inside it.
- Till today, most of the world's power generation depends on coal. United States produces half of its electricity with coal. In China, over 3/4th power is generated by coal. No doubt all efforts are going on to exploit other renewable sources of electricity generation such as wind, water and the sun.

Video Resources

Videos Links for circuit

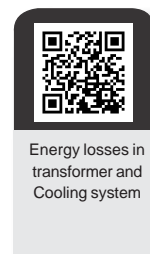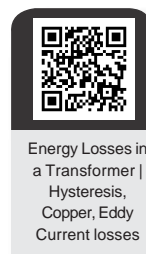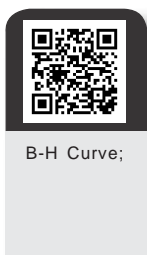

3.1. MAGNET

A **magnet** is a material or object that exhibits a magnetic field around it (see Fig. 3.1) and has the ability to attract iron (ferromagnetic) pieces. Although, magnetic field is invisible but it is responsible for the most notable property of a magnet. A magnet has a north and south pole at opposite ends.

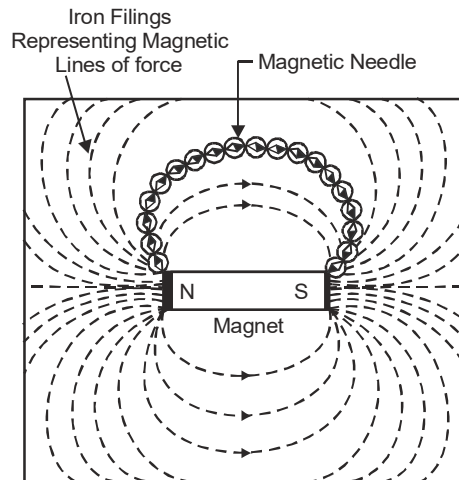


Fig. 3.1: Magnet bar with its field

A magnet contains electrons that have both uneven orbits and uneven spins. Those magnetic atoms are aligned in nice straight rows inside each domain. And those domains are also lined up all in the same direction. If a piece of metal satisfies ALL these conditions only then it become a magnet.

3.2. TYPES OF MAGNETIC MATERIALS

All materials can be classified in terms of their magnetic behavior. The two most common types of magnetism are diamagnetism and paramagnetism, which account for the magnetic properties of most of the periodic table of elements at room temperature. These elements are usually referred to as nonmagnetic, whereas those which are referred to as magnetic are actually classified as ferromagnetic.

When a material is placed within a magnetic field, the magnetic forces of the material's electrons will be affected. This effect is known as Faraday's Law of Magnetic Induction. However, materials can react quite differently to the presence of an external magnetic field. This reaction is dependent on a number of factors, such as the atomic and molecular structure of the material, and the net magnetic field associated with the atoms. The magnetic moments associated with atoms have three origins. These are the electron motion, the change in motion caused by an external magnetic field, and the spin of the electrons.

In most atoms, electrons occur in pairs. Electrons in a pair spin in opposite directions. So, when electrons are paired together, their opposite spins cause their magnetic fields to cancel each other. Therefore, no net magnetic field exists. Alternately, materials with some unpaired electrons will have a net magnetic field and will react more to an external field. Most materials can be classified as diamagnetic, paramagnetic or ferromagnetic.

Diamagnetic materials: The material which have a weak, negative susceptibility to magnetic fields are called diamagnetic materials.

These materials are slightly repelled by a magnetic field and they do not retain the magnetic properties when the external field is removed. In diamagnetic materials all the electron are paired so there is no permanent net magnetic moment per atom. Diamagnetic properties arise from the realignment of the electron paths under the influence of an external magnetic field. Most elements in the periodic table, including copper, silver, and gold, are diamagnetic.

Paramagnetic materials: The material which have a small, positive susceptibility to magnetic fields are called paramagnetic materials.

These materials are slightly attracted by a magnetic field and they do not retain the magnetic properties when the external field is removed. Paramagnetic properties are due to the presence of some unpaired electrons, and from the realignment of the electron paths caused by the external magnetic field. Paramagnetic materials include magnesium, molybdenum, lithium, and tantalum.

Ferromagnetic materials: The material which have a large, positive susceptibility to an external magnetic field are called ferromagnetic materials.

These materials exhibit a strong attraction to magnetic fields and are able to retain their magnetic properties after the external field has been removed. Ferromagnetic materials have some unpaired electrons so their atoms have a net magnetic moment. They get their strong magnetic properties due to the presence of magnetic domains. In these domains, large numbers of atom's moments (10¹² to 10¹⁵) are aligned parallel so that the magnetic force within the domain is strong. When a ferromagnetic material is in the un-magnetized state, the domains are nearly randomly organized and the net magnetic field for the part as a whole is zero. When a magnetizing force is applied, the domains become aligned to produce a strong magnetic field within the part. Iron, nickel, and cobalt are examples of ferromagnetic materials.

3.3. ELECTROMAGNETISM

The phenomenon by which magnetism is produced by the effect of electric current is called electromagnetism.

Important Terms

While studying magnetic circuits, generally, we come across the following terms :

1. **Magnetic field :** The region around a magnet where its poles exhibit a force of attraction or repulsion is called *magnetic field*.
2. **Magnetic flux (ϕ) :** The amount of magnetic lines of force set-up in a magnetic circuit is called *magnetic flux*. Its unit is weber (Wb). It is analogous to *electric current I* in electric circuit.
3. **The magnetic flux density at a point is the flux per unit area at right angles to the flux at that point.**

It is, generally, represented by letter '*B*'. Its unit is Wb/m² or Tesla, *i.e.*

$$B = \frac{\phi}{A} \text{ Wb/m}^2 \text{ or T (1 Wb/m}^2 = 1 \times 10^4 \text{ Wb/cm}^2)$$

4. **Permeability :** *The ability of a material to conduct magnetic lines of force through it is called the permeability of that material.*

It is generally represented by μ (*mu*, a Greek letter). The greater the permeability of a material, the greater is its conductivity for the magnetic lines of force and *vice-versa*. The permeability of air or vacuum is the poorest and is represented as μ_0 (where $\mu_0 = 4 \pi \times 10^{-7}$ H/m).

Relative permeability : The absolute (or actual) permeability μ of a magnetic material is much greater than absolute permeability of air μ_0 . The relative permeability of a magnetic material is given in comparison with air or vacuum.

Hence, the ratio of the permeability of material μ to the permeability of air or vacuum μ_0 is called the relative permeability μ_r of the material.

$$\text{i.e.} \quad \mu_r = \frac{\mu}{\mu_0} \quad \text{or} \quad \mu = \mu_0 \mu_r$$

Obviously, the relative permeability of air would be $\mu_0/\mu_0 = 1$. The value of relative permeability of all the non-magnetic materials is also 1. However, its value is as high as 8000 for soft iron, whereas, its value for mumetal (iron 22% and nickel 78%) is as high as 1 20 000.

- 5. Magnetic field intensity :** The force acting on a unit north pole (1 Wb) when placed at a point in the magnetic field is called the magnetic intensity of the field at that point. It is denoted by H .

In magnetic circuits, it is defined as mmf per unit length of the magnetic path. It is denoted by H , mathematically,

$$H = \frac{\text{m.m.f.}}{\text{length of magnetic path}} = \frac{NI}{l} \text{ AT / m}$$

- 6. Magnetomotive force (m.m.f.) :** The magnetic pressure which sets-up or tends to set-up magnetic flux in a magnetic circuit is called *magnetomotive force*. As per work law it may be defined as under :

The work done in moving a unit magnetic pole (1 Wb) once round the magnetic circuit is called *magnetomotive force*. In general

$$m.m.f. = NI \text{ ampere-turns (or AT)}$$

It is analogous to *e.m.f.* in an electric circuit.

- 7. Reluctance (S) :** The opposition offered to the magnetic flux by a magnetic circuit is called its *reluctance*.

It depends upon length (l), area of cross-section (a) and permeability ($\mu = \mu_0 \mu_r$) of the material that makes up the magnetic circuit. It is measured in AT/Wb.

$$\text{Reluctance, } S = \frac{l}{a \mu_0 \mu_r}$$

It is analogous to *resistance* in an electric circuit.

- 8. Permeance.** It is a measure of the ease with which flux can be set-up in the material. It is just reciprocal of reluctance of the material and is measured in Wb/AT or *henry*.

$$\text{Permeance} = \frac{1}{\text{reluctance}} = \frac{a \mu_0 \mu_r}{l} \text{ Wb/AT or H}$$

It is analogous to *conductance* in an electric circuit.

- 9. Reluctivity :** It is specific reluctance and analogous to *resistivity* in electric circuit.

3.4. MAGNETISATION OR B – H CHARACTERISTICS

The graph plotted between flux density B and magnetising force H of a material is called the *magnetisation or B – H Curve* of that material.

The general shape of the $B - H$ Curve of a magnetic material is shown in fig. 3.2 The shape of the curve is non-linear This indicates that the relative permeability ($\mu_r = B/\mu_0 H$) of a magnetic material is not constant but it varies. The value of μ_r largely depends upon the value of flux density.

The first part of magnetisation curve is OA . In OA flux density rises with the rise in magnetising force H .

The second part of the magnetisation curve is AB . In AB we see that the curve becomes steep and straight *i.e.* after point A , the rise in flux density (B) is quite high even when the magnetising force H increases slightly.

The third portion of the magnetisation curve is B onwards. The curve becomes almost a horizontal straight line. This straight lining of magnetisation curve is called magnetic saturation and point B is called point of saturation. After B the rise in flux density B is negligible. This shows that with the rise in magnetising force, flux density increases but if the magnetising force goes on increasing, then a stage will arrive when change in flux density (B) will be negligible. This condition is called magnetic saturation and after magnetic saturation, the flux density remains constant.

The $B - H$ curves of some of the common magnetic materials are shown in fig.3.3. The $B - H$ curve for a non-magnetic material is shown in fig.3.4. It is a straight line curve since $B = \mu_0 H$ or $B \propto H$ as the value of μ_0 is constant.

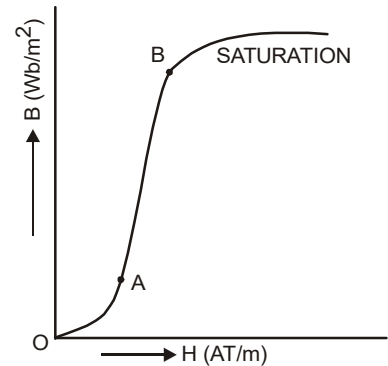


Fig. 3.2: B-H curve

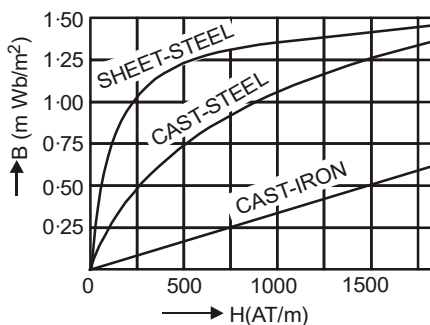


Fig. 3.3: B-H curve of various magnetic materials

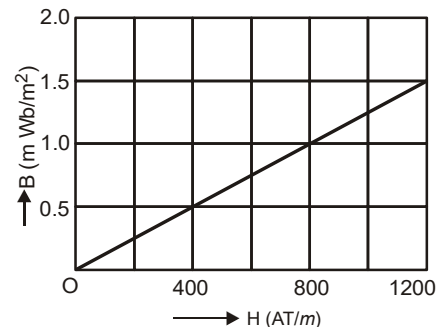


Fig.3.4: B-H Curve for non-magnetic materials

3.5. TRANSFORMER

A *transformer* is a static device which transfers a.c. electrical power from one circuit to the other at the same frequency but the voltage level is usually changed as shown in fig. 3.5(a). When the voltage is raised on the output side ($V_2 > V_1$), the transformer is called a step up transformer, whereas, the transformer in which the voltages is lowered on the output side ($V_2 < V_1$) is called a step down transformer.

Necessity

In our country, usually electrical power is generated at 11 kV. For economical reasons, a.c. power is transmitted at very high voltages (220 kV or 400 kV) over long distances, therefore, a

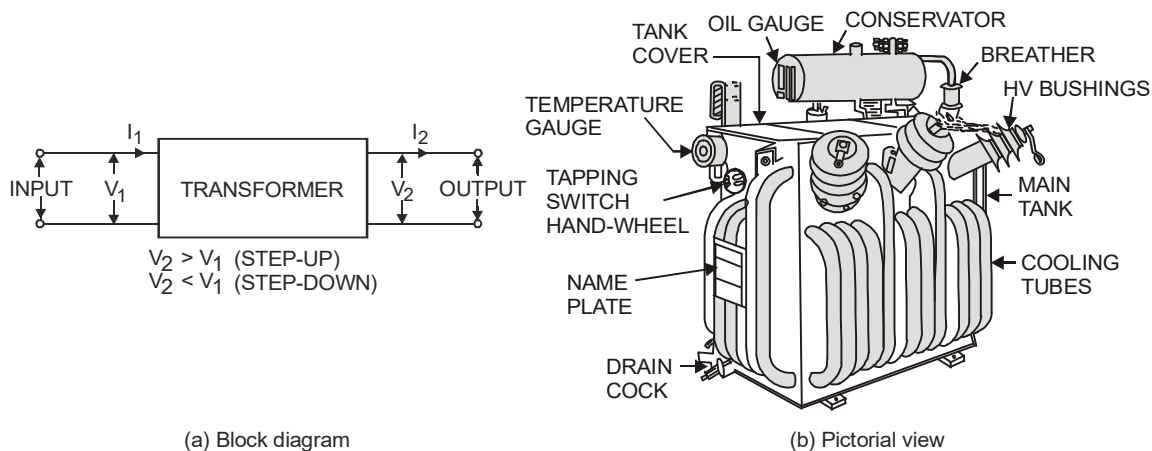


Fig. 3.5: Transformer

step up transformer is applied at the generating station. Then to feed different areas, voltages are stepped down to different levels (for economical reasons) by transformer at various substations. Ultimately for utilisation of electrical power, the voltage is stepped down to 400/230 V for safety reasons.

Thus, transformer plays an important role in the power system. The pictorial view of a power transformer is shown in fig. 3.5(b). The important accessories are labeled on it.

3.5. WORKING PRINCIPLE OF A TRANSFORMER

*The basic principle of a transformer is **electromagnetic induction***

A simple form of a transformer is shown in fig. 3.6. it essentially consists of two separate windings placed over the laminated silicon steel core. The winding to which a.c supply is connected is called primary winding and the winding to which load is connected is called a secondary winding.

When a.c. supply of voltage V_1 is connected to primary winding, an alternating flux is set up in the core. This alternating flux when links with the secondary winding, an *e.m.f.* is induced in it called mutually induced *e.m.f.* The direction of this induced *e.m.f.* is opposite to the applied voltage V_1 , according to Lenz's law as shown in fig. 3.7.

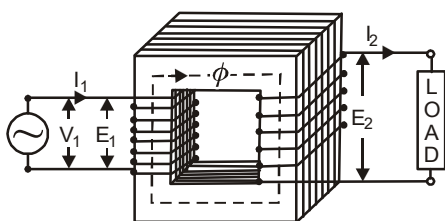


Fig. 3.6: Transformer core and windings

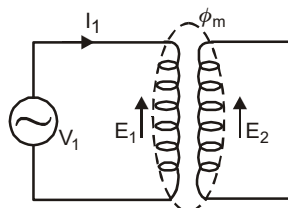


Fig. 3.7: Coupling of primary and secondary

The same alternating flux also links with the primary winding and produces self induced e.m.f. E_1 . This induced e.m.f. E_1 also acts in opposite direction to the applied voltage V_1 according to Lenz's law.

Although, there is no electrical connection between primary and secondary winding but electrical power is transferred from primary circuit to the secondary circuit through mutual flux.

The induced e.m.f. in the primary and secondary winding depends upon the rate of change of flux

linkages $\left(i.e. N \frac{d\phi}{dt} \right)$. The rate of change of flux $(d\phi / dt)$ is the same for both primary and

secondary. Therefore, the induced e.m.f. in primary is proportional to number of turns of the primary winding ($E_1 \propto N_1$) and in secondary is proportional to number of turns of the secondary winding ($E_2 \propto N_2$).

\therefore In case, $N_2 > N_1$, the transformer is step up transformer and

When $N_2 < N_1$, the transformer is step down transformer.

Turn ratio : The ratio of primary to secondary turns is called turn ratio, *i.e.*, turn ratio = N_1 / N_2 .

Transformation ratio : The ratio of secondary voltage to primary voltage is called voltage transformation ratio of the transformer. It is represented by K .

$$K = \frac{E_2}{E_1} = \frac{N_2}{N_1} \quad (\text{since } E_2 \propto N_2 \text{ and } E_1 \propto N_1)$$

3.7. TRANSFORMER CONSTRUCTION



The main elements of a transformer are ; two coils and a laminated steel core. The two coils are insulated from each other as well as from the steel core. The core of the transformer is constructed from laminations of sheet or silicon steel assembled to provide a continuous magnetic

path. At usual flux densities the silicon steel material has low hysteresis losses. The core is laminated to minimise the eddy current loss. The laminations are insulated from each other by a light coating of varnish or by an oxide layer. The thickness of laminations varies from 0.35 mm to 0.5 mm for a frequency of 50 Hz.


According to the core construction and the manner in which the primary and secondary are placed around it, the transformers are named as (i) core type transformers (ii) shell type transformers.

Core-type transformers


In a simple core type transformer the magnetic core is built up of laminations to form a rectangular frame. The laminations are cut in the form of L-shape strips as shown in fig. 3.8. In order to avoid high reluctance at the joints where laminations are butted against each other the alternate layers are stacked differently to eliminate continuous joint as shown fig.3.9.

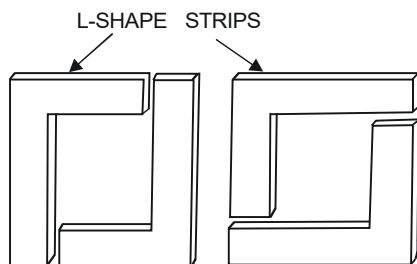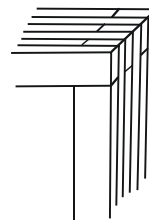**Fig. 3.8:** L-shaped laminations**Fig. 3.9:** Staggering of laminations

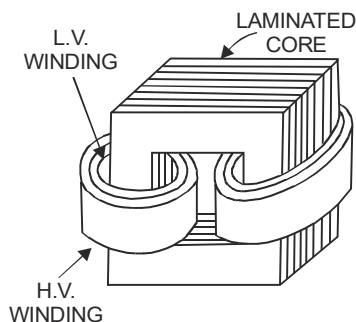In actual transformer construction, the primary and secondary windings are interleaved to reduce the leakage flux. Half of each winding is placed side by side or concentrically on either limb or leg of the core as shown in fig. 3.10(a). However, for simplicity, the two windings are shown in fig. 3.10(b) located on separate limbs of the core.



(a) Placement of windings

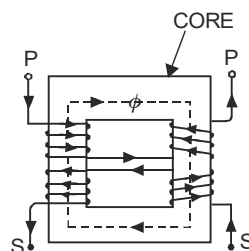

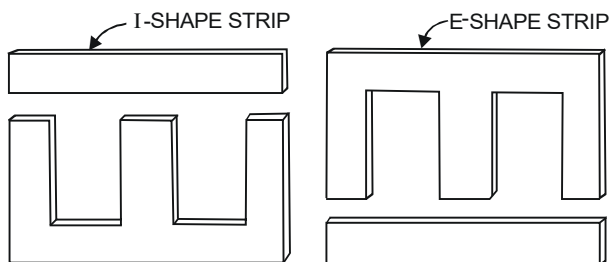
(b) Winding placed on core

Fig. 3.10: Transformer core with windings

While placing these windings, an insulation layer (bakelite former) is provided between core and lower winding and between the two windings. To reduce the insulation, low voltage winding is always placed nearer the core as shown in fig. 3.10(a). The windings used are form wound (usually cylindrical in shape) and the laminations are inserted later on.

Shell-type transformers

In case of shell type transformer, each lamination is cut in the form of long strips of E's and I's as shown in fig. 3.11. In order to avoid high reluctance at the joints where the laminations are butted against each other, the alternate layers are stacked differently to eliminate continuous joints.

**Fig. 3.11:** E&I laminations

In a shell-type transformer, the core has three limbs. The central limb carries whole of the flux, where as the side limbs carry half of the flux. Therefore, the width of the central limb is about double to that of the outer limbs.

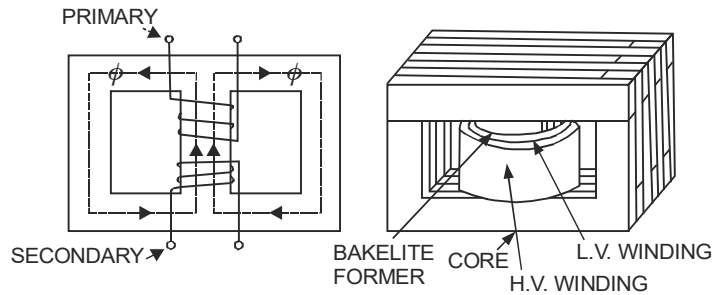


Fig. 3.12: Winding placed on core

Both the primary and secondary windings are placed on the central limb side by side or concentrically (see fig.3.12). The low voltage winding is placed nearer the core and high voltage winding is placed outside the low voltage winding to reduce the cost of insulation placed between core and low voltage winding. In this case also the windings are form wound in cylindrical shape and the core laminations are inserted later on.

The whole assembly *i.e.* core and winding is then usually placed in tank filled with transformer oil. The transformer oil provides better cooling to the transformer and acts as a dielectric medium between winding and outer tank which further reduces the size of outer tank of the transformer.

3.8. AN IDEAL TRANSFORMER

An ideal transformer is one which has no ohmic resistance and no magnetic leakage flux *i.e.* all the flux produced in the core links with primary as well as secondary. Hence, transformer has no copper losses and core losses. It means an ideal transformer consists of two purely inductive coils wound on a loss free core. Although in actual practice, it is impossible to realize such a transformer, yet for convenience, it is better to start with an ideal transformer and then extend it to an actual transformer.

In an ideal transformer there is no power loss, therefore, output must be equal to input.

$$\begin{aligned}
 &\text{i.e.} \quad E_2 I_2 \cos \phi = E_1 I_1 \cos \phi \quad \text{or} \quad E_2 I_2 = E_1 I_1 \quad \text{or} \quad \frac{E_2}{E_1} = \frac{I_1}{I_2} \\
 &\text{since} \quad E_2 \propto N_2; E_1 \propto N_1 \quad \text{and} \quad E_1 \cong V_1; E_2 \cong V_2 \\
 &\quad \quad \frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K \quad (\text{transformation ratio})
 \end{aligned}$$

Hence, primary and secondary currents are inversely proportional to their respective turns.

*The ratio of secondary turns to primary turns is called **transformation ratio** of the transformer and is represented by K.*

Behaviour and phasor diagram

Consider an ideal transformer whose secondary is open as shown in fig. 3.13(a). When its primary is connected to sinusoidal alternating voltage V_1 , a current I_m flows through it. Since the primary coil is pure inductive, the current I_m lags behind the applied voltage V_1 by 90° . This

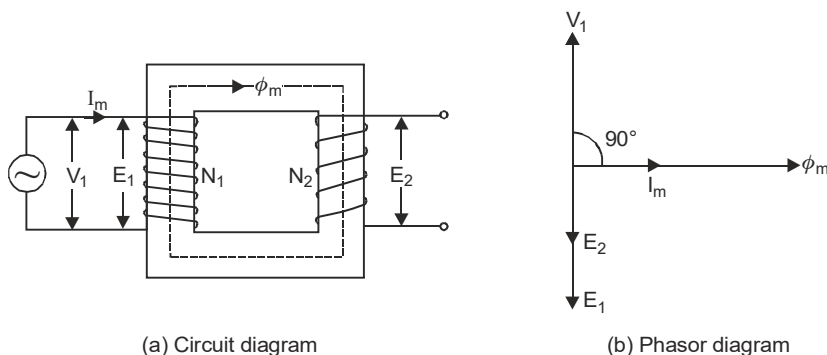


Fig. 3.13: Ideal transformer

current sets up alternating flux (or mutual flux ϕ_m) in the core and magnetises it. Hence it is called magnetising current. Flux is in phase with I_m as shown in the phasor diagram in fig. 3.13(b). The alternating flux links with both primary and secondary windings. When it links with primary, it produces self induced *e.m.f.* E_1 in opposite direction to that of applied voltage V_1 . When it links with secondary winding, it produces mutually induced *e.m.f.* E_2 in opposite direction to that of applied voltage. Both the *e.m.f.s.* E_1 and E_2 are shown in phasor diagram in fig.3.13(b).

3.9. TRANSFORMER ON D.C.

A transformer can not work on d.c supply. If a rated d.c voltage is applied across the primary, a flux of constant magnitude will be set up in the core. Hence, there will not be any self induced e.m.f. (which is only possible with the rate of change of flux linkages) in the primary winding to oppose the applied voltage. As the resistance of the primary winding is very low, the primary current will be quite high as given by the ohm's law.

$$\text{Primary current} = \frac{\text{d.c. applied voltage}}{\text{resistance of primary winding}}$$

This current is much more than the rated full load current of primary winding. Thus it will produce lot of heat ($I^2 R$) loss and burns the insulation of the primary winding, consequently the transformer will be damaged. That is why, d.c is never applied to a transformer.

3.10. E.M.F. EQUATION

When sinusoidal voltage is applied to the primary winding of a transformer, a sinusoidal flux, as shown in fig.3.14. is set up in the iron core which links with primary and secondary winding.

- Let, ϕ_m = Maximum value of flux in Wb;
 f = supply frequency in Hz (or c/s) ;
 N_1 = No. of turns in primary ;
 N_2 = No. of turns in secondary.

As shown in fig. 10, flux changes from

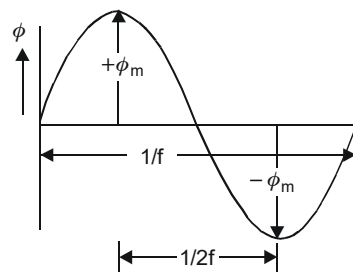


Fig. 3.14: Sinusoidal flux

+ ϕ_m to $-\phi_m$ in half a cycle i.e. $\frac{1}{2f}$ second,

Average rate of change of flux

$$= \frac{\phi_m - (-\phi_m)}{1/2f} = 4f \phi_m \text{ Wb/s}$$

Now, the rate of change of flux per turn is the average induced e.m.f. per turn in volt.

\therefore Average e.m.f. induced per turn = $4f \phi_m$ volt

For a sinusoidal wave, $\frac{\text{R.M.S. value}}{\text{Average value}} = \text{Form factor} = 1.11$

\therefore R.M.S. value of e.m.f. induced/turn, $E = 1.11 \times 4f \phi_m = 4.44f \phi_m$ volt

Since primary and secondary have N_1 and N_2 turns respectively.

\therefore R.M.S. value of e.m.f. induced in primary,

$$\begin{aligned} E_1 &= (\text{e.m.f. induced/turn}) \times \text{No. of primary turns} \\ &= 4.44 N_1 f \phi_m \text{ volt} \end{aligned} \quad \dots(i)$$

Similarly, r.m.s. value of e.m.f. induced in secondary,

$$E_2 = 4.44 N_2 f \phi_m \text{ volt} \quad \dots(ii)$$

Again, we can find the voltage ratio,

$$\frac{E_2}{E_1} = \frac{4.44 N_2 f \phi_m}{4.44 N_1 f \phi_m} \text{ or } \frac{E_2}{E_1} = \frac{N_2}{N_1} = K \text{ (transformation ratio)}$$

Equation (i) and (ii) can be written in the form of maximum flux density B_m using relation,

$$f_m = B_m \times A_i \text{ (where } A_i \text{ is iron area)}$$

$\therefore E_1 = 4.44 N_1 f B_m A_i$ volts and $E_2 = 4.44 N_2 f B_m A_i$ volt.

Example 3.1 : The primary winding of a 50 Hz single phase transformer has 500 turns and is fed from 6500 V supply. The secondary winding has 25 turns. Find peak value of flux in the core and secondary voltage.

Solution :

Here, $f = 50 \text{ Hz}$; $N_1 = 500$; $E_1 = 6500 \text{ V}$; $N_2 = 25$

Now, $E_1 = 4.44 N_1 f \phi_m$

Peak value of flux, $\phi_m = \frac{E_1}{4.44 N_1 f}$

$$= \frac{6500}{4.44 \times 500 \times 50} = 0.05856 \text{ Wb} = 58.56 \text{ mWb (Ans.)}$$

Secondary voltage,
$$E_2 = \frac{N_2}{N_1} \times E_1 = \frac{25}{500} \times 6500 = 325 \text{ V (Ans.)}$$

Example 3.2 : A 3300/300 V, 50 Hz, single-phase transformer is built on a core having an effective cross-sectional area of 130 cm^2 and 80 turns on the low voltage winding. Calculate (a) the value of the maximum flux density (b) number of turns on the high voltage winding.

Solution : Here, $E_1 = 3300 \text{ V}$; $E_2 = 300 \text{ V}$; $f = 50 \text{ Hz}$; $N_2 = 80$;

$$A = 130 \text{ cm}^2 = 130 \times 10^{-4} \text{ m}^2$$

We know, $E_2 = 4.44 N_2 f A B_m$

$$\begin{aligned} \text{Maximum value of flux density, } B_m &= \frac{E_2}{4.44 f N A} \\ &= \frac{300}{4.44 \times 50 \times 80 \times 130 \times 10^{-4}} = 1.3 \text{ T (Ans.)} \end{aligned}$$

$$\begin{aligned} \text{(b) Number of turns on high-voltage winding, } N_1 &= \frac{E_1}{E_2} \times N_2 \left(\text{since } \frac{N_2}{N_1} = \frac{E_2}{E_1} \right) \\ &= \frac{3300}{300} \times 80 = 880 \text{ (Ans.)} \end{aligned}$$

Example 3.3 : A 30 kVA transformer has 600 turns on the primary and 50 turns on the secondary winding. The primary is connected to 3300 V, 50 Hz mains, calculate (i) primary and secondary currents at full load ; (ii) The secondary e.m.f. and (iii) The maximum flux in the core. Neglect magnetic leakage, resistance of the winding and the primary no load current in relation to the full load current.

Solution : (i) At full load,
$$I_1 = \frac{30 \times 10^3}{3300} = 9.1 \text{ A (Ans.)}$$

Now
$$\frac{I_1}{I_2} = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

secondary current,
$$I_2 = \frac{N_1}{N_2} \times I_1 = \frac{600}{50} \times 9.1 = 109.1 \text{ A (Ans.)}$$

(ii) Secondary e.m.f.,
$$E_2 = \frac{N_2}{N_1} \times E_1 = \frac{50}{600} \times 3300 = 275 \text{ V (Ans.)}$$

(iii) Using relation,
$$E_1 = 4.44 N_1 f \phi_m$$

$$3300 = 4.44 \times 600 \times 50 \times \phi_m$$

or
$$\phi_m = \frac{3300}{4.44 \times 600 \times 50} = 24.77 \text{ mWb (Ans.)}$$

Example 3.4 : A single-phase, 50 Hz transformer has 35 primary and 350 secondary turns. The net cross sectional area of core is 300 cm^2 . If the primary winding is connected to a 230 V, 50 Hz supply, calculate (i) Peak value of flux density in the core ; (ii) Voltage induced in the secondary winding. Neglect losses, what is the primary current when the secondary current is 120 amperes ?

Solution : $E_1 = 4.44 N_1 f B_m A_i$
 where, $E_1 = 230 \text{ V}$; $N_1 = 35$; $f = 50 \text{ Hz}$ and $A_i = 300 \times 10^{-4} \text{ m}^2$
 or $230 = 4.44 \times 35 \times 50 \times 300 \times 10^{-4} \times B_m$
 \therefore Max flux density, $B_m = \mathbf{0.987 \text{ Tesla (or Wb/m}^2\text{) (Ans.)}$

Using relation, $K = \frac{N_2}{N_1} = \frac{E_2}{E_1} = \frac{I_1}{I_2}$
 $E_2 = \frac{N_2}{N_1} \times E_1 = \frac{350}{35} \times 230 = \mathbf{2300 \text{ V (Ans)}}$
 $I_1 = \frac{N_2}{N_1} \times I_2 = \frac{350}{35} \times 100 = \mathbf{1000 \text{ A (Ans)}}$

Example 3.5 : A 200 kVA, 3300/240 volts, 50 Hz. Single –phase transformer has 100 turns on the secondary winding. Assuming an ideal transformer, calculate (i) primary and secondary current on full load ; (ii) the maximum value of flux ; (iii) the number of primary turns.

Solution : $I_1 = \frac{200 \times 1000}{3300} = \mathbf{60.6 \text{ A (Ans.) ;}}$

$I_2 = \frac{200 \times 1000}{240} = \mathbf{833.3 \text{ A (Ans.)}}$

$E_2 = 4.44 N_2 f \phi_m$;

$240 = 4.44 \times 100 \times 50 \times \phi_m$

$\therefore \phi_m = \mathbf{10.81 \text{ m Wb (Ans.)}}$

Now, $\frac{N_1}{N_2} = \frac{E_1}{E_2}$ or $\frac{N_1}{100} = \frac{3300}{240}$ or $N_1 = \mathbf{1375 \text{ turns (Ans)}}$

PRACTICE EXERCISE

1. The primary winding of a 50 Hz single phase transformer has 480 turns and is fed from 6400 V supply. The secondary winding has 20 turns. Find peak value of flux in the core and secondary voltage. (**Ans.** 0.06Wb, 266.67 V)
2. A 3300/250 V, 50 Hz, single-phase transformer is built on a core having an effective cross-sectional area of 125 cm^2 and 71 turns on the low voltage winding. Calculate (a) the value of the maximum flux density (b) number of turns on the high voltage winding. (**Ans.** 1.269 T, 937)

3. A 25 kVA transformer has 500 turns on the primary and 40 turns on the secondary winding. The primary is connected to 3000 V, 50 Hz mains, calculate (i) primary and secondary currents at full load ; (ii) The secondary e.m.f. and (iii) The maximum flux in the core. Neglect magnetic leakage, resistance of the winding and the primary no load current in relation to the full load current. (Ans. 8.33A, 104.15 A, 240V, 0.027 Wb)
4. A single-phase, 50 Hz transformer has 30 primary and 350 secondary turns. The net cross sectional area of core is 250 cm². If the primary winding is connected to a 230 V, 50 Hz supply, calculate (i) Peak value of flux density in the core ; (ii) Voltage induced in the secondary winding. Neglect losses, what is the primary current when the secondary current is 100 amperes ? (Ans. 1.38 Tesla or Wb/m², 2683.33 V, 1166.67 A)
5. A 200 kVA, 3300/240 volts, 50 Hz. Single –phase transformer has 80 turns on the secondary winding. Assuming an ideal transformer, calculate (i) primary and secondary current on full load ; (ii) the maximum value of flux ; (iii) the number of primary turns. (Ans. 60.6A, 833.3A, 13.51mWb, 1100 turns)

3.11. PRACTICAL (ACTUAL) TRANSFORMER

An actual transformer has primary and secondary winding resistance. These windings also have inductances due to leakage fluxes which develop inductive reactance. These effects cause voltage drop in a transformer. Also there is copper loss in primary and secondary winding due to their resistances. Since alternating magnetic flux is set-up in core that causes iron or magnetic (hysteresis and eddy current) losses in it.

All these facts are further explained in articles to follow

3.12. RESISTANCE OF TRANSFORMER WINDINGS

Actual transformers have some primary and secondary winding resistance represented by R_1 and R_2 respectively. These resistances are shown external to the windings in fig.3.15.

Equivalent resistance

To make the calculations easy the resistance of the two windings can be transferred to either side. The resistance is transferred from one side to the other in such a manner that percentage voltage drop remains the same when represented on either side.

Let the primary resistance R_1 be transferred to the secondary side and the new value of this resistance be R_1' called equivalent resistance of primary referred to secondary side as shown in fig.3.16(a). I_1 and I_2 be the full load primary and secondary currents respectively.

$$\text{Then } \frac{I_2 R_1'}{V_2} \times 100 = \frac{I_1 R_1}{V_1} \times 100 \text{ (\% voltage drops)}$$

$$\text{or } R_1' = \frac{I_1}{I_2} \times \frac{V_2}{V_1} \times K^2 R_1$$

∴ Total equivalent resistance referred to secondary.

$$R_{es} = R_2 + R_1' = R_2 + K^2 R_1$$

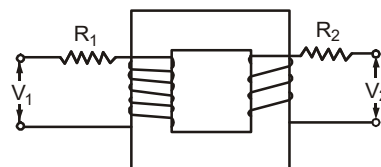


Fig. 3.15: Resistance of primary and secondary winding

Now consider resistance R_2 , when it is transferred to primary, let its new value be R_2' called equivalent resistance of secondary referred to primary as shown in fig. 3.16(c).

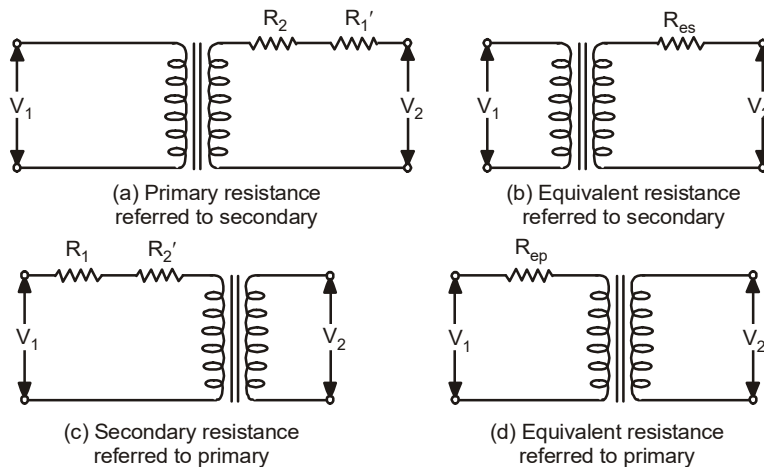


Fig. 3.16: Transfer of resistance

$$\text{Then } \frac{I_1 R_2'}{V_1} \times 100 = \frac{I_2 R_2}{V_2} \times 100 \text{ or } R_2' = \frac{I_2}{I_1} \times \frac{V_1}{V_2} \times R_2 = \frac{R_2}{K^2}$$

\therefore Total equivalent resistance referred to primary,

$$R_{ep} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

3.13. REACTANCES IN TRANSFORMER WINDINGS

In ideal transformer, it was assumed that when a.c. supply is given to the primary winding of a transformer, an alternating flux is set up in the core and whole of this flux links with both the primary and secondary windings. However, in an actual transformer, both the windings produce some flux that links only with the winding that produces it.

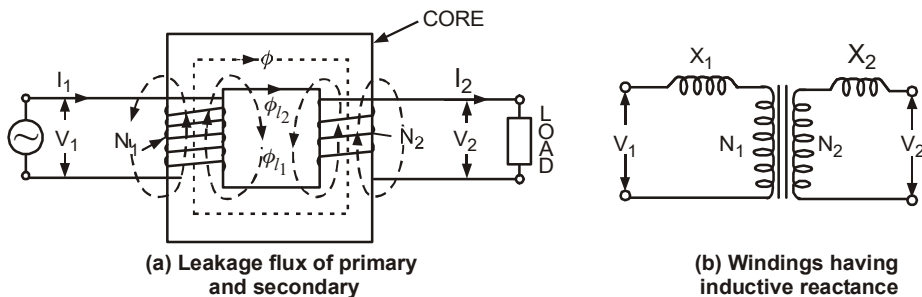


Fig.3.17: Inductive reactance of primary and secondary

*The flux that links with both the windings of the transformer is called **mutual flux** and the flux which links only with one winding of the transformer and not to the other is called **leakage flux**.*

The primary ampere turns produce some flux ϕ_{l_1} which is set up in air and links only with primary winding, as shown in fig.3.17(a), is called *primary leakage flux*.

Similarly, secondary ampere turns produce some flux ϕ_{l_2} which is set up in air and links only with secondary winding is called *secondary leakage flux*.

The primary leakage flux ϕ_{l_1} is proportional to the primary current I_1 and secondary leakage flux ϕ_{l_2} is proportional to secondary current I_2 . The primary leakage flux ϕ_{l_1} produces self inductance L_1 ($\equiv N_1 \phi_{l_1} / I_1$) which in turn produces leakage reactance $X_1 (= 2\pi f L_1)$. Similarly, secondary leakage flux ϕ_{l_2} produces leakage reactance $X_2 (= 2\pi f L_2)$. The leakage reactance (inductive) have been shown external to the windings in fig. 3.17(b).

Equivalent reactance

To make the calculations easy the reactances of the two winding can be transferred to any one side. The reactance from one side to the other is transferred in such a manner that percentage voltage drop remains the same when represented on either side.

Let the primary reactance X_1 be transferred to the secondary and the new value of this reactance is X_1' called equivalent reactance of primary referred to secondary, as shown in fig.3.18(a).

$$\text{Then } \frac{I_2 X_1'}{V_2} \times 100 = \frac{I_1 X_1}{V_1} \times 100 \quad (\% \text{ voltage drops})$$

$$\text{or } X_1' = \frac{I_1}{I_2} \times \frac{V_2}{V_1} \times X_1 = K^2 X_1$$

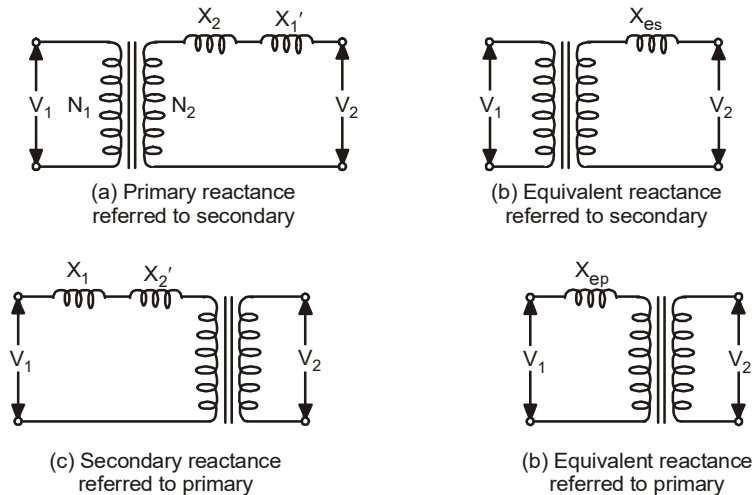


Fig. 3.18: Transfer of reactance

\therefore Total equivalent reactance referred to secondary.

$$X_{es} = X_2 + X_1' = X_2 + K^2 X_1$$

Now, let us consider secondary reactance X_2 when it is transferred to primary side its new value is X_2' called equivalent reactance of secondary referred to primary, as shown in fig.3.18(c).

Then
$$\frac{I_1 X_2'}{V_1} \times 100 = \frac{I_2 X_2}{V_2} \times 100$$

or
$$X_2' = \frac{I_2}{I_1} \times \frac{V_1}{V_2} \times X_2 = \frac{X_2}{K^2}$$

∴ Total equivalent reactance referred to primary.

$$X_{ep} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

Example 3.6. A 2000/200 volt transformer has a primary resistance 2.5 ohm and reactance 4.5 ohm, the secondary resistance 0.025 ohm and reactance 0.045 ohm. Determine total resistance and reactance referred to primary side.

Solution : Primary resistance, $R_1 = 2.5$ ohm

Primary reactance, $X_1 = 4.5$ ohm

Secondary resistance, $R_2 = 0.025$ ohm

Secondary reactance, $X_2 = 0.045$ ohm

$$\text{Transformation ratio, } K = \frac{V_2}{V_1} = \frac{200}{2000} = 0.1$$

Total resistance referred to primary side,

$$R_{ep} = R_1 + \frac{R_2}{K^2} = 2.5 + \frac{0.025}{(0.1)^2} = 5 \Omega \text{ (Ans.)}$$

Total reactance referred to primary side,

$$X_{ep} = X_1 + \frac{X_2}{K^2} = 4.5 + \frac{0.045}{(0.1)^2} = 9 \Omega \text{ (Ans.)}$$

Example 3.7. A single phase transformer having voltage ratio 2500/250V (primary to secondary) has a primary resistance and reactance 2 ohm and 4.5 ohm respectively. The corresponding secondary values are 0.025 and 0.04 ohm. Determine the total resistance and reactance referred to secondary side. Also calculate the impedance of transformer referred to secondary side.

Solution :

Here, $R_1 = 2 \Omega$; $X_1 = 4.5 \Omega$; $R_2 = 0.025 \Omega$; $X_2 = 0.04 \Omega$

$$\text{Transformation ratio, } K = \frac{V_2}{V_1} = \frac{250}{2500} = 0.1$$

Total resistance referred to secondary side,

$$\begin{aligned} R_{es} &= R_2 + R_1 \phi = R_2 + R_1 \times K^2 \\ &= 0.025 + 2 \times (0.1)^2 = 0.045 \Omega \text{ (Ans.)} \end{aligned}$$

Total reactance referred to secondary side,

$$X_{es} = X_2 + X_1 \phi = X_2 + X_1 \times K^2$$

$$= 0.04 + 4.5 \times (0.1)^2 = 0.085 \, \Omega \text{ (Ans.)}$$

Impedance of transformer referred to secondary side,

$$\begin{aligned} Z_{es} &= \sqrt{(R_{es})^2 + (X_{es})^2} = \sqrt{(0.045)^2 + (0.085)^2} \\ &= 0.096 \, \Omega \text{ (Ans.)} \end{aligned}$$

PRACTICE EXERCISE

1. A 2000/200 volt transformer has a primary resistance 2.3 ohm and reactance 4.2 ohm, the secondary resistance 0.025 ohm and reactance 0.04 ohm. Determine total resistance and reactance referred to primary side. (Ans. 4.8 Ω , 8.2 Ω)
2. A single phase transformer having voltage ratio 2500/250V (primary to secondary) has a primary resistance and reactance 1.8 ohm and 4.2 ohm respectively. The corresponding secondary values are 0.02 and 0.045 ohm. Determine the total resistance and reactance referred to secondary side. Also calculate the impedance of transformer referred to secondary side. (Ans. 0.038 Ω , 0.087 Ω , 0.095 Ω .)

3.14. CIRCUIT DIAGRAM OF AN ACTUAL TRANSFORMER

An actual transformer has (i) Primary and secondary resistances R_1 and R_2 , (ii) primary and secondary leakage reactances X_1 and X_2 and (iii) iron and copper losses. The equivalent circuit of an actual transformer is shown in fig. 3.19.

Primary impedance,

$$\overline{Z}_1 = R_1 + j X_1$$

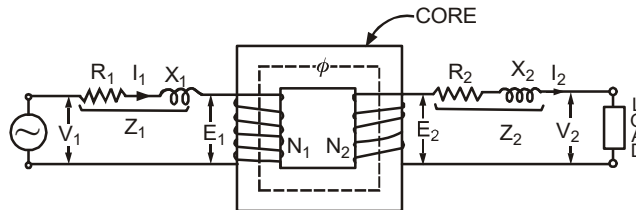


Fig. 3.19: Complete circuit diagram of a real transformer

Supply voltage is V_1 . The resistance and leakage reactance of primary winding are responsible for some voltage drop in primary winding.

$$\therefore \overline{V}_1 = \overline{E}_1 + \overline{I}_1 (R_1 + j X_1) = \overline{E}_1 + \overline{I}_1 \overline{Z}_1$$

Secondary impedance, $\overline{Z}_2 = R_2 + j X_2$

Similarly, the resistance and leakage reactance of secondary winding are responsible for some voltage drop in secondary winding. Hence,

$$\overline{V}_2 = \overline{E}_2 - \overline{I}_2 (R_2 + j X_2) = \overline{E}_2 - \overline{I}_2 \overline{Z}_2$$

3.15. SIMPLIFIED EQUIVALENT CIRCUIT

The simplified equivalent circuit of a transformer is drawn by representing all the parameters of the transformer either on the secondary or on the primary side. The no load current I_0 is neglected as its value is very small as compared to full load current, therefore, $I_1' = I_1$

(i) Equivalent circuit when all the quantities are referred to secondary.

The primary resistance when referred to secondary side, its value is $R_1' = K^2 R_1$ and the total or equivalent resistance of transformer referred to secondary, $R_{es} = R_2 + R_1'$. Similarly, the primary

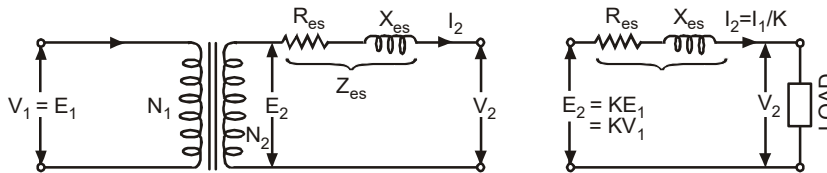


Fig. 3.20: Equivalent circuit of a transformer when all the quantities are referred to secondary side

reactance when referred to secondary side, its value is $X_1' = K^2 X_1$ and the total or equivalent reactance of transformer referred to secondary, $X_{es} = X_2 + X_1'$. All the quantities when referred to the secondary side are shown in fig. 3.20.

Total or equivalent impedance referred to secondary side,

$$Z_{es} = R_{es} + j X_{es}$$

There is some voltage drop in resistance and reactance of transformer referred to secondary. Hence,

$$\overline{V_2} = \overline{E_2} - \overline{I_2} (R_{es} + j X_{es}) = \overline{E_2} - \overline{I_2} \overline{Z_{es}}$$

3.16. EXPRESSION FOR NO LOAD SECONDARY VOLTAGE

For a loaded transformer when all the quantities are referred to secondary side, its phasor diagram can be drawn as shown in fig.3.21.

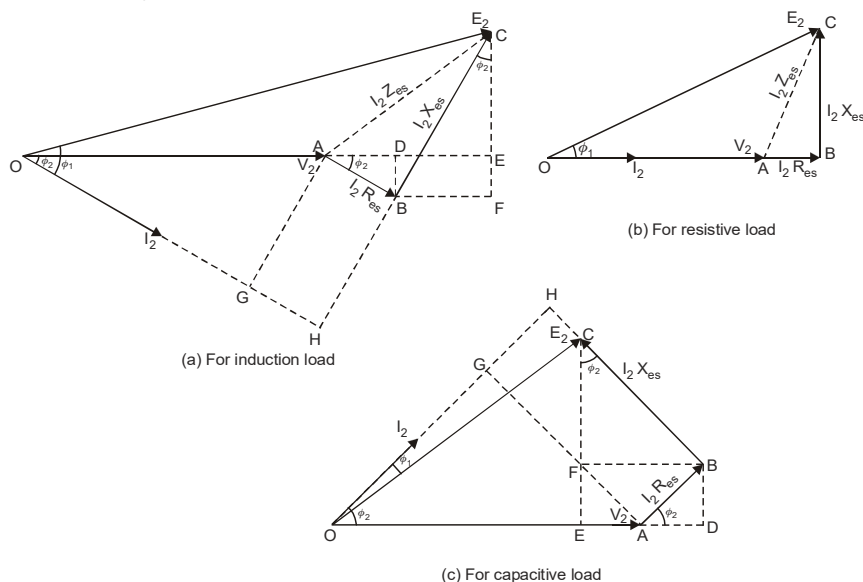


Fig. 3.21: Phasor diagrams

Complete the phasor diagram as shown in fig. 3.21. From the phasor diagram we can derive the approximate as well as exact expressions for no load secondary voltage.

(i) Approximate expression ;

(a) for lagging p.f. (inductive load),

Consider right angle triangle OEC [see fig 3.21(a)].

$$OC \cong OE = OA + AD + DE = OA + AD + BF$$

or $E_2 = V_2 + I_2 R_{es} \cos \phi_2 + I_2 X_{es} \sin \phi_2$

(b) for unity p.f. (resistive load),

Consider rt. \angle triangle OBC [see fig. 3.21(b)]

$$OC \cong OB = OA + AB ; E_2 = V_2 + I_2 R_{es}$$

(c) for leading p.f. (capacitive load),

Consider rt. \angle triangle OEC [see fig.3.21(c)]

$$OC \cong OE = OA + AD - DE = OA + AD - BF$$

or $E_2 = V_2 + I_2 R_{es} \cos \phi_2 - I_2 X_{es} \sin \phi_2$

(ii) Exact expression :

(a) for a lagging p.f. (inductive load),

Consider rt. \angle triangle OHC [see fig. 3.21(a)]

$$\begin{aligned} OC &= \sqrt{(OH)^2 + (HC)^2} = \sqrt{(OG + GH)^2 + (HB + BC)^2} \\ &= \sqrt{(OG + AB)^2 + (GA + BC)^2} \end{aligned}$$

or $E_2 = \sqrt{(V_2 \cos \phi_2 + I_2 R_{es})^2 + (V_2 \sin \phi_2 + I_2 X_{es})^2}$

$$\text{Primary p.f., } \cos \phi_1 = \frac{OH}{OC} = \frac{OG + GH}{OC} = \frac{OG + AB}{OC} = \frac{V_2 \cos \phi_2 + I_2 R_{es}}{E_2}$$

(b) for unity p.f., (resistive load)

Consider rt. \angle triangle OBC [see fig. 3.21(b)]

$$OC = \sqrt{(OB)^2 + (BC)^2}$$

or $OC = \sqrt{(OA + AB)^2 + (BC)^2}$

$$\text{or } E_2 = \sqrt{(V_2 + I_2 R_{es})^2 + (I_2 X_{es})^2}$$

$$\text{Primary p.f., } \cos \phi_1 = \frac{OB}{OC} = \frac{OA + AB}{OC} = \frac{V_2 + I_2 R_{es}}{E_2}$$

(c) for leading p.f. (capacitive load),

Consider rt. \angle triangle OHC [see fig.3.21(c)]

$$\begin{aligned} OC &= \sqrt{(OH)^2 + (HC)^2} = \sqrt{(OG + GH)^2 + (HB - BC)^2} \\ &= \sqrt{(OG + AB)^2 + (GA - BC)^2} \end{aligned}$$

$$\text{or } E_2 = \sqrt{(V_2 \cos \phi_2 + I_2 R_{es})^2 + (V_2 \sin \phi_2 - I_2 X_{es})^2}$$

$$\text{Primary p.f., } \cos \phi_1 = \frac{HC}{OC} = \frac{OG + GH}{OC} = \frac{OG + AB}{OC} = \frac{V_2 \cos \phi_2 + I_2 R_{es}}{E_2}$$

3.17. VOLTAGE REGULATION

When a transformer is loaded, with a constant supply voltage, the terminal voltage changes due to voltage drop in the internal parameters of the transformer *i.e.* primary and secondary resistances and inductive reactances. The internal voltage drop also depends upon the load and its power factor. The algebraic difference between the no-load and full-load terminal voltage is measured in terms of voltage regulation.

*At a constant supply voltage, the change in secondary terminal voltage from no-load to full-load with respect to no load voltage is called **voltage regulation** of the transformer.*

Let, E_2 = Secondary terminal voltage at no-load.

V_2 = Secondary terminal voltage at full-load.

$$\text{Then, voltage regulation} = \frac{E_2 - V_2}{E_2} \text{ (per unit)}$$

$$\text{In the form of percentage, \% Reg} = \frac{E_2 - V_2}{E_2} \times 100$$

When all the quantities are referred to the primary side of the transformer ;

$$\% \text{ Reg} = \frac{V_1 - E_1}{V_1} \times 100$$

APPROXIMATE EXPRESSION FOR VOLTAGE REGULATION

The approximate expression for the no-load secondary voltage is derived in article 15.

$$(i) \text{ For inductive load : } E_2 = V_2 + I_2 R_{es} \cos \phi_2 + I_2 X_{es} \sin \phi_2$$

or $E_2 - V_2 = I_2 R_{es} \cos \phi_2 + I_2 X_{es} \sin \phi_2$

or $\frac{E_2 - V_2}{E_2} \times 100 = \frac{I_2 R_{es}}{E_2} \times 100 \cos \phi_2 + \frac{I_2 X_{es}}{E_2} \times 100 \sin \phi_2$

where, $\frac{I_2 X_{es}}{E_2} \times 100 = \text{percentage resistance drop and}$

$\frac{I_2 R_{es}}{E_2} \times 100 = \text{percentage reactance drop}$

$\therefore \% \text{ Reg} = \% \text{ resistance drop} \times \cos \phi_2 + \% \text{ reactance drop} \times \sin \phi_2$

Similarly

(ii) For resistive load : $\% \text{ Reg} = \% \text{ resistance drop}$

(iii) For capacitive load :

$\therefore \% \text{ Reg} = \% \text{ resistance drop} \times \cos \phi_2 - \% \text{ reactance drop} \times \sin \phi_2$

Example 3.8 : A single phase transformer with a ratio 1 : 2 has primary resistance of 0.25 ohm and reactance of 0.5 ohm and the corresponding values for the secondary are 0.8 ohm and 1.8 ohm respectively. Determine the no load secondary terminal voltage of the transformer if it is delivering 10 A and 400 V at 0.8 p.f. lagging.

Solution : Primary resistance, $R_1 = 0.25 \Omega$

Primary reactance, $X_1 = 0.5 \Omega$

Secondary resistance, $R_2 = 0.8 \Omega$

Secondary reactance, $X_2 = 1.8 \Omega$

Secondary current, $I_2 = 10 \text{ A}$

Load p.f., $\cos \phi_2 = 0.8 \text{ lagging}$

Secondary terminal voltage at load, $V_2 = 400 \text{ V}$

Transformation ratio, $K = \frac{2}{1} = 2$

Primary resistance referred to secondary $R'_1 = K^2 R_1 = 2 \times 2 \times 0.25 = 1.0 \Omega$

Primary reactance referred to secondary $X'_1 = K^2 X_1 = 2 \times 2 \times 0.5 = 2.0 \Omega$

Equivalent resistance referred to secondary $R_{es} = R_2 + R'_1 = 0.8 + 1.0 = 1.8 \Omega$

Equivalent reactance referred to secondary $X_{es} = X_2 + X'_1 = 1.8 + 2.0 = 3.8 \Omega$

Load p.f., $\cos \phi_2 = 0.8 \therefore \sin \phi_2 = \sin \cos^{-1} 0.8 = 0.6$

Secondary terminal voltage at no load,
$$\begin{aligned} E_2 &= \sqrt{(V_2 \cos \phi_2 + I_2 R_{es})^2 + (V_2 \sin \phi_2 + I_2 X_{es})^2} \\ &= \sqrt{(400 \times 0.8 + 10 \times 1.8)^2 + (400 \times 0.6 + 10 \times 3.8)^2} \\ &= \sqrt{(338)^2 + (278)^2} = 437.64 \text{ V (Ans.)} \end{aligned}$$

Example 3.9 : A single phase transformer with a ratio 5 : 1 has primary resistance of 0.4 ohm and reactance of 1.2 ohm and the secondary resistance of 0.01 ohm and reactance of 0.04 ohm. Determine the percentage regulation when delivering 125 A at 600 V at (i) 0.8 p.f. lagging (ii) 0.8 p.f. leading.

Solution : Data given, $R_1 = 0.4 \Omega$; $X_1 = 1.2 \Omega$; $R_2 = 0.01 \Omega$;

$$X_2 = 0.04 \Omega ; I_2 = 125 \text{ A and } V_2 = 600 \text{ V}$$

Transformation ratio, $K = 1/5 = 0.2$

Now,

$$R_1' = K^2 R_1 = (0.2)^2 \times 0.4 = 0.016 \Omega ;$$

$$R_{es} = R_2 + R_1' = 0.01 + 0.016 = 0.026 \Omega$$

$$X_1' = K^2 X_1 = (0.2)^2 \times 1.2 = 0.048 \Omega$$

$$X_{es} = X_2 + X_1' = 0.04 + 0.048 = 0.088 \Omega$$

(i) For p.f. $\cos \phi_2 = 0.8$ lag ; $\sin \phi_2 = \sin \cos^{-1} 0.8 = 0.6$

Secondary induced voltage,

$$\begin{aligned} E_2 &= V_2 + I_2 R_{es} \cos \phi_2 + I_2 X_{es} \sin \phi_2 \\ &= 600 + 125 \times 0.026 \times 0.8 + 125 \times 0.088 \times 0.6 \\ &= 600 + 2.6 + 6.6 = 609.2 \text{ V} \end{aligned}$$

$$\% \text{ Reg} = \frac{E_2 - V_2}{E_2} \times 100 = \frac{609.2 - 600}{609.2} \times 100 = \mathbf{1.51 \% (Ans.)}$$

(ii) For p.f., $\cos \phi_2 = 0.8$ leading ; $\sin \phi_2 = 0.6$

Secondary induced voltage,

$$\begin{aligned} E_2 &= V_2 + I_2 R_{es} \cos \phi_2 - I_2 X_{es} \sin \phi_2 \\ &= 600 + 125 \times 0.026 \times 0.8 - 125 \times 0.088 \times 0.6 \\ &= 600 + 2.6 - 6.6 = 596 \text{ V} \end{aligned}$$

$$\% \text{ Reg} = \frac{E_2 - V_2}{E_2} \times 100 = \frac{596 - 600}{596} \times 100 = \mathbf{-0.67 \% (Ans.)}$$

Example 3.10 : Calculate the regulation of transformer in which ohmic loss is 1% of the output and reactance drop 5% of the voltage when the power factor is (i) 0.8 lagging (ii) 0.8 leading (iii) unity.

Solution : Ohmic loss or resistance drop = 1% ; Reactance drop = 5%

(i) When p.f., $\cos \phi_2 = 0.8$ lagging ; $\sin \phi_2 = \sin \cos^{-1} 0.8 = 0.6$

$$\begin{aligned} \% \text{ Reg} &= \% \text{ resistance drop} \times \cos \phi_2 + \% \text{ reactance drop} \times \sin \phi_2 \\ &= 1 \times 0.8 + 5 \times 0.6 = \mathbf{3.8\% (Ans.)} \end{aligned}$$

(ii) When p.f., $\cos \phi_2 = 0.8$ leading ; $\sin \phi_2 = \sin \cos^{-1} 0.8 = 0.6$

$$\begin{aligned} \% \text{ Reg} &= \% \text{ resistance drop} \times \cos \phi_2 - \% \text{ reactance drop} \times \sin \phi_2 \\ &= 1 \times 0.8 - 5 \times 0.6 = \mathbf{-2.2 \% (Ans.)} \end{aligned}$$

(iii) When p.f. is unity $\% \text{ Reg} = \% \text{ resistance drop} = \mathbf{1\% (Ans.)}$

PRACTICE EXERCISE

1. A 10 kVA, 1-phase transformer with 2000/400 V at no load, has resistance and leakage reactance of primary winding 5.5 W and 12 W respectively, the corresponding values of secondary winding being 0.5 W and 0.45 W. Determine the value of secondary voltage at full load, 0.8 pf lagging, when the primary applied voltage is 2000 V. (Ans. 377.65V)
2. A 10 kVA, 2000/400 V, single phase transformer has resistance and leakage reactance as follows :–
 Primary winding : Resistance = 5.5 ohms, Reactance = 12 ohms
 Secondary winding : Resistance = 0.2 ohm, Reactance = 0.45 ohm
 Determine the value of the secondary voltage at full load, 0.8 p.f. leading, when the primary supply voltage is 2000 V. (Ans. 405.55V)
3. The primary and secondary windings of a 40 kVA, 6600/250 V single phase transformer have resistance of 10 ohm and 0.02 ohm respectively. The total leakage reactance is 35 ohm as referred to primary winding. Find full load regulation of at a p.f. 0.8 lagging. (Ans, 3.56%)

3.18. LOSSES IN A TRANSFORMER

The losses which occur in an actual transformer are :

- (i) Core or iron losses (ii) Copper losses
- (i) **Core or iron losses** : When ac supply is given to the primary winding of a transformer an alternating flux is set up in the core, therefore, hysteresis and eddy current losses occur in the magnetic core.
 - (a) **Hysteresis loss** : When the magnetic material is subjected to reversal of flux, power is required for the continuous reversal of molecular magnets. This power is dissipated in the form of heat and is known as hysteresis loss ($P_h = K_h V f B_m^{1.6}$). This loss can be minimized by using silicon steel material for the construction of core.
 - (b) **Eddy current loss** : Since flux in the core of a transformer is alternating, it links with the magnetic material of the core itself also. This induces an e.m.f. in the core and circulates eddy currents. Power is required to maintain these eddy currents. This power is dissipated in the form of heat and is known as eddy current loss ($P_e = K_e V f^2 t^2 B_m^2$). This loss can be minimised by making the core of thin laminations.

It is already seen in article–8 that the flux set up in the core of the transformer remains constant from no load to full load. Hence, iron loss are independent of the load and are known as constant losses.

- (ii) **Copper losses** : Copper losses occur in both the primary and secondary windings due to their ohmic resistance. If I_1 , I_2 are the primary and secondary currents and R_1 , R_2 are the primary and secondary resistances respectively.

$$\text{Then, total copper losses} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{ep} = I_2^2 R_{es}$$

The currents in the primary and secondary winding vary according to the load, therefore, these losses vary according to the load and are known as variable losses.

Example 3.11. A 50 kVA, 2000/200 V, single phase, 50 Hz transformer has primary resistance of 3.5 ohm and reactance of 4.5 ohm. The secondary resistance and reactance are 0.015 ohm and 0.02 ohm respectively. Find (i) equivalent resistance, reactance and impedance referred to the primary side (ii) Total copper losses in the transformer.

Solution : Transformer rating = 50 kVA, 2000/200 V, 1- ϕ , 50 Hz

Primary resistance, $R_1 = 3.5 \Omega$

Primary reactance, $X_1 = 4.5 \Omega$

Secondary resistance, $R_2 = 0.015 \Omega$

Secondary reactance, $X_2 = 0.02 \Omega$

(i) Transformation ratio, $K = \frac{V_2}{V_1} = \frac{200}{2000} = 0.1$

Equivalent resistance referred to primary side,

$$\begin{aligned} R_{ep} &= R_1 + R_2' \\ &= R_1 + \frac{R_2}{K^2} = 3.5 + \frac{0.015}{(0.1)^2} = 3.5 + 1.5 = 5 \Omega \text{ (Ans.)} \end{aligned}$$

Equivalent reactance referred to primary side,

$$\begin{aligned} X_{ep} &= X_1 + X_2' \\ &= X_1 + \frac{X_2}{K^2} = 4.5 + \frac{0.02}{(0.1)^2} = 4.5 + 2.0 = 6.5 \Omega \text{ (Ans.)} \end{aligned}$$

Equivalent impedance referred to primary side,

$$Z_{ep} = \sqrt{R_{ep}^2 + X_{ep}^2} = \sqrt{(5)^2 + (6.5)^2} = 8.2 \Omega \text{ (Ans.)}$$

(ii) Primary rated current, $I_1 = \frac{50 \times 1000}{2000} = 25 \text{ A}$

Full-load copper losses in transformer,

$$P_c = I_1^2 R_{ep} = (25)^2 \times 5 = 3125 \text{ W (Ans.)}$$

3.19. EFFICIENCY OF A TRANSFORMER

The efficiency of a transformer is defined as the ratio of output to the input power, the two being measured in same units (either in watts or in kW).

$$\text{Transformer efficiency, } \eta = \frac{\text{output power}}{\text{input power}} = \frac{\text{output power}}{\text{output power} + \text{losses}}$$

$$\text{or } \eta = \frac{\text{output power}}{\text{output power} + \text{iron losses} + \text{copper losses}} = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_i + P_c}$$

where, V_2 = Secondary terminal voltage

I_2 = Full load secondary current

$\cos \phi_2 = p.f.$ of the load

$P_i =$ Iron losses = Hysteresis losses + eddy current losses (constant losses)

$P_c =$ Full load copper losses = $I_2^2 R_{es}$ (variable losses)

If x is the fraction of the full load, the efficiency of the transformer at this fraction is given by the relation ;

$$\eta_x = \frac{x \times \text{output at full load}}{x \times \text{output at full load} + P_i + x^2 P_c} = \frac{x V_2 I_2 \cos \phi_2}{x V_2 I_2 \cos \phi_2 + P_i + x^2 I_2^2 R_{es}}$$

The copper losses vary as the square of the fraction of the load.

3.20. CONDITION FOR MAXIMUM EFFICIENCY

The efficiency of a transformer at a given load and p.f. is expressed by the relation

$$\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_i + I_2^2 R_{es}} = \frac{V_2 \cos \phi_2}{V_2 \cos \phi_2 + P_i / I_2 + I_2 R_{es}}$$

The terminal voltage V_2 is approximately constant. Thus for a given p.f., efficiency depends upon the load current I_2 . In expression (i), the numerator is constant and the efficiency will be maximum if denominator is minimum. Thus the maximum condition is obtained by differentiating the quantity in the denominator w.r.t. the variables I_2 and equating that to zero *i.e.*

$$\frac{d}{d I_2} \left(V_2 \cos \phi_2 + \frac{P_i}{I_2} + I_2 R_{es} \right) = 0 \quad \text{or} \quad 0 - \frac{P_i}{I_2^2} + R_{es} = 0$$

or
$$I_2^2 R_{es} = P_i$$

i.e. **Copper losses = Iron losses**

Thus, the efficiency of a transformer will be maximum when copper (or variable) losses are equal to iron (or constant) losses.

$$\therefore \eta_{max} = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + 2 P_i} \quad [\text{since } P_c = P_i]$$

From equation (ii), the value of output current I_2 at which the efficiency of the transformer will be maximum is given by ;

$$I_2 = \sqrt{\frac{P_i}{R_{es}}}$$

If x is the fraction of full load kVA at which the efficiency of the transformer is maximum.

Then, copper losses = $x^2 P_c$ (where P_c is the full load Cu losses)

Iron losses = P_i

For maximum efficiency, $x^2 P_c = P_i$; $x = \sqrt{\frac{P_i}{P_c}}$

\therefore Output kVA corresponding to maximum efficiency

$$\begin{aligned}
 &= x \times \text{full load kVA} = \text{full load kVA} \times \sqrt{\frac{P_i}{P_c}} \\
 &= \text{full load kVA} \times \sqrt{\frac{\text{iron losses}}{\text{copper losses at full load}}}
 \end{aligned}$$

Example 3.12 : In a 25 kVA, 2000/200 V power transformer the iron and full load copper losses are 350 W and 400 W respectively. Calculate the efficiency at unity power factor at (i) full load and (ii) half load.

Solution :
$$\eta_x = \frac{x \text{ kVA} \times 1000 \times \cos \phi}{x \text{ kVA} \times 1000 \times \cos \phi + P_i + x^2 P_c}$$

where, $\cos \phi = 1$; $P_i = 350 \text{ W}$; $P_c = 400 \text{ W}$

(i) At full-load $x = 1$

$$\therefore \eta = \frac{1 \times 25 \times 1000 \times 1}{1 \times 25 \times 1000 \times 1 + 350 + 1 \times 1 \times 400} \times 100 = 97.087 \% \text{ (Ans)}$$

(ii) At half-load ; $x = 0.5$

$$\therefore \eta = \frac{0.5 \times 25 \times 1000 \times 1}{0.5 \times 25 \times 1000 \times 1 + 350 + (0.5)^2 \times 400} \times 100 = 96.525 \% \text{ (Ans)}$$

Example 3.13 : At full load current, the iron and copper losses in a 100 kVA transformer are each equal to 2.5 kW. Find the efficiency of the transformer at a load of 75 kVA and 0.8 power factor lagging.

Solution : Efficiency of a transformer at any fraction x of full load,

$$\eta_x = \frac{x \text{ kVA} \times \cos \phi}{x \text{ kVA} \times \cos \phi + P_i + x^2 P_c} \times 100$$

Where, Transformer rated capacity = 100 kVA

Operating load = 75 kVA

$$\text{Fraction of load, } x = \frac{75}{100} = 0.75$$

Iron losses, $P_i = 2.5 \text{ kW}$

Full load copper losses, $P_c = 2.5 \text{ kW}$

Power factor of load, $\cos \phi = 0.8$ lagging

$$\begin{aligned}
 \therefore \eta_x &= \frac{0.75 \times 100 \times 0.8}{0.75 \times 100 \times 0.8 + 2.5 + (0.75)^2 \times 2.5} \times 100 \\
 &= 93.88\% \text{ (Ans.)}
 \end{aligned}$$

Example 3.14 : The efficiency of a 1000 KVA, 110/220 V, 50 Hz single phase transformer is 98.5% at half load at 0.8 power factor leading and 98.8% at full load unit power factor. Find (i) Iron loss (ii) Full load copper loss.

Solution : Efficiency at any fraction x of the load ;

$$\eta_x = \frac{x \text{ kVA} \times \cos \phi}{x \text{ kVA} \times \cos \phi + P_i + x^2 P_c} \times 100$$

where, P_c is full-load copper loss and P_i is the iron loss.

(i) When, $x = 0.5$; $\cos \phi = 0.8$; $\eta_x = 98.5\%$

$$\therefore 98.5 = \frac{0.5 \times 1000 \times 0.8}{0.5 \times 1000 \times 0.8 + P_i + (0.5)^2 P_c} \times 100$$

$$\text{or } 400 + P_i + 0.25 P_c = \frac{400 \times 100}{98.5} \text{ or } P_i + 0.25 P_c = 6.1 \text{ kW} \quad \dots(i)$$

(ii) When, $x = 1$; $\cos \phi = 1$; $\eta_x = 98.8\%$

$$\therefore 98.8 = \frac{1 \times 1000 \times 1}{1 \times 1000 \times 1 + P_i + (1)^2 P_c} \times 100$$

$$\text{or } 1000 + P_i + P_c = \frac{1000 \times 100}{98.8}$$

$$\text{or } P_i + P_c = 12.15 \text{ kW} \quad \dots(ii)$$

Subtracting equation (i) from (ii), we get,

$$0.75 P_c = 6.05$$

$$\text{or } P_c = 8.07 \text{ kW (Ans.)}$$

$$\text{and } P_i = 12.15 - 8.07 \text{ kW} = 4.08 \text{ kW (Ans.)}$$

Example 3.15 : In a 25 kVA, 2000 V/200 V transformer the iron and copper losses are 200 W and 400 W respectively. Calculate the efficiency at half load and 0.8 power factor lagging. Determine also the maximum efficiency and the corresponding load.

Solution : Transformer rating = 25 kVA ; Iron losses, $P_i = 200 \text{ W}$;

Full load copper losses, $P_c = 400 \text{ W}$

$$\text{Fraction of load, } x = \frac{1}{2} = 0.5 ; \text{ Power factor, } \cos \phi = 0.8$$

$$\begin{aligned} \text{Efficiency, } \eta_x &= \frac{x \times \text{kVA} \times 1000 \cos \phi}{x \times \text{kVA} \times 1000 \cos \phi + P_i + x^2 P_c} \times 100\% \\ &= \frac{(0.5) \times 25 \times 10^3 \times 0.8}{0.5 \times 25 \times 10^3 \times 0.8 + 200 + (0.5)^2 \times 400} \times 100\% \\ &= 97.08 \% \text{ (Ans.)} \end{aligned}$$

For maximum efficiency $P_i = x^2 P_c$

Fraction of load at which efficiency is maximum,

$$x = \sqrt{\frac{P_i}{P_c}} = \sqrt{\frac{200}{400}} = 0.707$$

$$\begin{aligned}\text{Maximum efficiency, } \eta_{\max} &= \frac{x \times \text{kVA} \times 1000 \times \cos \phi}{x \times \text{kVA} \times 1000 \times \cos \phi + 2P_i} \\ &= \frac{0.707 \times 25 \times 10^3 \times 0.8}{0.707 \times 25 \times 10^3 \times 0.8 + 2 \times 200} = 97.25\% \text{ (Ans.)}\end{aligned}$$

$$\text{Load at max. efficiency} = x \text{ rated kVA} = 0.707 \times 25 = 17.675 \text{ kVA (Ans.)}$$

PRACTICE EXERCISE

1. The primary and secondary windings of a 500 kVA transformer have resistance of 0.42 ohm and 0.0011 ohm respectively. The primary and secondary voltages are 600 V and 400 V respectively. The iron loss is 2.9 kW. Calculate the efficiency at half full load at a power factor of 0.8 lagging. (Ans. 98.07%)
2. A 220/400 V, 10 kVA, 50Hz, single-phase transformer has copper loss of 120 W at full load. If it has an efficiency of 98% at full load, unity power factor, determine the iron losses. What would be the efficiency of the transformer at half full-load at 0.8 p.f. lagging. (Ans. 84.08W; 97.23%)
3. A 40 kVA transformer has a core loss of 400 watt and full-load copper loss of 800 watt. If the power factor of the load is 0.9 lagging, calculate :
 - (i) the full-load efficiency, and
 - (ii) percentage of the full-load at which the maximum efficiency occurs.
 (Ans. 96.77%; 70.7%)

3.21. AUTO-TRANSFORMER

An auto-transformer is a transformer with only one winding wound on a laminated core. A part of this winding is common to both primary and secondary sides. On load, a part of the load current is

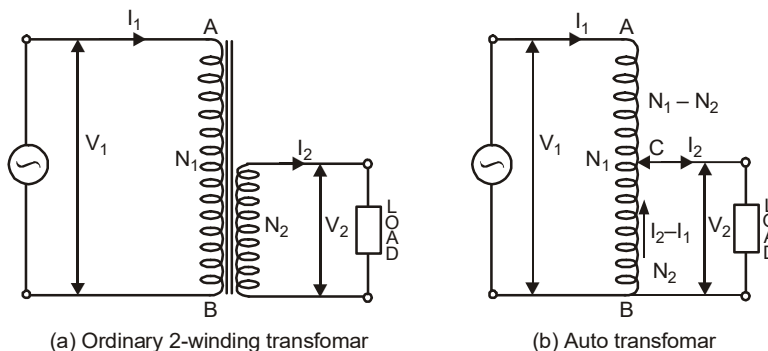


Fig. 3.22: Ordinary two winding and auto-transformer

obtained direct from the supply and remaining part is obtained by transformer action. In an ordinary transformer the primary and secondary windings are electrically insulated from each other but connected magnetically [see fig.3.22(a)], whereas, in an auto-transformer the primary and secondary windings are

connected magnetically and electrically. Fig.3.22(b). shows the primary winding AB from which a tapping at C is taken, such that CB acts as a secondary winding. The supply voltage is applied across AB and the load is connected across CB . The tapping may be fixed or variable.

When a.c. voltage V_1 is applied across AB , an alternating flux is set up in the core, it induces an e.m.f. E_1 in the winding AB . The part of this e.m.f. is taken in the secondary circuit.

Let V_1 = primary applied voltage ; V_2 = secondary voltage across the load ;

I_1 = primary current ; I_2 = load current.

N_1 = number of turns between A and B and

N_2 = number of turns between C and B

Neglecting no-load current, leakage reactance and losses, $V_1 = E_1$ and $V_2 = E_2$

$$\therefore \text{Transformation ratio, } K = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

As the secondary ampere turns are opposite to primary ampere turns so the current I_2 is in phase opposition to I_1 . The secondary voltage is less than the primary, therefore, current I_2 is more than I_1 . The resultant current flowing through section BC is $(I_2 - I_1)$.

Now, ampere turns due to section BC = current \times turns

$$= (I_2 - I_1) N_2 = \left(\frac{I_1}{K} - I_1 \right) \times N_1 K = I_1 N_1 (1 - K) \quad \dots(i)$$

Ampere turns due to section AC = $I_1 (N_1 - N_2)$

$$= I_1 N_1 \left(1 - \frac{N_2}{N_1} \right) = I_1 N_1 (1 - K) \quad \dots(ii)$$

Equations (i) and (ii) show that the ampere turns due to section BC and AC balance each other which is the characteristic of transformer action.

Saving of copper :

Volume, and hence weight of copper, is proportional to the length and area of X -section of the conductor. The length of conductor is proportional to number of turns whereas area of X -section is proportional to the current flowing through it. Hence the weight of copper is proportional to the product of current and number of turns.

Now, with reference to fig. 3.22(b), weight of copper required in an auto-transformer.

W_a = weight of Cu in section AC + weight of Cu in section CB

$$\therefore W_a \propto I_1 (N_1 - N_2) + (I_2 - I_1) N_2 \propto I_1 N_1 + I_2 N_2 - 2 I_1 N_2$$

If an ordinary two winding transformer is to perform the same duty, then with reference to fig. 3.22(a). Total weight of copper required in the ordinary transformer.

W_0 = weight of Cu on its primary + weight of Cu on its secondary.

$$\therefore W_0 \propto I_1 N_1 + I_2 N_2$$

Now, the ratio of weight of copper in auto-transformer to the weight of copper in an ordinary transformer,

$$\begin{aligned}\frac{W_a}{W_0} &= \frac{I_1 N_1 + I_2 N_2 - 2 I_1 N_2}{I_1 N_1 + I_2 N_2} = \frac{I_1 N_1 + I_2 N_2}{I_1 N_1 + I_2 N_2} - \frac{2 I_1 N_2}{I_1 N_1 + I_2 N_2} \\ &= 1 - \frac{2 I_1 N_2 / I_1 N_1}{I_1 N_1 / I_1 N_1 + I_2 N_2 / I_1 N_1} = 1 - K\end{aligned}$$

$$\text{or } W_a = (1 - K) W_0$$

Saving of copper affected by using an auto-transformer

= wt. of cu required in an ordinary transformer – wt. of copper required in an auto-transformer.

$$= W_0 - W_a = W_0 - (1 - K) W_0 = K W_0$$

∴ Saving = $K \times$ Wt. of copper required for two winding transformer

Hence, saving in copper increases as the transformation ratio approaches to unity, therefore, auto transformers are used when K is nearly equal to unity.

Uses of auto-transformer : (i) It is used as an *auto-transformer starter* to give upto 50 to 60% of full voltage to the stator of a squirrel cage induction motor during starting.

(ii) It is used to give a small boost to a distribution cable to correct the voltage drop.

(iii) It is used as a regulating transformer (the tap point C is variable in this case).

Disadvantages : Although auto-transformers have less cost, better regulation and low losses as compared to the ordinary two winding transformer of same rating. But still they are not widely used due to one major disadvantage that the secondary winding is not insulated from the primary. If an auto transformer is used to supply low voltage from a high voltage and there is a break in the secondary winding, the full *primary voltage comes across the secondary terminals which may be dangerous to the operator and equipment (load)*. Therefore, it is advisable not to use an auto transformer for interconnecting high voltage and low voltage system. Their use is only limited to the places where slight variation of output voltage from the input voltage is required.

Example 3.16 : The primary and secondary voltages of an auto transformer are 500 V and 400 V respectively. Show with the aid of diagram the current distribution in the winding when the secondary current is 100 A. calculate the economy of copper in this particular case.

$$\text{Solution : Transformation ratio, } K = \frac{V_2}{V_1} = \frac{400}{500} = 0.8$$

$$\text{Using the relation, } \frac{I_1}{I_2} = K$$

$$\text{Primary current, } I_1 = K I_2 = 0.8 \times 100 = \mathbf{80 \text{ A (Ans)}}$$

$$\text{Current in section BC} = I_2 - I_1 = 100 - 80 = \mathbf{20 \text{ A (Ans)}}$$

For distribution of current in different sections of the winding please see fig. 31 (b).

$$\text{Economy or saving of copper} = K W_0 = 0.8 W_0$$

$$\text{Percentage saving} = 0.8 \times 100 = \mathbf{80\% (Ans)}$$

3.22. THREE-PHASE TRANSFORMERS

Three phase system is invariably adopted for generation, transmission and distribution of electrical power due to economical reasons. Usually, power is generated at the generating stations at 11 kV (or 33 kV), whereas, it is transmitted at 400 kV, 220 kV, 132 kV or 66 kV due to economical reasons. At the receiving stations, the voltage level is decreased and power is transmitted through shorter distances. While delivering power to the consumers, the voltage level is decreased to as low as 400V (line value) for safety reasons.

To handle 3-phase electrical power and to increase the voltage level at the generating stations and to decrease the voltage level at the receiving stations, 3-phase step-up and step down transformers are employed.

3.23. MERITS OF THREE-PHASE TRANSFORMERS

The voltage level in 3-phase system at the generating stations and at the receiving stations can be changed by employing three single-phase transformers (inter connecting them in star or delta) or by employing one three phase transformer. Generally, one three phase transformer is preferred over single phase transformers because of the following reasons.

- (i) It requires smaller quantity of iron and copper.
 - (ii) It has smaller size and can be accommodated in smaller tank and hence needs smaller quantity of oil for cooling.
 - (iii) It has less weight and occupies less space.
 - (iv) It needs fewer number of bushings.
 - (v) Over and above, it costs nearly 15% lesser than a bank of three single phase transformers of equal rating.
 - (vi) It operates at slightly better efficiency and regulation.
- Hence, three phase transformers are invariably employed in the power system to step-up and step-down the voltages. Although, these transformers suffer from the following disadvantage.
- (i) It is more difficult and costly to repair 3-phase transformers.
 - (ii) It is difficult to transport single large unit of 3-phase transformer than to transport three single phase transformers individually.

3.24. CONSTRUCTION OF THREE-PHASE TRANSFORMERS

Form construction point of view, 3-phase transformers are also classified as

- (i) Core type transformers (ii) Shell type transformers
- (i) **Core type transformers :** In core type 3-phase transformers, the core has three limbs of equal area of cross-section. Three limbs are joined by two horizontal (top and bottom) members called yokes. The area of cross- section of all the limbs and yokes is the same since at every instant magnitude of flux set-up in each part is the same. The core consists of laminations of silicon steel material having oxide film coating on both the sides for insulation. The laminations are usually of *E* and *I* shape and are staggered alternately.

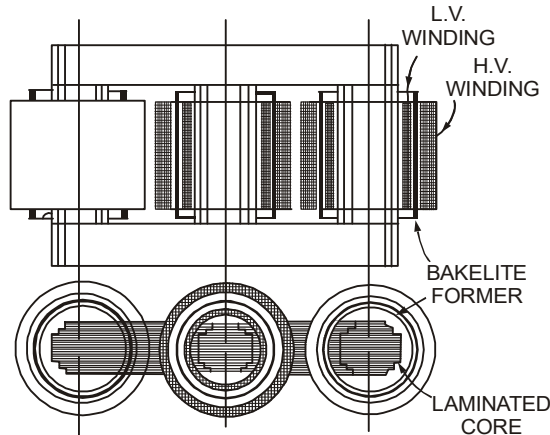


Fig.3.23: Three-phase transformer (core-type)

The complete section of a 3-phase core type transformer with its plan is shown in fig.3.23. This type of transformers are usually wound with circular cylindrical coils. The low voltage (*LV*) winding is wound nearer the core and high voltage (*HV*) winding is wound over low voltage winding as shown in fig.3.23. Insulation is always provided between the core and low voltage winding and between low voltage winding and high voltage winding.

(ii) **Shell type transformers** : In shell type transformers, the core construction is such that the windings are embedded in the core instead of surrounding the iron as shown in fig.3.24. The area of cross section of the central limbs is double to that of the side limbs and horizontal members.

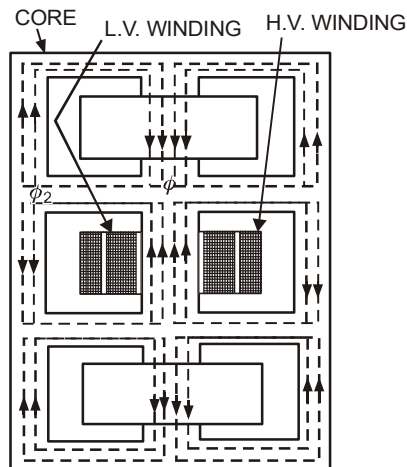


Fig. 3.24: Shell-type 3-phase transformer

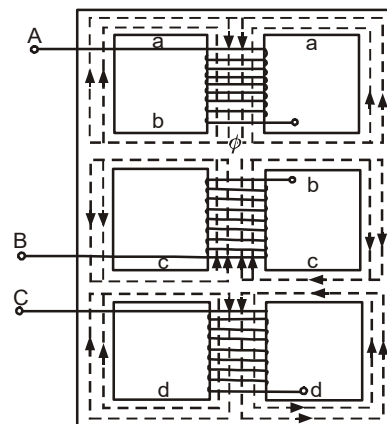


Fig. 3.25: flux distribution in the core of a 3-phase shell-type transformer

The low voltage and high voltage windings of the three-phases are wound on the central limbs. These windings are placed vertically in the three portions as shown in fig.3.25.

3.25 CONNECTIONS OF THREE-PHASE TRANSFORMERS

The three primary and three secondary windings of a three-phase transformers may be connected in star or delta, accordingly the transformers are named as:

- (i) Star-star connected 3-phase transformers
- (ii) Delta-Delta connected 3-phase transformers
- (iii) Delta-Star connected 3-phase transformers
- (iv) Star-Delta connected 3-phase transformers
- (i) **Star-Star connected 3-phase transformers :** Bunches of three windings of 3-phase transformer connected in Star (Y) on both primary and secondary sides are shown in fig.3.26 and fig. 3.27. If the ratio of transformation of each transformer is K , the same ratio will exist between the line voltages on the primary and secondary sides. This connection works satisfactorily only when load is balanced.

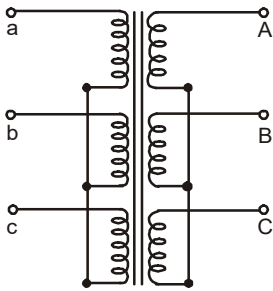


Fig. 3.26: Windings connected in star-star

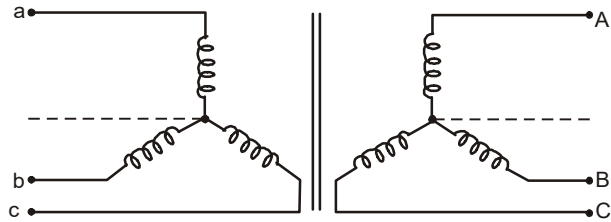


Fig. 3.27: Y-Y Connections

The advantages and disadvantages of these connections are

Advantages

- (i) This type of connections require less number of turns as each phase winding carries 57.8% $\left(\frac{E_L}{\sqrt{3}}\right)$ of the line voltage. Hence it is cheaper.
- (ii) Conductors for the winding have larger cross-sectional area as line and phase currents are the same, therefore, the winding is stronger to bear the stresses imposed upon it during heavy loads or short circuit.
- (iii) Very high voltages are possible as the dielectric stress on the insulating material is less due to the lesser voltage *i.e.* $\frac{1}{\sqrt{3}}$ line voltage.

Disadvantages

- (i) If one of the phase fails in this connection the other phases go out of action and possibly the transformer may shut down.
- (ii) In case, there is unbalancing of the secondary phases, it may vary star point potential which may assume any value with respect to earth if it is not earthed. The shifting of neutral point can be prevented by connecting the star point of primary to the star point of the alternator.

- (iii) Even if the star point of the primary is earthed, still if there is a third harmonic present in the alternator voltage, it causes interference to the telephone lines run on the same routes. The triple frequency currents can be eliminated by means of tertiary winding on each transformer.
- (iv) The regulation of the phases will be poor if the star points of both the primary and secondary are not earthed.
- (ii) **Delta-Delta connected 3-phase transformers :** Bunches of these windings of a 3-phase transformer are connected in delta on both the primary and secondary sides as shown in fig. 3.28. and fig.3.29. The line voltages are now simply the voltages across the individual transformer windings and there is no visible neutral.

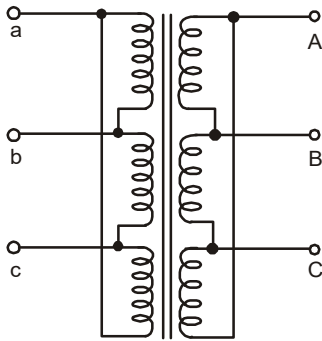


Fig. 3.28: Windings connected in delta-delta

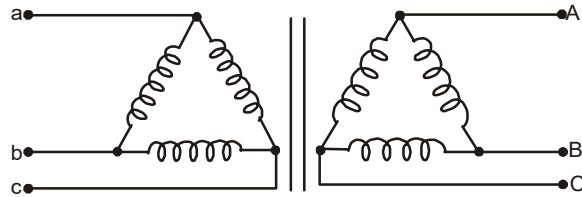


Fig. 3.29: D-D Connections

In this case, it is necessary that the transformation ratio of all the three sets of windings be same, otherwise circulating currents round the windings will be set up even at no load. The voltages on the primary and secondary sides of a given line will be more or less in the same phase, only small difference may be found due to the reactance of the winding. These connections have the following advantages :

1. In this case, there is no distortion of the flux, since the third harmonic component of the exciting current (magnetising current) finds a return path in each of the primary windings.
2. No difficulty is experienced from unbalanced loading as in the Y/Y connection. The three phase voltages remain practically equal regardless of the degree of load unbalance.
3. The cross sectional area of the wire is reduced as the phase current is $\frac{1}{\sqrt{3}}$ times the line current, and hence it is comparatively cheaper as the copper used is less.
4. These connections are more suitable for large transformers working on low voltages and high currents.
5. If one of the three windings becomes disabled for any reason, the delta-delta connections continue to operate uninterrupted in open delta or $V-V$ connection. Mostly for this advantage the delta connections are preferred.

It has only one disadvantage that no neutral is available. The neutral can be created by star connecting three equal resistances, inductances and capacitances to the three line conductors.

- (iii) **Delta-Star connected 3-phase transformers.** In these connections, primary is connected in delta and secondary in star as shown in fig.3.30. and fig. 3.31. The primary input voltage then must be equal the primary voltage of the individual transformer winding and the exciting current drawn by the bank

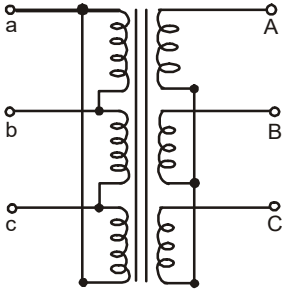


Fig. 3.30: Windings connected in delta-star

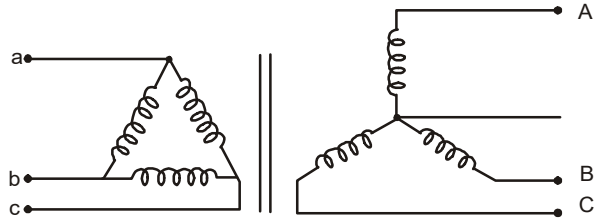


Fig. 3.31: Δ-Y connection

connected in delta may be of any required wave form. If the impressed voltages are balanced and sinusoidal, the output voltages also are balanced and sinusoidal. The ratio of secondary to primary line voltage is $\sqrt{3}$ times the transformation ratio of transformer.

$$i.e. \quad \frac{E_2}{E_1} = \frac{\sqrt{3} E_2(ph)}{E_1(ph)} = \sqrt{3}k$$

Where, E_2 = Secondary line voltage
 E_1 = Primary line voltage

Also secondary line currents are $\frac{1}{\sqrt{3} K}$ times the primary line currents.

$$\frac{I_2}{I_1} = \frac{I_2(ph)}{\sqrt{3} I_1(ph)} \quad \text{or} \quad \frac{I_2}{I_1} = \frac{1}{\sqrt{3} K}$$

Out of all the arrangements of connections, this type is one commonly used in distribution system, because it can be used to supply both 3 phase power equipment and single phase lighting circuits.

The advantages of delta-star connections over the delta-delta connections is that for high voltages less insulation is required.

(iv) **Star- Delta connected 3-phase transformers.** When the primaries are connected in star and secondaries in delta as shown in fig. 3.32. and 3.33, exactly the opposite of that which is described above in delta-star would hold. Such a combination then would be suitable for stepping up the voltages at the generating stations.

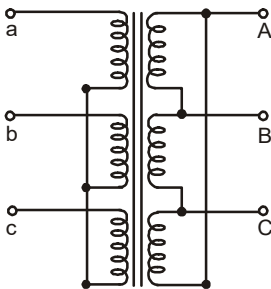


Fig. 3.32: Windings connected in star-delta

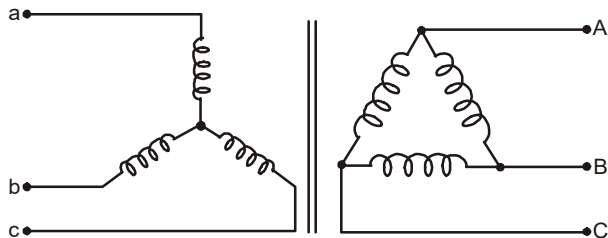


Fig. 3.33: Y-Δ connections

$$\text{In these connections : } \frac{E_2}{E_1} = \frac{E_2(ph)}{\sqrt{3} E_1(ph)} = \frac{1}{\sqrt{3}} K$$

and
$$\frac{I_2}{I_1} = \frac{\sqrt{3} I_2(ph)}{I_1(ph)} = \frac{\sqrt{3}}{K}$$

Example 3.17 : A 3-phase step down transformer is connected to 6600 volt mains and takes a current of 24 amperes. Calculate the secondary line voltage, line current and output for the following connections (i) Delta/delta (ii) Star/star (iii) Delta/star (iv) Star/delta. The ratio of turns of per phase is 12. Neglect losses.

Solution : Ratio of turns per phase = 12

Transformation ratio,
$$K = \frac{1}{12}$$

(i) Delta-Delta connections :

In Delta connections, line voltage = phase voltage.

Primary line voltage = 6600

Primary phase voltage = 6600 V

Secondary phase voltage = $\frac{6600}{12} = 550 \text{ V}$

Secondary line voltage = **550 V (Ans)**

Line current = $\sqrt{3} \times \text{phase current}$

\therefore Primary phase current = $\frac{24}{\sqrt{3}}$

Secondary phase current = $\frac{24}{\sqrt{3}} \times 12$

Secondary line current = $\sqrt{3} \times \frac{24}{\sqrt{3}} \times 12 = \mathbf{288 \text{ A (Ans)}}$

Output = $\sqrt{3} V_L I_L = \frac{\sqrt{3} \times 550 \times 288}{1000} \text{ kVA} = \mathbf{274.36 \text{ kVA (Ans)}}$

(ii) Star-Star Connections :

In star connections, line voltage = $\sqrt{3} \times \text{phase voltage}$

Also, line current = phase current.

Primary phase voltage = $\frac{6600}{\sqrt{3}}$

Secondary phase voltage = $\frac{6600}{\sqrt{3} \times 12}$

$$\text{Secondary line voltage} = \sqrt{3} \times \frac{6600}{\sqrt{3} \times 12} = \mathbf{550 \text{ V}} \text{ (Ans)}$$

$$\text{Primary line current} = 24 \text{ A}$$

$$\text{Secondary line current} = 24 \times 12 = \mathbf{288 \text{ A}} \text{ (Ans)}$$

$$\text{Output in kVA} = \frac{\sqrt{3} \times 550 \times 288}{1000} = \mathbf{274.36 \text{ kVA}} \text{ (Ans)}$$

(iii) Delta/Star Connections :

$$\text{Primary phase voltage} = 6600 \text{ volts}$$

$$\text{Secondary phase voltage} = \frac{6600}{12} = 550 \text{ V}$$

$$\text{Secondary line voltage} = \sqrt{3} \times 550 = \mathbf{952.63 \text{ V}} \text{ (Ans)}$$

$$\text{Primary phase current} = \frac{24}{\sqrt{3}}$$

$$\text{Secondary phase current} = \frac{24}{\sqrt{3}} \times 12 = 166.27 \text{ A}$$

$$\text{Secondary line current} = \mathbf{116.27 \text{ A}} \text{ (Ans)}$$

$$\text{Output in kVA} = \frac{\sqrt{3} \times 952.63 \times 166.27}{1000} = \mathbf{274.36 \text{ kVA}} \text{ (Ans)}$$

(iv) Star/Delta connections :

$$\text{Primary phase voltage} = \frac{6600}{\sqrt{3}}$$

$$\text{Secondary phase voltage} = \frac{6600}{\sqrt{3}} \times \frac{1}{12} = \mathbf{317.54 \text{ V}} \text{ (Ans)}$$

$$\text{Secondary line voltage} = \mathbf{317.54 \text{ V}} \text{ (Ans)}$$

$$\text{Primary line current} = \text{primary phase current} = \mathbf{24 \text{ A}} \text{ (Ans)}$$

$$\text{Secondary phase current} = 24 \times 12 = 288 \text{ A}$$

$$\text{Secondary line current} = \sqrt{3} \times 288 = \mathbf{498.83 \text{ A}} \text{ (Ans)}$$

$$\text{Output in kVA} = \frac{\sqrt{3} \times 317.54 \times 498.83}{1000} = \mathbf{274.36 \text{ kVA}} \text{ (Ans)}$$

3.26. POWER TRANSFORMER AND ITS AUXILIARIES

The transformers used in the power system for transfer of electric power or energy from one circuit to the other are called power transformers. The rating of a transformer includes voltage, frequency and kVA. The kVA rating is the kVA output that a transformer can deliver at the rated voltage and frequency under general service conditions without exceeding the standard limit of temperature rise (usually 45° to 60°C). The power transformer has the following important parts :

1. **Magnetic circuit :** The magnetic circuit comprises of transformer core. The transformer core may be core type or shell type in construction. The power transformers used in the power system are mostly three phase transformers. In a core type 3-phase transformer core has three limbs of equal area of cross-section.
2. **Electrical circuit :** In three phase transformers there are three primary (*H.V.*) windings and three secondary (*L.V.*) windings. Whole of the *L.V.* winding is wound over one limb next to the core, then whole of the *H.V.* winding is wound over the *L.V.* winding. In between the *L.V.* winding and *H.V.* winding and between core and *L.V.* winding insulation is provided.
3. **Transformer oil :** Transformer oil is a mineral oil obtained by fractional distillation of crude petroleum. The oil is used only in the oil cooled transformers. The oil not only carries the heat produced due to losses in the transformer, by convection from the windings and core to the transformer tank, but also has even more important function of insulation.

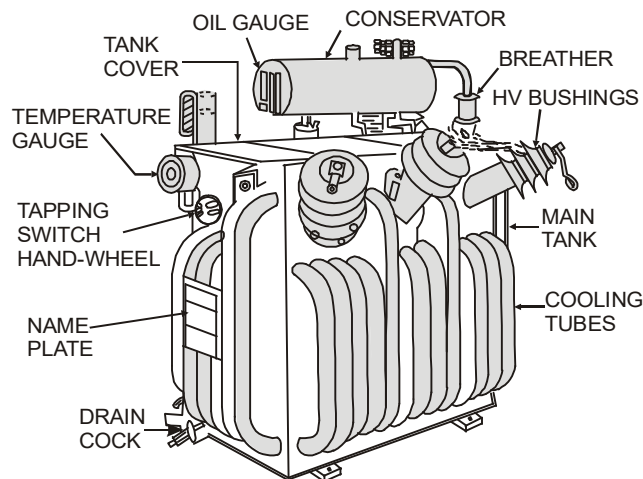


Fig. 3.34: Distribution transformer

When transformer delivers power, heat is produced due to the iron and copper losses in the transformer. This heat must be dissipated effectively otherwise the temperature of the winding will increase. The raise in temperature further increases the losses. Thus, the efficiency of the transformer will decrease. As there is no rotating part in the transformer, it is difficult to cool down the transformer as compared to rotating machines. Various methods are adopted to cool down the transformers of different rating. The common methods are air natural cooling, oil immersed natural cooling, oil immersed forced oil circulation natural cooling, oil immersed forced oil circulation with air blast cooling, oil immersed forced oil circulation with water cooling etc.

Generally, for cooling of distribution transformers, oil immersed natural cooling method is adopted. Cooling tubes or small cooling radiators are used with the main tanks, as shown in fig.3.34, to increase the surface area for the dissipation of heat.

- 4. Tank Cover :** A number of parts are arranged on the tank cover of which most important are :
- (i) **Bushing :** The internal winding of the transformer are connected to the lines through copper rods or bars which are insulated from the tank cover, these are known as bushings. Upto 33 kV ordinary porcelain bushing can be used. Above this voltage oil filled bushings or condenser bushing are employed.
 - (ii) **Oil conservator tank :** Oil conservator is also known as an oil expansion chamber. It is a small cylindrical air tight and oil tight vessel. The oil conservator is connected with a tube to the main transformer tank at the tank cover. This tank is partially filled with oil. The expansion and contraction of oil, changes the oil level in the conservator.
 - (iii) **Breather :** The transformer oil should not be allowed to come in contact with atmospheric air, since a small amount of moisture causes a great decrease in the dielectric strength of transformer oil. All the tank fittings are made air tight. When oil level in the oil conservator changes, air moves in and out of the conservator. This action is known as breathing.

The breathed air is made to pass through an apparatus called breather to abstract moisture. Breather, contains *Silica-gel* or some other drying agent such as *calcium chloride*. This ensures that only dry air enters the transformer tank.

- (iv) **Buchholz Relay :** This is installed in between the main tank and the oil conservator. It is a gas relay which gives warning of any fault developing inside the transformer, and if the fault is dangerous, the relay disconnects the transformer circuit. This relay is installed in the transformer having capacity more than 750 kVA.

All the important parts of a 200 kVA, 11 kV/400 V oil immersed natural cooled distribution transformer are shown in fig 3.34.

PROJECT



Project-1:
How To Make 12V
2A Transformer



Project-2:
How To Make
Simple Inverter 12v
To 220v IRFZ44N,
No IC



Project-3:
How to make 230V
5000W Free Energy

SUMMARY

1. *Magnet*: A magnet is a material or object that exhibits a magnetic field around it and has the ability to attract iron (ferromagnetic) pieces.
2. *Types of Magnetic Materials*: All materials can be classified in terms of their magnetic behaviour such as diamagnetic, paramagnetic or ferromagnetic.
 - (i) *Diamagnetic materials*: The material which have a weak, negative susceptibility to magnetic fields are called *diamagnetic materials*.
 - (ii) *Paramagnetic materials*: The material which have a small, positive susceptibility to magnetic fields are called *paramagnetic materials*.
 - (iii) *Ferromagnetic materials*: The material which have a large, positive susceptibility to an external magnetic field are called *ferromagnetic materials*.
3. *Important terms*: The important terms related to magnetism are:
 - (i) *Magnetic field* : The region around a magnet where its poles exhibit a force is called *magnetic field*.
 - (ii) *Magnetic flux* : The magnitude of magnetic lines of force set-up in a magnetic circuit as called *magnetic flux*.
 - (iii) *Magnetic flux density* : The flux per unit area at right angles to the flux at a point is called *magnetic flux density* at that point.
 - (iv) *Permeability* : The ability of a material to conduct magnetic lines of force through it is called the *permeability* of that material.
 - (v) *m.m.f.* : The work done in moving a unit magnetic pole once round the magnetic circuit is called m.m.f., $m.m.f. = NI$ AT.
 - (vi) *Reluctance (S)* : The opposition offered to the magnetic flux by a magnetic circuit is called its reluctance. $S = \frac{l}{a \mu_0 \mu_r}$ AT/Wb
 - (vii) *Magnetic flux (ϕ)* : The amount of magnetic lines of force set-up in a magnetic circuit is called magnetic flux.
 - (viii) *Relation between m.m.f., reluctance and flux*.

$$\phi = \frac{\text{m.m.f.}}{\text{reluctance}} \text{ or } \phi = \frac{NI}{l} a \mu_0 \mu_r.$$
 - (ix) *Permeance* : It is reciprocal to reluctance.
4. *B—H Curve* ; The graph between B and H of a material is called $B - H$ curve of that material. It shows the properties of the material.
5. *Transformer* : A static device which transfers a.c electrical power from one circuit to the other at same frequency but usually at different voltage level is called a transformer. It works on the basic principle of electromagnetic induction (mutually induced e.m.f).
6. *Ideal transformer* : Losses are neglected ; $E_1 I_1 \cos \phi = E_2 I_2 \cos \phi$

7. *Transformer on d.c.* : It is never applied on d.c. otherwise it will burn since there is no counter of self induced e.m.f. and it draws heavy current on d.c.
8. *E.M.F. equation* : $E_2 = 4.44 N_2 f \phi_m = 4.44 N_2 f B_m A_i$
9. *Transformer winding resistance* : $R_1 ; R_2 ; R_1' = R_1 \times K^2 ; R_{es} = R_2 + R_1' ;$

$$R_2' = R_2/K^2 ; R_{ep} = R_1 + R_2'$$

10. *Leakage flux* : A part of the flux produced by a winding which is not linking with the other is called leakage flux. It develops leakage reactance X_1 and X_2 , $X_1\phi = X_1 K^2 ; X_{es} = X_2 + X_1\phi ; X_2\phi = X_2/K^2 ; X_{ep} = X_1 + X_2\phi$
11. *Voltage regulation* : At constant supply voltage, the change in secondary terminal voltage from no-load to full load is called voltage regulation. It is generally taken as percentage of no-load voltage.

$$\% \text{ Reg} = \frac{E_2 - V_2}{E_2} \times 100$$

12. *Losses in a transformer* : 1. Iron loss (P_i), 2. Cu. loss (P_c at full-load)
13. *Efficiency of a transformer* : $\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_i + P_c} ; \eta_x = \frac{x V_2 I_2 \cos \phi_2}{x V_2 I_2 \cos \phi_2 + P_i + x^2 P_c}$
14. *Condition for max. efficiency* : Cu. loss = Iron loss ; $I_2 = \sqrt{P_i / R_{es}}$
15. *Auto-transformer* : A transformer, having only one winding, a part of which acts as primary and the other as secondary is called an auto transformer. Saving in copper = $K \times \text{Wt. of Cu. required for two winding transformer.}$
16. *Three-phase transformer* : A static device that transfers 3-phase power from one circuit to the other keeping frequency to be the same but (usually) changing the voltage level is called a 3-phase transformer.
17. *Merits of 3-phase transformers* : They require smaller quantity of iron and copper, have smaller size, occupy less space, light in weight, better efficiency and regulation, smaller cost etc.
18. *Construction of 3-phase transformers* : They are either core type or shell type.
19. *Connections of three-phase transformers* : According to the interconnection of primaries and secondaries, these transformers may be classified as (i) Star-star connected (ii) Delta-delta connected (iii) Delta-star connected (iv) star-delta connected.
20. *Distribution/power transformer and its auxiliaries* : A transformer employed in the power system to step-up or step-down the voltage as per the need is called *power transformer*. The main auxiliaries of these transformers are (i) conservator tank (ii) cooling tubes (iii) breather, (iv) Buchholz relay (v) temperature gauge etc.

NUMERICAL FOR PRACTICE

1. A sinusoidal flux 0.2 Wb (max.) links with 55 turns of a transformer secondary coil. Calculate the r.m.s. value to the induced e.m.f. in the secondary. The supply frequency is 50 Hz.
(Ans. 244.2 V)
2. The design requirements of a 6600/400 V, 50 Hz, single phase, core type transformer are : e.m.f. per turn 15 V; maximum flux density 1.5 Tesla (i.e. Wb/m²). Find a suitable number of primary and secondary turns and the net cross sectional area of core.
(Ans. 440 ; 26.67 ; 450 cm²)
3. A single phase transformer has 400 primary and 1000 secondary turns. The net cross sectional area of the core is 60 cm². If the primary winding is connected to a 50Hz supply at 500 V, calculate the value of maximum flux density in the core and the e.m.f. induced in secondary winding. Draw the vector diagram representing the condition.
(Ans. 0.938 Tesla, 1250 V)
4. A 33 kVA, 2200/220 V, 50 Hz single phase transformer has the following parameters :
Primary winding (hv side) ; resistance $r_1 = 2.4 \Omega$, leakage reactance $x_1 = 6.0 \Omega$.
Secondary winding (lv side) : resistance $r_2 = 0.03 \Omega$, leakage reactance $x_2 = 0.07 \Omega$.
Find the primary resistance and leakage reactance referred to secondary.
(Ans. 0.024 Ω and 0.06 Ω)
5. A single-phase transformer with a ratio of 4 :1 has primary resistance and reactance of 0.5 ohm and 1.5 ohm and the corresponding values for the secondary are 0.034 ohm and 0.1 ohm respectively. Determine the percentage regulation when delivering 120 A at 600 V at p.f.
(i) 0.707 lagging (ii) 0.8 leading.
(Ans. 3.53% ; - 3.26%)
6. Calculate the value of voltage regulation at 0.8 p.f. lagging for a transformer with resistance drop 2% and reactance drop 4% of the voltage.
(Ans. 4.0%)
7. A 230/460 V, single-phase transformer has a primary resistance of 0.2 ohm and reactance 0.5 ohm. The corresponding values for the secondary are 0.75 Ω and 1.8W Ω respectively. Find the secondary terminal voltage when supplying 10 A at 0.8 p.f. lagging.
(Ans. 424.8 V)
8. The primary and secondary windings of a 500 kVA transformer have resistance of 0.42 ohm and 0.0011 ohm respectively. The primary and secondary voltages are 6600 V and 400 V respectively. The iron loss is 2.9 kW. Calculate the efficiency at half full load at a power factor of 0.8 lagging.
(Ans. 98.07%)
9. A 50 kVA transformer has an efficiency of 98% at full-load at 0.8 p.f and an efficiency of 96.9% at $\frac{1}{4}$ full load, 0.8 p.f. Determine the iron loss and full load copper loss.
(Ans. 287 W ; 529 W)
10. A 440/110 V transformer has an effective primary resistance of 0.3 ohm and a secondary resistance of 0.02 ohm. If iron loss on normal input voltage is 150 W, calculate the secondary current at which maximum efficiency will occur. What is the value of this maximum efficiency for unity power factor load ?
(Ans. 62.22 A ; 94.8 %)

11. In a 25 kVA, 1100/400 V, single phase transformer, the iron and copper loss at full load are 350 and 400 watt respectively. Calculate the efficiency on unity power factor at half load. Determine the load on maximum efficiency. (Ans. 96.52% ; 23.85 kW)
12. A 2000/200 V transformer has primary resistance and reactance of 2 ohm and 4 ohm respectively. The corresponding secondary values are 0.025 ohm and 0.04 ohm. Determine : (i) Equivalent resistance and reactance of primary referred to secondary ; (ii) Total resistance and reactance referred to secondary ; (iii) Equivalent resistance and reactance of secondary referred to primary ; (iv) Total resistance and reactance referred to primary. (Ans. 0.02 Ω ; 0.04 Ω ; 0.045 Ω ; 0.08 Ω ; 2.5 Ω ; 4 Ω ; 4.5 Ω ; 8 Ω)

MULTI-CHOICE QUESTIONS

- during unsaturated portion of a B-H curve
(A) $B < H$ (B) $B > H$ (C) $B \propto H$ (D) $B = 0$
- Transformer core is laminated
(A) because it is difficult to fabricate solid core
(B) because laminated core provides high flux density
(C) to reduce eddy current losses.
(D) to avoid hysteresis losses.
- A transformer with output of 250 kVA at 3000 V, has 600 turns on its primary and 60 turns on secondary winding. What will be the transformation ratio of the transformer ?
(A) 10 (B) 0.1 (C) 100 (D) 0.01
- If R_1 is the resistance of primary winding of the transformer and K is transformer ratio (N_2/N_1) then the equivalent primary resistance referred to secondary will be
(A) KR_1^2 (B) KR_1 (C) K^2R_1 (D) R_1/K^2
- The condition for maximum efficiency of the transformer is that
(A) copper losses are half of the iron losses
(B) copper losses are square of the iron losses
(C) copper losses are equal to the iron losses
(D) copper losses are zero
- The induced e.m.f. in the transformer secondary will depend on
(A) frequency of the supply only.
(B) Number of turns in secondary only.
(C) Frequency and flux in core.
(D) Frequency, number of secondary turns and flux in the core.
- A transformer is never connected in the d.c. line because
(A) there is no need to step up or step down the d.c. voltage
(B) Faraday's law is not valid as the rate of changed of flux is zero.

- (C) Losses in the d.c. circuit are high.
 (D) It is not economical.
8. The eddy current loss in the transformer occurs in the
 (A) primary winding (B) core
 (C) secondary winding (D) none of the above.
9. Which of the following electrical machines has the highest efficiency?
 (A) d.c. generator (B) a.c. generator (C) transformer (D) induction motor.
10. The condition for maximum efficiency of the transformer is that
 (A) copper losses are half of the iron losses
 (B) copper losses are square of the iron losses
 (C) copper losses are equal to the iron losses
 (D) copper losses are zero
11. If the iron losses and full load copper losses are given then the load at which the efficiency of a transformer is maximum, is given by
 (A) full load $\times \frac{\text{iron loss}}{f.l.cu \text{ loss}}$ (B) full load $\times \sqrt{\frac{\text{iron loss}}{f.l.cu \text{ loss}}}$
 (C) full load $\times \left(\frac{\text{iron loss}}{f.i. \text{ cu. loss}} \right)$ (D) full load $\times \sqrt{\frac{f.I.cu. \text{ loss}}{\text{iron loss}}}$
12. The transformation ratio of a 3-phase transformer is given by the relation.
 (A) $\frac{E_{2(L)}}{E_{1(L)}}$ (B) $\frac{E_{2(ph)}}{E_{1(ph)}}$ (C) $\frac{E_{2(L)}}{E_{1(ph)}}$ (D) $\frac{E_{2(ph)}}{E_{1(L)}}$
13. The cost of single 3-phase transformer in comparison to a bank of three 1-phase transformers of equal rating is
 (A) 15% less (B) 15% more (C) 50% less (D) 50% more
14. Usually HV winding is placed
 (A) next to the core (B) over the low voltage winding
 (C) both a and b (D) none of these

SHORT ANSWER QUESTIONS

1. What is a magnet ?
2. What do you understand by magnetic field ?
3. Define magnetic flux density.
4. Explain the term MMF.
5. Define relative permeability.
6. Define reluctance in a magnetic circuit and give its formula.

7. Explain B-H characteristics of a magnetic material.
8. What is a transformer ?
9. What are step-up and step-down transformers ?
10. What are the applications of step-up and step-down transformers ?
11. Which are the two windings present in a transformer ?
12. Explain the working principle of a transformer.
13. What are the functions of a transformer ?
14. Define voltage transformation ratio.
15. From construction point of view, name different types of transformers ?
16. Why the core of a transformer is laminated ?
17. Why is a transformer also called the static device ?
18. Why do we use iron - core in a Transformer ?
19. Explain with reasons what happens when a power transformer is connected to dc supply of the same voltage rating ?
20. Why is the efficiency of a transformer maximum among electrical equipments ? Explain.
21. What is the difference between an ideal and practical transformers ?
22. How does leakage flux occur in a transformer ?
23. Write a short note on a star-Delta transformer.

TEST QUESTIONS

1. Why the B-H curve of iron is not a straight line?)
2. Define the terms : permeability, reluctance and permeance.
3. How is B-H curve of ferromagnetic material different from that of non-magnetic material ? Name all the salient regions of B-H curve of magnetic material.
4. What is a transformer ? What is its necessity in the power system ?
5. Explain the working principle of a transformer.
6. State why the core of a transformer is laminated ?
7. State why silicon steel is selected for the core of a transformer ?
8. Give the constructional details of a core-type transformer.
9. In a transformer explain how power is transferred from one winding to the other.
10. Show that $(E_1/E_2) = (I_2/I_1) = (T_1/T_2)$ in a transformer.
11. What happens when d.c. voltage is applied to the primary of a transformer ?
12. Derive an expression for the e.m.f. induced in a transformer winding. Show that the e.m.f. induced per turn in primary is equal to the e.m.f. per turn in secondary.
13. Explain what is meant by regulation of a transformer.
14. What are the various losses in a transformer ? Where do they occur and how do they vary with load ?

15. Define efficiency of a transformer and find the condition for obtaining maximum efficiency.
16. In what ways does an auto transformer differ from a conventional two winding transformer?
What are its application?

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												

ANSWERS TO MULTI-CHOICE QUESTIONS

Multi-choice questions :

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (C) | 2. (C) | 3. (B) | 4. (C) | 5. (C) |
| 6. (D) | 7. (B) | 8. (B) | 9. (C) | 10. (C) |
| 11. (B) | 12. (B) | 13. (A) | 14. (B) | |



Experiment No. 3

Transformers: Observation of the no-load current waveform on an oscilloscope (non-sinusoidal wave-shape due to B-H curve nonlinearity should be shown along with a discussion about harmonics). Loading of a transformer: measurement of primary and secondary voltages, currents, and power.

Objectives:

1. To make the students familiar with transformer and explore the characteristics of a common power transformer in its simplest form.

Apparatus/Instruments/Components required

1. Transformer (230/12-0-12V)
2. Function generator or single-phase autotransformer (variac)
3. Oscilloscope (Two-channel)
4. Digital multi-meter

Theory

Transformer is a static electric device/machine that transfers ac electric power from one circuit to the other. Transformers are most often used for three principal reasons:

1. To *change ac voltage level* while transferring electric power from one circuit to the other. If the voltage level is increased at the output side, the transformer is called step-up transformer. Whereas it is called a step-down transformer when the voltage level is decreased at the output side.
2. For *electrical isolation* for safety of equipment.
3. For *impedance matching*, these are often used to connect two components with mismatched impedances. For instance, to obtain maximum power output from an audio amplifier, a high impedance stereo amplifier and a low impedance speaker are connected together with an impedance matching transformer.

Often, we can assume that transformer is ideal device that means it has no internal power loss and all magnetic flux link with the primary as well as secondary. The ideal model suits to large power transformer where the losses are very small as compared to the power transferred. An ideal transformer delivers all the input power to the load, i.e. power input is equal to power output

$$V_1 I_1 = V_2 I_2$$

Circuit diagram

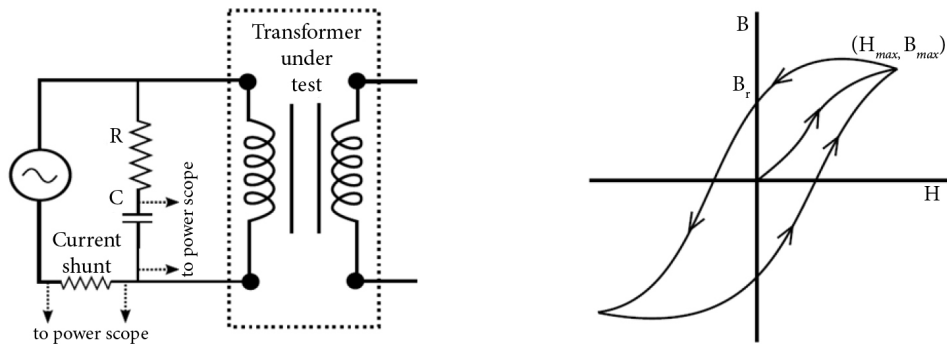


Fig.P3.1(a): Connections to trace B-H Curve **Fig. P3.1(b):** B-H Curve

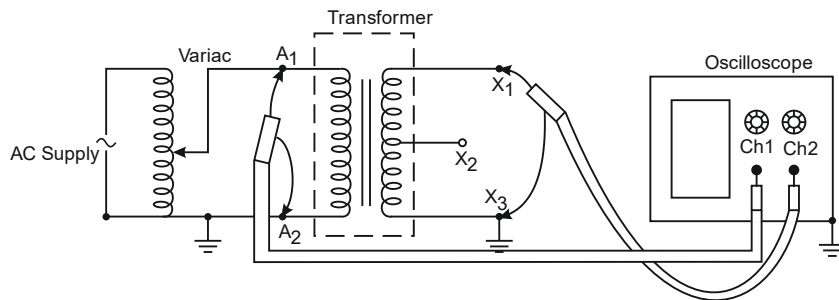


Fig. P3.2: Transformer testing at no load

Procedure:

1. Connect the apparatus as per the circuit shown in fig. P3.1(a).
2. Get your connections checked by the teacher in-charge.
3. Switch-ON the supply through switch if switch is connected in the circuit.
4. Connect a CRO across the terminals marked dotted and adjust its knobs to obtain the curve shown in fig.P3.1(b).
5. If the transformer is to be tested at no-load, make the connections as shown in fig. P3.2 and proceed further.
 - (a) Use the CRO to measure the transformer voltages mentioned below and record the results in tabulated form.
 - V_{pp} across primary A_1 and A_2 (On channel-1)
 - V_{pp} across primary X_1 and X_3 (On channel-2)

- V_{pp} from centre-tap to one side of the secondary X_1 to X_2 (Move the channel-2 ground lead to X_3 for measurements)
 - V_{pp} from centre-tap to other side of the secondary X_2 to X_3 (Move the channel-2 lead to X_2 to X_3 for measurements)
6. To check the loading of a single-phase transformer, connect an ammeter, voltmeter and a wattmeter in the primary as well as in the secondary side of the transformer.
 7. Apply a variable load on the secondary side and take the readings of ammeter, voltmeter and wattmeter connected on both the sides of the transformer at different loads.

Conclusion:

1. The shape of the hysteresis loop is almost the same as studied in the theory.
2. When load is connected at the output, the current changes in the secondary as per the load and the input current in the primary changes proportionately. The wattmeter reading on both sides *i.e.* on primary and secondary is the same ($W_2 = W_1$).

Viva:

1. What is a transformer?
2. What are the major applications of transformers?
3. If the load on a transformer is increased to double, the current in the secondary increases to double, what about the primary current?
4. What do you mean by no-load current?

Experiment No. 4

Three-phase transformers: Star and Delta connections. Voltage and Current relationships (line-line voltage, phase-to-neutral voltage, line and phase currents). Phase-shifts between the primary and secondary side. Cumulative three-phase power in balanced three-phase circuits.

Objective:

To verify the relation between line and phase values of voltages and currents when a 3-phase transformer or three single- phase transformers are connected in different configurations.

Apparatus/Instruments/Components required:

1. Three single phase transformers (preferably each of 1 kVA, 230/115 V rating or one three phase transformers of rating.....)
2. Four voltmeters of range.....
3. Four ammeters of range.....
4. Balanced 3-phase load..... (Say three heaters of same rating duly checked).
5. Three-phase ac supply.
6. Connecting leads etc.

Circuit diagram:

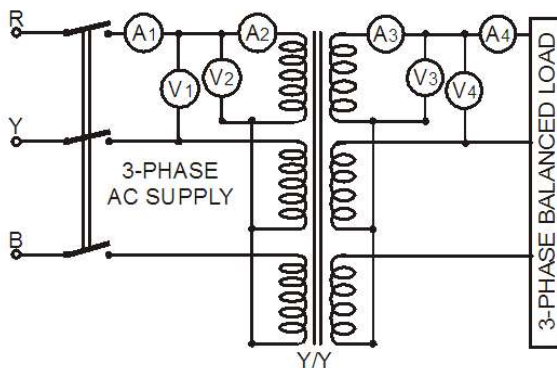


Fig. P 4.1: Star-star connected transformer

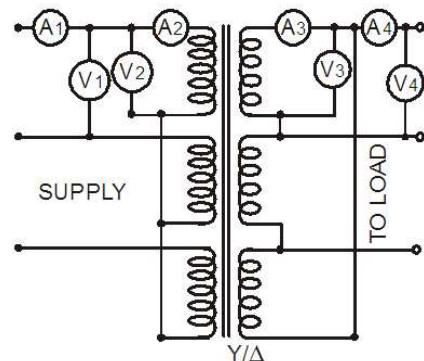


Fig. P 4.2: Star-delta connected transformer

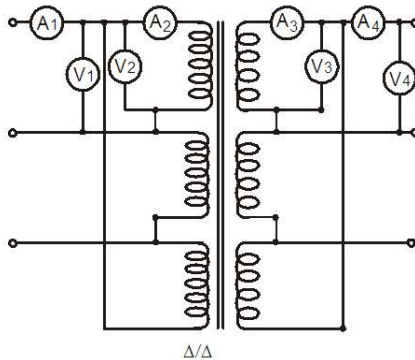


Fig.P 4.3:Delta-deltaconnected transformer

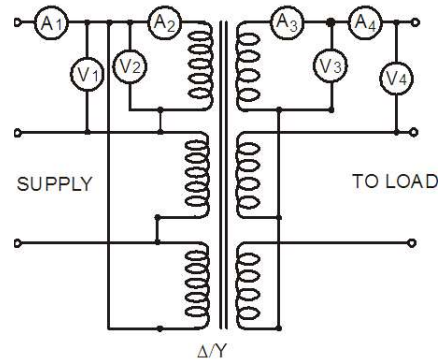


Fig. P 4.4: Delta-star connected transformer

Theory: In different configurations:

When the windings are connected in star, $V_{ph} = \frac{V_L}{\sqrt{3}}$ and $I_{ph} = I_L$

When the windings are connected in delta $V_{ph} = V_L$ and $I_{ph} = \frac{N_2 V_L}{N_1 V_{ph}}$

$$\text{Transformation ratio } K = \frac{N_2}{N_1} = \frac{V_{ph2}}{V_{ph1}}$$

Procedure:

1. Make the connections in various configurations as per circuits show in fig. P4.1, P4.2, P4.3, and P4.4
2. Get the connections checked by the teacher in-charge.
3. Switch-ON the TPST switch.
4. Take the readings of all the voltmeters and ammeters connected on both the sides, then record them in the observation table.
5. Find the relation between voltages and between currents on both the sides separately.
6. Repeat the experiment for each configuration.

Observation Table:**Primary side**

Configuration	Voltmeter readings		Ammeter readings		Relation between	
	$V_1 = V_{L1}$	$V_2 = V_{ph1}$	$A_1 = I_{L1}$	$A_2 = I_{ph1}$	Voltage V_1 / V_2	Current A_1 / A_2

Secondary Side

Configuration	Voltmeter readings		Ammeter readings		Relation between	
	$V_3 = V_{ph2}$	$V_4 = V_{L2}$	$A_3 = I_{ph2}$	$A_2 = I_{L2}$	Voltage V_4 / V_3	Current A_4 / A_3

Results:

1. It is observed that in star connections $\frac{V_L}{V_{ph}} = \sqrt{3}$ and $\frac{I_L}{I_{ph}} = 1$

Whereas in delta connections $\frac{V_L}{V_{ph}} = 1$ and $\frac{I_L}{I_{ph}} = \sqrt{3}$

Power in 3-phase balanced circuit $= 3 V_{ph} I_{ph} \cos \phi = \sqrt{3} V_L I_L \cos \phi$

Viva:

1. In star connected system, what is the relation between line voltage and phase voltage?
2. In star connected system, what is the relation between line current and phase current?
3. In delta connected system, what is the relation between line voltage and phase voltage?
4. In delta connected system, what is the relation between line current and phase current?
5. In 3-phase system, what is the equation for power consumption?

4

Electrical Machines

RATIONALE

Induction machines or induction motor are the backbone of any industry. Induction motors may be single-phase or three phase. The single phase induction motors are usually built in small sizes (upto 3 H.P) and are employed with light loads to handle domestic appliances. Three phase induction motors are the most commonly used a.c. motors in the industry because they have simple and rugged construction, low cost, high efficiency, reasonably good power factor, self starting torque and low maintenance. Almost more than 90% of the mechanical power used in industry is provided by three phase induction motors.

In this chapter, we shall deal with all the important aspects of a three phase induction motors as well as the functioning of 1-phase induction motors, dc motors and synchronous generators.

UNIT OUTCOMES

U4-O1: Unit-4 Learning Outcome-1

To know about the constructional features and working of a 3-phase induction motor.

U4-O2: Unit-4 Learning Outcome-2

To analyse the behaviour of a 3-phase induction motor with the help of torque-slip curve.

U4-O3: Unit-4 Learning Outcome-3

To analyse the effect of slip on the major losses of a 3-phase induction motor.

U4-O4: Unit-4 Learning Outcome-4

To analyse various starters employed to start a 3-phase induction motor.

U4-O5: Unit-4 Learning Outcome-5

To analyse the characteristics of various single-phase induction motors such as split phase motor, shaded pole motor, universal motor separately excited dc motors etc. and their applications.

UNIT SPECIFIC

- Working principle of a 3-phase induction motor and how to reverse its direction of rotation.
- To analyse the behaviour of a 3-phase induction motor with the help of torque-slip curve.
- Major losses in a 3-phase induction motor and the effect of slip on them.
- The necessity of a starter for 3-phase induction motor and their types.
- Methods to control the speed of a 3-phase induction motor.

- Inherently, single-phase induction motors are not self-starting, how to make them self-starting
- Working principle, characteristics and applications of shaded pole motor, universal motor and separately excited dc motors.
- Constructional features of an ac generator/alternator

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES.






Unit II Outcomes	EXPECTED MAPPING WITH COURSE OUTCOMES (1-weak Correlation; 2-Medium correlation; 3-Strong Correlation)		
	CO-1	CO-2	CO-3
U4-O1	1	3	--
U4-O2	1	3	--
U4-O3	1	3	--
U4-O4	1	3	--
U4-O5	--	3	--


Interesting facts

- Hans Christian Oersted was the first scientist who showed that electric current produces magnetic effect. It was an accidental discovery. The direction of the magnetic lines of force depends on the direction of the current that flows through the conductor.
- Similarity with gravity- Electricity works somewhat in a similar fashion as that of gravity. Gravity attracts, whereas electricity can attract or repel.


Video Resources

Videos Links for circuits

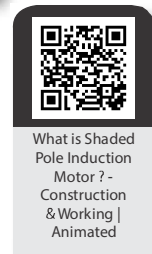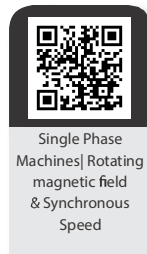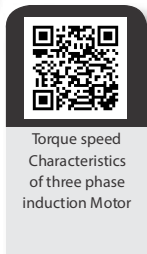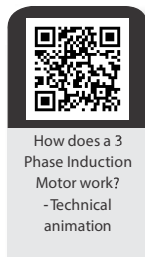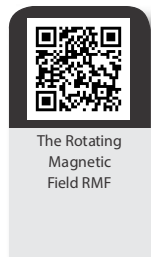


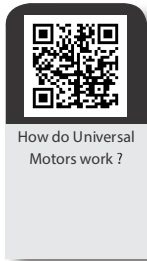

How do Universal
Motors work ?

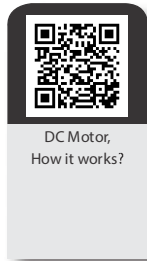

DC Motor,
How it works?

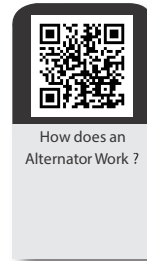

How does an
Alternator Work ?

4.1. CONSTRUCTIONAL FEATURES OF A 3-PHASE INDUCTION MOTOR

A 3-phase induction motor consists of two main parts namely stator and rotor.

1. **Stator** : It is the stationary part of the motor. It has three main parts, namely. (i) Outer frame, (ii) Stator core and (iii) Stator winding.

- (i) **Outer frame** : It is the outer body of the motor. Its function is to support the stator core and to protect the inner parts of the machine. For small machines the frame is casted but for large machines it is fabricated.

To place the motor on the foundation, feet are provided in the outer frame as shown in fig.4.1.

- (ii) **Stator core** : The stator core is to carry the alternating magnetic field which produces hysteresis and eddy current losses, therefore, core is built up of high grade silicon steel stamping. The stampings are assembled under hydraulic pressure and are keyed to the frame. Each stamping is insulated from the other with a thin varnish layer. The thickness to the stamping usually varies from 0.3 to 0.5 mm. Slots are punched on the inner periphery of the stampings, as shown in fig. 4.2, to accommodate stator winding.

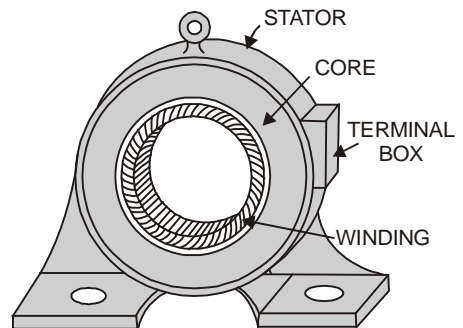


Fig. 4.1: Stator

- (iii) **Stator winding** : The stator core carries a three phase winding which is usually supplied from a three phase supply system. The six terminals of the winding (two of each phase) are connected in the terminal box of the machine. The stator of the motor is wound for definite number of poles, the exact number being determined by the requirement of speed. It will be seen that greater the number of poles, the lower is the speed and vice-versa, since

$$N_s \propto \frac{1}{P} \left(\because N_s = \frac{120f}{P} \right). \text{ The three- phase}$$

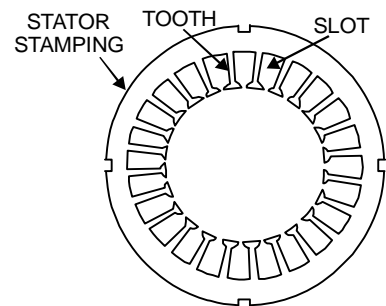


Fig. 4.2: Stator stamping

winding may be connected in star or delta externally through a starter.

2. **Rotor** : It is the rotating part of the motor. There are two types of rotors, which are employed in 3 phase induction motors.

(i) Squirrel cage rotor (ii) Phase wound rotor.

- (i) **Squirrel cage rotor** : The motors employing this type of rotor are known as *Squirrel cage induction motors*. Most of the induction motors are of this type because of simple and rugged construction of rotor. A squirrel cage rotor consists of a laminated cylindrical core having semi-closed circular slots at the outer periphery. Copper or aluminium bar conductors are placed in these slots and short circuited at each end by copper or aluminium rings, called short circuiting rings, as shown in fig.4.3. Thus, the rotor winding is permanently short circuited and it is not possible to add any external resistance in the rotor circuit.

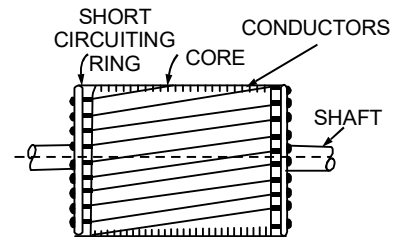


Fig. 4.3: Squirrel cage rotor

The rotor slots are usually not parallel to the shaft but are skewed. Skewing of rotor has the following advantages :

- (a) It reduces humming thus ensuring quiet running of a motor,
 - (b) It results in a smoother torque curves for different positions of the rotor,
 - (c) It reduces the magnetic locking of the stator and rotor,
 - (d) It increases the rotor resistance due to the increased length of the rotor bar conductors.
- (ii) **Phase wound rotor** : Phase wound rotor is also called slip ring rotor and the motors employing this type of rotor are known as *phase wound* or *slipring induction motors*. Slip ring rotor consists of a laminated cylindrical core having semi-closed slots at the outer periphery and carries a 3-phase insulated winding. The rotor is wound for the same number of poles as that of stator. The three finish terminals are connected together forming star point and the three start terminals are connected to three copper slipings fixed on the shaft (see fig.4.4).

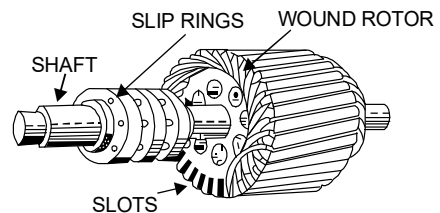


Fig. 4.4: Phase wound rotor

In this case, depending upon the requirement any external resistance can be added in the rotor circuit. In this case also the rotor is skewed.

A mild steel shaft is passed through the centre of the rotor and is fixed to it with key. The purpose of shaft is to transfer mechanical power.

4.2. PRODUCTION OF REVOLVING FIELD

Consider a stator on which three different windings represented by three concentric coils a_1a_2 , b_1b_2 and c_1c_2 respectively are placed 120° electrically apart.

Let a 3-phase supply, as shown in fig. 4.5, is applied to the stator. Three phase currents will flow through the three coils and produce their own magnetic fields. The positive half cycle of the alternating current is considered as inward flow of current in the start terminals and negative half cycle is considered as outward flow of current in the start terminals. The direction of flow of current is opposite in the finish terminals of the same coil.

Let at any instant t_1 , current in coil side a_1 be inward and in b_1 and c_1 outward. Whereas, the current in the other sides of the same coils is opposite *i.e.* in coil side a_2 is outward and b_2 and c_2 is inward. The resultant field and its direction (F_m) is marked in fig. 4.6.

At instant t_2 when θ is 60° , current in coil sides a_1 and b_1 is inward and in c_1 is outward. Whereas, the current in the opposite sides is opposite. The resultant field and its direction is shown in fig. 4.7, which is rotated through an angle $\theta = 60^\circ$ from its previous position.

At instant t_3 when θ is 120° , current in coil side b_1 is inward and in c_1 and a_1 is outward. The resultant field and its direction is shown in fig. 4.8. Which is rotated through an angle $\theta = 120^\circ$ electrical from its first position.

Thus, in one cycle, the resultant field completes one revolution. Hence, we conclude that when 3-phase supply is given to a 3-phase wound stator, a resultant field is produced which revolves at a constant speed, called synchronous speed ($N_s = 120^\circ f / P$).

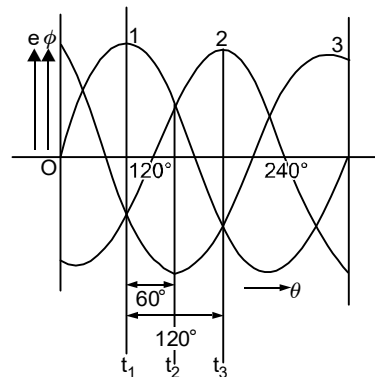


Fig. 4.5: Wave diagram of magnetic flux produced in the stator core

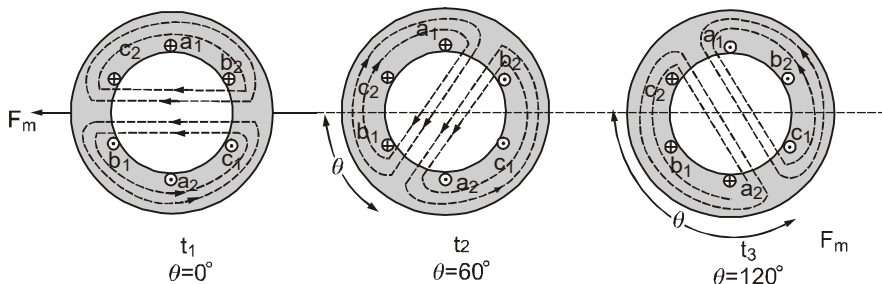


Fig. 4.6: Resultant axis of magnetic field at instant t_1

Fig. 4.7: Resultant axis of magnetic field at instant t_2

Fig. 4.8: Resultant axis of magnetic field at instant t_3

In this case, we have seen that when supply from phase 1, 2 and 3 is given to coil a_1a_2 , b_1b_2 and c_1c_2 , respectively, an anticlockwise rotating field is produced. If the supply to coil a_1a_2 , b_1b_2 and c_1c_2 is given from phase 1, 3 and 2 respectively, the direction of rotating field is reversed. Thus, to reverse the direction of rotation of rotating field the connections of any two supply terminals are inter changed.

4.3. PRINCIPLE OF OPERATION

When 3-phase supply is given to the stator of a 3-phase wound induction motor, a revolving field is set up in the stator. At any instant, the magnetic field set-up by the stator is shown in fig. 4.9. The direction of the resultant field is marked by an arrow head F_m . Let this field is rotating in an anti-clockwise direction at an angular speed of ω_s radians per second *i.e.* synchronous speed.

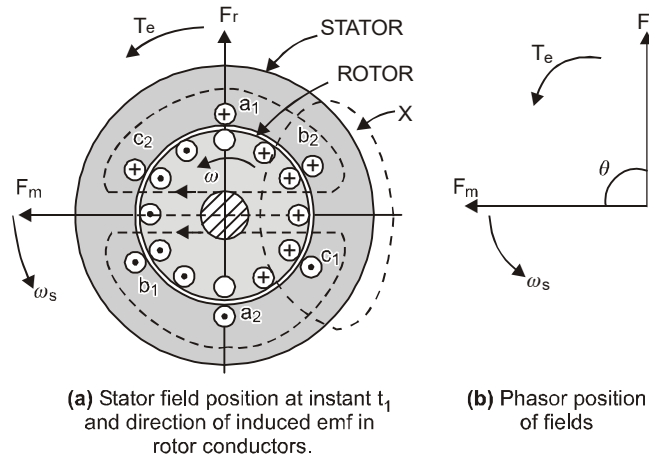


Fig. 4.9: Working principle of 3-phase Induction motor

The stationary rotor conductors cut the revolving field and due to electromagnetic induction an e.m.f. is induced in the rotor conductors. As the rotor conductors are short circuited, current flows through them in the direction as marked in the figure. Rotor current carrying conductors set up a resultant field F_r . This field tries to come in line with the stator main field F_m . Due to this an electromagnetic torque T_e is developed in the anticlockwise direction. Thus, rotor starts rotating in same direction in which stator field is revolving.

Alternately : Reproducing section X of fig. 4.9 (a) as shown in fig. 4.10, when the revolving stator field see fig. 4.10 (a) cuts the stationary rotor conductors, an e.m.f. is induced in the conductors by induction. As rotor conductors are short circuited, current flows through them, as marked in fig. 4.10, (b) which sets up field around them. A resultant field is set up, as shown in fig. 4.10 (c) which exerts force on the rotor conductors. Thus, the rotor starts rotating in the same direction in which stator field is revolving.

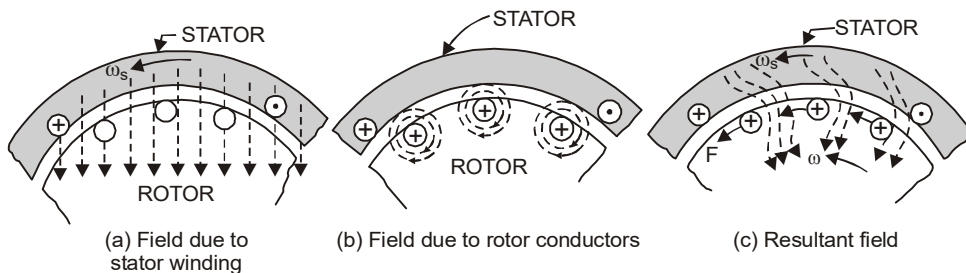


Fig. 4.10: Field developed in the motor

The rotor picks up speed and tries to attain the synchronous speed but fails to do so. It is because if the rotor attains the synchronous speed then the relative speed between revolving stator field and rotor will be zero, no e.m.f. will be induced in rotor conductors. No e.m.f. means no current, no rotor field F_r and hence no torque is produced. Thus, *an induction motor never runs at synchronous speed*. It always seems at a speed less than synchronous speed.

Since, *the principle of operation of this motor depends upon electromagnetic induction, hence the name induction motor*.

4.4. REVERSAL OF DIRECTION OF ROTATION OF 3-PHASE INDUCTION MOTORS

In Art. 2 it has been seen that a revolving field is set up in the stator of a 3-phase induction motor when 3-phase supply is given to its winding and the direction of rotation depends upon the supply sequence.

In Art. 3, it has been seen that rotor of a three phase induction motor rotates in the same direction as that of the revolving field.

The direction of rotation of the revolving field or that of the rotor can be reversed if the sequence of supply is reversed. The supply sequence can be reversed by interchanging the connections of any two supply leads at the stator terminals.

Hence, *the direction of rotation of a 3-phase induction motor can be reversed by interchanging the connections of any two supply leads at the stator terminals*.

4.5. SLIP

The rotor of an induction motor always rotates at a speed less than synchronous speed. The difference between the flux speed (N_s) and the rotor speed (N) is called slip. It is usually expressed as a percentage of synchronous speed (N_s) and is represented by symbol S .

Mathematically,

$$\% \text{ slip, } \quad \% S = \frac{N_s - N}{N_s} \times 100 \quad \text{or Fractional slip, } S = \frac{N_s - N}{N_s}$$

$$\text{Rotor speed, } \quad N = N_s (1 - S)$$

The difference between synchronous speed and rotor speed is called *slip speed* i.e.,

$$\text{Slip speed} = N_s - N$$

The value of slip at full load varies from about 6% small motors to about 2% for large motors.

Importance of slip : Slip plays an important role in the operation of an induction motor. We have already seen that the difference between the rotor speed and synchronous speed of flux determine the rate at which the flux is cut by rotor conductors and hence the magnitude of induced e.m.f. i.e. $e_2 \propto N_s - N$

$$\text{Rotor current, } i_2 \propto e_2 \text{ and torque, } T \propto i_2 \quad \text{or } T = KN_s \left(\frac{N_s - N}{N_s} \right)$$

$$\therefore \quad T = K (N_s - N)$$

$$\text{or} \quad T = K_1 S \quad \text{Hence} \quad T \propto S$$

Thus, greater the slip greater will be the induced e.m.f. or rotor current and hence larger will be the torque developed.

At no-load, induction motor requires small torque to meet with the mechanical, iron and other losses, therefore, slip is small. When the motor is loaded, greater torque is required to drive the load, therefore, the slip increases and rotor speed decreases slightly.

Thus, it is seen that slip in an induction motor adjusts itself to such a value so as to meet the required driving torque under normal operation.

4.6. FREQUENCY OF ROTOR CURRENTS

The frequency of rotor currents depends upon the relative speed between rotor and stator field. When the rotor is stationary, the frequency of rotor currents is the same as that of the supply frequency. But once the rotor starts rotating, the frequency of rotor currents depends upon slip speed ($N_s - N$). Let at any speed N , the frequency of rotor currents be f_r . Then

$$f_r = \frac{(N_s - N)P}{120} = \frac{(N_s - N)}{N_s} \cdot \frac{N_s P}{120} = S \times f$$

Example 4.1. : *A 3-phase induction motor is wound for 6 poles and is supplied from a 50 Hz system. Calculate : (i) Synchronous speed. (ii) Actual speed of the motor when running at 3% slip (iii) Frequency of e.m.f. induced in rotor.*

Solution :

$$\text{Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = \mathbf{1000 \text{ r.p.m. (Ans.)}}$$

$$\text{Actual speed of motor, } N = N_s (1 - S) \text{ where, } S = 0.03$$

$$N = 1000 (1 - 0.03) = \mathbf{970 \text{ r.p.m. (Ans)}}$$

$$\text{Frequency of rotor e.m.f., } f_r = Sf = 0.03 \times 50 = \mathbf{1.5 \text{ Hz (Ans)}}$$

Example 4.2. : *A 5 HP, 230 V, 3-phase, 50 Hz, 4 pole squirrel cage induction motor operates at full load slip of 4% when rated voltage and rated frequency are applied. Determine (i) full load speed. (ii) full load torque in Newton-metre . (iii) frequency of rotor current under this condition and (iv) speed of rotation of the stator m.m.f.*

$$\text{Solution : Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$$

$$\text{Full load speed, } N = N_s (1 - S) = 1500 (1 - 0.04) = \mathbf{1440 \text{ r.p.m. (Ans)}}$$

$$\text{Output} = \omega T = 5 \times 735.5 \text{ W (where } \omega = 2\pi N/60)$$

$$\text{Or } T = \frac{5 \times 735.5 \times 60}{2\pi \times 1440} = \mathbf{24.39 \text{ Nm (Ans)}}$$

$$\text{Rotor current frequency, } f_r = Sf = 0.04 \times 50 = \mathbf{2 \text{ Hz (Ans)}}$$

$$\text{Speed of rotation of stator m.m.f.} = N_s = \mathbf{1500 \text{ r.p.m. (Ans)}}$$

Example 4.3. : Power to an induction motor is supplied by an 8 pole, 3-phase, 750 r.p.m. alternator. The full load speed of the motor is 1440 r.p.m. Find the percentage slip and number of poles in the motor.

Solution : Speed of the alternator, $N_{sa} = 750$ r.p.m.

No. of poles of the alternator, $P_a = 8$

Generated or supply frequency, $f = \frac{P_a N_{sa}}{120} = \frac{8 \times 750}{120} = 50$ Hz

Motor Speed, $N = 1440$ r.p.m.

No. of poles of motor, $P = \frac{120f}{N} = \frac{120 \times 50}{1440} = 4.16 = 4$ (Ans)

Synchronous speed, $N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500$ r.p.m.

Percentage slip, $S = \frac{N_s - N}{N_s} \times 100 = \frac{1500 - 1440}{1500} \times 100 = 4\%$ (Ans)

Example 4.4. : A 200 HP, 3-Phase, 400 V, 50 Hz induction motor has a speed of 1425 r.p.m at full load. The machine has 4 poles. Calculate the slip. How many complete alternations will the rotor e.m.f. make per minute.

Solution :

Here, $f = 50$ Hz, $P = 4$, $N = 1425$ r.p.m.

Synchronous speed, $N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500$ r.p.m.

Slip, $S = \frac{N_s - N}{N_s} = \frac{1500 - 1425}{1500} = 0.05$ or 5% (Ans)

Frequency of rotor e.m.f. $f_r = Sf = 0.05 \times 50 = 2.5$ Hz or 2.5 c/s

Alternations of rotor e.m.f. per min = $2.5 \times 60 = 150$ c/ min (Ans)

PRACTICE EXERCISE

1. A 3-phase induction motor is wound for 4 poles and is supplied from a 50 Hz system. Calculate : (i) Synchronous speed. (ii) Actual speed of the motor when running at 4% slip (iii) Frequency of e.m.f. induced in rotor. (Ans, 1500 r.p.m.; 1440 r.p.m.; 2 Hz)
2. A 10 HP, 230 V, 3-phase, 50 Hz, 6 pole squirrel cage induction motor operates at full load slip of 4% when rated voltage and rated frequency are applied. Determine (i) full load speed. (ii) full load torque in Newton-metre. (iii) frequency of rotor current under this condition and (iv) speed of rotation of the stator m.m.f. (Ans, 960 r.p.m. ; 73.16 Nm ; 2 Hz ; 1000 r.p.m.)

3. Power to an induction motor is supplied by a 12 pole, 3-phase, 500 r.p.m. alternator. The full load speed of the motor is 1440 r.p.m. Find the percentage slip and number of poles in the motor. (Ans, 4; 4%)
4. A 500 HP, 3-Phase, 440 V, 50 Hz induction motor has a speed of 950 r.p.m at full load. The machine has 6 poles. Calculate the slip. How many complete alternations will the rotor e.m.f. make per minute. (Ans, 0.05 or 5%; 150 c/min)

4.7. SPEED OF ROTOR FIELD OR M.M.F.

When three-phase currents are supplied to the stator winding of a poly phase induction motor, a resultant field is set up which rotates at a constant speed called synchronous speed ($N_s = 120f/P$).

This rotating field induces poly phase e.m.fs. in the rotor winding and if rotor winding is closed, poly phase currents circulate in it. These currents set up a revolving field in the rotor which rotates at a speed $N_r = 120f_r/P$ with respect to rotor.

Now $N_r = 120 \times Sf/P = SN_s$

When rotor itself is rotating at a speed N r.p.m. in the space.

$$\therefore \text{Speed of rotor field in space} = N + N_r = (1 - S) N_s + SN_s = N_s - SN_s + SN_s = N_s$$

Thus, rotor magnetic field also rotates, in space, at the same speed and in the same direction as that of stator field. Hence, the two fields are magnetically locked with each other and are stationary with respect to each other.

4.8. ROTOR E.M.F.

The revolving magnetic field set up in the stator by poly phase currents is common to both stator and rotor winding. This field induces e.m.fs. in both the windings. The stator induced e.m.f. per phase is given by the relation;

$$E_1 = 4.44 k_{w1} T_1 f \phi_m \quad \dots(i)$$

Where k_{w1} = winding factor *i.e.* product or coil span factor k_c and distribution factor k_d .

T_1 = No. of turns/phase of stator winding;

f = stator or supply frequency and

ϕ_m = maximum value of flux.

$$\text{The rotor induced e.m.f./phase, } E_2 = 4.44 kw_2 T_2 f_r \phi_m \quad \dots(ii)$$

Where f_r is the rotor current frequency, and under stationary condition *i.e.*, at the start $f_r = f$. Therefore, rotor induced e.m.f./phase at stand still or start, $E_{2s} = 4.44 kw_2 T_2 f \phi_m$

Dividing eq. (ii) by (i), we get,

$$\frac{E_{2s}}{E_1} = \frac{4.44 kw_2 T_2 f \phi_m}{4.44 kw_1 T_1 f \phi_m} = \frac{T_2}{T_1} = K \quad (\text{i.e. transformation ratio})$$

From eq. (ii), induced e.m.f. in the rotor under running condition,

$$E_2 = 4.44 k w_2 T_2 (Sf) \phi_m = SE_{2s}$$

The induced e.m.f. in the rotor circuit is maximum at the start and varies according to the value of slip under running condition. Since, the value of normal slip under loaded condition is nearly 5% therefore, the rotor induced e.m.f. is nearly 5% of the maximum value.

4.9. ROTOR RESISTANCE

Since the rotor winding is made of some conducting material (copper or aluminium), it has a definite resistance ($R = \rho l/a$). Its value remains constant and is denoted by R_2 .

4.10. ROTOR REACTANCE

Whole of the flux produced by the rotor currents does not link with the stator winding. The part of rotor flux which links the rotor conductors but not with the stator winding is called leakage flux and hence develops leakage inductance (L_2). The leakage flux and hence the inductance is very small if the rotor conductors are placed at the outermost periphery of the rotor as shown in fig.4.11. Depending upon the rotor current frequency, rotor reactance will be developed.

$$\text{Rotor reactance, } X_2 = 2\pi f_r L_2 = 2\pi Sf L_2 = S(2\pi f L_2)$$

When the rotor is standstill *i.e.*, at the start, when slip, $S = 1$

$$\text{The value of rotor reactance} = X_{2s} = 2\pi f L_2$$

$$\text{Thus, under normal running, rotor reactance, } X_2 = SX_{2s}$$

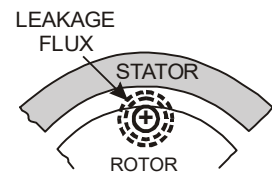


Fig. 4.11: Rotor leakage flux

4.11. ROTOR IMPEDANCE

The total opposition offered to the flow of rotor current by the rotor circuit is called the rotor impedance.

$$\text{Rotor impedance, } \bar{Z}_2 = R_2 + jX_2 = R_2 + jSX_{2s}$$

$$\text{Magnitude of rotor impedance, } Z_2 = \sqrt{(R_2)^2 + (SX_{2s})^2}$$

4.12. ROTOR CURRENT AND POWER FACTOR

The rotor circuit diagram of an induction motor is shown in figure 4.12.

Under running condition;

$$\text{Rotor induced e.m.f.} = E_2 = SE_{2s}$$

$$\text{Rotor impedance, } Z_2 = \sqrt{R_2^2 + X_2^2} = \sqrt{(R_2)^2 + (SX_{2s})^2}$$

$$\text{Rotor current, } I_2 = \frac{E_2}{Z_2}$$

$$= \frac{E_2}{\sqrt{(R_2)^2 + (X_2)^2}} = \frac{SE_{2s}}{\sqrt{(R_2)^2 + (SX_{2s})^2}}$$

$$\text{Rotor power factor, } \cos\phi_2 = \frac{R_2}{Z_2} = \frac{R_2}{\sqrt{(R_2)^2 + (SX_{2s})^2}}$$

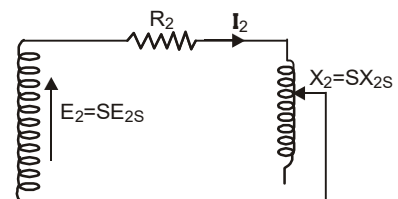


Fig. 4.12: Rotor circuit $X_2 = SX_{2s}$

4.13. SIMPLIFIED EQUIVALENT CIRCUIT OF ROTOR

The various parameters and electrical quantities are represented on the circuit diagram, as shown in fig. 4.13 The rotor current is given by the expression :

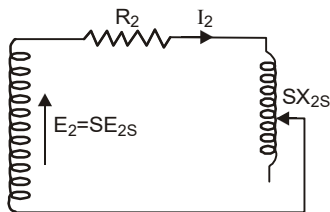


Fig. 4.13: Rotor circuit X_2 variable

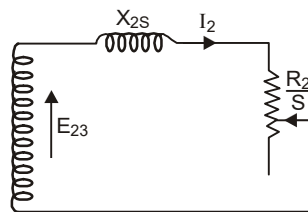


Fig.4.14: Rotor circuit X_2 is fixed to X_{2s}


$$I_2 = \frac{SE_{2s}}{\sqrt{(R_2)^2 + (SX_{2s})^2}}$$

The other expression for the rotor current is


$$I_2 = \frac{E_{2s}}{\sqrt{(R_2 / S)^2 + (X_{2s})^2}} \quad (\text{dividing the numerator and denominator by } S)$$

This expression gives a convenient form of equivalent circuit as shown in fig. 4.14.

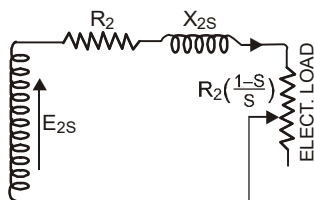The resistance is a function of slip and can be splitted into two parts ; $\frac{R_2}{S} = R_2 + R_2 \left(\frac{1-S}{S} \right)$ Where $R_2 \left(\frac{1-S}{S} \right)$ represents electrical load on the rotor.



(a) Equivalent circuit

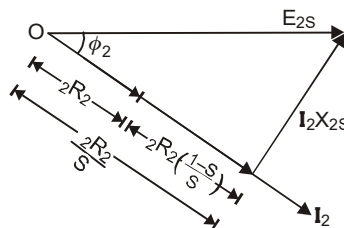

(b) Phasor diagram

Fig. 4.15: Rotor equivalent circuit and phasor diagram

Thus, the final simplified equivalent rotor circuit is shown in fig.4.15 (a). Where R_2 is rotor resistance and X_{2s} is standstill leakage reactance. The resistance $R_2 \left(\frac{1-S}{S} \right)$ is fictitious resistance representing load.

The power consumed by this fictitious resistance *i.e.* $I_2^2 R_2 \left(\frac{1-S}{S} \right)$ is the electrical power which is converted into mechanical power to pick the load. After subtracting the mechanical losses, we get the output power available at the shaft.

Thus, electrical power converted into mechanical power, $= I_2^2 R_2 \left(\frac{1-S}{S} \right)$ watt

From the simplified equivalent circuit the phasor diagram of rotor circuit is drawn as shown in fig.4.15 (b).

Rotor current I_2 lags behind the rotor standstill induced e.m.f E_{2s} by an angle ϕ .

The voltage drop across R_2 i.e. $I_2 R_2$ and across $R_2 \left(\frac{1-S}{S} \right)$ i.e. $I_2 R_2 \left(\frac{1-S}{S} \right)$ are in phase with current I_2 , whereas the voltage drop in X_{2s} i.e. $I_2 X_{2s}$ leads the current I_2 by 90° .

The vector sum of all the three drops is equal to E_{2s} i.e.

$$E_{2s} = I_2 \sqrt{(R_2 / S)^2 + (X_{2s})^2}$$

Power factor of rotor circuit,

$$\cos \phi = \frac{R_2 / S}{\sqrt{(R_2 / S)^2 + (X_{2s})^2}}$$

4.14. LOSSES IN AN INDUCTION MOTOR

The major losses in an induction motor are :

1. **Stator losses** : The losses which occur in the stator of an induction motor are called stator losses.
 - (i) Stator copper losses – $I_1^2 R_1$ (per phase)
 - (ii) Stator iron losses- These are the hysteresis and eddy current losses.
2. **Rotor losses** : which occur in the rotor of an induction motor are called rotor losses.
 - (i) Rotor copper losses – $I_2^2 R_2$ (per phase)
 - (ii) Rotor iron losses- Since under normal running condition rotor frequency is very small, therefore. These losses are so small that they are neglected.
3. **Mechanical losses** : The sum of windage and friction losses are called mechanical losses.

4.15. POWER FLOW DIAGRAM

Electrical power input is given to the stator. There are stator copper and iron losses and the remaining power i.e stator output is transferred to the rotor through magnetic flux called rotor input. In the rotor there are rotor copper losses and the remaining power is converted into

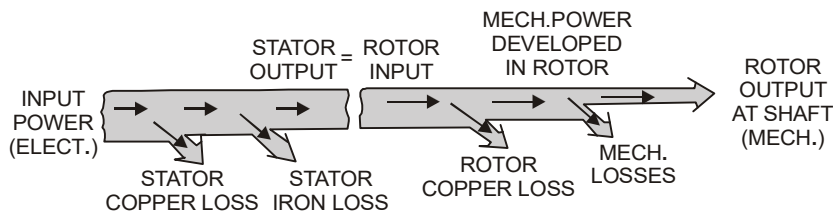


Fig. 4.16: Power flow diagram

mechanical power called mechanical power developed in the rotor. Then there are mechanical losses and the remaining power is available at the shaft called mechanical power output.

The power flow diagram is shown in fig. 4.16.

4.16. RELATION BETWEEN ROTOR COPPER LOSS, SLIP AND ROTOR INPUT

We have seen that the electrical power developed in the rotor is converted into mechanical power which is given by the relation :

$$\text{Mech. power developed in the rotor} = I_2^2 R_2 \left(\frac{1-S}{S} \right) \quad \dots(i)$$

$$\text{The rotor copper losses} = I_2^2 R_2 \quad \dots(ii)$$

From power flow diagram :

$$\text{Rotor input} = \text{Mech. power developed} + \text{rotor copper losses}$$

$$= I_2^2 R_2 \left(\frac{1-S}{S} \right) + I_2^2 R_2 = \left(\frac{I_2^2 R_2}{S} \right) \quad \dots(iii)$$

$$\text{From eq. (i) and (ii), we get, } \frac{\text{Rotor copper loss}}{\text{Mech. power developed}} = \frac{I_2^2 R_2}{I_2^2 R_2 \left(\frac{1-S}{S} \right)}$$

$$\therefore \text{ Rotor copper loss} = \left(\frac{S}{1-S} \right) \text{ Mech. power developed}$$

$$\text{From. eq. (ii) and (iii), we get, } \frac{\text{Rotor copper loss}}{\text{Rotor input}} = \frac{I_2^2 R_2}{I_2^2 R_2 / S}$$

$$\therefore \text{ Rotor copper loss} = S \times \text{Rotor input}$$

Note : All the values are the phase values.

4.17. ROTOR EFFICIENCY

The ratio of rotor output (*i.e.*, mechanical power developed in rotor neglecting mechanical losses) to the rotor input is called the rotor efficiency.

$$\text{Rotor efficiency} = \frac{\text{Mech. Power developed}}{\text{Rotor input}} = \frac{I_2^2 R_2 \left(\frac{1-S}{S} \right)}{I_2^2 R_2 / S} = (1-S)$$

Example 4.5 : A 10 H.P., 4 pole, 25 Hz, 3-phase, wound rotor induction motor is taking 9100 watt from the line. Core loss is 290 watt, stator copper loss is 568 watt, rotor copper loss is 445 watt, friction and windage losses are 100 watt. Determine ; (a) power transferred across air gap ; (b) mechanical power in watt developed by rotor ; (c) mechanical power output in watt ; (d) efficiency ; (e) slip.

Solution : Power input to motor or stator = 9100 watt

$$\begin{aligned} \text{Power transferred across air gap} &= \text{Stator input} - \text{Stator core loss} - \text{Stator copper loss} \\ &= 9100 - 290 - 568 = \mathbf{8242 \text{ W}} \quad (\text{Ans}) \end{aligned}$$

Mechanical power developed in rotor = rotor input – Rotor copper loss = 8242 – 445 = 7797

$$\begin{aligned}\text{Rotor output} &= \text{Mechanical power developed} - \text{Mechanical loss} \\ &= 7797 - 100 = \mathbf{7697 \text{ W}} \quad (\text{Ans.})\end{aligned}$$

$$\text{Motor efficiency} = \frac{\text{Output}}{\text{input}} \times 100 = \frac{7697}{9100} \times 100 = \mathbf{84.58 \%} \quad (\text{Ans})$$

$$\text{Slip, } S = \frac{\text{Rotor copper loss}}{\text{Rotor input}} = \frac{445}{8242} = \mathbf{0.05399} \quad (\text{Ans})$$

Example 4.6 : A 4 pole, 3-phase, 50 Hz, 400 V induction motor has a delta connected stator and a star connected rotor. Each phase of rotor winding has one-fourth the number of turns on each phase of stator winding. The full load speed is 1455 r.p.m. The rotor resistance is 0.3 ohm, and rotor standstill reactance is 1 ohm per phase. The stator and rotor windings are similar. Stator losses equal 100 W. Friction and windage losses are equal to 50 W. Calculate.

- (i) blocked rotor voltage per phase (ii) rotor current per phase at full load
(iii) total rotor power input at full load (iv) rotor power loss at full load
(v) efficiency.

Solution : Here, $P = 4$; $f = 50 \text{ Hz}$; $V_2 = 400 \text{ V}$; $\frac{N_2}{N_1} = \frac{1}{4}$;

$N = 1455 \text{ r.p.m}$; $R_2 = 0.3 \Omega$; $X_{2s} = 1 \Omega$; Stator loss = 100 W; Mech loss = 50 W
Stator induced e.m.f. per phase, $E_1 = V_L = 400 \text{ V}$ (delta connected)

$$\text{Now, } \frac{E_{2s}}{E_1} = \frac{N_2}{N_1} = \frac{1}{4}$$

$$\therefore \text{Blocked rotor voltage per phase, } E_{2s} = \frac{400}{4} = \mathbf{100 \text{ V}} \quad (\text{Ans})$$

$$\text{Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$$

$$\text{Slip, } S = \frac{N_s - N}{N_s} = \frac{1500 - 1455}{1500} = 0.03$$

$$\text{Rotor current, } I_2 = \frac{SE_{2s}}{\sqrt{(R_2)^2 + (SX_{2s})^2}} = \frac{0.03 \times 100}{\sqrt{(0.3)^2 + (0.03 \times 1)^2}} = \mathbf{9.95 \text{ A}} \quad (\text{Ans})$$

$$\text{Rotor copper loss} = 3I_2^2 R_2 = 3 \times (9.95)^2 \times 0.3 = \mathbf{89 \text{ W}} \quad (\text{Ans})$$

$$\text{Power input to rotor} = \frac{\text{Rotor copper loss}}{\text{Slip}} = \frac{89}{0.03} = \mathbf{2967 \text{ W}} \quad (\text{Ans})$$

Input to the motor = rotor input + stator losses = 2967 + 100 = 3067 W

Output at the shaft = rotor input – rotor copper loss – mech. loss = 2967 – 89 – 50 = 2828 W

$$\text{Efficiency} = \frac{\text{output}}{\text{Input}} \times 100 = \frac{2828}{3067} \times 100 = \mathbf{92.2 \%} \quad (\text{Ans})$$

Example 4.7 : A 60 H.P., 6-pole, 3-phase induction motor delivers load output at 960 r.p.m. at 0.8 power factor when supplied with 400 V. 50 Hz supply. Losses due to windage and friction come to 3 H.P. and the stator losses are 2kW. Find out : (a) Total rotor copper loss ; (b) efficiency, and (c) line current.

Solution : Rotor output = 60 H.P = $60 \times 735.5 = 44130$ W

Mechanical losses = 3 H.P. = $3 \times 735.5 = 2206$ W

Mechanical power developed = Rotor output + Mechanical losses = $44130 + 2206 = 44336$ W

$$\text{Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ r.p.m.}$$

$$\text{Slip, } S = \frac{N_s - N}{N_s} = \frac{1000 - 960}{1000} = 0.04$$

$$\text{Rotor copper loss} = \frac{S}{1-S} \text{ mech. power developed} = \frac{0.04}{1-0.04} \times 44336 = 1931 \text{ W}$$

Stator losses = 2kW = 2000W

$$\begin{aligned} \text{Input to stator or motor} &= \text{Mech. power developed} + \text{Rotor Cu loss} + \text{Stator losses} \\ &= 44336 + 1931 + 2000 = 50267 \text{ W} \end{aligned}$$

$$\text{Efficiency, } \eta = \frac{\text{Output}}{\text{Input}} = \frac{44130}{50267} \times 100 = 87.79\% \text{ (Ans.)}$$

$$\text{Line current, } I_2 = \frac{\text{Input power}}{\sqrt{3} \times \text{Line voltage} \times \text{p.f.}} = \frac{50267}{\sqrt{3} \times 400 \times 0.8} = 90.67 \text{ A (Ans.)}$$

Example 4.8 : A 4-pole, 50 Hz, 3-phase induction motor has an efficiency of 85% for useful output power at the shaft of 17 kW. For this load the total stator losses are 900 W and the windage and friction losses are 1100 W. Calculate the slip, torque developed by the rotor and torque available at the rotor shaft.

Solution : No. of poles, $P = 4$;

Supply frequency, $f = 50$ Hz

Motor efficiency, $\eta = 85\% = 0.85$;

Output power = 17 kW = 17000 W.

Stator losses = 900 W ;

Mechanical losses = 1100 W

$$\text{Input power} = \frac{\text{Output power}}{\eta} = \frac{17000}{0.85} = 20000 \text{ W}$$

$$\text{Stator output or rotor input} = \text{Input power} - \text{Stator losses} = 20000 - 900 = 19100 \text{ W}$$

$$\text{Mech. power developed} = \text{Output power} + \text{Mech. losses} = 17000 + 1100 = 18100 \text{ W}$$

$$\text{Rotor Cu losses} = \text{Rotor input} - \text{Mech. power developed} = 19100 - 18100 = 1000 \text{ W}$$

$$\text{Slip, } S = \frac{\text{Rotor Cu loss}}{\text{Rotor input}} = \frac{1000}{19100} = 0.05235$$

$$\text{Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$$

$$\text{Rotor speed, } N = N_s (1 - S) = 1500 (1 - 0.05235) = 1421.47 \text{ r.p.m.}$$

$$\text{Angular speed, } \omega = \frac{2\pi N}{60} = \frac{2\pi \times 1421.47}{60} = 148.85 \text{ rad/sec.}$$

$$\text{Mech. power developed in the rotor} = \omega T$$

$$\therefore \text{Torque developed, } T = \frac{\text{Mech. power developed}}{\omega} = \frac{18100}{148.85} = \mathbf{121.6 \text{ Nm (Ans.)}}$$

$$\text{Torque at the shaft, } T_m = \frac{\text{Rotor output}}{\omega} = \frac{17100}{148.85} = \mathbf{114.2 \text{ Nm (Ans.)}}$$

Example 4.9 : A 3-phase induction motor has an efficiency of 90% and runs at a speed of 480 r.p.m. The motor is supplied from 400 V mains and it takes a current of 75 A at 0.77 p.f. Calculate the B.H.P. (metric) of the motor and pull on the belt when driving the line shaft through pulley of 0.75 m diameter.

Solution : Supply voltage, $V_L = 400 \text{ V}$; Rotor speed, $N = 480 \text{ r.p.m.}$

Motor efficiency, $\eta = 90\% = 0.9$; Current drawn from mains, $I_L = 75 \text{ A}$

Motor p.f., $\cos \phi = 0.77 \text{ lag.}$ Diameter of pulley, $d = 0.75 \text{ m}$

$$\text{Radius of pulley, } r = \frac{0.75}{2} = 0.375 \text{ m}$$

$$\text{Input power} = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 75 \times 0.77 = 40010 \text{ W}$$

$$\text{Output power} = \text{Input power} \times \eta = 40010 \times 0.9 = 36009 \text{ W}$$

$$\text{B.H.P. of the motor} = \frac{\text{Output power}}{735.5} = \frac{36009}{735.5} = \mathbf{48.958 \text{ (Ans.)}}$$

$$\text{Angular speed, } \omega = \frac{2\pi N}{60} = \frac{2\pi \times 480}{60} = 16\pi$$

$$\text{Torque at the shaft, } T_m = \frac{\text{Output power}}{\omega} = \frac{36009}{16\pi} = 716.376 \text{ Nm}$$

Now, torque, $T_m = \text{Pull on the belt} \times \text{radius of pulley}$

$$\therefore \text{Pull on the belt} = \frac{T_m}{r} = \frac{716.376}{0.375} = 1910.34 \text{ N} = \frac{1910.34}{9.81} = \mathbf{194.73 \text{ kg (Ans.)}}$$

PRACTICE EXERCISE

1. The power input to a 3-phase induction motor is 80 kW. The stator losses total 1.5 kW. Find the total mechanical power developed if the motor is running with a slip of 4%.
(Ans. 75.36 kW)
2. A 50 H.P., 3- ϕ , 6-pole induction motor delivers full load output at 960 r.p.m. at 0.8 p.f. when supplied with 400V, 50Hz supply. Losses due to windage and friction come out to be 2H.P. and stator losses are 2 kW. Find out. (a) total rotor Cu loss ; (b) efficiency and (c) line current.
(Ans. 1594 W; 87.9%; 75.49A)

3. A 400 V, 6 pole, 50 Hz, 3-phase induction motor develops 20 HP inclusive of mechanical losses when running at 965 r.p.m., the power factor being 0.87 lagging. Calculate (i) the slip (ii) rotor copper losses (iii) the total input if the stator losses are 1500 watt (iv) line current and (v) the number of cycles made per minute by the rotor e.m.f.

(Ans. 3.5%; 833.5W; 16743.5W; 27.78A; 1.75 Hz)

4. A 4-pole, 3-phase, 50 Hz induction motor supplies a useful torque of 159 Newton-metre. Calculate at 4% slip : (i) The rotor input ; (ii) Motor input ; (iii) Motor efficiency, if the friction and windage losses total 500 watt and stator losses are 1000 watt.

(Ans. 25497 W; 26497 W; 90.49%)

5. A 440 V, 50 Hz, 6-pole, 3-phase induction motor draws an input power of 81 kW from the mains. The rotor e.m.f. makes 120 complete cycle per minute. Its stator losses are 1 kW and rotor current per phase is 65 ampere. Calculate :

(i) Rotor copper losses per phase ;

(ii) Rotor resistance per phase ;

(iii) Torque developed.

(Ans. 1067 W; 0.2525 ohm; 763.94 Nm)

4.18. TORQUE DEVELOPED BY AN INDUCTION MOTOR

We have already seen that the electrical power of 3-phase induction motor converted into mechanical power is given by the relation ;

$$P_0 = 3I_2^2 R_2 \left(\frac{1-S}{S} \right) \quad \dots(i)$$

also,

$$P_0 = \omega T \quad \dots(ii)$$

Where, ω = angular speed of the rotor in rad/sec. and

T = torque developed by an induction motor in Nm.

Equating eq. (i) and (ii), we get

$$\omega T = 3I_2^2 R_2 \left(\frac{1-S}{S} \right) = 3 \frac{I_2^2 R_2}{S} \cdot \frac{1-S}{\omega}$$

or

$$T = \frac{3}{\omega_2} \cdot \frac{I_2^2 R_2}{S} \quad [\text{since } \omega = \omega_s (1 - S)]$$

where ω_s = angular synchronous speed in rad/sec.

As

$$I_2 = \frac{SE_{2s}}{\sqrt{(R_2)^2 + (SX_{2s})^2}}$$

\therefore

$$T = \frac{3}{\omega_2} \left(\frac{SE_{2s}}{\sqrt{(R_2)^2 + (SX_{2s})^2}} \right)^2 \cdot \frac{R_2}{S}$$

or

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{[(R_2)^2 + (SX_{2s})^2]} = \frac{3}{\omega_s} \frac{E_{2s}^2 R_2 / S}{[(R_2 / S)^2 + (X_{2s})^2]}$$

This is the expression for full load torque.

4.19. CONDITION FOR MAXIMUM TORQUE AND EQUATION FOR MAXIMUM TORQUE

The full load torque developed in an induction motor is given by the relation :

$$T = \frac{3}{\omega_2} \frac{SE_{2s}^2 R_2}{[(R_2)^2 + (SX_{2s})^2]}$$

or
$$T \propto \frac{SR_2}{R_2^2 + S^2 X_{2s}^2} \quad \left(\text{since } \frac{3}{\omega_s} E_{2s}^2 \text{ is constant}\right)$$

The torque developed will be maximum at a particular value of slip. As, slip (S) is a variable quantity, therefore, to obtain the condition for maximum torque, the above expression for torque is differentiated with respect to S and equated to zero.

$$\frac{dT}{dS} = \frac{(R_2^2 + S^2 X_{2s}^2) R_2 - SR_2(0 + 2SX_{2s}^2)}{(R_2^2 + S^2 X_{2s}^2)^2} = 0$$

or
$$(R_2^2 + S^2 X_{2s}^2) R_2 = 2R_2 S^2 X_{2s}^2$$

or
$$R_2^2 = (SX_{2s})^2 \text{ or } R_2 = SX_{2s}$$

or
$$S = R_2/X_{2s} \text{ is the slip at which torque is maximum.}$$

To obtain the expression for maximum torque substitute the value of $R_2 = SX_{2s}$ in the expression for full load torque, we get,

$$\text{Maximum torque, } T_m = \frac{3}{\omega_s} \frac{SE_{2s}^2 (SX_{2s})}{[(SX_{2s})^2 + (SX_{2s})^2]} = \frac{3E_{2s}^2}{2\omega X_{2s}}$$

Thus, the maximum torque is independent of rotor resistance but it is inversely proportional to rotor reactance at standstill (*i.e.*, X_{2s}). Therefore, to achieve higher value of maximum torque, the leakage reactance of the rotor should be kept minimum. This is achieved (i) by placing the rotor conductors very near to the outer periphery of the rotor and (ii) by reducing the air gap between stator and rotor to smallest possible value.

4.20. STARTING TORQUE

At start rotor is stationary and the value of slip is one *i.e.*, $S = 1$.

Thus, to obtain the expression for starting torque, substitute the value of slip, $S = 1$ in the expression of full load torque ;

$$\therefore \text{Starting torque, } T_s = \frac{3}{\omega_s} \frac{E_{2s}^2 R_2}{[(R_2)^2 + (X_{2s})^2]}$$

Sometimes maximum torque is required at start. In that case, in the condition for maximum torque substitute the value of $S = 1$.

$$R_2 = SX_{2s} = X_{2s} \text{ (since } S = 1 \text{ at start)}$$

Thus, to obtain maximum torque at start, the value of rotor resistance must be equal to rotor leakage reactance at standstill. Therefore, at start some external resistance is added in the rotor circuit. This is only possible in case of slip ring induction motors. This is the reason, why slip ring induction motors are

applied where heavy loads are required to be picked up at start such as in lifts, crains, elevators etc. Once the motor picks up the load the external resistance is gradually reduced to zero.

In case of squirrel cage induction motors, the rotor resistance is fixed and is kept quite low in comparison to rotor reactance, otherwise the rotor copper losses would be high and the efficiency of the motor would fall to low value. However to obtain higher starting torque in case of squirrel cage induction motors another cage is embedded in the rotor and the motor is called a *double cage induction motor*.

4.21. TORQUE-SLIP CURVE

The full load torque developed by an induction motor is given by the expression;

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{[R_2^2 + (SX_{2s})^2]}$$

To draw the torque-slip or torque-speed curve the following points are considered :

- (i) At synchronous speed (N_s) ; slip, $S = 0$ and torque $T = 0$.
- (ii) When rotor speed is very near to synchronous speed *i.e.*, when the slip is very low the value of the term $(SX_{2s})^2$ is very small in comparison to R_2^2 [*i.e.*, $(SX_{2s})^2 \ll R_2^2$] and is neglected.

Therefore, torque is given by the expression ;

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{R_2^2} = KS, \text{ or } T \propto S$$

Thus, at low values of slip, torque is approximately proportional to slip S and the torque-slip curve is a straight line, as shown in fig. 4.17.

- (iii) As the slip increases torque increases and attains its maximum value when $S = R_2/X_{2s}$. This maximum value of torque is also known as **break down or pull out torque**.

- (iv) With further increase in slip due to increase in load beyond the point of maximum torque *i.e.* when slip is high, the value of term $(SX_{2s})^2$ is very large in comparison to R_2^2 [*i.e.*, $(SX_{2s})^2 \gg R_2^2$]. Therefore, R_2^2 is neglected as compared to $(SX_{2s})^2$ and the torque is given by the expression.

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{X^2 X_{2s}^2} = K' \frac{1}{S} \text{ or } T \propto \frac{1}{S}$$

Thus, at higher value of slip (*i.e.*, the slip beyond that corresponding to maximum torque), torque is approximately inversely proportional to slip S and the torque-slip curve is a rectangular hyperbola, as shown in fig.4.18.

Thus, with the increase of slip beyond the point of maximum torque, due to increase in load, torque decrease. The result is that the motor could not pick-up the load and slows down and eventually stops. This results in *blocked rotor or short circuited motor*.

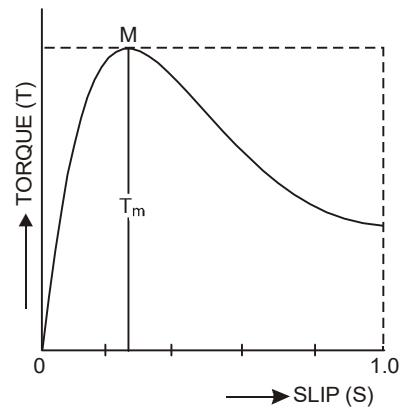


Fig. 4.17: T-S curve

4.22. TORQUE-SPEED CURVE AND OPERATING REGION

The torque-speed curve of an induction motor is shown in fig. 4.18. It is the same curve which is already drawn, the only difference is that speed is taken on the abscissa instead of slip.

From the curve, it is clear that induction motor develops the same torque at point X and Y . However at point X the motor is unstable because with the increase in load speed decreases and the torque developed by the motor also decreases.

Therefore, the motor could not pick up the load and the result is that the motor slows down and eventually stops. The miniature circuit breakers will be tripped open if the circuit has been so protected.

At point Y , the motor is stable because in this region with the increase in load speed decreases but the torque developed by the motor increases. Thus the motor will be in position to pick up the extra load effectively.

Thus, on the torque-speed curve region BC is the unstable region and **region AB is the stable or operating region** of the induction motor as shown in fig.4.18.

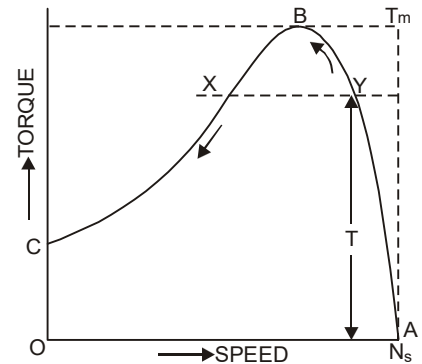


Fig. 4.18: Operating region of T-S curve

Example 4.10 : A 3-phase induction motor has a 4-pole star-connected stator winding. The motor runs at a line voltage of 400 V, 50 Hz supply. The rotor resistance and standstill reactance per phase are 0.15 and 1.0 ohm respectively. The ratio of rotor to stator turns is 0.7. Calculate the total torque at 4% slip.

Solution : Here, $P = 4$; $f = 50 \text{ Hz}$; $R_2 = 0.15 \Omega$; $X_{2s} = 1.0 \Omega$; $S = 4\%$
Supply voltage (line value), $V_L = 400 \text{ V}$

Stator induced voltage (phase value), $E_1 = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$

Ratio of rotor to stator turns, $\frac{T_2}{T_1} = 0.7 = \frac{E_{2s}}{E_1}$

\therefore Rotor induced e.m.f. at standstill, $E_{2s} = 0.7 E_1 = 0.7 \times 231 = 161.7 \text{ V}$

Synchronous speed, $N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$

Synchronous angular speed, $\omega_s = \frac{2\pi N_s}{60} = \frac{2\pi \times 1500}{60} = 50 \pi \text{ rad/sec.}$

Torque developed, $T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{[R_2^2 + (SX_{2s})^2]}$

$$= \frac{3}{50\pi} \times \frac{0.04 \times (161.7)^2 \times 0.15}{[(0.15)^2 + (0.04 \times 1.0)^2]} = 730.78 \text{ Nm} \quad (\text{Ans})$$

Example 4.11 : A 6-pole, 50 Hz, 3-phase induction motor has a rotor resistance of 0.02 ohm per phase and standstill reactance of 0.8 ohm per phase. Calculate the speed at which maximum torque is developed.

Solution : Here, $P = 6$; $f = 50$ Hz ; $R_2 = 0.02 \Omega$; $X_{2s} = 0.8 \Omega$

Condition for maximum torque is ; $R_2 = SX_{2s}$

$$\therefore \text{Torque will be maximum at a slip, } S = \frac{R_2}{X_{2s}} = \frac{0.02}{0.8} = 0.025$$

$$\text{Synchronous speed, } N_s = \frac{120f}{P} = \frac{120 \times 50}{6} = 1000 \text{ r.p.m.}$$

$$\begin{aligned} \text{Speed at which the torque will be maximum, } N &= N_s (1 - S) \\ &= 1000 (1 - 0.025) = \mathbf{975 \text{ r.p.m.}} \quad (\text{Ans}) \end{aligned}$$

PRACTICE EXERCISE

1. A 3-phase induction motor has a 4-pole star-connected stator winding. The motor runs at a line voltage of 200 V, 50 Hz supply. The rotor resistance and standstill reactance per phase are 0.1 and 0.9 ohm respectively. The ratio of rotor to stator turns is 0.67. Calculate the total torque at 4% slip. **(Ans, 40.48 Nm)**
2. A 4-pole, 50 Hz, 3-phase induction motor has a rotor resistance of 0.21 ohm per phase and standstill reactance of 0.7 ohm per phase. Calculate the speed at which maximum torque is developed **(Ans, 1455 r.p.m.)**

4.23. NECESSITY OF A STARTER

The current drawn by a motor from the mains, depends upon the rotor current. The rotor current under running condition is given by the expression ;

$$I_2 = \frac{SE_{2s}}{\sqrt{R_2^2 + (SX_{2s})^2}}$$

$$\text{At start slip } S = 1, \text{ therefore, rotor current. } I_{2s} = \frac{E_{2s}}{\sqrt{R_2^2 + X_{2s}^2}}$$

This current is very large as compared to its full load current. Thus, when a squirrel cage induction motor is directly connected to the supply mains, it draws very large current (nearly 5 to 7 times of the full load current) from the mains. This heavy current may not be dangerous for the motor because it occurs for a short duration of time, but it causes the following affects :

- (i) It produces large voltage drop in the distribution lines and thus affects the voltage regulation of the supply system.
- (ii) It adversely affects the other motors and loads connected to the same lines.

Hence it is not advisable to start large capacity induction motors by direct switching. Rather, such motors should be started by means of some starting device known as *starter*.

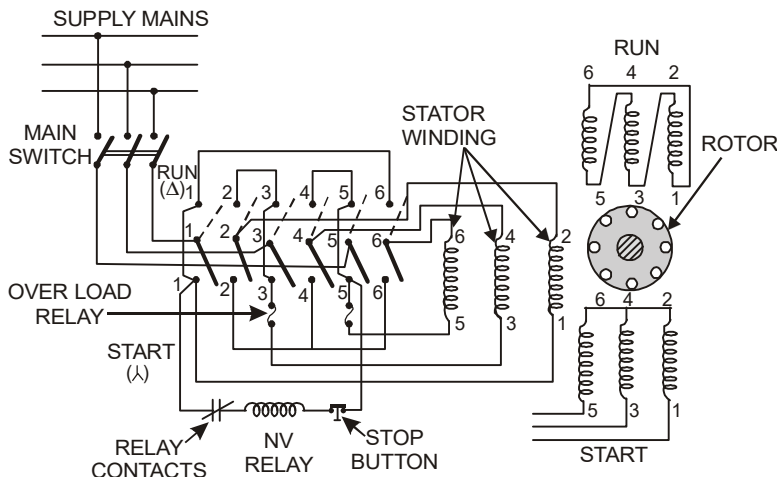


Fig. 4.20: Star-delta starter

the motor are made in star fashion so that reduced voltage is applied across each winding. After the motor attains speed the same windings through a change-over switch, as shown in fig. 4.20 are connected in delta across the same supply. The starter is provided with overload and under voltage protection devices also.

Since at start stator windings are connected in star connection, so voltage across each phase winding is reduced to $1/\sqrt{3}$ of line voltage, therefore, starting current/phase becomes equal to

$$I_{sc}/\sqrt{3} = \text{Starting line current}$$

Starting line current by direct switching with stator winding connected in delta = $\sqrt{3} I_{sc}$

$$\therefore \frac{\text{Line current with star delta starter}}{\text{Line current with direct switching}} = \frac{I_{sc}/\sqrt{3}}{\sqrt{3}I_{sc}} = \frac{1}{3}$$

Thus, it concludes that when a 3-phase motor is started by a star/delta starter, the current drawn by it is limited to 1/3rd of the value that it would draw without starter.

3. Auto-transformer Starter : In the previous method, the current can only be reduced to 1/3 times the short circuit current. Whereas, in this method, the voltage applied across the motor and hence current can be reduced to a very low value at the time of start. At the time of start, the motor is connected to supply through auto-transformer by a 6 pole double throw switch. When the motor is accelerated to about full speed, the operating handle is moved to run position. By this, motor is directly connected to the line as shown in fig.

4.21

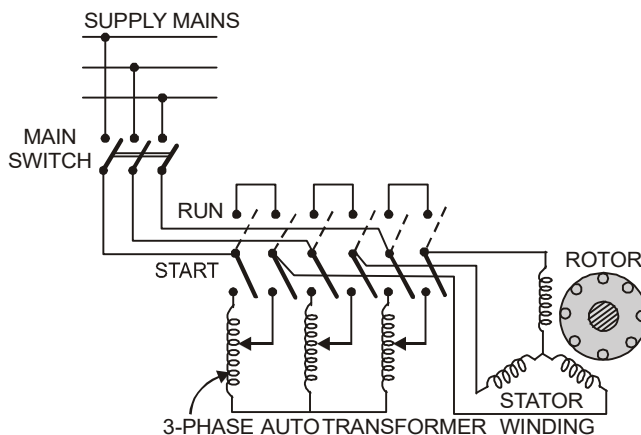


Fig. 4.21: Auto-transformer starter

Overload protection and under voltage protection is provided as explained in the first method.

Although this type of starter is expensive but is most suitable for both the star-connected and delta-connected induction motors. It is most suitable for starting of large motor.

Large size motors draw huge amount of current from the mains if they are connected to mains without starter. However, if they are connected to the mains through star/delta starter, the current is limited to 1/3rd value which is still, so large that it would disturb the other loads connected to the same lines. Hence, to limit the initial rush of current to low values *auto-transformer starters* are preferred. With the help of auto-transformer starters, we can limit the starting current to any predetermined value as explained below :

Let the motor be started by an auto transformer having transformation ratio K .

If I_{sc} is the starting current when normal voltage is applied.

Applied voltage to stator at start = KV

Then motor input current $I_s = KI_{sc}$

Supply current = Primary current of Auto transformer

$$= K \times \text{Secondary current of Auto-transformer} = KKI_{sc} = K^2I_{sc}$$

If 20% (*i.e.* 1/5 th) voltage is applied to the motor through auto-transformer starter, the current

drawn from the mains is reduced to $\left(\frac{1}{5}\right)^2$ *i.e.* 1/25th times.

4.25. STARTING METHOD OF SLIP RING INDUCTION MOTORS

To start a slip ring induction motor, a 3-phase rheostat is connected in series with the rotor circuit through brushes as shown in fig. 4.22. This is called *rotor rheostat starter*. This is made of three separate variable resistors joined together by means of a 3-phase armed handle which forms a star point. By moving the handle equal resistance in each phase can be introduced.

At start, whole of the rheostat resistance is inserted in the rotor circuit and the rotor current is reduced to

$$I_{2s} = \frac{E_{2s}}{\sqrt{(R_2 + R)^2 + (X_{2s})^2}}$$

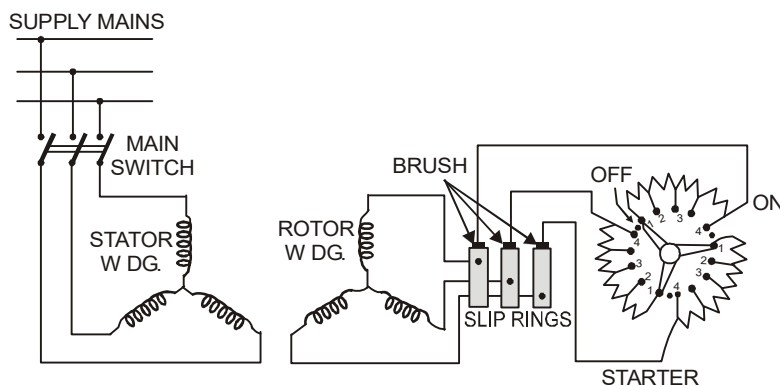


Fig. 4.22: Rotor rheostat starter

Correspondingly it reduces the current drawn by the motor from the mains at start.

When the motor picks up speed the external resistance is reduced gradually and ultimately whole of the resistance is taken out of circuit and slip rings are short-circuited.

By inserting external resistance in the rotor circuit, not only the starting current is reduced but at the same time starting torque is increased due to improvement in power factor :

At starts :

$$\text{Power factor without starter, } \cos \phi_s = \frac{R_2}{\sqrt{(R_2)^2 + (X_{2s})^2}}$$

$$\text{Power factor with starter, } \cos' \phi_s = \frac{(R_2 + R)}{\sqrt{(R_2 + R)^2 + (X_{2s})^2}}$$

$$\text{Hence, } \cos' \phi_s > \cos \phi_s$$

4.26. SPEED CONTROL OF INDUCTION MOTORS

The speed of an induction motor is given by the relation

$$N = N_s (1 - S) \text{ or } N = \frac{120f}{P} (1 - S)$$

Hence the speed of the motor depends upon three factors *i.e.*, frequency, slip and number of poles for which the motor is wound. Thus, the speed of an induction motor can be controlled by changing or controlling any one of these three quantities.

4.27. SPEED CONTROL BY CHANGING THE SLIP

The speed of an induction motor can be changed by changing its slip, and the slip can be changed (1) by changing the rotor circuit resistance (2) by changing the supply voltage and (3) by injecting voltage in the rotor circuit.

1. Speed control by changing the Rotor Circuit Resistance

In the wound type motor the slip may be changed by introducing resistance in the rotor circuit and hence speed is changed.

Torque developed in an induction motor is given by the expression :

$$T = \frac{3}{\omega_s} \frac{E_{2s}^2 R_2 / S}{[(R_2 / S)^2 + (X_{2s})^2]}$$

The torque will remain constant if $\frac{R_2}{S}$ is constant. For a given torque, the slip at which a motor works is proportional to the rotor resistance.

The torque-speed curve (dotted) of a slip ring induction rotor is shown in fig. 4.23. When an external

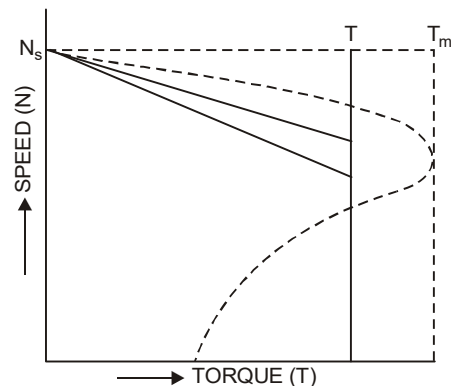


Fig. 4.23: Graph between speed and torque

resistance is added in the rotor circuit, speed decreases for the same torque T , so that ratio $\frac{R_2}{S}$ remains constant.

The disadvantages of this method of speed control are

- (i) *Poor efficiency* : By the introduction of external resistance in the rotor circuit, there is extra power loss ($I_2^2 R$) in the rotor circuit which reduces the overall efficiency of the motor.
- (ii) *Poor speed regulation* : When speed of the induction motor is controlled by adding some external resistance in the rotor circuit, the change in speed is larger when load on the machine changes from one value to the other. Hence the machine operates at a *poor regulation*.

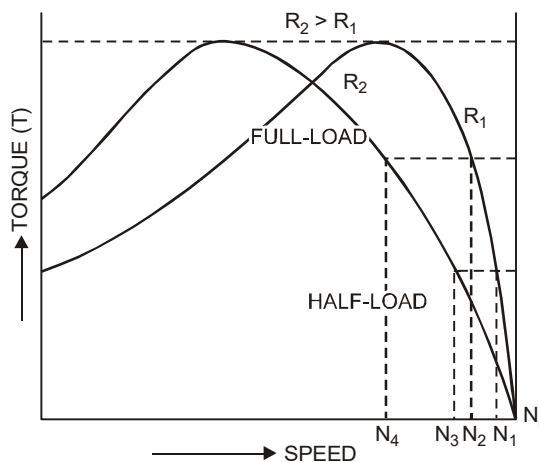


Fig. 4.24: Speed-torque curve keeping R_2/S constant

For illustration, refer to fig 4.24. When the rotor resistance is R_1 and the load on the machine changes from half-load to full-load, the speed of the motor decreases from N_1 to N_2 . However, when some resistance is added in the rotor circuit so that its value becomes R_2 (i.e., $R_2 > R_1$), then the speed changes from N_3 to N_4 when load on the motor changes from half-load to full-load. It is very clear that $N_3 - N_4$ is larger than $N_1 - N_2$. Hence the machine operates at a *poor regulation*.

- 2. Speed Control by Controlling the supply voltage** : Slip or speed of a motor can also be changed by controlling the voltage fed to the motor. We have already seen that the torque developed by the motor is directly proportional to the square of the supply voltage. If the supply voltage is decreased, the torque developed by the motor decreases rapidly ($T \propto V^2$) and to pick-up the load slip increases or speed decreases.

For illustration, look at fig.4.25. At rated voltage and given load, the speed of the motor is N_1 . If the supply voltage is reduced (say to 90%), the speed of the motor decreases to N_2 to pick-up the given load.

This method is never used for the speed control of three-phase large induction motors because the voltage control devices are very costly and bulky. However, this method is usually employed with single-phase induction motors e.g. ceiling fans etc.

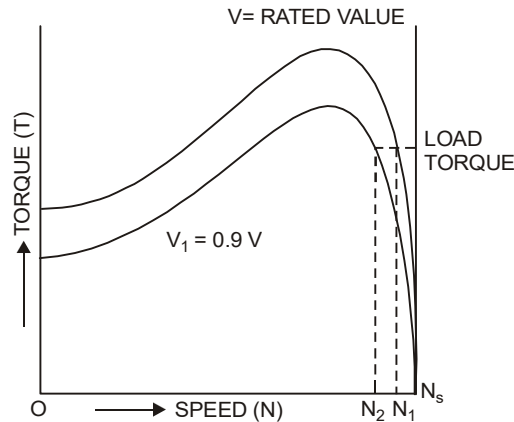


Fig. 4.25: Speed-torque characteristics change in supply voltage

3. **Speed Control by Injecting voltage in the rotor circuit :** The speed of an induction motor can also be controlled by injecting a voltage at slip frequency directly into the rotor circuit. This method was first of all introduced by K.H. Schrage of Sweeden and the motor in which this method is employed is called *Schrage motor*. If the injected e.m.f. has a component directly opposite to the rotor induced e.m.f., the motor speed decreases. On the other hand, if the injected e.m.f. has a component in phase with the rotor induced e.m.f. the motor speed increases and may rises beyond the synchronous speed.

Now a days, schrage motors are not preferred because of their heavy cost and bulky construction but these are still employed in large printing presses like newspaper printing.

4.28. SPEED CONTROL BY CHANGING THE SUPPLY FREQUENCY

The frequency of the power supply is constant, therefore, to control the speed of an induction motor by this method, the induction motor is connected to the alternator operating independently. To control the speed, the frequency of the alternator is changed. This is a costly affair.

Recent improvements in the capabilities of controlled rectifiers (*SCR*) and continued decreases in the cost of their manufacturing, it has made it possible to control the speed of induction motor by controlling the supply frequency fed to the motor. By this method 5 to 10% of rated speed of induction motors can be controlled. However, if the speed is to be controlled beyond this value, the motor has to be designed accordingly.

4.29. SPEED CONTROL BY CHANGING THE POLES

By means of suitable switch, the stator winding connections can be changed in such a manner that the number of stator poles are changed. This changes the actual speed of motor since actual speed of the motor is approximately inversely proportional to the number of poles.

By suitable connections one winding can give two different speeds.

Suppose there are four coils per phase. If these are connected in such a way that they carry current in same direction then it will form eight poles altogether as shown in fig. 4.26 (a). Now if the connections are such that the alternate coils carry current in opposite directions, we get four poles altogether as shown in fig. 4.26(b).

If more than two speeds are required. Two separate winding are housed in same slots and if each is arranged to give two speeds then two windings can give four different speeds.

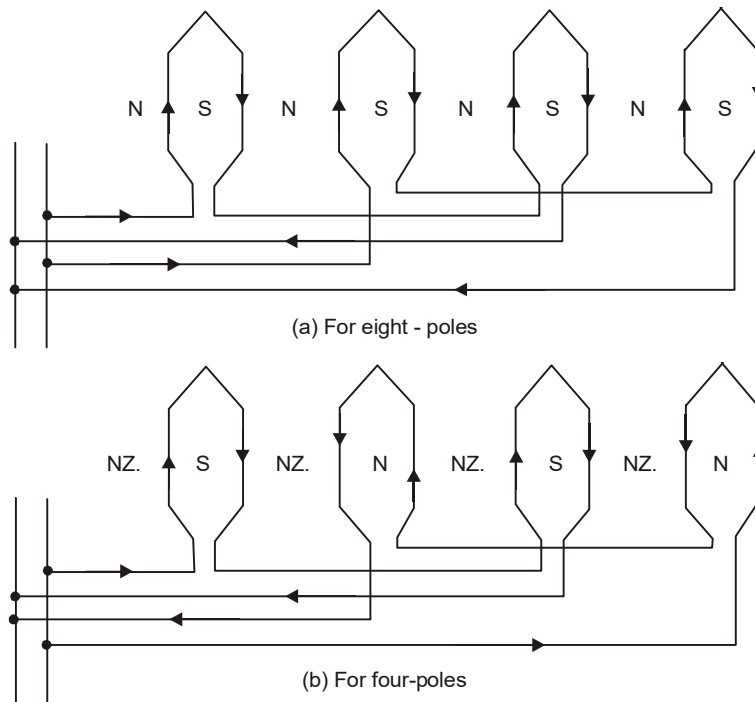


Fig. 4.26: Speed control by changing number of poles

In squirrel cage motors, the rotor poles are adjusted automatically. However, in wound type motors, care has to be taken to change the rotor poles accordingly.

4.30. SPEED CONTROL BY CASCADE METHOD

A method of speed control of induction motor involving two or more motors is known as *cascade method of speed control*. The two machines are mechanically coupled with each other, one of them must be a slip ring induction motor. Mostly both slip ring motors are used having transformation ratio equal to unity. In this case supply is connected to the stator of one of the induction motor and the induced e.m.f. of the rotor from slip rings is fed to the stator or rotor of the second induction motor.

If P_1 and P_2 are the number of poles of the two machines and f is the supply frequency, then the set can give the following different speeds :

- (i) When machine I works alone :

$$\text{The synchronous speed} = \frac{120f}{P_1}$$

- (ii) When machine II works alone ;

$$\text{The synchronous speed} = \frac{120f}{P_2}$$

- (iii) When machine I and II are connected in cumulative cascade *i.e.*, the torque of the two motors are in same direction ;

$$\text{The synchronous speed of the set} = \frac{120f}{P_1 + P_2}$$

- (iv) When machine I and II are connected in differential cascade *i.e.*, the torque of the motors are in opposite direction ;

$$\text{The synchronous speed of the set} = \frac{120f}{P_1 - P_2}$$

4.31. APPLICATIONS OF THREE-PHASE INDUCTION MOTORS

The applications of squirrel cage induction motors and slip-ring (phase wound) induction motors are given below :

1. **Squirrel cage induction motors** : These motors are mechanically robust and are operated almost at constant speed. These motors operate at high power factor and have high over load capacity. However, these motors have low starting torque. (*i.e.*, these motors can not pick-up heavy loads) and draw heavy current at start. On the bases of these characteristics, these motors are best suited for :

(i) Printing machinery	(ii) Flour mills
(iii) Saw mills	(iv) Shaft drives of small industries
(v) Pumps	(vi) Prime-movers with small generators etc.
2. **Slip-ring (or phase-wound) induction motors** : These motors have all the important characteristics (advantage) of squirrel cage induction motors and at the same time have the ability to pick-up heavy loads at start drawing smaller current from the mains. Accordingly these motors are best suited for ;

(i) Rolling mills	(ii) Lifts and hoists
(iii) Big flour mills	(iv) Large pumps
(iv) Line shafts of heavy industries	(vi) Prime-moves with medium and large generators.

4.32. NATURE OF FIELD PRODUCED IN SINGLE PHASE INDUCTION MOTORS

The field produced in a single-phase induction motor can be explained by *double revolving field* theory which is given below :—

This theory is based on the “Ferraris Principle” that pulsating field produced in single phase motor can be resolved into two components of half the magnitude and rotating in opposite direction at the same synchronous speed.

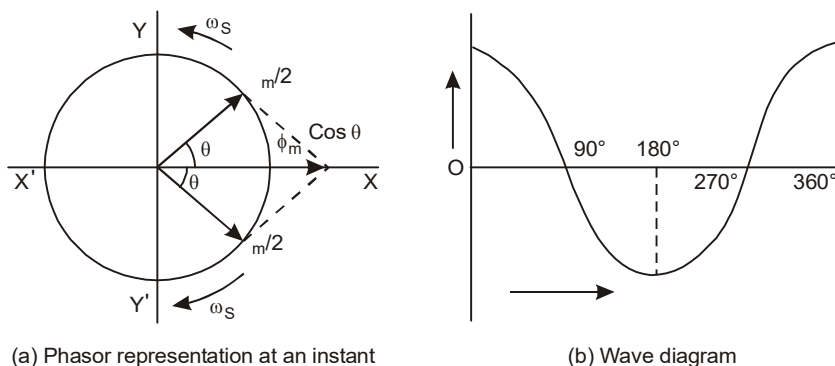


Fig. 4.27: Two- field revolving theory

Thus the alternating flux which passes across the air gap of single phase induction motor at stand still consists of combination of two fields of same strength which are revolving with same speed, one in clockwise direction and the other in anticlockwise direction. The strength of each one of these fields will be equal to one half of the maximum field strength of the actual alternating field as shown in fig. 4.27 (a).

Let ϕ_m be the pulsating field which has two components each of magnitude $\phi_m/2$. Both are rotating at the same angular speed ω_s rad/sec but in opposite direction as shown in fig. 4.27 (a). The resultant of the two fields is $\phi_m \cos \theta$. This shows that resultant field varies according to cosine of the angle θ . The wave shape of the resultant field is shown in fig. 4.27 (b).

Thus an alternating field can be represented by the two fields each of half the magnitude rotating at same angular speed of ω_s radians/sec but in opposite direction.

4.33. TORQUE PRODUCED BY 1-PHASE INDUCTION MOTOR

The two revolving fields will produce torques in opposite directions. Let the two revolving fields be field No. 1 and field No. 2 revolving in clockwise and anticlockwise direction produces torque in clockwise direction, whereas, the anticlockwise field produces torque in anticlockwise direction. The clockwise torque is plotted as positive and anticlockwise as negative. At stand still, slip for both fields is one. Synchronous speed in clockwise direction will give condition of zero slip for field 1 but it will give slip = 2 for field No. 2. Similarly synchronous speed in a counter clockwise direction will give condition of zero slip for field 2 but slip = 2 for field No. 1. The resultant torque developed in the rotor is shown by the curve passing through zero position as shown in fig. 4.28. Now if we look at the resultant torque we see that the starting torque (torque at slip = 1) is zero. And except at starting there is always some magnitude of resultant torque, which shows if this type of motor once started in any direction it will develop torque in that direction and rotor will pick-up the required speed.

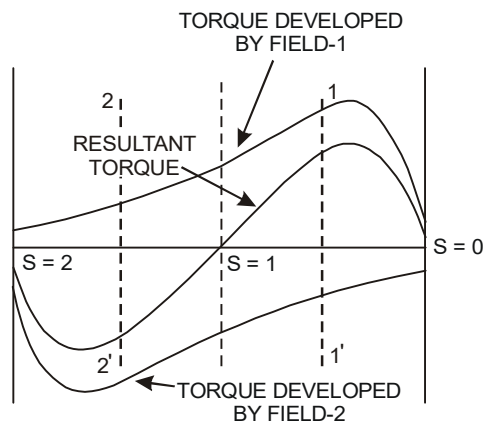


Fig. 4.28: Torque developed by two fields

The above analysis shows that single phase induction motor with single winding develops no starting torque but if the rotor is rotated in any direction by some auxiliary means it will develop torque in the same direction in which it has been rotated to start. So the problem is to find out the auxiliary means to give the starting torque to the motor.

4.34. TYPES OF 1-PHASE AC MOTORS

Various methods (means) are employed to obtain the starting torque in single-phase induction motors. Accordingly they are classified as ;

1. Split phase motors
2. Shaded pole motors
3. A.C. Series motors or Commutator motors.

4.35. SPLIT PHASE MOTORS

Construction

The outer frame and stator core of a split-phase motor is similar to the outer frame and stator core of a 3-phase induction motor. The starting and running windings are placed in the stator slots. Both the windings are put in parallel as shown in fig. 4.29(a). The purpose is to get two different currents sufficiently displaced from each other so that a revolving field is produced. The main winding which is highly inductive is connected across the line in the usual manner. The auxiliary or starting winding has a greater resistances and lesser reactance as compared to main winding.

The current in the starting winding I_s lags the supply voltage by lesser angle ϕ_s whereas the current in the main winding I_m being highly inductive lags the supply voltage by greater angle ϕ_m as shown in figure 4.29(b). The two currents have a phase difference of θ electrical. Thus, a revolving

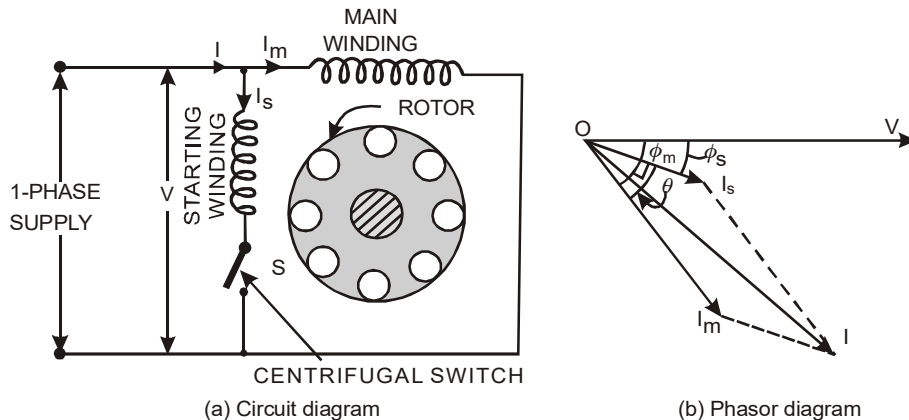


Fig. 4.29: Split-phase motor

field is set-up in the stator and a starting torque is developed in the rotor. Consequently rotor starts rotating and picks up the speed. A centrifugal switch which is normally closed is incorporated in series with the starting winding. When the motor attains a speed about 75% of synchronous speed, the centrifugal switch is opened automatically with the help of centrifugal force and puts the starting winding out of circuit. It is important that the centrifugal switch should open otherwise the auxiliary winding being made of thin wire will be over heated and may damage.

Performance and characteristics : A typical torque speed characteristics are shown in fig. 4.30, the starting torque is about twice the full load torque. The current at start is about 6 to 8 times. The speed falls with increase in load by only about 5% to 7% otherwise it is a constant speed motor. Speed is governed by the relation.

$$N_s = \frac{120 f}{P} \text{ r.p.m.}$$

Actual speed is less than synchronous speed N_s . For the same weight its rating is about 60% to that of the poly phase induction motor. It has lower p.f. and lesser efficiency. P.f. is about 0.6 and efficiency is also about 60%.

Applications : As starting torque is not so high so this machine is not used where large starting torque is required. It is used for smaller sizes about 0.25 h.p. It is used in washing machines, fans, blowers, wood working tools, grinders and various other low starting torque applications.

Reversal of direction of rotation : The direction of rotation of a 1-phase (split phase) induction motor can be reversed by reversing (interchanging) the connections of either starting winding or running winding.

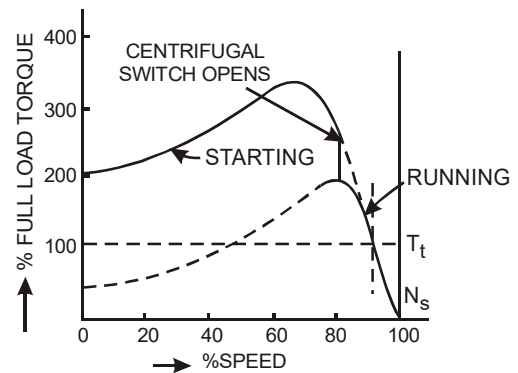



Fig. 4.30: Torque-speed curve

4.36. CAPACITOR MOTORS


It is also a split phase motor. In this motor, a capacitor is connected in series with the starting winding. This is an improved form of the above said split phase motor. In these motors, the angular displacement between I_s and I_m can be made nearly 90° and high starting torques can be obtained since starting torque is directly proportional to sine of angle θ . The capacitor in the starting winding may be connected permanently or temporarily. Accordingly, capacitor motors may be

1. Capacitor start motors.
2. Capacitor run motors.
3. Capacitor start and capacitor run motors.

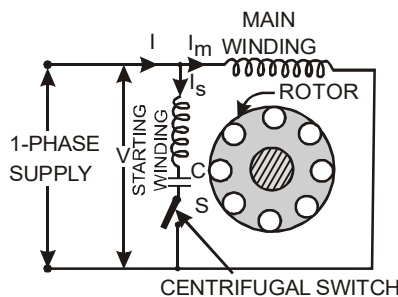1. **Capacitor start motors :** In the capacitor start induction motor capacitor C is of large value such that the motor will give high starting torque. Capacitor employed is of short time duty rating.



(a) Circuit diagram

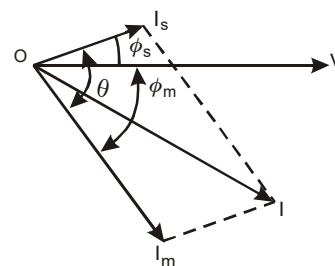

(a) Phasor diagram

Fig. 4.31: Capacitor start motor

Capacitor is of electrolytic type. Electrolytic capacitor C is connected in series with the starting winding along with centrifugal switch S as shown in fig.4.31 (a). When the motor attains the speed of about 75% of synchronous speed starting winding is cut-off. The construction of the motor and winding is similar to usual split phase motor. It is used where high starting torque is required such as refrigerators.

Performance and characteristics : Speed is almost constant with in 5% slip. This type of motor develops high starting torque about 4 to 5 times the full load torque. It draw low starting current. A typical torque speed curve is shown in fig.4.32. The direction of rotation can be changed by interchanging the connection of either starting or running winding.

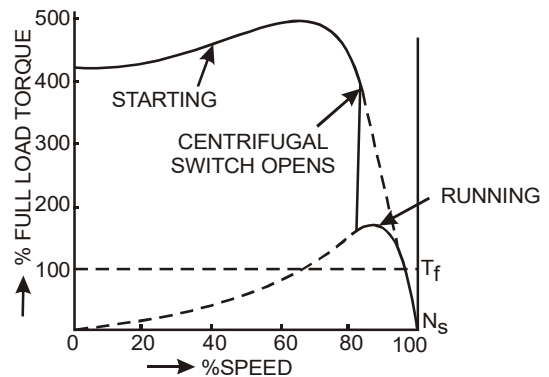


Fig. 4.32: Torque-speed characteristics of capacitor start motor

- 2. Capacitor run motors (fan motors) :** In these motors, a paper capacitor is permanently connected in the starting winding, as shown in fig. 4.33 (a). In this case, electrolytic capacitor can not be used since

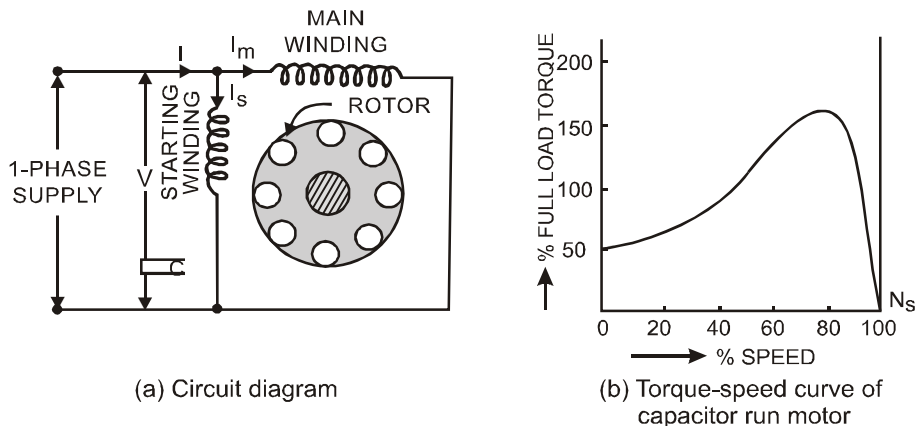


Fig. 4.33: Capacitor run motor

this type of capacitor is designed only for short time rating and hence can not be permanently connected in the winding. Both main as well as starting winding is of equal rating.

Performance and characteristics. Starting torque is lower about 50 to 100% of full load torque. Power factor is improved may be about unity. Efficiency is improved to about 75%. A typical characteristics have been shown in fig. 4.33 (b). It is usually used in fans, room coolers, portable tools and other domestic and commercial electrical appliances.

- 3. Capacitor start and capacitor run motors :** In this case, two capacitors are used one for starting purpose and other for running purpose as shown in fig. 4.34 (a). The capacitor used for starting purpose C_S is of electrolytic type and is disconnected from the supply when the motor attains 75% of synchronous speed with the help of centrifugal switch S . Whereas, the other capacitor C_R which remains in the circuit of starting winding during running condition is a paper capacitor. This type of motor gives best running and starting operation. Starting capacitor C_S which is of higher value than the value of running capacitor C_R .

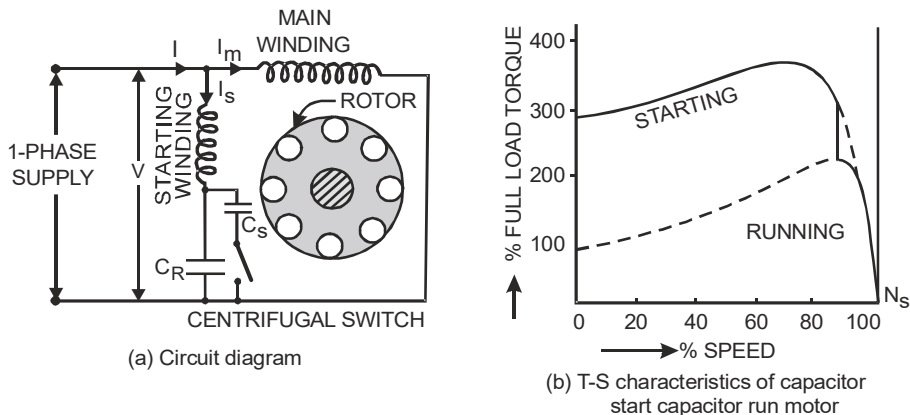


Fig. 4.34: Capacitor start capacitor run motor

Performance and characteristics : Such motors operate as two phase motors giving best performance and noiseless operation. Starting torque is high, starting current is low and give better efficiency and higher p.f. The only disadvantage is high cost. A typical torque speed curve is shown in fig.4.34 (b).

4.37. SHADED POLE MOTOR

Construction

Shaded pole motor is constructed with salient poles in stator. Each pole has its own exciting winding as shown in fig.4.35.(a). A 1/3rd portion of each pole core is surrounded by a copper strip

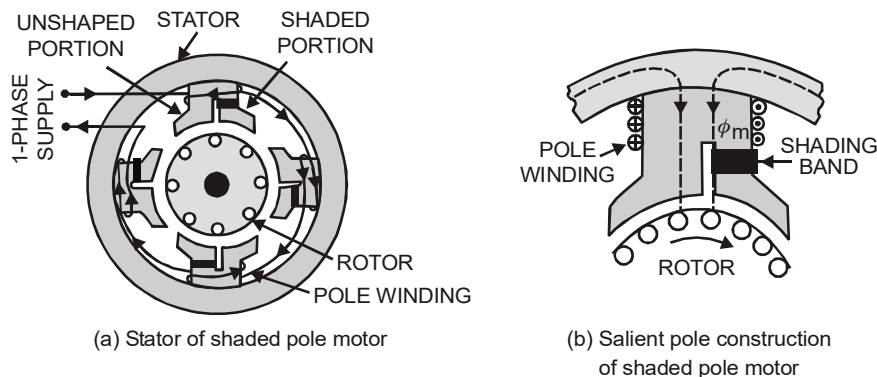


Fig. 4.35: Shaded pole motor

forming a closed loop called the shading band as shown in fig.4.35 (a) and (b). Rotor is usually squirrel cage type.

When a single phase supply is given to the stator (exciting) winding, it produces alternating flux. When the flux is increasing in the pole, a portion of the flux attempts to pass through the shaded portion of the pole. This flux induces voltage and hence current in the copper ring, and by Lenz's law the direction of current is such that it opposes the causes *i.e.* increase of flux in shaded portion. Hence in the beginning, the greater portion of flux passes through unshaded side of each pole and resultant lies on unshaded side of the pole. When the flux reaches its maximum value, its rate of change is zero, thereby the e.m.f. and

hence current in the shading coil becomes zero. Flux is uniformly distributed over the pole phase and the resultant field lies at the centre of the pole. After that the main flux tends to decrease, the current induced in the shading coil now tends to increase the flux on the shaded portion of the pole and resultant lies on the shaded portion of the pole as shown in fig.4.36.

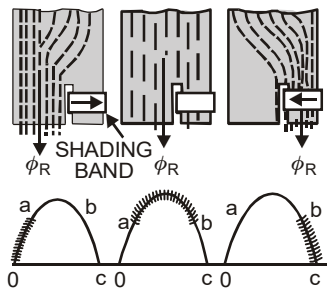


Fig. 4.36: Flux distribution in the pole during half cycle

Hence, a revolving field is set up which rotates from unshaded portion of the pole to the shaded portion of the pole as marked by the arrow head in fig. 4.36. Thus, by electromagnetic induction, a starting torque develops in the rotor and the rotor starts rotating. After that its rotor picks up the speed.

Performance and characteristics : A typical speed torque characteristics is shown in fig. 4.37. Starting torque is very small about 50% of full load torque. Efficiency is low because of continuous power loss in shading coil. These motors are used for small fans, electric clocks, gramophones etc.

Its direction of rotation depends upon the position of the shading coil, *i.e.*, which portion of the pole is wrapped with shading coil. The direction of rotation is from unshaded portion of the pole to the shaded portion. Its direction of rotation cannot be reversed unless the position of the poles is reversed.

4.38. A.C. SERIES MOTOR OR COMMUTATOR MOTOR

When a 1-phase a.c. supply is given to a d.c. series motor, a unidirectional torque is developed in it. In fact, during positive half cycle, same current flows in the series field winding and armature

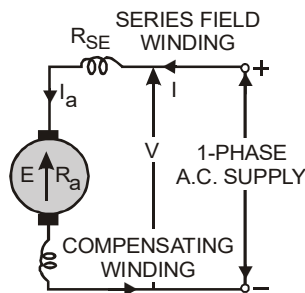


Fig. 3.38: Circuit diagram of ac series motor

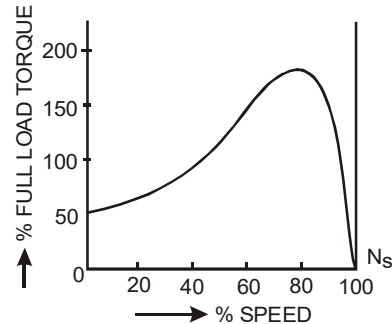


Fig. 4.37: Torque-speed characteristics of shaded-pole motor

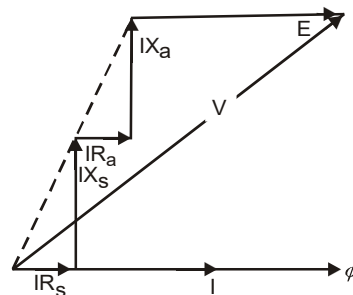


Fig. 4.39: Voltage distribution

winding which develops a torque in one direction (say clockwise). During the negative half cycle, current flowing through series field winding is reversed and at the same time current flowing through the armature also reverses, therefore, torque is developed in the same direction (*i.e.* clockwise direction). Thus, a continuous rotation is obtained.

Mathematically we know

Torque in D.C. series motors, $T \propto \phi_{se} I_a$ where ϕ_{se} is the series field winding flux and I_a is the armature current.

Now when A.C. supply is given to series motor $T \propto \phi_{se} I_a$ for positive half cycle. For negative half cycle $T \propto (-\phi_{se})(-I_a) \propto \phi_{se} I_a$. Thus same torque is produced during positive and negative half cycle. However, some modifications are necessary in a d.c. series motor for its satisfactory operation on a.c. which are given below :

- (1) The iron structure of field and yoke are laminated.
- (2) The series field winding is so designed that it will produce relatively small m.m.f as compared to d.c. This is done by reducing the number of turns. The smaller field m.m.f would result in reduced air gap flux. Therefore, in order to develop the necessary torque the number of armature conductors have to be increased proportionately.
- (3) Increase in armature conductors would result in increased inductive reactance of the armature so the net inductive reactance may not be reduced. In order to overcome this difficulty compensating winding is connected in series with armature as shown in fig.4.38. This completely neutralises the inductive effect of the armature winding.
- (4) The reluctance of the magnetic circuit is reduced to have high flux with reduced m.m.f. So magnetic material used should be of high permeability and air gap should be small.

As shown in the vector diagram (fig. 4.39) large voltage drop occurs in resistance and reactance of the armature and field winding. Voltage left for operation is only E .

$$\text{Where } \bar{E} = \bar{V} - (\bar{I}R_S + \bar{I}X_S + \bar{I}R_a + \bar{I}X_a)$$

Where $I R_S \longrightarrow$ voltage drop in series winding resistance

$I X_S \longrightarrow$ voltage drop in series winding reactance

$I R_a \longrightarrow$ voltage drop in armature resistance

$I X_a \longrightarrow$ voltage drop in armature reactance.

Performance and characteristics : The speed-torque characteristic for d.c. and a.c. series motors are shown in fig.4.40. The torque varies as square of the current and the speed varies inversely proportional to the current approximately. The efficiency will not be good as that of corresponding d.c. machine because of greater eddy current loss and effects of p.f.

These motors have their wide applications where high speed (20000 r.p.m.) is required *e.g.* mixer grinders, blowers, hair dryers etc.

4.39. UNIVERSAL MOTOR

A motor which can be operated on ac as well as on dc supply at the rated voltage is called **universal motor**.

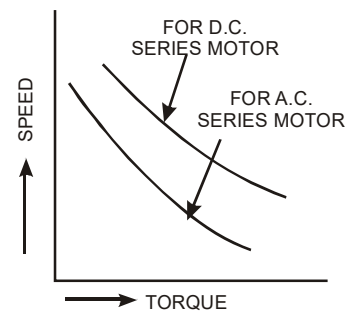


Fig. 4.40: Torque-speed characteristics

Basically, universal motor is an ac series motor. It is just an improved form of a dc series motor. The core size of an universal motor is more than the core size of a dc series motor of the same rating.

Construction

The motor has two main parts namely.

1. Stator and 2. Rotor.

1. Stator. It is the stationary part of the motor. It consists of *magnetic frame* (or *yoke*), *pole core* and *pole shoe* and *field* or *exciting winding* as shown in fig. 4.41.

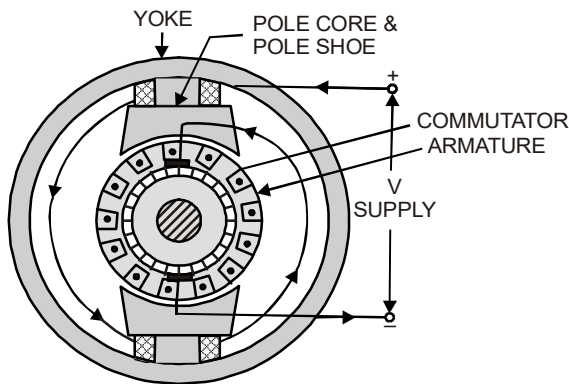


Fig. 4.41: Universal motor

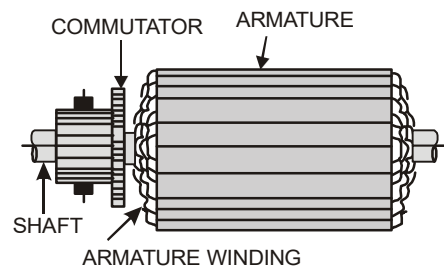


Fig. 4.42: Rotor of a universal motor

The magnetic frame, pole core and pole shoe are made of silicon steel stampings. The stampings are insulated from each other by varnish layer. The hysteresis losses are very small in silicon steel and eddy current losses are reduced due to stampings. The field winding made of enameled copper is wound around the poles to produce the required flux..

2. Rotor. It is the rotating part of the motor. It consists of *shaft*, *armature*, *armature winding* and *commutator*, as shown in fig.4.42.

Shaft is a part of rotor which transfers mechanical power or energy to the load. It is made-up of mild steel. Armature is made-up of stampings of silicon steel material since it is to carry the magnetic field. It is keyed to the shaft. Slots are cut at its outer periphery to accommodate armature winding. The ends of armature winding are braced to the commutator segments. Commutator is made-up of wedge shaped segments forming a ring. The wedges are insulated from each other by an insulating layer of micanite. The commutator is also keyed to the shaft.

Carbon brushes are pressed over the commutator surface to deliver current to the machine.

Principle

When a current carrying conductor is placed in the magnetic field, a force is exerted on it and torque develops. In other words, when the rotor field produced by the rotor current carrying conductors, tries to come in line with the main field, torque develops and rotor rotates.

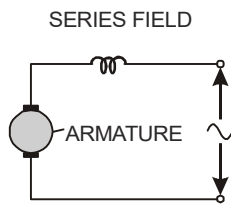


Fig.4.43: Circuit diagram

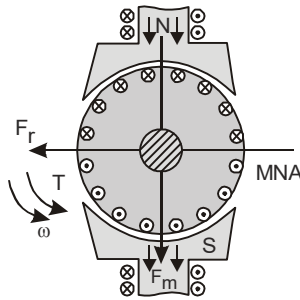


Fig.4.44: Torque developed during positive half cycle

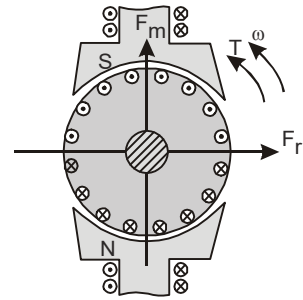


Fig.4.45: Torque developed during negative half cycle

Working

The armature winding and stator field winding both are connected in series, as shown in fig. 4.43. When 1-phase, ac supply is given to the motor, current flows through the field winding and armature winding. The field winding sets up main stator field F_m , and the armature winding sets up rotor field F_r as shown in fig.4.44. Rotor field F_r tries to align itself with the main field F_m and an anticlockwise torque is produced.

During negative half cycle, the direction of flow of current in the field winding as well as in the armature winding is reversed, as shown in fig.4.45. The two windings set up their fields in the direction as shown in fig. 4.45, again anticlockwise torque is produced in the rotor. Thus, unidirectional torque is produced in the motor.

To obtain continuous torque, commutator reverses the direction of flow of current in the coil or conductors which cross the magnetic neutral axis (MNA)

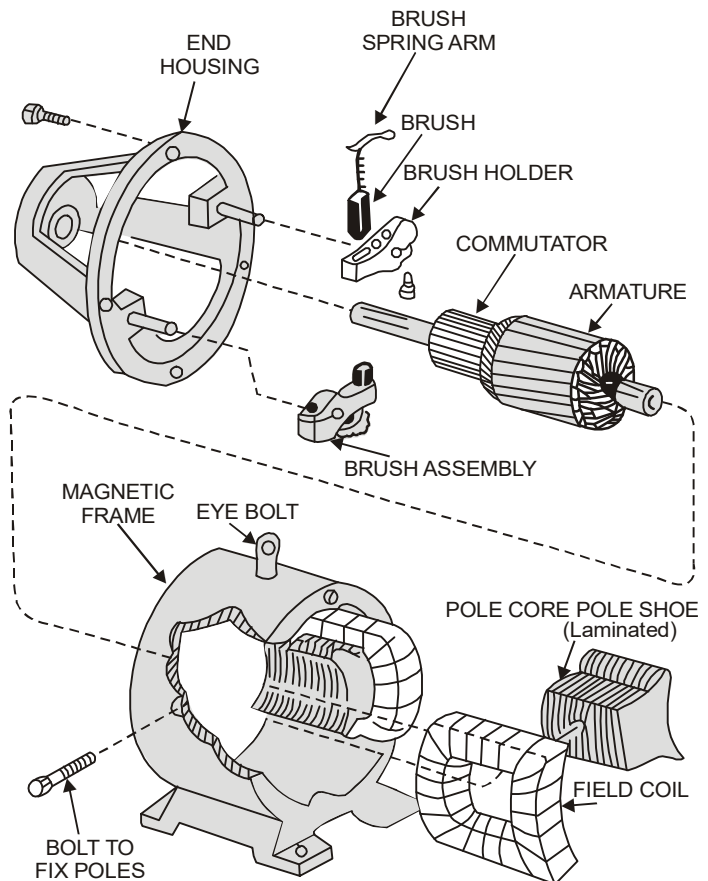


Fig. 4.46: Dis-assembled view of a dc machine

Applications : In large sizes of $\frac{3}{4}$ HP, these are used in vacuum cleaners and industrial sewing machines. In smaller sizes of $\frac{1}{4}$ HP or less, these are used in electric hand drills, mixers, can openers, blenders, electric shavers, hair dryers etc.

4.40. D.C. MOTOR

A machine which converts mechanical power into d.c. electrical power is called a d.c. generator. The same machine when used to convert d.c. electrical power into mechanical power is known as a d.c. motor. From construction point of view there is no difference between a d.c. generator and motor. The d.c. motors are very useful where wide range of speeds and good speed regulation is required such as electric fraction.

4.41. MAIN CONSTRUCTIONAL FEATURES

The complete assembly of various parts in a scattered form of a d.c. machine is shown in fig.4.46. The essential parts of a d.c. machine are described below :

1. Magnetic frame or Yoke :

The outer cylindrical frame to which main poles and inter poles are fixed and by means of which the machine is fixed to the foundation is called the *yoke*. It serves two purposes :

- (i) It provides mechanical protection to the inner parts of the machine.
- (ii) It provides a low reluctance path for the magnetic flux.

The yoke is made of cast iron for smaller machines and for larger machines, it is made of cast steel or fabricated rolled steel since these materials have better magnetic properties as compared to cast iron.

2. Pole core and pole shoes : The pole core and pole shoes are fixed to the magnetic frame or yoke by bolts. They serve the following purposes :

- (i) They support the field or exciting coils.
- (ii) They spread out the magnetic flux over the armature periphery more uniformly.
- (iii) Since pole shoes have larger X-section, the reluctance of magnetic path is reduced.

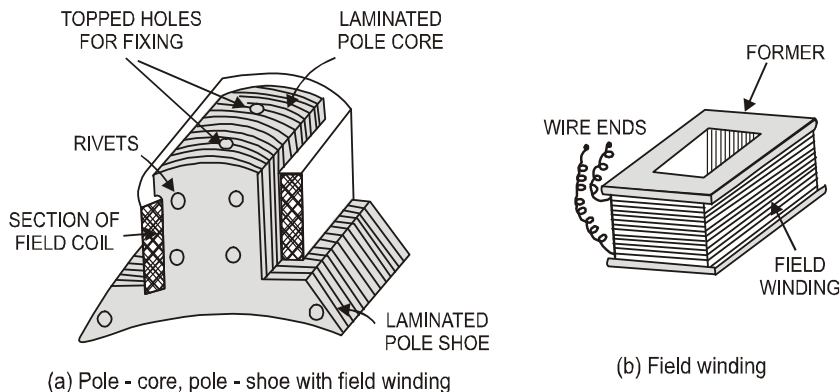


Fig. 4.47: Pole with field winding

Usually, the pole core and pole shoes are made of thin cast steel or wrought iron laminations which are riveted together under hydraulic pressure as shown in fig.4.47 (a).

3. **Field or Exciting coils :** Enamelled copper wire is used for the construction of field or exciting coils. The coils are wound on the former [see fig 4.47(b)] and then placed around the pole core as shown in fig 4.47(a). When direct current is passed through the field winding, it magnetises the poles which produce the required flux. The field coils of all the poles are connected in series in such a way that when current flows through them, the adjacent poles attain opposite polarity as shown in fig. 4.48.

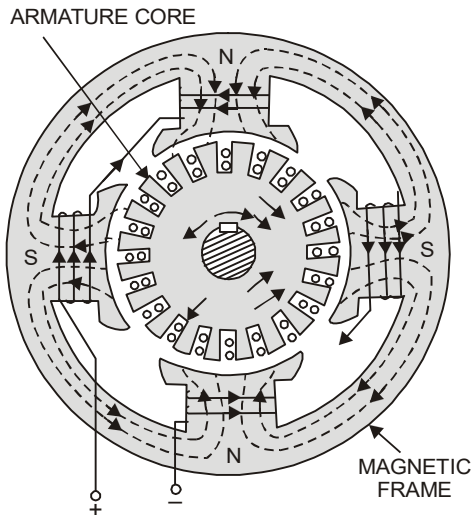


Fig. 4.48: Stator and armature

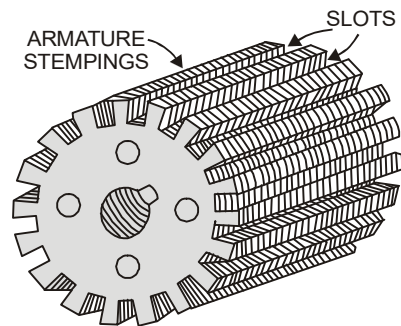


Fig. 4.49: Armature of a dc machine

4. **Armature core :** It is cylindrical in shape and keyed to the rotating shaft. At the outer periphery slots are cut, as shown in fig.4.49, which accommodate the armature winding. The armature core serves the following purposes :

- (i) It houses the conductors in the slots. (ii) It provides an easy path for magnetic flux.

Since armature is a rotating part of the machine, reversal of flux takes place in the core, hence hysteresis losses are produced. To minimise these losses silicon steel material is used for its construction. The rotating armature cuts across the magnetic field which induces an e.m.f in it. This e.m.f. circulates eddy currents which results in eddy current loss in it. To reduce these losses, armature core is laminated, in other words we can say that about 0.3 to 0.5 mm thick stampings are used for its construction. Each lamination or stamping is insulated from the other by varnish layer (see fig.4.49).

5. **Armature winding :** The insulated conductors housed in the armature slots are suitably connected. This is known as armature winding. The armature winding is the heart of a d.c. machine. It is a place where conversion of power takes place *i.e.* in case of generator, mechanical power is converted into electrical power and in case of motor, electrical power is converted into mechanical power. On the basis of connections, there are two types of armature windings named (i) Lap winding and (ii) Wave winding.

- (i) *Lap winding* : In lap winding, the conductors are connected in such a way that number of parallel paths are equal to the number of poles. Thus, if machine has P poles and Z armature conductors, then there will be P parallel paths, each path will have Z/P conductors in series. In this case, the number of brushes is equal to the number parallel paths. Out of which half the brushes are positive and the remaining (half) are negative.
- (ii) *Wave winding* : In wave winding, the conductors are so connected that they are divided into two parallel paths irrespective of the number of poles of the machine. Thus, if machine has Z armature conductors, there will be only two parallel paths each having $Z/2$ conductors in series. In this case, the number of brushes is equal to two *i.e.* number of parallel paths.

6. Commutator : It is the most important part of a d.c machine and serves the following purposes :-

- (i) It connects the rotating armature conductors to the stationary external circuit through brushes.
- (ii) It converts the alternating current induced in the armature conductors into unidirectional current in the external load circuit in generator action, whereas, it converts the alternating torque into unidirectional(continuous)

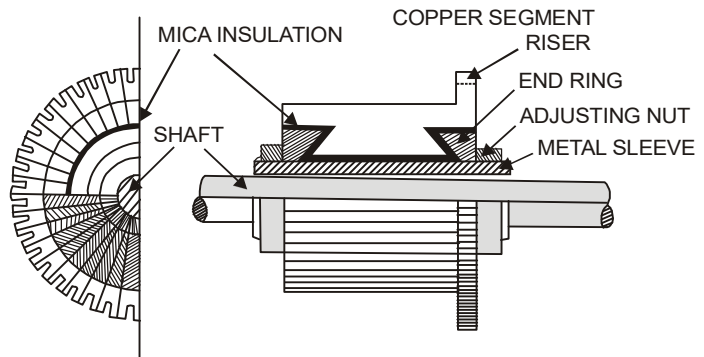


Fig. 4.50: Commutator

torque produced in the armature in motor action.

The commutator is of cylindrical shape and is made up of wedge-shaped hard drawn copper segments. The segments are insulated from each other by a thin sheet of mica. The segments are held together by means of two V-shaped rings that fit into the V-grooves cut into the segments. Each armature coil is connected to the commutator segment through riser. The sectional view of the commutator assembly is shown in fig. 4.50

- 7. Brushes :** The brushes are pressed upon the commutator and form the connecting link between the armature winding and the external circuit. They are usually made of high grade carbon because carbon is conducting material and at the same time in powdered form provides imbricating effect on the commutator surface. The brushes are held in particular position around the commutator by brush holders and rocker.
- 8. Brush rocker :** It holds the spindles of the brush holders. It is fitted on to the stationary frame of the machine with nut and bolts. By adjusting its position, the position of the brushes over the commutator can be adjusted to minimize the sparking at the brushes.
- 9. End housings :** End housings are attached to the ends of the main frame and support bearings. The front housing supports the bearing and the brush assemblies whereas the rear housing usually supports the bearing only.
- 10. Bearings :** The ball or roller bearings are fitted in the end housings. The function of the bearings is to reduce friction between the rotating and stationary parts of the machine. Mostly high carbon steel is used for the construction of bearings as it is very hard material.

- 11. Shaft :** The shaft is made of mild steel with a maximum breaking strength. The shaft is used to transfer mechanical power from or to the machine. The rotating parts like armature core, commutator, cooling fan etc. are keyed to the shaft.

4.42. ARMATURE RESISTANCE

The resistance between the armature terminals is called *armature resistance*. It is generally represented by R_a . The value of armature resistance is usually quite small (less than one ohm). Armature resistance depends upon the following factors :

- Length, area of cross-section and material of armature winding.
- Type of armature winding *i.e.* lap or wave winding. This will show the manner in which the conductors (*i.e.* their series-parallel combination) are connected.

4.43. WORKING PRINCIPLE OF D.C. MOTORS

The operation of a d.c motor is based on the principle that when a current carrying conductor is placed in a magnetic field, a mechanical force is experienced by it. The direction of this force is determined by *Fleming's Left Hand Rule* and its magnitude is given by the relation:

$$F = Bil \text{ newton}$$

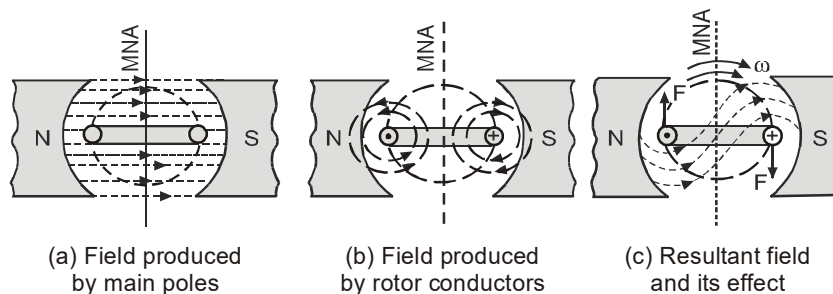


Fig. 4.51: Magnetic field developed in a dc machine

For simplicity, consider only one coil of the armature placed in the magnetic field produced by a bipolar machine [see fig 4.51(a)]. When d.c. supply is connected to the coil, current flows through it which sets up its own field as shown in fig 4.51 (b). By the interaction of the two fields (*i.e.* field produced by the main poles and the coil), a resultant field is set up as shown in fig 4.51 (c). The tendency of this is to come to its original position *i.e.* in straight line due to which force is exerted on the two coil sides and torque develops which rotates the coil.

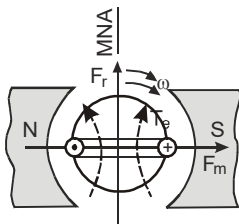


Fig. 4.52: Position of axis of main field and rotor field

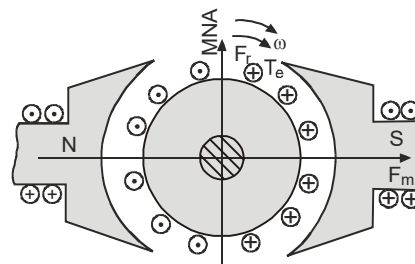


Fig. 4.53: Torque development

Alternately, it can be said that the main poles produce a field F_m . Its direction is marked in fig 4.52. When current is supplied to the coil (armature conductors), it produces its own field marked as F_r . This field tries to come in line with the main field and an electromagnetic torque develops in clockwise direction as marked in fig.4.52.

In actual machine, a large number of conductors are placed on the armature. All the conductors, placed under the influence of one pole (say North pole) carry the current in one direction (outward). Whereas, the other conductors placed under the influence of other pole *i.e.* south pole, carry the current in opposite direction as shown in fig 4.53. A resultant rotor field is produced. Its direction is marked by the arrow-head F_r . This rotor field F_r tries to come in line with the main field F_m and torque (T_e) develops. Thus, rotor rotates.

It can be seen that to obtain a continuous torque, the direction of flow of current in each conductor or coil side must be reversed when it crosses the magnetic neutral axis (MNA). This is achieved with the help of a commutator.

Function of a commutator

The function of a commutator in d.c. motor is to reverse the direction of flow of current in each armature conductor when it crosses the M.N.A. to obtain continuous torque.

4.44. BACK E.M.F.

It has been seen that when current is supplied to the armature conductors placed in the main magnetic field, torque develops and armature rotates, the armature conductors cut across the magnetic field and an e.m.f. is induced in these conductors. The direction of this induced e.m.f. in the armature conductors is determined by Fleming's Right Hand Rule. It is marked in fig.4.54 (b).

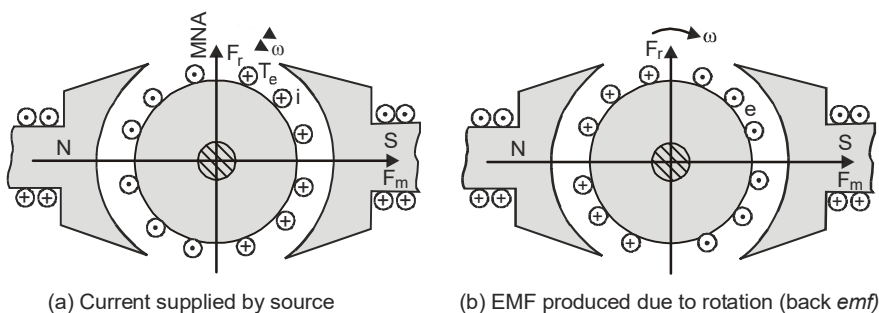


Fig. 4.54:

Fig. 4.55: Circuit diagram

It can be seen that the direction of this induced e.m.f. is opposite to the applied voltage. That is why this induced e.m.f. is called back e.m.f. (E_b). The magnitude of this induced e.m.f. is given by the relation; $E_b = \frac{PZ\phi N}{60A}$

A simple conventional circuit diagram of the machine working as motor is shown in fig.4.55. In this case, the supply voltage is always greater than the induced or back e.m.f. (*i.e.* $V > E_b$). Therefore, current is always supplied to the motor from the mains and the relation among the various quantities will be ; $E_b = V - I_a R_a$

Significance of back emf

The current flowing through the armature is given by the relation :

$$I_a = \frac{V - E_b}{R_a}$$

When mechanical load applied on the motor increases, its speed decreases which reduces the value of E_b . As a result the value $(V - E_b)$ increases which consequently increases I_a . Hence, motor draws extra current from the mains.

Thus, the back emf regulates the input power as per the load.

4.45. TYPES OF D.C. MOTORS

On the basis of the connections of armature and their field winding, d.c. motors can be classified as ;

1. **Separately excited d.c. motors** : The conventional diagram of a separately excited d.c. motor is shown fig 4.56. Its voltage equation will be;

$$E_b = V - I_a R_a - 2v_b$$

2. **Self excited d.c. motors** : These motors can be further classified as ;

- (i) **Shunt motors** : Their conventional diagram is shown in fig 4.57.

$$\text{Important relations : } I_{sh} = V/R_{sh} ; I_a = I_L - I_{sh}$$

$$E_b = V - I_a R_a - 2v_b$$

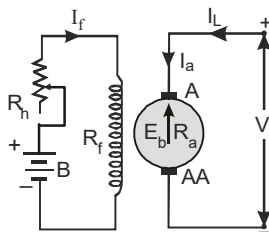


Fig. 4.56: Circuit of separately excited motor

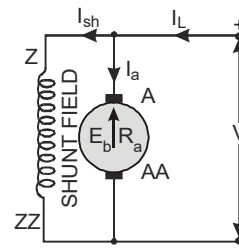


Fig. 4.57: Circuit of shunt motor

- (ii) **Series motor** : Its conventional diagram is shown in fig.4.58.

$$\text{Important relations : } I_L = I_a = I_{se} ; E_b = V - I_a (R_a + R_{se}) - 2v_b$$

- (iii) **Compound motor** : Its conventional diagram is shown in fig.4.59.

$$E_b = V - I_a (R_a + R_{se}) - 2v_b$$

In all the above voltage equations, the brush voltage drop v_b is some times neglected since its value is very small.

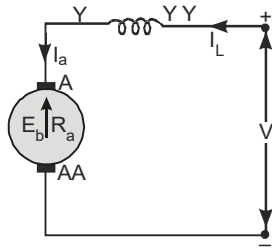


Fig. 4.58: Circuit of series motor

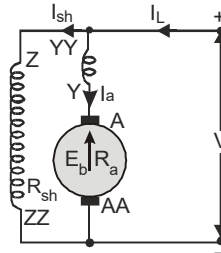


Fig. 4.59: Circuit of compound motor

4.46. CHARACTERISTICS OF D.C. MOTORS

The performance of a d.c. motor can be easily judge from its characteristic curves, known as motor *characteristics*. The characteristics of a motor are those curves which show relation between the two quantities. On the basis of these quantities, the following characteristics can be obtained :

1. **Speed and Armature current i.e. $N - I_a$ Characteristics :** It is the curve drawn between speed N and armature current I_a . It is also known as *speed characteristics*.
2. **Torque and Armature current i.e. $T - I_a$ Characteristics :** It is the curve drawn between torque developed in the armature T and armature current I_a . It is also known as *electrical characteristic*.
3. **Speed and Torque i.e. $N - T$ characteristics :** It is the curve drawn between speed N and torque developed in the armature T . It is also known as *mechanical characteristics*.

The following important relations must be kept in mind while discussing the motor characteristics:

$$E_b \propto N \phi \quad \text{or} \quad N \propto \frac{E_b}{\phi} \quad \text{and} \quad T \propto \phi I_a$$

4.47. CHARACTERISTICS SEPARATELY EXCITED DC MOTORS

The conventional diagram of this motor is shown in fig 4.60. In these motors, the field current $I_f = V/R_f$ remains constant since the supply voltage V is constant. Hence, the flux in these motors is practically constant.

1. $N - I_a$ characteristics

We know that, $N \propto \frac{E_b}{\phi}$ Since flux is constant ; $N \propto E_b$ or $N \propto V - I_a R_a$

If the armature drop ($I_a R_a$) is negligible, the speed of the motor will remain constant for all values of load as shown by the dotted line AB in fig 4.61. But strictly speaking, as the armature current increases due to the increase of load, armature drop $I_a R_a$ increases and speed of the motor decreases slightly as shown by the straight line AC in fig 4.61 (neglecting armature reaction). Moreover, the characteristic curve does not start from a point of zero armature current because a small current, no-load armature current I_{a0} , is necessary to maintain rotation of the motor at no load.

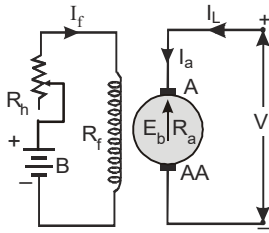


Fig. 4.60: Separately excited dc motor

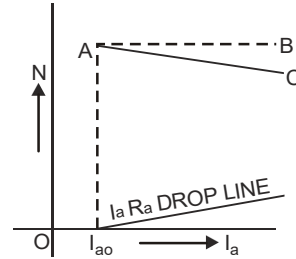


Fig. 4.61: N-Ia characteristics

Since there is no appreciable change in the speed of a separately excited dc motor from no load to full load that is why it is considered to be a constant speed motor. This motor is best suited where almost constant speed is required and the load may be thrown off totally and suddenly.

2. $T - I_a$ Characteristics

We know that, $T \propto \phi I_a$

Since flux is constant (independent to the voltage supplied to the armature), $T \propto I_a$

Hence, the electrical characteristic (*i.e.* $T - I_a$) is a straight line passing through the origin as shown in fig. 4.62. It is clear from the characteristic curve that a large armature current is required at the start if machine is on heavy load. Hence, these motors are not started with heavy loads.

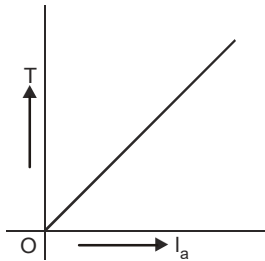
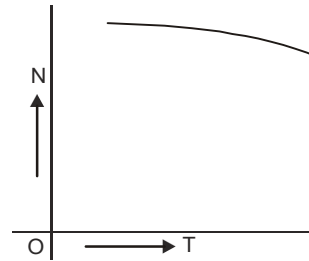
Fig. 4.62: $T-I_a$ characteristics

Fig. 4.63: N-T characteristics

3. $N - T$ Characteristics

The $N - T$ characteristic is derived from the first two characteristics. When load torque increases, armature current I_a increases but speed decreases slightly. Thus with the increase in load or torque, the speed decreases slightly as shown in fig 4.63.

4.48. SPEED CONTROL OF SEPARATELY EXCITED MOTORS

The most common and accurate speed control method of separately excited d.c. motors is Ward-Leonard system as explained below :

Ward-Leonard System : This system is used to supply variable voltage to the motor. As shown in fig. 4.63, a d.c. generator G is mechanically coupled with a prime mover PM which rotates the generator at constant speed. The field winding of the d.c. generator is connected to a constant voltage d.c. supply line through a field regulator and reversing switch. The d.c. motor M is fed from the generator G and its field winding is connected directly to a constant d.c. supply line.

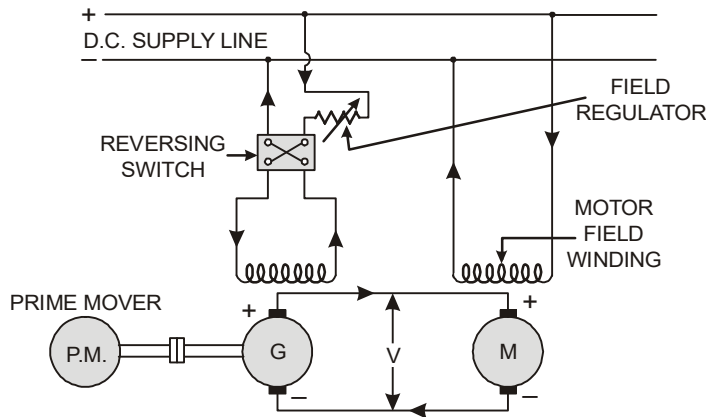


Fig. 4.64: Ward-leonard method of speed control of resparately excited dc motors

The voltage of the generator fed to the motor, can be varied from zero to its maximum value by means of its field regulator.

By reversing the direction of the field current by means of the reversing switch, the polarity of the generated voltage can be reversed and hence the direction of rotation of motor *M*. Hence, by this method, the speed and direction of rotation both can be controlled very accurately.

The capital investment in this system is very high as two extra machines (a generator and a prime mover) are required. This system of speed control is best suited where almost unlimited speed control in either direction of rotation is required *e.g.* in steel rolling mills, paper industry, elevators, cranes, diesel-electric propulsion of ships etc.

4.49. SPEED REGULATION

The speed regulation of a d.c. motor is defined as the change in speed from full load to no load and is expressed as a percentage of the full load speed.

$$\therefore \quad \% \text{ Speed regulation} = \frac{\text{N.L. speed} - \text{F.L. speed}}{\text{F.L. speed}} \times 100 = \frac{N_0 - N}{N} \times 100$$

4.50. SYNCHRONOUS MACHINE

A synchronous machine is an a.c. machine whose satisfactory operation depends upon the maintenance of the following relationship :

$$N_s = \frac{120f}{P} \quad \text{or} \quad f = \frac{PN_s}{120}$$

Where N_s is the synchronous sped in *r.p.m.* ; f is the supply frequency and P is the number of poles of the machine.

When connected to an electric power system, a synchronous machine always maintains this relationship. If a synchronous machine working as a motor fails to maintain this average speed (N_s), the machine will not develop sufficient torque to maintain its rotation and will stop. Then the motor is said to be *pulled out of step*.

In case, the synchronous machine is operating as a generator, it has to run at a fixed speed called synchronous speed to generate power at a particular frequency since all the electrical equipment and machines are designed to operate at this frequency. In India the value of power frequency is 50 Hz.

4.51. BASIC PRINCIPLES

A *synchronous machine* is just an **electro-mechanical transducer** which converts mechanical energy into electrical energy or vice-versa. The fundamental phenomenon which make these conversions possible are :

- (i) the law of electro-magnetic induction and (ii) law of interaction.
- (ii) *Law of electromagnetic induction* : This relates to the production of *e.m.f.*, i.e. *e.m.f.* is induced in a conductor whenever it cuts across the magnetic field (see fig. 4.65). This is called *Faraday's first law of electromagnetic induction*.

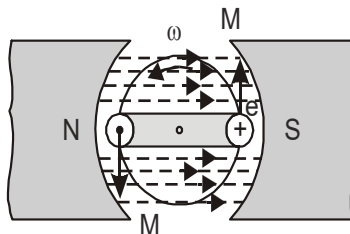


Fig. 4.65: Generator action

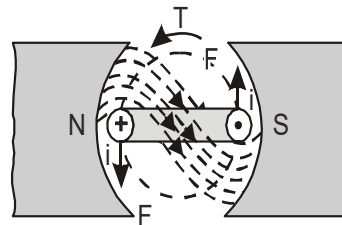


Fig. 4.66: Motor action

- (iii) *Law of interaction* : This law relates to the phenomenon of production of *force*, or *torque* i.e. whenever a current carrying conductor is placed in the magnetic field, by the interaction of the magnetic fields produced by the current carrying conductor and the main field, force is exerted on the conductor and torque is developed (see fig.4.66).

4.52. PRODUCTION OF SINUSOIDAL ALTERNATING E.M.F.

When a conductor or coil cuts across the magnetic field an *e.m.f.* is induced in it by the phenomenon called electromagnetic induction. This can be achieved either by rotating a coil in the stationary magnetic field or by keeping the coil stationary and rotating the magnetic field. (The magnetic field can be rotated by placing the field winding on the rotating part of the machine).

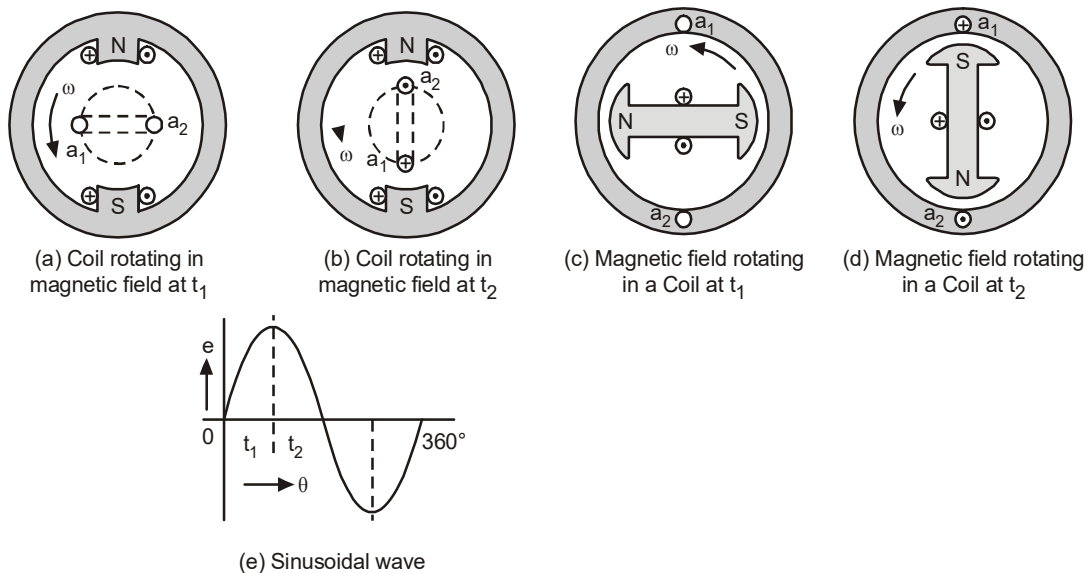


Fig. 4.67: Generation of alternating *emf*

For illustration see fig. 4.67 (a) and (b), two positions of a coil rotating in a stationary magnetic field is shown. Whereas, in fig. 4.67 (c) and (d), two positions of a rotating electro-magnet in a coil placed on stationary armature is shown. At first instant, the *e.m.f.* induced in the coil is zero since flux cut by the coil is zero. However, at second instant, the *e.m.f.* induced in the coil is maximum (say positive). The two instants t_1 and t_2 are marked on the wave diagram shown in fig. 4.67 (e). In one revolution the induced *e.m.f.* completes one cycle and its wave shape is shown in fig. 4.67 (e).

4.53. RELATION BETWEEN FREQUENCY SPEED AND NUMBER OF POLES

In fig. 4.68, a machine is shown having P number of poles on the rotor revolving at a speed at N_s *r.p.m.* When a conductor passes through a pair of poles one cycle of *e.m.f.* is induced in it.

$$\therefore \text{No. of cycle made per revolution} = \frac{P}{2}$$

$$\text{No. of revolutions made per second} = \frac{N_s}{60}$$

$$\therefore \text{No. of cycles made per second}$$

$$= \text{No. of cycles/revolution} \times \text{No. of revolutions/s}$$

$$f = \frac{P}{2} \times \frac{N_s}{60} = \frac{PN_s}{120} \text{ cycles/s or Hz}$$

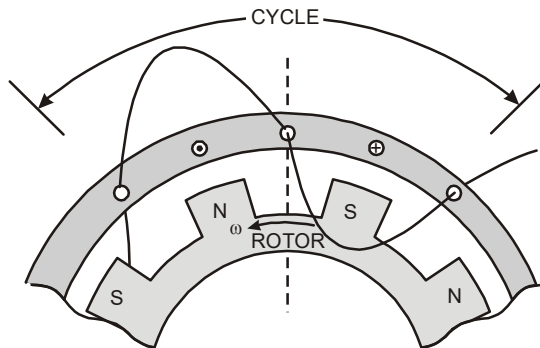


Fig. 4.68: Rotor having number poles

4.54. CONSTRUCTIONAL FEATURES OF SYNCHRONOUS MACHINES

Only in small synchronous machines the field system is placed on stator and armature winding on rotor, but in larger machines, the field winding is placed on the rotor and armature winding is placed on the stator, as shown in fig.4.69. The rotating field and stationary armature system is preferred over stationary field and rotating armature system.

The important parts of a synchronous machine are given below :

1. Stator 2. Rotor 3. Miscellaneous

1. Stator : The outer stationary part of the machine is called stator, it has the following important parts :

- (i) **Stator frame :** It is the outer body of the machine made of cast iron and it protects the inner parts of the machine. It can be also made of any other strong material since it is not to carry the magnetic field. Cast iron is used only because of its high mechanical strength.

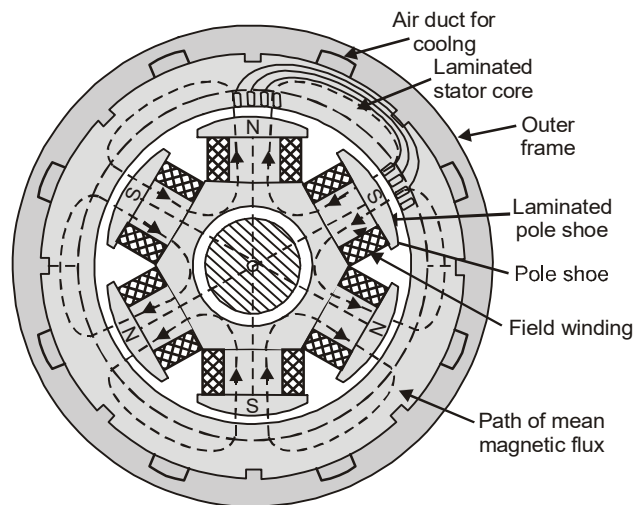


Fig. 4.69: Constructional features of salient pole alternator

- (ii) **Stator Core :** The stator core is made of silicon steel material. It is made from number of stampings which are insulated from each other. Its function is to provide an easy path for the magnetic lines of force and accommodate the stator winding.
- (iii) **Stator Winding :** Slots are cut on the inner periphery of the stator core in which 3-phase or 1-phase winding is placed. Enamelled copper is used as winding material.
- 2. Rotor :** The rotating part of the machine is called rotor. From construction point of view, there are two types of rotors named as
 - (i) Salient pole type rotor ;
 - (ii) Non-salient pole type rotor.

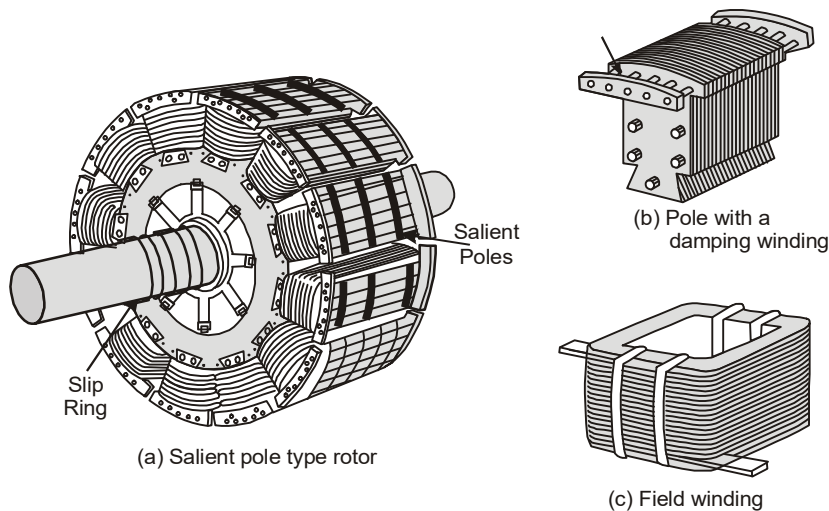


Fig. 4.70: Parts of an alternator

- (i) **Salient pole type rotor** : In this case, projected poles are provided on the rotor. Salient pole type construction is suited for medium and low speeds and are usually employed at hydro-electric and diesel power plants as synchronous generators. Since the speed of these machines (generators) is quite low, to obtain the required frequency, the machines have large number of poles as shown in fig 4.69 and 4.60 To accommodate such a large number of poles, these machines have larger diameter and small length. For a speed of 200 *r.p.m.* (alternators coupled with water turbines) the diameter of the machines is as large as 14 metre and length is only 1 metre. The salient pole type rotor has the following important parts
- Spider** : Spider is made of cast iron to provide an easy path for the magnetic flux. It is keyed to the shaft and at the outer surface, pole core and pole-shoe are keyed to it (see fig. 4.70).
 - Pole core and pole shoe** : It is made of laminated sheet material [see fig 4.70 (b)]. Pole core provides least reluctance path for the magnetic field and pole shoe distributes the field over the whole periphery uniformly to produce sinusoidal wave form of the generated *e.m.f.*
 - Field winding or Exciting winding** : Field winding is wound on the former [see fig. 4.70 (c)] and then placed around the pole core. D.C. supply is given to it through slip rings. When direct current flows through the field winding, it produces the required magnetic field.
 - Damper winding** : At the outer most periphery, holes are provided in which copper bars are inserted and short-circuited at both the sides by rings forming damper winding.

- (ii) **Non-salient pole type rotor** : In this case, there are no projected poles but the poles are formed by the current flowing through the rotor (exciting) winding. Non-salient pole type construction is suited for the high speeds. The steam turbines rotate at a high speed (3000 *r.p.m.*). When these turbines are used as prime-mover for this machine working as a generator, a small number of poles are required for given frequency. Hence, these machines have smaller diameter and larger length. Non salient pole type rotors have the following parts :

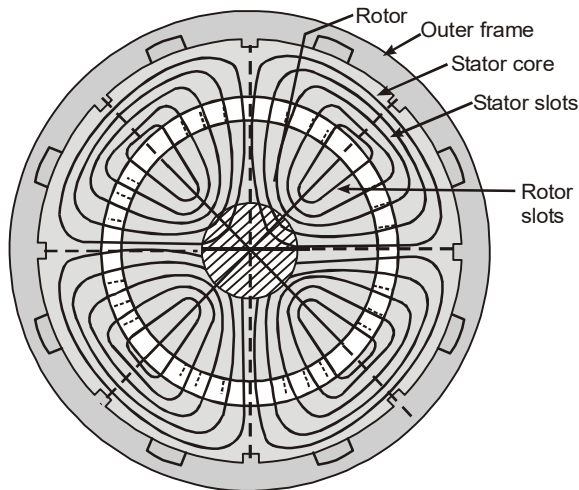


Fig. 4.71: Non-salient pole type alternator

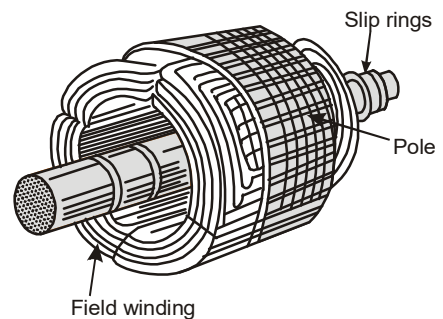


Fig. 4.72: Non-salient pole type rotor

- (a) **Rotor core** : Rotor core is made of silicon steel stampings. It is keyed to the shaft. At the outer periphery slots are cut in which exciting coils are placed. It provides an easy path to the magnetic flux.
- (b) **Rotor winding or Exciting winding** : It is placed in rotor slots and current is passed through the winding in such a way that poles are formed according to the requirement (see fig.4.72).

3. Miscellaneous Part : The following are few important miscellaneous parts ;

- (a) **Brushes** : Brushes are made of carbon and these just slip over the slip rings. D.C. supply is given to the brushes. From brushes current flows to the slip rings and then to the exciting winding.
- (b) **Bearings** : Bearings are provided between the shaft and outer stationary body to reduce the friction. The material used for their construction is high carbon steel.
- (c) **Shaft** : Shaft is made of mild steel. Mechanical power is taken or given to the machine through shaft.

4.55. ADVANTAGES OF ROTATING FIELD SYSTEM OVER STATIONARY FIELD SYSTEM

Following are the important advantages of rotating field system over stationary field system :

- (i) The armature winding is more complex than the field winding. Therefore, it is easy to place armature winding on stationary structure.
- (ii) In the modern alternators (synchronous generators), high voltage is generated, therefore, heavy insulation is provided and it is easy to insulate the high voltage winding when it is placed on stationary structure.
- (iii) The size of the armature conductors is much more to carry heavy current, therefore, high centrifugal stresses are developed. Thus, it is preferred to place them on stationary structure.
- (iv) The size of slip rings depends upon the magnitude of flow of current, therefore, it is easy to deliver small current for excitation, through slip rings of smaller size when rotating field system is used.
- (v) It is easier to build and properly balance high speed rotors when they carry the lighter field system.
- (vi) The weight of rotor is small when field system is provided on rotor and as such friction losses are produced.
- (vii) Better cooling system can be provided when the armature is kept stationary.

4.56. THREE-PHASE SYNCHRONOUS MACHINES

Only small *a.c. machines* employed in household applications are single-phase machines. The large a.c. machines are usually three-phase machines. The major application of synchronous machines is as a generator employed at the generating stations.

At all the generating stations, three-phase synchronous generators are invariably employed because of the following reasons :

- (i) For the same size of frame and material, three-phase machines have nearly 1.5 times and output to that of single-phase machines.
- (ii) Power can be transmitted and distributed more economically when it is in the form of three-phase than when it is in the form of single-phase. Therefore, 3-phase synchronous generators are employed for generation of electrical power.
- (iii) In the industries, for power conversion, three-phase induction motors are employed invariably since they are robust, more efficient, self starting, operate at high power factor and very cheap in cost. Three-phase power is required for their operation, therefore, it is preferred to generate (3-phase synchronous generators), transmit and distribute electrical power adopting 3-phase system.

4.57. E.M.F. EQUATION

Let P = No. of poles ; ϕ = Flux per pole in webers ;
 N = Speed in *r.p.m.* ; f = frequency in Hz ;
 Z_{ph} = No. of conductors connected in series per phase
 T_{ph} = No. of turns connected in series per phase
 $*K_c$ = Coil span factor ; $**K_d$ = Distribution factor

Flux cut by each conductor during one revolution = $P \phi$ weber

Time take to complete one revolution = $\frac{60}{N}$ second

Average *e.m.f.* induced per conductor = $\frac{P \phi}{60 / N} = \frac{P \phi N}{60}$

Average *e.m.f.* induced per phase,

$$= \frac{P \phi N}{60} \times Z_{ph} = \frac{P \phi N}{60} \times 2T_{ph} \quad \left(\because T_{ph} = \frac{Z_{ph}}{2} \right)$$

$$= 4 \times \phi \times T_{ph} \times \frac{PN}{120} = 4 \phi f T_{ph}$$

R.M.S. values of *e.m.f.* induced per phase,

$$E_{ph} = \text{Average value} \times \text{form factor}$$

$$E_{ph} = 4 \phi f T_{ph} \times 1.11 = 4.44 \phi f T_{ph} \text{ volt}$$

Taking into consideration the coil span factor (K_c) and distribution factor (K_d) of the winding.

Actual *e.m.f.* induced per phase

$$E_{ph} = 4.44 K_c K_d \phi f T_{ph} \text{ volt}$$

Example 4.12 : A three-phase 50 Hz, synchronous generator runs at 250 r.p.m. Find the number of poles of the machine ? What type of prime-mover would you expect for this machine ?

Solution : Frequency, $f = 50$ Hz

$$\text{Speed, } N_s = 250 \text{ r.p.m.; Then } P = \frac{120f}{N_s} = \frac{120 \times 50}{250} = 24 \text{ (Ans.)}$$

Since the speed of the synchronous generator is very low the prime-mover would be a *water turbine (hydraulic-turbine)*. For such a large number of poles the machine would be a *salient-pole type*.

* Coil span factor (K_c)

The ratio of induced e.m.f. in a coil when the winding is short pitched to the induced e.m.f. in the same coil when it is full pitched is called a coil span factor or pitch factor or chorded factor. It is generally denoted by K_c and its value is always less than unity.

$$\therefore \text{Coil span factor, } K_c = \frac{2e \cos \beta/2}{2e} = \cos \beta/2 \text{ where } \beta \text{ is the angle through which the coil is short pitched.}$$

** Distribution factor (K_d)

The ratio of induced e.m.f. in the coil group when the winding is distributed in number of slots to the induced e.m.f. in the coil group when the winding is concentrated in one slot is called a distribution factor or breadth factor. It is generally denoted by K_d and its value is always less than unity.

$$\therefore \text{Distrubution factor, } K_d = \frac{\sin \frac{m \alpha}{2}}{m \sin \frac{\alpha}{2}} \text{ where, } m = \text{No. of slots per pole per phase and}$$

$\alpha = 180^\circ/\text{No. of slots per pole i.e. slot pitch.}$

Example 4.13. Calculate the no-load terminal voltage of a 3-phase, 6-pole, star connected alternator running at 1000 r.p.m. having following data : sinusoidally distributed flux per pole = 60 m Wb ; Total No. of armature slots = 60 ; No. of conductors per slot = 10 ; Distribution factor ; $K_d = 0.96$. Assume full pitch windings.

Solution : For full pitch winding ; Coil span factor, $K_c = 1$

Distribution factor is given, therefore, it is not to be calculated.

$$\text{No. of turns/phase, } T_{ph} = \frac{60 \times 10}{2 \times 3} = 100$$

$$\text{Supply frequency, } f = \frac{PN_s}{120} = \frac{6 \times 1000}{120} = 50 \text{ Hz}$$

$$\begin{aligned} \text{E.M.F. induced per phase, } E_{ph} &= 4.44 K_c K_d f \phi T_{ph} \\ &= 4.44 \times 1 \times 0.96 \times 50 \times 60 \times 10^{-3} \times 100 = 1278.7 \text{ V} \end{aligned}$$

Since the alternator is star connected ;

$$\text{No load terminal voltage, } E_L = \sqrt{3} E_{ph} = \sqrt{3} \times 1278.7 = \mathbf{2215 \text{ V (Ans.)}}$$

Example 4.14 : Calculate the no-load terminal voltage of a 3-phase, 12-pole, star connected alternator running at 500 r.p.m. having following data :

Sinusoidally distributed flux per pole = 55 m Wb

Total No. of armature slots = 72

Number of conductors/slot = 8

Distribution factor = 0.96

Assume full pitch windings.

Solution : No. of poles, $P = 12$; Speed, $N_s = 500 \text{ rpm}$
 Flux, $\phi = 55 \times 10^{-3} \text{ Wb}$; No. of slots = 72
 No. of conductors/slot = 8 ; Distribution factor, $K_d = 0.96$

For full pitch winding,

Coil span factor, $K_c = 1$

Distribution factor is given, therefore, it is not to be calculated

$$\text{No. of turns/phase, } T_{ph} = \frac{72 \times 8}{2 \times 3} = 96$$

$$\text{Supply frequency, } f = \frac{PN_s}{120} = \frac{12 \times 500}{120} = 50 \text{ Hz}$$

$$\begin{aligned} \text{E.M.F. induced per phase, } E_{ph} &= 4.44 K_c K_d f \phi T_{ph} \\ &= 4.44 \times 1 \times 0.96 \times 50 \times 55 \times 10^{-3} \times 96 = 1125.3 \text{ V} \end{aligned}$$

Since the alternator is star connected ;

$$\text{No load terminal voltage, } E_L = \sqrt{3} E_{ph} = \sqrt{3} \times 1125.3 = \mathbf{1949 \text{ V (Ans.)}}$$


PRACTICE EXERCISE

1. A three-phase 50 Hz, synchronous generator runs at 187.5 r.p.m. Find the number of poles of the machine ? What type of prime-mover would you expect for this machine ? (Ans, 32)
2. Calculate the no-load terminal voltage of a 3-phase, 4-pole, star connected alternator running at 1500 r.p.m. having following data : sinusoidally distributed flux per pole = 66 m Wb ; Total No. of armature slots = 72 ; No. of conductors per slot = 10 ; Distribution factor ; $K_d = 0.96$. Assume full pitch windings. (Ans, 2924V)
3. Calculate the no-load terminal voltage of a 3-phase, 8-pole, star connected alternator running at 750 r.p.m. having following data :

Sinusoidally distributed flux per pole	= 55 m Wb
Total No. of armature slots	= 72
Number of conductors/slot	= 10
Distribution factor	= 0.96

 Assume full pitch windings. (Ans, 2436.3 V)

PROJECT

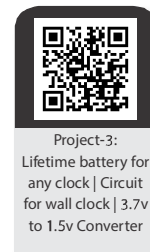

SUMMARY

1. *Three-phase induction motor* : A machine that converts 3-phase a.c. electric, power into mech. power by using an electromagnetic induction phenomenon is called a *3-phase induction motor*.
2. *Types of induction motors* : According to the construction of rotor there are two types of induction motors namely *squirrel cage I.M.* and *phase-wound I.M.*

3. *Production of revolving field* : When a 3-phase supply is given to a 3-phase wound stator of an induction motor, a resultant field of magnitude $1.5 \phi_m$ is step-up which revolves in space at a constant speed called synchronous speed N_s ($N_s = 120/fP$).
4. *Working principle* : At start, stationary rotor conductors cut across the revolving magnetic field and an e.m.f. is induced in them by the electromagnetic induction phenomenon. Current flows through the rotor conductors as they are short circuited and produce rotor field. By the interaction of rotor and stator magnetic field, torque develops and rotor starts rotating in the same direction as that of the revolving field.
5. *Reversal of direction of rotation* : The direction of rotation of 3-phase induction motor can be reversed by interchanging the connections of any two supply leads at the stator terminals.
6. *Slip* : The rotor of a 3-phase motor never obtains synchronous speed because at that speed there would be no relative speed between rotor conductors and stator revolving field and induction phenomenon is not possible. Its speed is always less than synchronous speed. The difference between synchronous speed and rotor speed is called slip. It is generally denoted as a fraction of synchronous speed. $S = (N_s - N)/N_s$.
7. *Frequency of rotor currents* : $f_r = Sf$
8. *Rotor e.m.f.* : At stand still, $E_{2s} = 4.44 k w_2 T_2 f \phi$ or $E_{2s} = KE_1$
Under running conditions $E_2 = SE_{2s}$
9. *Rotor resistance* : R_2
10. *Rotor reactance* : At stand-still – X_{2s} ; At running conditions, $X_2 = SX_{2s}$
11. *Rotor current* : $I_2 = E_2/Z_2$ where $E_2 = SE_{2s}$ and $Z_2 = \sqrt{R_2^2 + (SX_{2s})^2}$
12. *Rotor p.f.* : $\cos \phi_2 = R_2/Z_2 = R_2/\sqrt{R_2^2 + (SX_{2s})^2}$
13. *Power flow* : Input elect. power to stator – stator cu. loss – stator iron loss = stator output or rotor input.
Rotor input – rotor cu. loss = mech. power developed in rotor.
Mech. power developed in rotor – mech. loss = output mech. power at the shaft.
14. *Relation between rotor Cu loss and slip* : Rotor cu. loss = $S \times$ Rotor input.
15. *Torque developed* :
$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{[(R_2^2) + (SX_{2s})^2]} = \frac{3}{\omega_s} \frac{E_{2s}^2 R_2 / S}{[(R_s / S)^2 + (X_{2s})^2]}$$
16. *Condition for max. torque* : $R_2 = SX_{2s}$ or $S = R_2/X_{2s}$
17. *Max. Torque* : $T_m = \frac{3E_{2s}^2}{2\omega_s X_{2s}}$ and $T_m \propto \frac{1}{X_{2s}}$
18. *Starter* : A device used to limit the inrush flow of current at start is known as starter. It contains no volt coil and over-load coil for motor protection.

19. *Direct On Line (DOL) Starter* : This starter does not limit the inrush flow of starting current but it contains *No-volt* and *Over-load relays* to protect the motors. It is used with the motors of smaller size (less than 3HP).
20. *Star-delta Starter* : It connects the stator winding first in star and then in delta thus reduced the starting current to $\frac{1}{3}$ rd value. It is employed with most of the 3-phase squirrel cage induction motors.
21. *Auto-transformer Starter* : It provides lower voltages to the stator winding at the start and has the ability to reduce the starting current to any predetermined value. It is used to start 3-phase squirrel cage induction motors of very large sizes.
22. *Starting of slip-ring induction motors* : In slip-ring induction motors, the starting current is limited by adding resistance in the rotor circuit at the start.
23. *Speed control of Induction Motors* : The speed of a 3-phase induction motor can be changed (i) by changing the slip, (ii) by changing the supply frequency and (iii) by changing the number of poles of an induction motor.
24. *Single-phase I.M.* : A machine that converts 1-phase a.c. elect. power into mech. power by using an electromagnetic induction phenomenon is called a 1-phase induction motor.
25. *Torque development in a 1-phase I.M.* : When 1-phase supply is given to the stator of a 1-phase I.M., two fields of magnitude $\phi_m/2$ are produced which rotate in opposite direction at synchronous speed. An equal and opposite torque is developed by the two fields and the resultant torque is zero at start. Thus, 1-phase I.M. is not a self starting motor. However, if the rotor is rotated in either direction by some external means, torque develops and rotor picks-up the speed in that direction.
26. *Split phase motor* : To obtain starting torque in 1-phase induction motors, the single winding is splitted into two parts having different resistance and inductance. They carry currents at different angles which produce a resultant field revolving in space at synchronous speed, this develops starting torque in the motor.
27. *Capacitor motors* : These may be (i) Capacitor start motors, (ii) Capacitor run motor and (iii) Capacitor start and capacitor run motors.
28. *Shaded pole motors* : These motors have projected poles with $1/3$ pole part rapped with a copper strip. This portion of the pole is called shaded part of the pole. Because of this, a revolving field is set-up in the stator and torque is developed.
29. *AC series motors*: These motors have the ability to develop high starting torque and can rotate at high speeds. The torque varies as square of the current and the speed varies inversely proportional to the current approximately.
30. *Universal motors*: A motor which can be operated on ac as well as on dc supply at the rated voltage is called *universal motor*.
31. *D.C. motor* : A machine that converts d.c. electrical power into mechanical power is known as d.c. motor. Its working depends upon the basic principle that when a current carrying conductor is placed in the magnetic field, a force is exerted on it and torque develops.
32. *Constructional features of a dc machine*: The essential parts of a d.c. machine are: Magnetic frame or Yoke, Pole core and pole shoes, Field or Exciting coils, Armature core, Armature winding, Commutator, Brushes, Brush rocker, End housings etc.

33. *Functions of commutator* : Commutator reverses the direction of flow of current in the armature conductors when they cross the M.N.A. to obtain continuous torque.
34. *Back e.m.f.* : When d.c. supply is given to motor armature rotates. The armature conductors cut across the main magnetic field and an e.m.f. is induced in them in opposite direction to that of supply voltage called back e.m.f. (E_b).

$$E_b = PZN \phi / 60 A ; E_b \propto N \phi \text{ or } N \propto E_b / \phi ; E_b < V \text{ and } E_b = V - I_a R_a$$

35. *Types of d.c. motors and important relations* :

$$\text{Separately excited : } I_a = I_L ; E_b = V - I_a R_a - 2v_b$$

$$\text{Shunt motors : } I_{sh} = V/R_{sh} ; I_a = I_L - I_{sh} ; E_b = V - I_a R_a - 2v_b$$

$$\text{Series motors : } I_{se} = I_a = I_L ; E_b = V - I_a (R_a + R_{se}) - 2v_b$$

$$\text{Compound motors : Cumulative } \phi_r = \phi_{sh} + \phi_{se} ; \text{ differential } \phi_r = \phi_{sh} - \phi_{se}$$

36. *Speed control of d.c. motors* : The speeds of dc motors can be controlled very accurately by employing field control and armature control methods.

$$37. \text{ Speed regulation} = \frac{NL \text{ speed} - FL \text{ speed}}{FL \text{ speed}}$$

38. *Synchronous machines* : A machines that rotates only at synchronous speed N_s is called a *synchronous machine*. Its satisfactory operation depends upon the relation.

$$N_s = \frac{120 f}{P}$$

39. *Alternator* : An *a.c.* machine that converts mechanical power or energy into *a.c.* electrical power or energy at a desired frequency (50 Hz in India) is called an *alternator*. It is also called as *synchronous generator* or simply *a.c. generator*.

Its basic principle of operation is *electro-magnetic induction*.

40. *Construction of Synchronous Machines* : Usually machines of large size have stationary armature and rotating field system because of economy and simple designing.

As per rotor construction, there are two types of synchronous machines namely,

(i) Salient pole type (ii) Non-salient pole type.

41. *Applications* : (i) *Salient pole type machines* (alternators) are operated at low speeds and are coupled with water turbines at *hydro-electric power plants*. These machines have large number of poles, larger diameter and smaller length. (ii) *Non-salient pole type machines* (alternators) are operated at high speeds and are coupled with steam turbines at *thermal power plants*. These machines have small number of poles, smaller diameter and larger length.

42. *Three-phase synchronous machines* : Larger *a.c.* machines are always 3-phase wound machines because of their high efficiency and economy.

43. *E.M.F. equation*

$$E_{ph} = 4.44 K_c K_d \phi f T_{ph}$$

SHORT ANSWER QUESTIONS

1. Can the outer frame of an Inductor motor be made of plastic, state why ?
2. Can the outer frame of a dc machine be made of plastic, state why ?
3. The rotor of an inductor motor is skewed, why ?
4. Can we reverse the direction of rotation of a 3-phase induction motor by just interchanging the connections of any two terminals at the input, if so state why ?
5. In a squirrel cage rotor, no insulation is provided between the rotor conductors and slots, why ?
6. An induction motor is also called asynchronous motor, why ?
7. Can an induction motor run at synchronous speed, state why ?
8. When 3-phase supply is given to the stator of a 3-phase wound induction motor, a revolving field is set-up. When the same supply is given to a 3-phase transformer no revolving field is set up, state why ?
9. The rotor conductors are placed at the outermost periphery of the rotor, Why ?
10. The air gap between stator and rotor of an inductor motor is kept as small as possible, why ?
11. The direct on line starter does not limit the starting current of an induction motor still it is called a starter not a switch, why ?
12. For very large 3-phase induction motors auto transformer starters are preferred over star delta starters, why ?
13. Large induction motors are not started direct on line, why ? *(PSB/HSB Dec. 1996)*
14. In lifts which type of 3-phase induction motor is employed, state why ?
15. An induction motor always draws power at lagging power factor, why ?
16. When load on an induction motor increases, its speed decreases, why ?
17. In case of 1-phase capacitor run motor if capacitor is damaged the motor does not start. However if it is rotated in either direction it picks up speed in that direction, why?
18. The direction of rotation of a shaded pole motor cannot be reversed, why?
19. The direction of rotation of a split-phase single-phase induction motor can be reversed, how?
20. Why universal motor is employed in mixer-grinder?
21. What are the functions of armature core ?
22. What is the function of field system ?
23. What are the main functions of yoke ?
24. What are the main functions of pole shoes ?
25. What are the advantages of carbon brushes ?
26. Why is armature of dc machines is made up of silicon steel ?
27. What is a dc Motor ?
28. What is the working principle of a dc Motor ?
29. What is Back EMF ?

30. What are the different types of *dc* Motors ?
31. What factors determine the number of poles of a synchronous generator ?
32. Why are the alternators rated in *kVA* ?

NUMERICAL FOR PRACTICE

1. If the e.m.f. in the stator of an 8 pole induction motor has a frequency of 50 Hz and that in rotor 1.5 Hz find the speed at which motor is running and its slip. (Ans. 727.5 r.p.m., 0.03)
2. An 8-pole alternator runs at 750 r.p.m. and supplies power to a 6-pole induction motor which has full load slip of 3%. Find the full load speed of the induction motor and the frequency of its rotor e.m.f. (Ans. 970 r.p.m., 1.5 Hz)
3. It is desired to obtain a speed of approximately 700 r.p.m. with a 3-phase induction motor. Determine number of poles for (i) 60 Hz motor ; (ii) 25 Hz motor. If the rated load slip of each motor is 5%, determine rated speed for each motor. (Ans. 10 ; 684 r.p.m., 4 ; 712.5 r.p.m.)
4. Determine the number of poles, the slip and the frequency of rotor currents at rated load for a 3-phase, 3 · 7 kW induction motor rated at :
 (i) 220 V, 50 Hz, 1440 r.p.m. (ii) 120 V, 400 Hz, 3800 r.p.m.
 (Ans. 4, 4%, 2 Hz 12, 5%, 20 Hz)
5. A balanced 3-phase, 50 Hz voltage is applied to a 3-phase 6-pole induction motor. When the motor delivers rated output the slip is found to be 0.04. Determine :
 (i) The speed of the revolving field relative to the stator structure.
 (ii) The frequency of the rotor currents.
 (iii) The speed of the rotor m.m.f. relative to the rotor structure.
 (iv) The speed of the rotor m.m.f. relative to the stator structure.
 (v) The speed of the rotor m.m.f. relative to the stator field distribution.
 (vi) Are the conditions right for the development of the net unidirectional torque ?
 (Ans. 1000 r.p.m. ; 2 Hz ; 40 r.p.m. ; 1000 r.p.m. ; zero ; yes)
6. A 6-pole, 3-phase, 50 Hz induction motor has a star connected rotor. The rotor has resistance and standstill reactance of 0.25 ohm and 2.5 ohm per phase respectively. The induced e.m.f. between sliprings at start is 100 V. If the full load speed is 960 r.p.m. Calculate (i) the slip, (ii) rotor induced e.m.f. per phase (iii) the rotor current and power factor at standstill and (iv) the rotor current and power factor at rated load.
 (Ans. 4% ; 57.735 V ; 22.98 A, 0.0995 lagging ; 8.577 A, 0.9285 lagging)
7. A 3-phase induction motor having a star-connected rotor has an induced e.m.f. of 80 V between sliprings at standstill on open circuit. The rotor has a resistance and reactance of 0.5 ohm and 2 ohm per phase respectively. Calculate the current per phase and p.f. when (i) sliprings are short circuited (ii) sliprings are connected to a star connected rheostat of 4 ohm per phase.
 (Ans. 95.22 A, 0.2425 lagging ; 9.38 A, 0.9138 lagging)

8. The power supplied to a 3-phase induction motor is 40 kW and the corresponding stator losses are 1.5 kW. Calculate :
- The total mechanical power developed and the rotor I^2R losses when the slip is 0.04.
 - The output power of the motor if the friction and windage losses are 0.8 kW.
 - The efficiency of the motor. Neglect the rotor iron losses.
- (Ans. 36.96 kW ; 1.54 kW ; 36.16 kW ; 90.4%)
9. The shaft output of a 3-phase induction motor is 75 kW. The friction and windage losses are 1000 watts. The stator core losses are 4000 W and the stator copper losses are 2500 W. If the slip is 3.5% what is the efficiency of the motor ?
- (Ans. 87.97%)
10. A 400 V, 6-pole, 50 Hz, 3-phase induction motor develops 20 H.P. inclusive of mechanical losses when running at 995 r.p.m., the power factor being 0.87. Calculate :
- Slip
 - The rotor copper losses
 - The line current. The stator copper loss is 1500 W.
- (Ans. 0.005 ; 73.92 W ; 27 A)
11. A 50 H.P., 6-pole, 3-phase induction motor delivers full load output at 955 r.p.m. and with 0.86 p.f. when connected to 500 V, 50 Hz mains. Friction and windage losses total 2 HP. and stator losses are 1.5 K.W. Determine for this load : (i) total rotor Cu losses ; (ii) the efficiency ; and (iii) the line current.
- (Ans. 1.802 kW; 88.51% ; 55.78 A)
12. A 6-pole, 3-phase induction motor runs at a speed of 960 r.p.m. and the shaft torque is 135.7 Nm. Calculate the rotor copper loss if the friction and windage losses amount of 150 watt. The frequency of supply is 50 Hz.
- (Ans. 574.67 W)
13. An induction motor has an efficiency of 85% when loaded at 50 H.P. At this load stator copper loss and rotor copper loss each equal iron loss. Mechanical losses are one third of the no load loss. Calculate rotor copper loss, rotor input and slip.
- (Hints : $\text{Input} = \frac{\text{Output}}{\eta}$; losses = Input – Output ; If rotor copper loss = K. Then total
- $$\text{losses} = K + K + K + \frac{1}{3}K$$
- (Ans. 1946.9 W, 39370.88 W, 0.04945)
14. A 3-phase, 50 Hz, synchronous generator runs at 166.67 r.p.m. What is the number of poles ? What of prime-over would you expect for this machine ?
- (Ans. 36, Hydraulic turbine)
15. The stator core of a 4-pole, 3-phase alternator has 36 slots. It carries a short pitch 3-phase winding with coil span equal to 8 slots. Determine the distribution and coil pitch factor.
- (Ans. 0.9598 ; 0.9848)
16. A 3-phase, 12-pole alternator has a star connected winding with 108 slots and 10 conductors per slot. The coils are full pitched. The flux per pole is 0.05 Wb sinusoidally distributed and speed is 600 rpm. Calculate the line voltage on open circuit. Assume distribution factor equal to 0.96.
- (Ans. 3986.7 V)

MULTI-CHOICE QUESTIONS

- Stator core of an induction motor is made of
 - laminated cast iron
 - mild steel
 - silicon steel stampings
 - soft wood.
- The stator winding of an induction motor can be designed for
 - any number of pole
 - any even number of poles
 - any odd number of poles
 - only for four poles.
- The rotor of squirrel cage induction motor is skewed because
 - it reduces humming thus ensures quiet running of the motor.
 - it results in a smoother torque curves for different positions of the rotor.
 - it avoids the magnetic locking of the stator and rotor.
 - all of these.
- Slip rings of phase-wound induction motor are made of :
 - wood
 - cast iron
 - steel
 - cooper
- There is no electrical connection between stator and rotor, still power is transferred from stator to rotor through
 - magnetic flux
 - air
 - water
 - magnet.
- In a large induction motor usually the value of full load slip is
 - 0.4%
 - 20%
 - 3 to 5%
 - 6 to 15%
- At start, the slip of the induction motor is
 - zero
 - 0.5
 - one
 - infinite.
- Under running conduction, the rotor reactance is directly proportional to
 - induced e.m.f.
 - rotor current
 - slip
 - supply voltage.
- At start the rotor power factor is
 - very high
 - very low
 - unity
 - zero.
- The rotor copper losses of an induction motor are directly proportional to
 - input to the motor
 - output of the motor
 - rotor resistance
 - slip.
- The condition for maximum torque is
 - $R_2 = S Z_{2s}$
 - $X_{2s} = S R_2$
 - $R_2 = X_{2s}$
 - $R_2 = S X_{2s}$
- The function of a starter is
 - to start the motor
 - to start and stop the motor
 - to limit the starting current
 - to limit the applied voltage
- Stator core of a single-phase, split winding induction motor is made of
 - laminated cast iron
 - mild steel
 - silicon steel stampings
 - soft wood.

14. In a single phase induction motor at start, the two revolving fields produce
 - (A) unequal torques in the rotor conductors
 - (B) no torque in the rotor conductors
 - (C) equal and opposite torque in the rotor conductors
 - (D) equal torques in same direction in the rotor conductors
15. During running condition if the starting winding of a split phase induction motor is disconnected.
 - (A) the motor will stop
 - (B) the motor winding will burn
 - (C) the main winding will be damaged
 - (D) the motor will continue to rotate
16. The starting torque of a capacitor start motor is
 - (A) more than a capacitor run motor
 - (B) less than a capacitor run motor
 - (C) less than a shaded pole motor
 - (D) less than a split-phase induction motor.
17. The direction of rotation of a split-phase induction motor can be reversed by
 - (A) reversing the connections of the supply terminals
 - (B) reversing the connections of the main winding only
 - (C) reversing the connections of the starting winding only
 - (D) either (b) or (c).
18. Which motor is best suited for domestic refrigerator ?
 - (A) 3-phase induction motor
 - (B) DC motor
 - (C) Capacitor start motor
 - (D) Shaded pole motor.
19. Which motor is best suited for domestic mixer-grinder?
 - (A) 3-phase induction motor
 - (B) Universal motor
 - (C) Capacitor start motor
 - (D) Shaded pole motor.
20. The yoke of a d.c. machine is made of
 - (A) copper
 - (B) carbon
 - (C) cast iron
 - (D) silicon steel
21. The armature core of a d.c. machine is made of
 - (A) copper
 - (B) carbon
 - (C) cast iron
 - (D) silicon steel
22. The segments of the commutator of a d.c. machine are made of
 - (A) brass
 - (B) copper
 - (C) carbon
 - (D) silicon steel
23. The segments of the commutator of a d.c. machine are insulated from each other by
 - (A) rubber
 - (B) porcelain
 - (C) mica
 - (D) varnish
24. The brushes of a d.c. machine are made of
 - (A) iron
 - (B) brass
 - (C) mica
 - (D) carbon
25. The speed of the d.c. motor can be varied
 - (A) by varying field current only,
 - (B) by varying armature resistance only,
 - (C) stray losses are equal to copper losses.
26. *The frequency of voltage generated in large alternators in India is*
 - (A) in Megacycles
 - (B) in kilocycles
 - (C) 60 Hz
 - (D) 50 Hz

27. The rotors preferred for alternators coupled to hydraulic turbines are
 (A) salient pole type (B) cylindrical rotor type
 (C) solid rotor type (D) any of above.
28. Salient pole type alternators are generally employed with
 (A) High speed prime movers
 (B) Low and medium speed prime movers
 (C) Hydrogen cooled prime movers
 (D) Low voltages alternators.
29. RMS value of voltage generated per phase in an alternator is given by
 (A) $E_{ph} = 4.44 K_c K_d N \phi f$ (B) $E_{ph} = 4.44 K_c K_d N \phi$
 (C) $E_{ph} = 4.44 K_c K_d N^2 \phi f$ (D) $E_{ph} = 1.11 K_c K_d N \phi f$
30. The rating of alternators is usually expressed in
 (A) full load current (B) Horse power (C) kVA (D) kW

TEST QUESTIONS

1. Explain the construction of 3-phase squirrel cage induction motor.
2. Discuss how a rotating field is produced in a 3-phase induction motor. How does the rotating field help in the production of torque.
3. Derive the relationship between the frequency of rotor currents and supply frequency in case of a 3-phase induction motor.
4. If one of the phase of a 3-phase induction motor is blown off while running without load, what will happen to its rotation.
5. Can induction motor (3-phase) run at synchronous speed ? Explain your answer.
6. Explain the terms slip, slip frequency, wound rotor, cage rotor.
7. How can the direction of rotation of 3-phase induction motor be reversed ?
8. Explain the principle of working of a three-phase induction motor and give the expression of percentage slip.
9. How much torque does an induction motor develop at synchronous speed ? Explain your answer.
10. List the different types of losses in an induction motor.
11. What are the various losses in an induction motor? On what factors do they depend ?
12. Derive an expression for the rotor copper loss in terms of slip and input to the rotor.
13. Obtain an expression for torque under running condition, for a 3-phase induction motor and then deduce the condition for maximum torque.
14. Derive the condition for maximum torque and also the expression for the maximum torque of a 3-phase induction motor.
15. Derive the simplified equation for torque for an induction motor.

16. Draw and explain the slip-torque characteristics of a 3-phase slip ring induction motor. Mark on it starting and maximum torque.
17. Why is starter necessary for starting 3-phase induction motors. Name various method of starting 3-phase squirrel cage induction motors and explain any one method in detail.
18. Name the various starters employed for the starting of 3-phase squirrel cage induction motor. Explain star-delta starter in detail.
19. Give various methods of starting large three-phase induction motors. Explain auto transformer starter in detail.
20. How many terminals do you expect to find on the terminal box of 3-phase squirrel cage induction motor to be used for starting by star-delta starter.
21. Explain how 3-phase wound type induction motor is started.
22. Explain how the speed of slip ring induction motor can be changed by changing the rotor circuit resistance. What are the limitations and disadvantages of this method ?
23. Name the different methods of speed control of a poly-phase squirrel cage type induction motor. Explain in brief the principle of pole changing method of speed control.
24. Explain that basically a single-phase induction motor is not a self-starting motor.
25. How will you make a single-phase induction motor self-starting ?
26. Show that a single-phase sinusoidal field can be replaced by two fields rotating around the air gap in opposite directions. Sketch a torque-slip curve due to each of these two fields. How can the fact that the single-phase induction motor has no starting torque be explained by these curves ? How do they explain the fact of the motor accelerating in the direction in which it is started ?

State the manner in which the starting torque of a single-phase motor may be obtained by splitting the phase.
27. Explain the construction and working of a single-phase capacitor start induction motor.
28. Why is a capacitor employed with a ceiling fan ?
29. A ceiling fan when switched on to a single-phase a.c. supply does not start rotating. What may be the reasons ?
30. Explain the construction (with sketch) and working of a capacitor-start capacitor-run single-phase induction motor. What are its advantages and practical applications ?
31. How can you change the direction of rotation of a single-phase induction motor ?
32. Describe the working and construction of a single-phase shaded pole motor.
33. Describe the working of an ac series motor.
34. Describe the working and construction of a universal motor.
35. Name the various parts of a d.c. machine and give the function of each part.
36. Explain the principle of operation of a d.c. motor.
37. Explain with suitable diagram the working of a d.c. motor.
38. Explain the function of commutator in a d.c. motor.
39. What is back e.m.f.? Explain.

40. Mention the various types of d.c. motors and their uses.
41. With the help of speed-armature current characteristics, show that a separately excited dc motor runs at almost constant speed irrespective of the load.
42. Sketch the speed-torque curve of a separately excited dc motor and discuss its nature.
43. Sketch the speed-load and torque-load characteristics of a separately excited dc motor.
44. Write a general expression for the speed of a d.c. motor in terms of supply voltage and flux per pole.
45. Describe Ward-Leonard method of speed control of a separately excited dc motor.
46. Deduce the relation between number of poles frequency and speed of an alternator.
47. Name the various part of a synchronous machine. Give the function and material used for each of them.
48. Give the constructional details of cylindrical rotor alternator.
49. Explain the difference between salient pole and cylindrical pole type of rotor used in alternators. Mention their applications.
50. Explain why the stator core of an alternator is laminated.
51. List the advantages of making field system rotating and armature stationary in case of an alternator.
52. Derive an expression for induced e.m.f. for an alternator.

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes											
	(1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												

ANSWERS TO MULTI-CHOICE QUESTIONS

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (C) | 2. (B) | 3. (C) | 4. (D) | 5. (A) |
| 6. (C) | 7. (C) | 8. (C) | 9. (B) | 10. (D) |
| 11. (D) | 12. (C) | 13. (C) | 14. (C) | 15. (D) |
| 16. (A) | 17. (D) | 18. (C) | 19. (B) | 20. (C) |
| 21. (D) | 22. (B) | 23. (C) | 24. (D) | 25. (D) |
| 26. (D) | 27. (A) | 28. (B) | 29. (A) | 30. (C) |



Experiment No. 5

Experiment: Demonstration of cut-out sections of machines: dc machine (commutator-brush arrangement), induction machine (squirrel cage rotor), synchronous machine (field winding-slip ring arrangement) and single-phase induction machine.

Objectives:

1. To make the students familiar with the constructional features of various electrical machines generally employed in electrical system.

Apparatus/Instruments/Components required

Cutaway sections/disassembled parts of various machines such as

1. DC Machine (commutator-brush arrangement)
2. Induction machine (squirrel cage rotor)
3. Synchronous machine (field winding-slip ring arrangement)
4. Single-phase induction machine.

1. DC Machine (commutator-brush arrangement)

Different parts of a dc machine are mentioned below:

Function and Material used for each part

1. **Magnetic frame or Yoke:** The outer cylindrical frame to which main poles and inter poles are fixed is called the yoke.
It provides a low reluctance path for the magnetic flux and protection the inner parts of the machine. The yoke is made of cast iron for smaller machines but in case of larger machines, it is made of cast steel or fabricated rolled steel.
2. **Pole core and pole shoes :** The pole core and pole shoes are fixed to the magnetic frame or yoke by bolts. They support the field or exciting coils and spread out the magnetic flux over the armature periphery more uniformly.
Usually, the pole core and pole shoes are made of thin cast steel laminations or stampings.
3. **Field or Exciting coils:** The coils are wound on the former and then placed around the pole core. Enamelled copper wire is used for the construction of field or exciting coils. When direct current is passed through the field winding, it magnetises the poles which produce the required flux.
4. **Armature core:** It is cylindrical in shape and keyed to the rotating shaft. At the outer periphery slots are cut which accommodate the armature winding.
It houses the conductors in the slots. It provides an easy path for magnetic flux.
5. **Armature winding:** The insulated conductors housed in the armature slots are suitably connected. This is known as armature winding.
It is a place where conversion of power takes place i.e. in case of generator, mechanical power is converted into electrical power and in case of motor, electrical power is converted into mechanical power. On the basis of connections, armature windings are named as Lap winding and Wave winding.


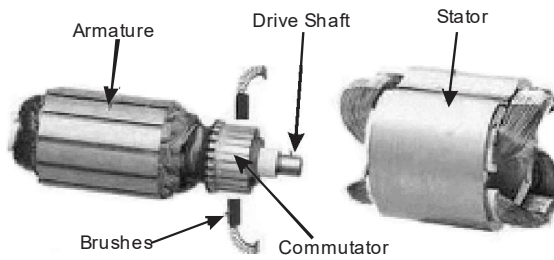


Fig. 3.1(a) Disassembled Parts of DC Machines

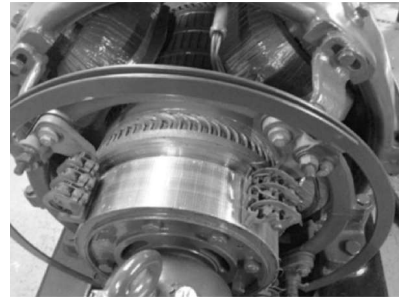

3.1(b) Commutator and Brushes


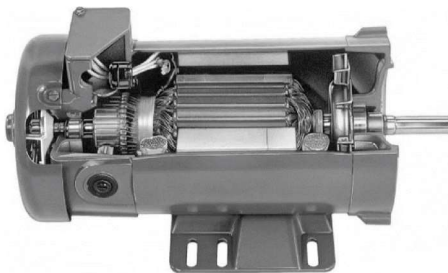


Fig. 3.1(c) Assembled view of a DC Machines

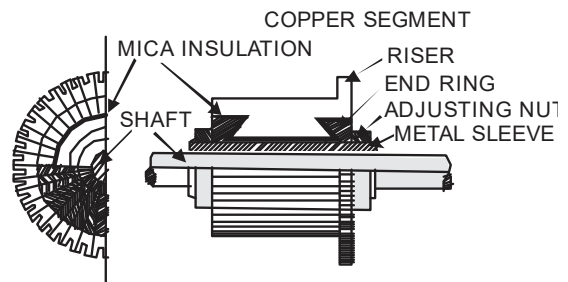

3.1(d) Half sectional view of a commutator

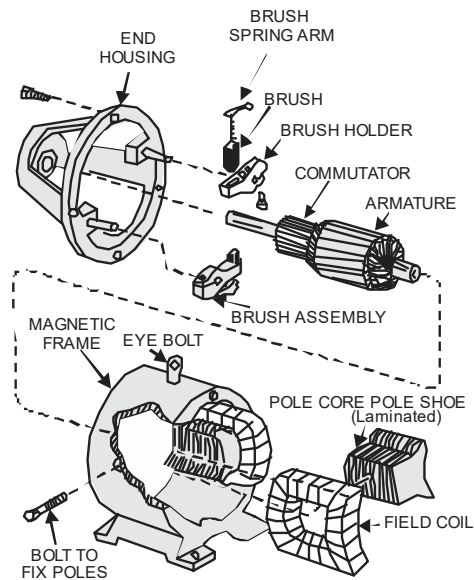


Fig. 3.1(d) Parts of a dc machine (pencil sketch)

6. **Commutator:** It is the most important part of a d.c machine and serves the following purposes: It connects the rotating armature conductors to the stationary external circuit through brushes. It converts the alternating current induced in the armature conductors into unidirectional current in the external load circuit in generator action., whereas it converts the alternating torque into unidirectional (continuous) torque produced in the armature in motor action.
The commutator is of cylindrical shape and is made up of wedge-shaped hard drawn copper segments. The segments are insulated from each other by a thin sheet of mica. Armature coil is connected to the commutator segment through riser.
7. **Brushes:** The brushes are pressed upon the commutator and form the connecting link between the armature winding and the external circuit. They are usually made of high-grade carbon because carbon is conducting material and at the same time in powdered form provides imbricating effect on the commutator surface. The brushes are held in particular position around the commutator by brush holders and rocker.
9. **End housings:** End housings are attached to the ends of the main frame and support bearings. The front housing supports the bearing and the brush assemblies whereas the rear housing usually supports the bearing only.
10. **Bearings:** The ball or roller bearings are fitted in the end housings. The function of the bearings is to reduce friction between the rotating and stationary parts of the machine. Mostly high carbon steel is used for the construction of bearings as it is very hard material.
11. **Shaft:** The shaft is made of mild steel with a maximum breaking strength. The shaft is used to transfer mechanical power from or to the machine.

2. Three-phase Induction machine (squirrel cage rotor)

A 3-phase induction motor consists of two main parts namely stator and rotor.

1. Stator: It is the stationary part of the motor. It contains

- (i) Outer frame, (ii) Stator core and (iii) Stator winding.
- (i) **Outer frame:** It is the outer body of the motor. Its function is to support the stator core and to protect the inner parts of the machine. It is made of some mechanically strong material such as cast iron, fabricated steel or synthetic plastic.
- (ii) **stator core:** The stator core is to carry the alternating magnetic field which produces hysteresis and eddy current losses; therefore, core is built up of high-grade silicon steel stamping. Slots are punched on the inner periphery of the stamping to accommodate stator winding.
- (iii) **Stator winding:** The stator core carries a three phase winding which is usually supplied from a three phase supply system. The six terminals of the winding (two of each phase) are connected in the terminal box of the machine. The stator of the motor is wound for definite number of poles, the exact number being determined by the requirement of speed. It will be seen that greater the number of poles, the lower is the speed and vice-versa, since. The three- phase winding may be connected in star or delta externally through a starter.

2. Rotor: It is the rotating part of the motor. There are two types of rotors, which are employed in 3-phase induction motors.

- (i) Squirrel cage rotor (ii) Phase wound rotor.

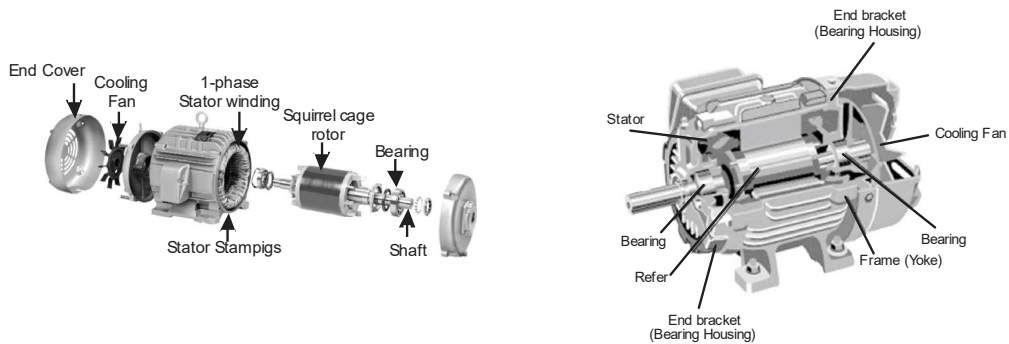


Fig. 3.2(a) Disassembled Parts of a 3-phase Induction Motor **Fig. 3.2(b)** Sectional view of a 3-phase Induction Motor

- (i) Squirrel cage rotor: The motors employing this type of rotor are known as Squirrel cage induction motors. Most of the induction motors are of this type because of simple and rugged construction of rotor. A squirrel cage rotor consists of a laminated cylindrical core having semi-closed circular slots at the outer periphery. Copper or aluminium bar conductors are placed in these slots and short circuited at each end by copper or aluminium rings, called short circuiting rings.


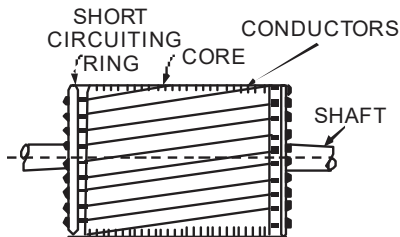


Fig. 3.2(c) Squirrel cage rotor

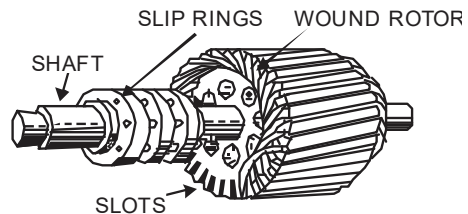

3.2(d) Phase-wound/Slip-ring rotor

- (ii) Phase wound rotor: Phase wound rotor is also called slip ring rotor and the motors employing this type of rotor are known as phase wound or slipring induction motors. Slip ring rotor consists of a laminated cylindrical core having semi-closed slots at the outer periphery and carries a 3-phase insulated winding. The rotor winding is star connected and the three remaining terminals are connected to three copper slip rings keyed the shaft. Shaft: A mild steel shaft is passed through the centre of the rotor and is fixed to it with key. The purpose of shaft is to transfer mechanical power.

3. Synchronous machine (field winging-slip ring arrangement)

Only in small synchronous machines the field system is placed on stator and armature winding on rotor, but in larger machines, the field winding is placed on the rotor and armature winding is placed on the stator.

The important parts of a synchronous machine are:

- (i) Stator (ii) Rotor (iii) Some Miscellaneous parts

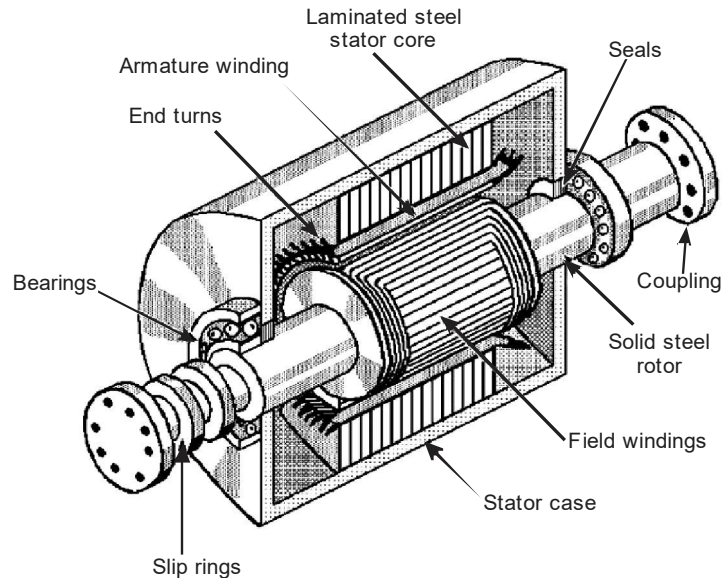


Fig. 3.3: Sectional view of a 1-phase Synchronous Motor

The construction details of a small synchronous machine are the same as that of a dc machine except that in this case, in place of a commutator, slip rings are employed because in these machines ac is not to be converted into dc. Armature winding design is also different.

4. Single-phase induction machine

A 1-phase induction motor consists of two main parts namely stator and rotor.

1. **Stator:** It is the stationary part of the motor. It contains

- (i) Outer frame, (ii) Stator core and (iii) Stator winding.

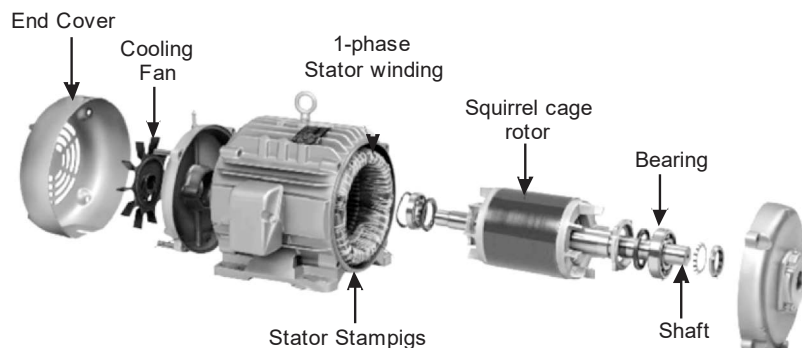


Fig. 3.4(a): Disassembled Parts of a 1-phase Induction Motor

- (i) **Outer frame:** It is the outer body of the motor. Its function is to support the stator core and to protect the inner parts of the machine. It is made of some mechanically strong material such as cast iron, fabricated steel or synthetic plastic.

- (ii) stator core: The stator core is to carry the alternating magnetic field which produces hysteresis and eddy current losses; therefore, core is built up of high-grade silicon steel stamping. Slots are punched on the inner periphery of the stampings to accommodate stator winding.
 - (iii) Stator winding: The stator core carries a single-phase windingsplitted into two parts; one is called running winding and the other one is called starting winding to make the motor self-starting. The motor is operated from single phase supply system
- 2. Rotor: It is the rotating part of the motor. A squirrel cage rotor is employed in these motors.**

Viva

1. What are the functions of armature core?
2. What is the function of exciting coils in dc machines?
3. What is the main functions of yoke in dc machines?
4. What are the main functions of pole shoes?
5. What is the function of carbon brushes?
6. Why is armature of dc machines is made up of silicon steel stampings?
7. What is the function of commutator in dc machines?
8. Can the outer frame of an Inductor motor be made of plastic? Justify.
9. Can the outer frame of a dc machine be made of plastic? Justify.
10. Why the stator core of an induction motor is laminated?
11. What is the function of sliprings in synchronous machines?
12. In synchronous machines, why sliprings are used in place of commutator?
13. In single-phase induction motors, why the single-phase winding is splitted into two parts?
14. Why stator core of a single-phase induction motors is made of silicon steel stampings?

Experiment No. 6

Torque Speed Characteristic of separately excited dc motor.

Objectives:

To make the students familiar with separately excited dc motor and to explore its Torque-Speed characteristics.

Apparatus/Instruments/Components required

1. A Separately excited dc motor,
2. DC supply (230/250 V),
3. An excitor or battery,
4. A rheostat to control field current,
5. Two dc voltmeters of range _____,
6. Two dc ammeters of range _____.

Theory

On the basis of the connections of armature and their field winding, dc motors can be classified as separately excited dc motors and self excited dc motors.

1. **Separately excited dc motors:** The conventional diagram of a separately excited d.c. motor is shown in fig 6.1. Its voltage equation will be; $E_b = V - I_a R_a - 2v_b$

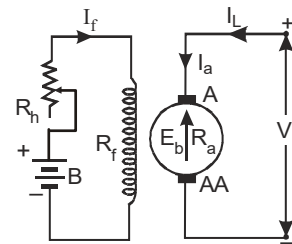


Fig. 6.1: Separately Excited DCMotor

Characteristics of D.C. Motors

The performance of a d.c. motor can be easily judged from its characteristic curves, known as motor characteristics. The characteristics of a motor are those curves which show relation between the two quantities. On the basis of these quantities, the following characteristics can be obtained:

1. Speed and Armature current i.e. $N - I_a$ Characteristics: It is the curve drawn between speed N and armature current I_a . It is also known as *speed characteristics*.
2. Torque and Armature current i.e. $T - I_a$ Characteristics: It is the curve drawn between torque developed in the armature T and armature current I_a . It is also known as *electrical characteristic*.
3. Speed and Torque i.e. $N - T$ characteristics: It is the curve drawn between speed N and torque developed in the armature T . It is also known as *mechanical characteristics*.

The following important relations must be kept in mind while discussing the motor characteristics:

$$E_b \propto N \phi \text{ or } N \propto \frac{E_b}{\phi} \text{ and } T \propto \phi I_a$$

Characteristics of Separately Excited DC Motors

The conventional diagram of this motor is shown in fig P6.1. In these motors, the field current $I_f = V/R_f$ remains constant since the supply voltage V is constant. Hence, the flux in d.c. shunt motors is practically constant.

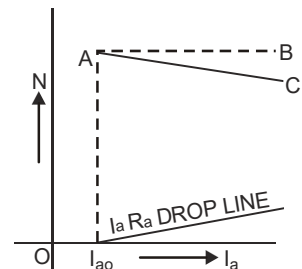


Fig. 6.2: N-Ia Characteristics

1. $N - I_a$ characteristics

We know that $N \propto \frac{E_b}{\phi}$

Since flux is constant: $N \propto E_b$ or $N \propto V - I_a R_a$

If the armature drop ($I_a R_a$) is negligible, the speed of the motor will remain constant for all values of load as shown by the dotted line AB in fig P6.2. But strictly speaking, as the armature current increases due to the increase of load, armature drop $I_a R_a$ increases, and speed of the motor decreases slightly as shown by the straight line AC in fig P6.2 (neglecting armature reaction). Moreover, the characteristic curve does not start from a point of zero armature current because a small current, no-load armature current I_{a0} , is necessary to maintain rotation of the motor at no load. Characteristics. Since there is no appreciable change in the speed of a dc shunt motor from no load to full load that is why it is considered to be a constant speed motor.

2. $T - I_a$ Characteristics

We know that $T \propto \phi I_a$

Since flux is constant, $T \propto I_a$

Hence, the electrical characteristic (i.e. $T - I_a$) is a straight line passing through the origin as shown in fig. P6.3. It is clear from the characteristic curve that a large armature current is required at the start if machine is on heavy load. Thus, these motors should never be started on load.

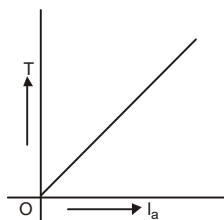


Fig. P 6.3: $T - I_a$ Characteristics

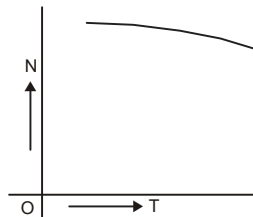


Fig. P 6.4: $N - T$ Characteristics

3. $N - T$ Characteristics

The $N - T$ characteristic is derived from the first two characteristics. When load torque increases, armature current I_a increases but speed decreases slightly. Thus, with the increase in load or torque, the speed decreases slightly as shown in fig 6.4.

However, when $N - T$ characteristics are to be drawn practically, the mechanical load on the machine is increased in steps and the load or armature current I_a is measured with the help of an ammeter connected in the armature circuit and the corresponding speed is measured with the help of a tachometer.

Circuit diagram

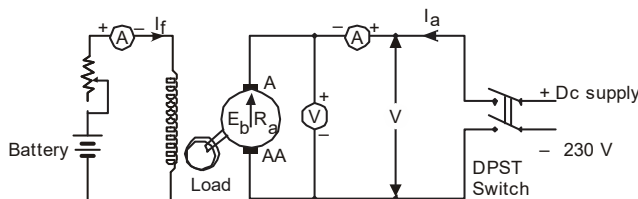


Fig. P6.5: Circuit to determine $N - T$ Characteristics

Procedure:

1. Connect the apparatus as per the circuit shown in fig.P6.5.
2. Get you connections checked by the teacher in-charge.
3. Switch-ON the supply through DPST switch.
4. Adjust the value of field current I_f by adjusting the value circuit resistance.
5. Don't apply any load on the machine and measure the armature current I_0 , it shows the load on the machine due to losses in the machine. Also measure the corresponding speed of the motor N_0 by.
6. Apply mechanical load on the motor, measure armature current I_{aI} , and find the corresponding speed N_I of the motor.
7. Increase the load on the machine in steps and take the corresponding readings and tabulate them.

Note: While performing the practical, the voltage across the armature and the field current has to be kept constant.

Observation table:

S.No.	Field Current I_f in ampere	Voltage across Armature V in volt	Armature Current $I_{a\text{in}}$ ampere	Motor Speed N in rpm
1.	I	V	I_{a0}	N_0

Conclusion:

1. The shape of the curve is almost the same as shown in fig. 6.4.
2. The curve reveals that the speed of this motor remains almost constant when load is applied on it.
3. It is called a constant speed motor.

Viva:

1. In a separately excited motor, do we need separate supply sources to supply power to field circuit and armature or both can be supplied from the same source, justify your answer?
2. Why is a separately excited motor called a constant speed motor?

Experiment No. 7

Synchronous speed of two and four-pole, three-phase induction motors. Direction reversal by change of phase-sequence of connections. Torque-Slip Characteristic of an induction motor. Generator operation of an induction machine driven at super-synchronous speed.

Objectives:

1. To make the students familiar with the synchronous speed of the revolving magnetic field in a 3-phase induction motors.
2. How to reverse the direction of rotation of a 3-phase induction motors.
3. Significance of Torque-Slip Characteristic of a 3-phase induction motor.
4. When and how an induction motor works as an induction generator.

Aparatus/Instruments/Components required

1. Three-phase ac supply.
2. Three-phase induction motor.
3. One starter (Star-delta starter)
4. Reversing Switch (change over switch)
5. Tachometer (mechanical or digital) for measuring speed.
6. Tools as mentioned in the beginning (i.e. Plier, screw driver, test pin etc.)
7. Connecting leads etc.

Theory

Production Of Revolving Field

Consider a stator on which three different windings represented by three concentric coils a_1a_2 , b_1b_2 and c_1c_2 respectively are placed 120° electrically apart. A1 When a 3-phase supply, as shown in fig. P7.1, is applied to the stator. Three phase currents will flow through the three coils and produce their own magnetic fields.

Three instant t_1 , t_2 and t_3 are marked. Accordingly, the direction and position of the resultant field F_m is shown in fig. P7.2. This reveals that in one cycle, the resultant field completes one revolution.

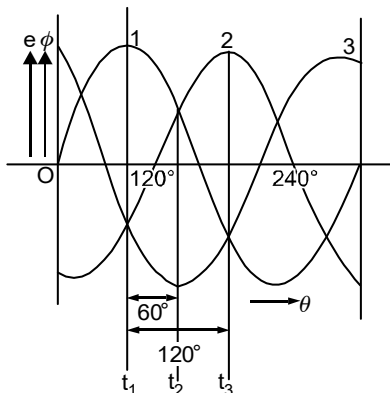


Fig. P7.1: Wave diagram of 3-phase supply

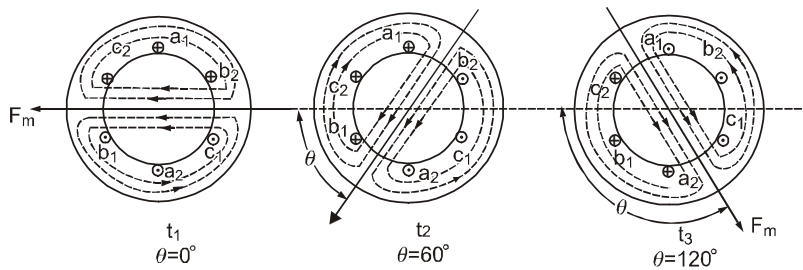


Fig. P7.2: Direction and position of the resultant revolving field

Hence, we conclude that when 3-phase supply is given to a 3-phase wound stator of an induction motor, a resultant field is produced which revolves at a constant speed in the direction of the phase sequence. The speed at which this field revolves is called synchronous speed and is given by the relation,

$$N_s = \frac{120 \times f}{P}$$

In this case, the supply from phases 1, 2 and 3 is given to coil a_1a_2 , b_1b_2 and c_1c_2 , respectively, an anticlockwise rotating field is produced. If the supply to coil a_1a_2 , b_1b_2 and c_1c_2 is given from phase 1, 3 and 2 respectively, the direction of rotating field is reversed.

Thus, to reverse the direction of rotation of rotating field the connections of any two supply terminals are inter changed.

Synchronous speed of two and four-pole, three-phase induction motors

For 2-pole, 3-phase induction motor, the synchronous speed will be.

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{2} = 3000 \text{ rpm}$$

For 4-pole, 3-phase induction motor, the synchronous speed will be.

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

Direction reversal by change of phase-sequence of connections

It has been seen that a revolving field is set up in the stator of a 3-phase induction motor when 3-phase supply is given to its winding and the direction of rotation depends upon the supply sequence.

The direction of rotation of the revolving field or that of the rotor can be reversed if the sequence of supply is reversed. The supply sequence can be reversed by interchanging the connections of any two supply leads at the stator terminals.

Hence, the direction of rotation of a 3-phase induction motor can be reversed by interchanging the connections of any two supply leads at the stator terminals.

Torque-Slip Characteristic of an induction motor

The full load torque developed by an induction motor is given by the expression,

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{[R_2^2 + (SX_{2s})^2]}$$

To draw the torque-slip or torque-speed curve the following points are considered :

- (i) At synchronous speed (N_s); slip, $S = 0$ and torque $T = 0$.
- (ii) When rotor speed is very near to synchronous speed i.e., when the slip is very low the value of the term $(SX_{2s})^2$ is very small in comparison to R_2^2 [i.e., $(SX_{2s})^2 \ll R_2^2$] and is neglected.

Therefore, torque is given by the expression.

$$\frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{R_2^2}$$

Thus, at low values of slip, torque is approximately proportional to slip S and the torque-slip curve is a straight line, as shown in fig. 7.2.

- (iii) As the slip increases torque increases and attains its maximum value when $S = R_2/X_{2s}$. This maximum value of torque is also known as **break down or pull-out torque**.

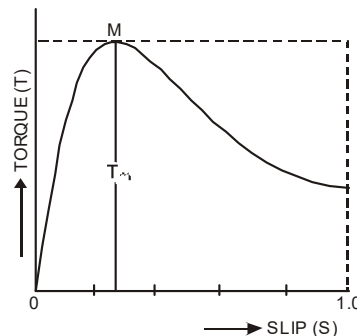


Fig. P7.3: Direction and position of the resultant revolving field

- (iv) With further increase in slip due to increase in load beyond the point of maximum torque i.e. when slip is high, the value of term $(SX_{2s})^2$ is very large in comparison to R_2^2 [i.e., $(SX_{2s})^2 \gg R_2^2$]. Therefore, R_2^2 is neglected as compared to $(SX_{2s})^2$ and the torque is given by the expression.

$$T = \frac{3}{\omega_s} \frac{SE_{2s}^2}{S^2 X_{2s}^2} \frac{R_2}{+S^2 X_{2s}^2} = \frac{3}{\omega_s} \frac{SE_{2s}^2 R_2}{2S^2 X_{2s}^2} \text{ or } T \propto \frac{1}{S}$$

Thus, at higher value of slip (i.e., the slip beyond that corresponding to maximum torque), torque is approximately inversely proportional to slip S and the torque-slip curve is a rectangular hyperbola, as shown in fig. P7.3.

Generator operation of an induction machine driven at super-synchronous speed

We that when 3-phase supply is given to a 3-phase wound stator of an induction machine, torque develops, and rotor picks up speed. In this case, machine works as a motor and the rotor speed is less than the synchronous speed of the revolving field.

However, if the rotor of a 3-phase induction machine is coupled to a prime mover which is capable to drive it at a speed higher than the synchronous speed then it will be observed that energy is fed back to the mains by the machine instead of drawing it. Under this condition the machine is said to be working as a generator. As the machine works on the induction phenomenon and no excitation is given to the machine, the machine is called as an *induction generator*.

The following points are worth noting regarding this machine.

1. The machine is connected to the mains and operated as a motor first and then can be operated as a generator by rotating the rotor at a speed more than synchronous speed with the help of a prime mover.

2. Machine can never be operated as a generator independently because no excitation is provided to any part of the machine. Moreover, induction phenomenon is only possible in this case if machine is operated first as a motor *i.e.* machine is connected to the mains, not working independently.
3. When the speed of the rotor is made more than the synchronous speed of the stator revolving field with the help of prime-mover, the mechanical energy supplied by the prime-mover is converted into electrical energy. Hence, the machine works as a generator.
4. The operating range of the machine as a generator is limited to a slip corresponding to the value of maximum torque.

Let us examine how to reverse the direction of rotation of a 3-phase induction motors.

Circuit diagram:

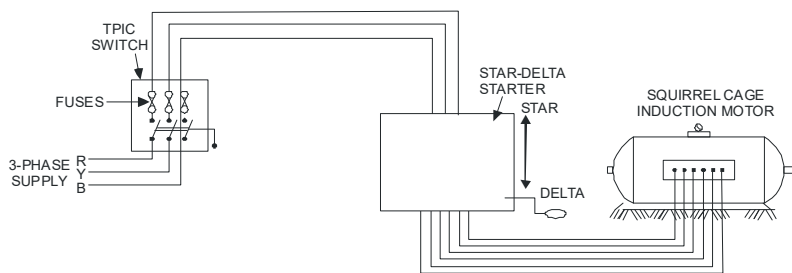


Fig.P7.4: Three-phase Induction Motor connected to supply through star-delta starter and TPIC Switch

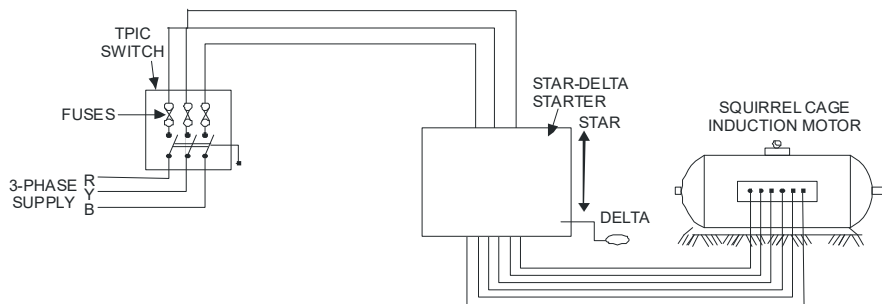


Fig.P7.5: Three-phase Induction Motor, rotation is reversed by interchanging terminals R and Y

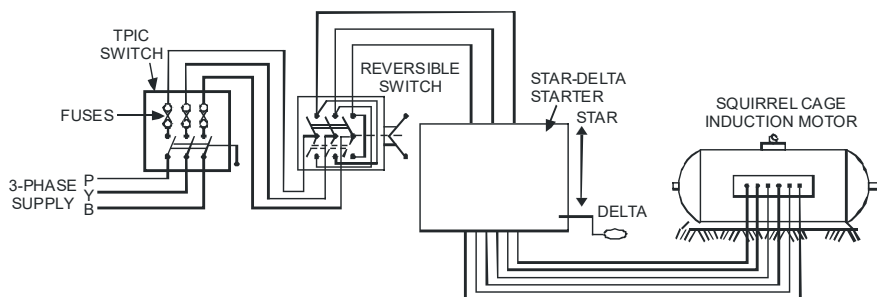


Fig. P7.6: Three-phase Induction Motor, rotation is reversed by interchanging terminals R and Y with the help of reversible switch

Procedure:

1. Make the connections to the motor through *TPIC* switch and a star-delta starter as shown in fig. 7.4.
2. Get the connections checked by the teacher in-charge.
3. Start the motor by throwing the handle first in star and then in delta position.
4. Observe the direction of rotation of the motor.
5. Stop the motor by pushing stop button at the starter and switch off the *TPIC* switch.
6. To reverse the direction of rotation of the motor interchange the leads of motor at any two terminals of the *TPIC* switch as shown in fig. P7.5.

Or

To reverse the direction of rotation of the motor, interchange the leads of motor at any two terminals in the reversible switch as shown in fig. 7.6.

7. Switch-ON the *TPIC* switch and start the motor again. Observe the direction of rotation of the motor.
8. If a motor is wound for 2-poles its speed at no load is slightly less than 3000 rpm since induction motor can run only at a speed less than synchronous speed whereas 4-pole induction motor can rotate at a speed slightly less than 1500 rpm. The rotating speed can be measured by tachometer.

Observations:

Direction of rotation of motor in first case – clockwise/counter-clockwise.

Direction of rotation of motor after interchanging the connections – clockwise/counter-clockwise.

Results:

The direction of rotation of the motor is reversed when connections at any two terminals are interchanged.

Conclusion:

1. An induction motor is asynchronous motor.

Viva:

1. What will be the synchronous speed of a 6-pole induction motor?
2. If the connection at RB terminals are interchanged will the direction of rotation of induction motor reverse, justify?
3. While working, if the speed of 3-phase induction motor is increased more than the synchronous speed by some means, what will you expect?

5

Power Converters

RATIONALE

In electrical systems (power engineering), power conversion is considered as conversion of electric energy from one form to another, such as conversion from AC to DC, DC to AC, DC to DC or AC to AC. Sometimes, it may be just changing the voltage or frequency or combination of these.

A power converter is an electrical or electro-mechanical device for converting electrical energy. It can be simply a transformer to change the voltage level of AC power, but on the other hand, it may include far more complex systems. The term, power converter, can also be used for a class of electrical machinery that is used to convert one frequency of alternating current into another frequency as mentioned earlier.

Power conversion systems may be classified in different ways depending upon applications.

One way of classifying power conversion systems is according to whether the input and output are alternating current (AC) or direct current (DC).

DC to DC power conversion: DC-to-DC converters come under this category. These are usually employed to change the dc voltage level. A voltage regulator and linear regulator convert DC to DC

DC to AC power conversion: A power inverter is used to convert DC to AC.

AC to DC power conversion: The devices which are used to convert AC to DC are rectifier, mains power supply unit (PSU) and switched-mode power supply.

AC to AC power conversion: The devices which are used to convert AC to AC are transformer/ autotransformer, voltage converter, voltage regulator, cycloconverter and variable-frequency transformer. There are also some devices and methods to convert power for single and three-phase operation.

As we know that standard power voltage and frequency varies from country to country and sometimes within a country even. In America it is usually 120 volt, 60 Hz, but in Europe, Asia, Africa and many other parts of the world, it is usually 230 volt, 50 Hz. Moreover in *aircrafts*, usually power at 400 Hz is used, so 50 Hz/60 Hz to 400 Hz frequency conversion is needed for use in the ground power unit used to power the airplane while it is on the ground. Conversely, internal 400 Hz internal power may be converted to 50 Hz or 60 Hz for convenience power outlets available to passengers during flight.

It is also true that for some electronic gadgets AC *adapters* (a type of power supply) are used to convert mains-voltage AC to low-voltage DC suitable for consumption by microchips. Similarly, *voltage converters* (also known as “travel converters”) are used when travelling between countries

that use ~120 V versus ~240 V AC mains power. There are also consumer “adapters” which merely form an electrical connection between two differently shaped AC power plugs and sockets, these are changing neither voltage nor frequency.

In this chapter, we shall go through some of the important converters.

UNIT OUTCOMES

U5-O1: Unit-5 Learning Outcome-1

To understand the working of power converter.

U5-O2: Unit-5 Learning Outcome-2

To analyse working and applications of a buck converter

U5-O3: Unit-5 Learning Outcome-3

To analyse working and applications of a boost converter

U5-O4: Unit-5 Learning Outcome-4

To analyse working and applications of a buck-boost converter

Meaning of modulation and analysis of various modulators.

UNIT SPECIFIC

- Working of power converters and simple linear voltage regulator.
- To analyse the working of buck converters.
- To analyse the working of boost converters.
- To analyse the working of buck-boost converters.
- Working of voltage source inverter.
- Necessity of modulation.
- Working of various types of modulators.

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES

Unit II Outcomes	EXPECTED MAPPING WITH COURSE OUTCOMES (1-weak Correlation; 2-Medium correlation; 3-Strong Correlation)		
	CO-1	CO-2	CO-3
U5-O1	1	3	--
U5-O2	1	3	--
U5-O3	1	3	--
U5-O4	1	3	--
U5-O5	1	3	--


Interesting facts

- The world’s biggest light bulb is located in Edison, New Jersey. It’s 14 feet tall, weighs eight tons, and sits on top of the Thomas Edison Memorial Tower.

- Electricity is present in our bodies – our nerve cells use it to pass signals to our muscles.
- Iceland is the country that uses the most electricity annually. Their consumption is about 23% more than the U.S.

Video Resources

Videos Links for circuit

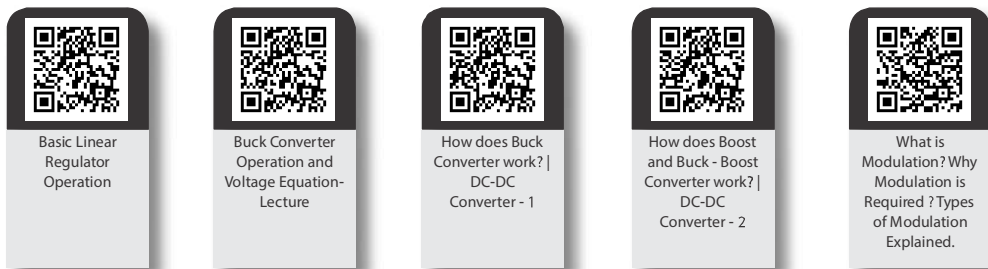

5.1. DC-DC POWER CONVERTERS

DC-DC power converters are employed in a variety of applications such as power supplies for personal computers, laptop, office equipment, spacecraft power systems, telecommunications equipment, dc motor drives etc. The input to a dc-dc converter is an unregulated dc voltage and it produces a regulated output voltage of different magnitude.

Classification of Converters

The dc-dc converters may be classified as:

Buck Converter: These are *step down* converters, their output voltage is less than the dc input voltage.

Boost converter: These are *step up* converters, their output voltage is more than the dc input voltage.

Buck-Boost converter: Their output voltage can be either higher or lower than the dc input voltage.

5.2. SIMPLE LINEAR VOLTAGE REGULATOR

DC voltage can be reduced or stepped down on the load side by using a simple linear voltage regulator, as shown in Fig. 5.1. The most basic form of step down transition is to use a resistor as a potential divider or voltage dropper. In some cases a zener diode may also be used to stabilise the voltage. The

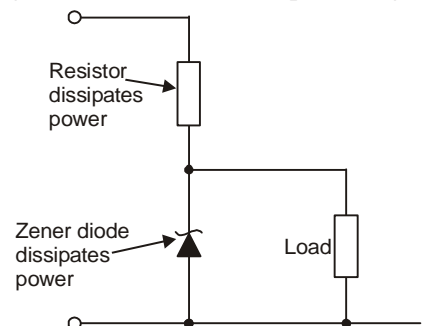


Fig. 5.1: Linear voltage regulator

issue with this form of voltage dropper or step down converter is that it is very wasteful in terms of power. Any voltage dropped across the resistor will be dissipated as heat, and any current flowing through the zener diode will also dissipate heat. Both of these elements result on the loss of valuable energy.

Moreover, in such cases, when voltage is decreased current is not increased. Whereas, in case of buck-converters, when voltage is stepped down, current is stepped up (*i.e.* $P_{in} = P_{out}$).

5.3. BUCK CONVERTERS

Buck converter is a DC-to-DC power converter which steps down voltage and steps up the current simultaneously such that input power supply remains the same as that of the output (load).

Conventional Circuit

The block diagram (conventional circuit) and pictorial view of a *buck converter* is shown in Fig. 5.2 and 5.3 respectively. It essentially consists of;

- **At least two semiconductor devices:** a diode and a transistor, however, in modern buck converters usually diode is replaced with a second transistor and transistor is replaced with *MOSFET* or *IGBT*.
- **At least one energy storage element:** a capacitor, inductor or the two in combination.
- **Extra capacitors (or sometimes a combination of capacitors and inductors):** these are used to filter ripples. These components are normally added to output (load-side) and input (supply-side); not shown here for simplicity.

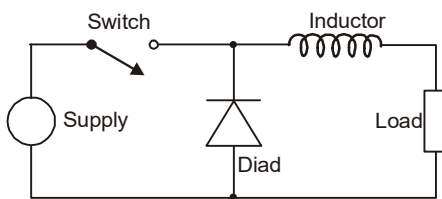


Fig. 5.2: Buck converter circuit diagram.

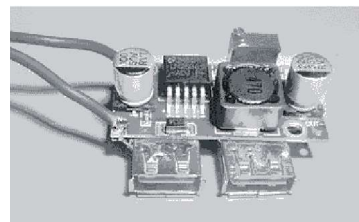


Fig. 5.3: Pictorial view of buck converter
The switch is typically a MOSFET, IGBT or BJT

Working

The two circuit configurations of a buck converter *i.e.* On-state, when the switch is closed, and Off-state, when the switch is open are shown in Fig. 5.4 and 5.5 respectively. The arrows indicate the direction of flow of conventional current.

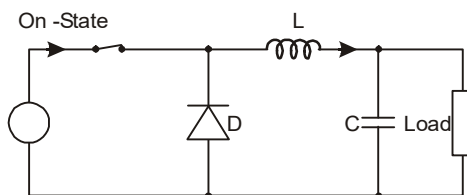


Fig. 5.4: On-state

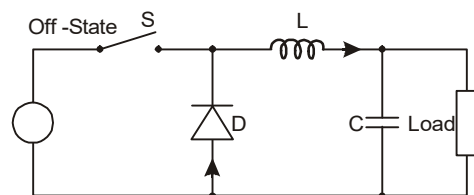


Fig. 5.5: Off-state

For ideal operation, it is assumed that

- All the components are perfect specifically, the switch and the diode have zero voltage drop when on and zero current flow when off, and the inductor has zero series resistance
- The input and output voltages do not change over the course of a cycle. It implies that the output capacitance is being infinite.

The functioning of buck converter is best understood in terms of the relation between current and voltage of the inductor.

Off-state

When the switch is open (off-state), as shown in Fig. 5.2, the current in the circuit is zero.

On-state

- When at first instant the switch is closed (on-state), as shown in Fig. 5.4, the current will begin to increase, and the inductor will produce an opposing voltage across its terminals in response to the changing current. This voltage drop counteracts the voltage of the source and therefore reduces the net voltage across the load. As the rate of change of current decreases, the voltage across the inductor also decreases, this increases the voltage across the load. During this time, the inductor stores energy in the form of a magnetic field.
- If the switch is opened while the current is still changing, then there will always be a voltage drop across the inductor, so the net voltage at the load will always be less than the input voltage *i.e.* source voltage.

Off-state

- When the switch is opened again (off-state), as shown in Fig. 5.5, the current will start decreasing. The decreasing current will produce a voltage drop across the inductor which will be opposite to the drop at on-state and hence, the inductor becomes a Current Source. The stored energy in the inductor's magnetic field is released which supports the current flow through the load. This off-state current is added to the current flowing during on-state, hence, the total current becomes greater than the average input current (being zero during off-state).
- Thus, during off-state, there is reduction in voltage but this reduction is compensated by the increase in average current. Ideally it preserves the power provided to the load. It all happens only because during off-state, the inductor is discharging its stored energy into the rest of the circuit.

If the switch is closed again before the inductor is fully discharged then the voltage at the load will always be greater than the input voltage.

The buck converters may work in continuous mode or discontinuous mode.

Continuous mode

A buck converter is said to be operated in continuous mode if the current through the inductor (I_L) never falls to zero during the commutation cycle. To describe the operating principle of buck converter in this mode, consider the plots as shown in Fig. 5.6.

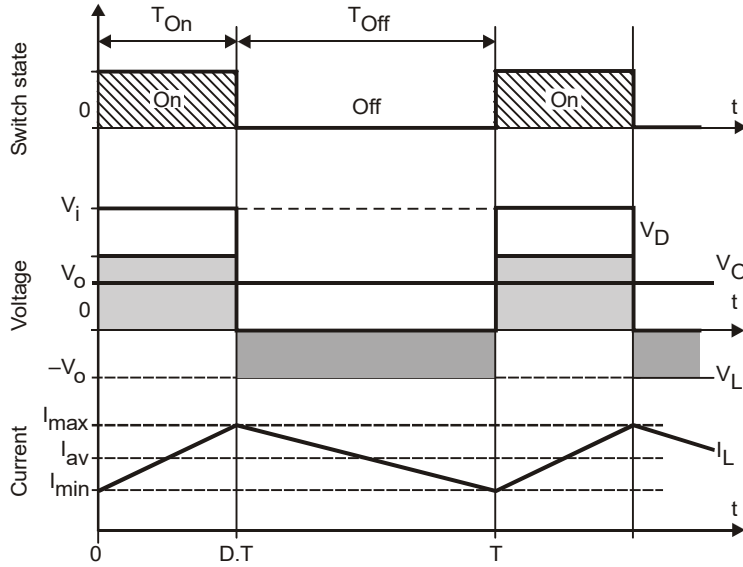


Fig. 5.6: Evolution of the voltages and currents with time in an ideal buck converter operating in continuous mode.

- When the switch is closed, as shown in Fig. 5.4, the voltage across the inductor is $V_L = V_i - V_o$. The current through the inductor rises linearly (in approximation, so long as the voltage drop is almost constant). At this instant, the diode is reverse-biased by the voltage source V , hence, no current flows through it;
- When the switch is opened, as shown in Fig. 5.5, the diode is forward biased. The voltage across the inductor is $V_L = -V_o$ (drop in diode is neglected). Current I_L decreases.

The energy stored in magnetic field of inductor L is $E = \frac{1}{2} L I_L^2$

Since I_L increases in L during on-time, the energy stored in it also increases and then decreases during the off-state. It shows that L is used to transfer energy from the input to the output of the converter.

- The rate of change of I_L can be determined from: $V_L = L \frac{dI_L}{dt}$
- During the on-state, the value of V_L will be equal to $V_i - V_o$ and during the off-state it will be $-V_o$. Therefore, the increase in current during the on-state is given by the relation:

$$\Delta I_{Lon} = \int_0^{t_{on}} \frac{V_L}{L} dt = \frac{(V_i - V_o)}{L} t_{on}, t_{on} = DT$$

Where D is called the *Duty Cycle* (a scalar quantity) which lies between 0 and 1.

- On the other hand, during off-state the current decreases. It is given by the relation:

$$\Delta I_{Loff} = \int_{t_{on}}^{T=t_{on}+t_{off}} \frac{V_L}{L} dt = \frac{V_o}{L} t_{off}, t_{off} = (1-D)T$$

- Assuming that the converter operates in the steady state condition, the energy stored in each component at the end of a commutation cycle T is equal to that at the beginning of the cycle. It shows that the magnitude of current I_L remains the same at $t = 0$ and at $t = T$ (see figure 5.6). From the above equations we get:

$$\Delta I_{L_{on}} + \Delta I_{L_{off}} = 0 \quad \text{or} \quad \frac{V_i - V_o}{L} t_{on} - \frac{V_o}{L} t_{off} = 0$$

- As per the above equations, the quantities can be represented graphically, as shown in Fig. 5.6. Here ΔL_{on} and ΔL_{off} are represented by different rectangles (gray and dark gray). Under steady-state conditions, the area of rectangle for the quantity $(V_i - V_o) t_{on}$ must be equal to the area of rectangle for the quantity $-V_o t_{off}$. From the Fig. 5.6, it is clear that $t_{on} = DT$ and $t_{off} = (1 - D) T$

$$\text{This yields; } (V_i - V_o) DT - V_o (1 - D) T = 0 \quad \text{or} \quad V_o - D V_i = 0 \Rightarrow D = \frac{V_o}{V_i}$$

- The above equation reveals that the output voltage of the converter varies linearly with the duty cycle for a given input voltage. As the duty cycle D is equal to the ratio between t_{on} and the period T , it cannot be more than 1. Therefore, $V_o \leq V_i$. This is why this converter is referred to as step-down converter.

For example, if 12 V dc is required to be stepped down to 3 V dc (i.e. the output voltage is one quarter of the input voltage) then we need a converter having a duty cycle of 25%.

Discontinuous mode

A buck converter is said to be operated in discontinuous mode if the current through the inductor (I_L) falls to zero for some duration of the commutation cycle. A buck converter is operated in this mode only when the amount of energy required by the load is too small. The only difference in the principle described above is that the inductor is completely discharged at the end of the commutation cycle as shown in figure 5.7. However, it affects on some of the previous equations.

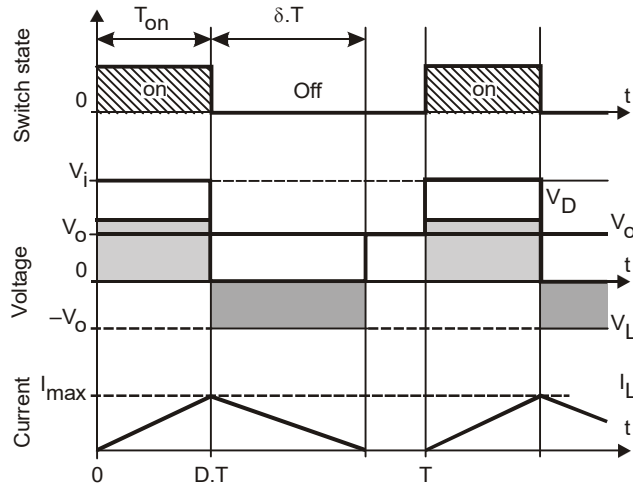


Fig. 5.7: Evolution of the voltages and currents with time in an ideal buck converter operating in discontinuous mode.

- In these converters, in every commutation cycle, the current falls to zero. This results in the discharging of the output capacitor which causes more switching losses. To minimize these losses a different control technique known as *pulse-frequency modulation* is adopted.
- Still it is considered that the converter operates in steady state. Therefore, the energy in the inductor is considered to be the same at the beginning as well as at the end of the cycle (here in discontinuous mode, it is zero). This means that the average value of the inductor voltage (V_L) is zero; *i.e.* the area of the light and dark rectangles in Fig. 5.7 are the same.

$$\text{This yields; } (V_i - V_o) DT - V_o \delta T = 0$$

$$\text{So the value of } \delta \text{ is, } \delta = \frac{V_i - V_o}{V_o} D$$

- The output current delivered to the load (I_o) is constant since we have considered that the output capacitor is large enough to maintain a constant voltage across its terminals during a commutation cycle. It implies that the current flowing through the capacitor has a zero average value. Therefore, we have : $I_L' = I_o$ where I_L' is the average value of the inductor current
- It can be seen in Fig 5.7 that the inductor current waveform has a triangular shape. Therefore, the average value of I_L can be sorted out geometrically as follow:

$$I_L' = \left(\frac{1}{2} I_{L\max} DT + \frac{1}{2} I_{L\max} \delta T \right) \frac{1}{T} = \frac{I_{L\max} (D + \delta)}{2} = I_o$$

- In the beginning, the inductor current is zero and rises during t_{on} up to $I_{L\max}$. Therefore, $I_{L\max}$ will be equal to:

$$I_{L\max} = \frac{V_i - V_o}{L} DT$$

- Substituting the value of $I_{L\max}$ in the previous equation, we get,

$$I_o = \frac{(V_i - V_o) DT (D + \delta)}{2L}$$

- After substituting the value of δ in the above expression , it yields as :

$$I_o = \frac{(V_i - V_o) DT \left(D + \frac{V_i - V_o}{V_o} D \right)}{2L} \quad \text{or} \quad V_o = V_i \frac{1}{\frac{2LI_o}{D^2 V_i T} + 1}$$

Conclusion: From the above expression, it is clear that the output voltage of a buck converter operating in discontinuous mode is

- much more complicated than its counterpart of the continuous mode
- the output voltage is now a function not only of the input voltage (V_i) and the duty cycle D , but it also depends upon the inductor value (L), the commutation period (T) and the output current (I_o).

Thus, continuous mode is always preferred over discontinuous mode.

Applications

Buck converters are remarkably efficient (often higher than 90%). These are very useful for converting a computer's main (bulk) supply voltage (often 12V) down to lower voltages needed by *USB*, *DRAM* and the *CPU* (1.8V or less).

5.4. BOOST CONVERTERS

Boost converter is a *DC-to-DC* power converter which steps up voltage and steps down the current simultaneously such that input power supply remains the same as that of the output (load).

Conventional circuit

The block diagram (conventional circuit) and pictorial view of a boost converter is shown in Fig. 5.8 and 5.9 respectively. It essentially consists of;

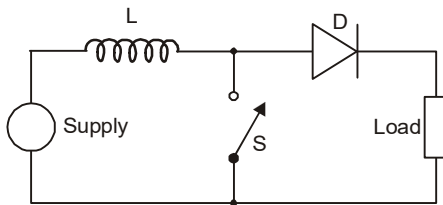


Fig. 5.8: Boost converter circuit diagram.



Fig. 5.9: Pictorial view of boost converter

The switch is typically a *MOSFET*, *IGBT* or *BJT*

- *At least two semiconductors* – a diode and a transistor, however, in modern buck converters usually diode is replaced with a second transistor and transistor is replaced with *MOSFET* or *IGBT*.
- *At least one energy storage element* – a capacitor, inductor or the two in combination.
- *Extra capacitors (or sometimes a combination of capacitors and inductors)* – these are used to filter ripples. These components are normally added to output (load-side) and input (supply-side); not shown here for simplicity.

Principle:

The basic principle of a boost converter is the tendency of an inductor to oppose the changes in current by creating and destroying a magnetic field. In this converter, the output voltage is always higher than the input voltage. A schematic of a boost power stage is shown in Fig. 5.10.

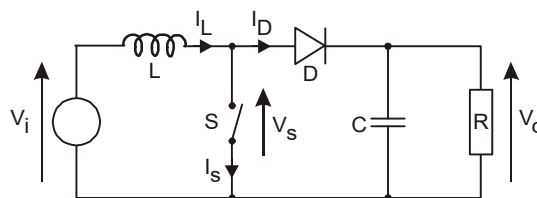


Fig. 5.10: Boost converter schematic

Working

The two circuit configurations of a boost converter *i.e.* On-state, when the switch is closed, and Off-state, when the switch is open are shown in Fig. 5.11 and 5.12 respectively. The arrows indicate the direction of flow of conventional current.

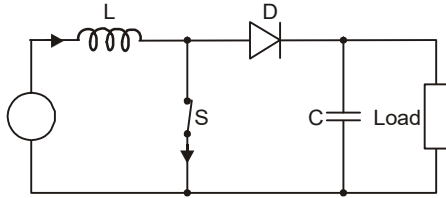


Fig. 5.11: On-state (Boost converter)

For ideal operation, it is assumed that

- All the components are perfect specifically, the switch and the diode have zero voltage drop when on and zero current flow when off, and the inductor has zero series resistance
- The input and output voltages do not change over the course of a cycle. It implies that the output capacitance is being infinite.

To understand its functioning proceed as follows:

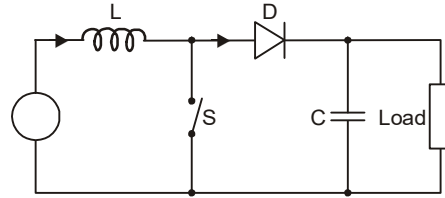


Fig. 5.12: Off-state (Boost converter)

On-state

- When the switch is closed (On-state), current flows through the inductor in clockwise direction, a magnetic field is developed and some energy is stored in it and the inductor attain a polarity.

Off-state

- When the switch is opened (Off-state), current will reduce since the impedance is higher. The magnetic field previously created will collapse to maintain the current towards the load. Thus, the *emf* of the two sources will be in series causing a higher voltage to charge the capacitor through the diode *D*.

Continuous mode

- If the switch is operating fast enough, the inductor will not discharge fully in between charging stages, and the load will always see a voltage greater than that of the input source alone when the switch is opened. Moreover, when the switch is in open position, the capacitor which is in parallel with the load is charged to this combined voltage.
- Again when the switch is closed, the right hand side is shorted out from the left hand side, in this stage the capacitor is able to provide the necessary voltage and energy to the load. During this time, the blocking diode prevents the capacitor from discharging through the switch. Obviously, the switch must be opened again fast enough to prevent the capacitor from discharging too much.

It concludes that a Boost converter works under 2 distinct states:

- in the On-state (when the switch is closed), this results in an increase in the inductor current;
- in the Off-state (when the switch is open), in this case the only path offered to inductor current is through the flyback diode D , the capacitor C and the load R . This results in transferring of energy accumulated during the On-state into the capacitor.

The boost converters may work in continuous mode or discontinuous mode.

Continuous mode

- A boost converter is said to be operated in continuous mode if the current through the inductor (I_L) never falls to zero during the commutation cycle. To describe the operating principle of boost converter in this mode, consider the plots as shown in Fig. 5.13.

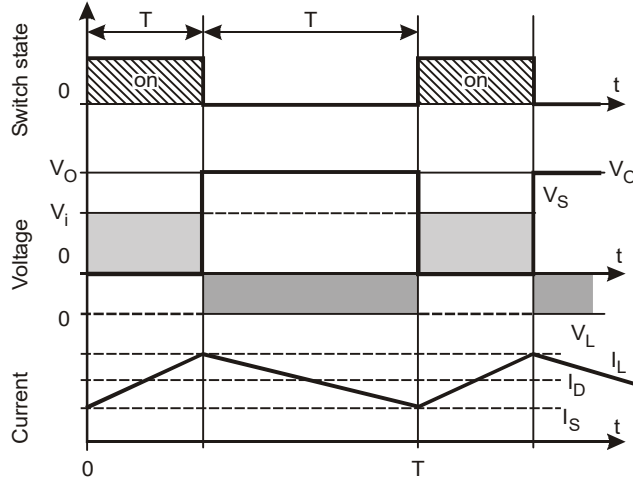


Fig. 5.13: Waveforms of current and voltage in a boost converter operating in continuous mode.

- When the switch is closed (on-state), as shown in Fig. 5.11, the voltage which appears across the inductor is V_i . This causes a change in current (I_L) flowing through the inductor during a time period (t), it is given by the formula:

$$\frac{\Delta I_L}{\Delta t} = \frac{V_i}{L} \text{ where } L \text{ is the inductance of the inductor}$$

At the end of the On-state, the current in the inductor increases to I_L , it changes as per the relation:

$$\Delta I_{L_{on}} = \frac{1}{L} \int_0^{DT} V_i dt = \frac{DT}{L} V_i \text{ where } D \text{ is the duty cycle.}$$

Duty cycle D represents the fraction of the commutation period T during which the switch is kept On. Therefore, D ranges between 0 (when S is off or never on) and 1 (when S is always on).

- When the switch is opened (off-state), as shown in Fig. 5.12, the inductor current flows through the load. As it is Assumed that there is zero voltage drop in the diode, and a capacitor is large enough for its voltage to remain constant, the evolution of I_L is:

$$V_i - V_o = L \frac{dI_L}{dt}$$

Hence, the variation of I_L during the Off-period will be:

$$\Delta I_{L_{on}} = \int_{DT}^T \frac{(V_i - V_o) dt}{L} = \frac{(V_i - V_o)(1-D)T}{L}$$

Since the converter operates in steady-state conditions, the amount of energy stored in the inductor is given by:

$$E = \frac{1}{2} L I_L^2$$

For proper functioning, the inductor current has to be the same at the start and at the end of the commutation cycle. It means the overall change in the current (that is the sum of the changes) is zero:

$$\text{Therefore, } \Delta I_{L_{on}} + \Delta I_{L_{off}} = 0$$

Substituting the value of $\Delta I_{L_{on}}$ and $\Delta I_{L_{off}}$ the above expression yields to:

$$\Delta I_{L_{on}} + \Delta I_{L_{off}} = \frac{V_i DT}{L} + \frac{(V_i - V_o)(1-D)T}{L} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = \frac{1}{1-D}$$

The above equation reveals that the output voltage is always higher than the input voltage (as the duty cycle varies from 0 to 1). Theoretically it may increase to infinity as D approaches 1.

That is why this converter is considered as a *step-up* converter.

Duty cycle can be determined by rearranging the above equation *i.e.*

$$D = 1 - \frac{V_i}{V_o}$$

Discontinuous mode

A boost converter is said to be operated in discontinuous mode if the inductor is completely discharged before the end of a whole commutation cycle. This commonly occurs under light loads. In this case, the current through the inductor falls to zero during part of the period (see waveforms in figure 5.14). Although the difference is slight but it has a strong effect on the output voltage equation. The voltage gain can be calculated as follows:

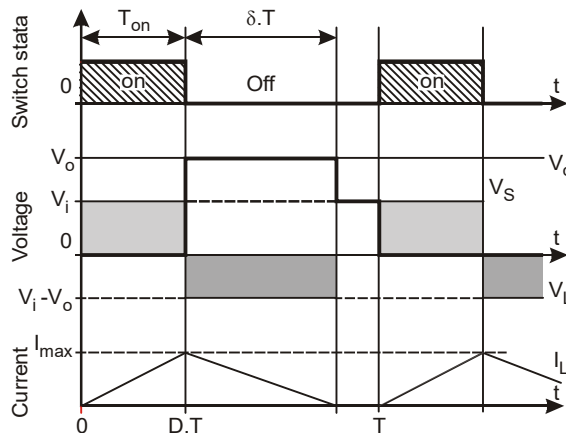


Fig. 5.14: Waveforms of current and voltage in a boost converter operating in discontinuous mode.

As at the beginning of the cycle, the inductor current is zero, its maximum value $I_{L_{max}}$ (at $t = DT$) is

$$I_{L_{max}} = \frac{V_i DT}{L}$$

During the off-period, I_L falls to zero after δT , $I_{L_{max}} + \frac{(V_i - V_o) \delta T}{L} = 0$

Solving the above two equations, we can determine the value of δ , i.e. $\delta = \frac{V_i D}{V_o - V_i}$

The load current I_o is equal to the diode current (I_D). It can be visualised in Fig. 5.14. The diode current is equal to the inductor current during the off-state. Therefore, the output current can be written as:

$$I_o = I_D = \frac{I_{L_{max}}}{2} \delta$$

Substituting the value of $I_{L_{max}}$ and δ the expressions yields to:

$$I_o = \frac{V_i DT}{2L} \cdot \frac{V_i D}{V_o - V_i} = \frac{V_i^2 D^2 T}{2L (V_o - V_i)}$$

Thus, the output voltage gain: $\frac{V_o}{V_i} = 1 + \frac{V_i D^2 T}{2LI_o}$

This expression of the output voltage gain in comparison to the output voltage gain for continuous mode is much more complicated. Moreover, in discontinuous operation, the output voltage gain not only depends on the duty cycle (D), but it also depends upon the inductor value (L), the input voltage (V_i), the commutation period (T) and the output current (I_o).

Applications

Boost converters are remarkably efficient (often higher than 90%). Battery power systems often stack cells in series to achieve higher voltage. However, sufficient stacking of cells is not possible in many high voltage applications due to lack of space. Boost converters can increase the voltage and reduce the number of cells. Two battery-powered applications that use boost converters are used in hybrid electric vehicles (*HEV*) and lighting systems.

Boost converter are used to step-up from 2.4 V provided by two AA rechargeable cells to 9 V for TI calculator. Boost converters also power devices at smaller scale applications, such as portable lighting systems. A *white LED* typically requires 3.3 V to emit light, and a boost converter can step up the voltage from a single 1.5 V alkaline cell to power the lamp.

5.5. BUCK-BOOST CONVERTERS

Buck–boost converter is a type of *DC-to-DC power converter* that has the ability to step-down or step-up the output voltage (magnitude) and steps-up or step-down the current simultaneously such that input power supply remains the same as that of the output (load).

Two different topologies (network technologies) are employed for *buck–boost converter*. Both of them can produce a range of output voltages, ranging from much larger (in absolute magnitude) than the input voltage, down to almost zero.

Conventional circuit

The block diagram (conventional circuit) and pictorial view of a buck-boost converter is shown in Fig. 5.15 and 5.16 respectively.

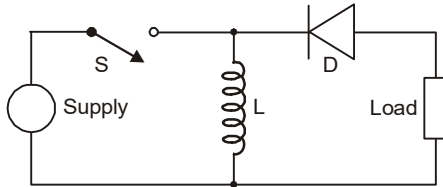


Fig. 5.15: The basic schematic of an inverting buck-boost converter.



Fig. 5.16: Pictorial view of a buck-boost converter

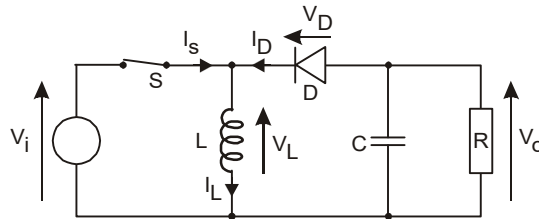


Fig. 5.17: Schematic of a buck-boost converter.

A detailed schematic diagram of a *buck-boost converter* is shown in Fig. 5.17. It essentially consists of;

- *At least two semiconductors* : a diode and a transistor, however, in modern buck converters usually diode is replaced with a second transistor and transistor is replaced with *MOSFET* or *IGBT*.
- *At least one energy storage element* : a capacitor, inductor or the two in combination.
- *Extra capacitors (or sometimes a combination of capacitors and inductors)* : these are used to filter ripples. These components are normally added to output (load-side) and input (supply-side); not shown here for simplicity.

The inverting topology or network technology

In this topology, the output voltage is of the *opposite polarity* than the input. This is a switched-mode power supply. It is a similar network technology which is used in boost converter and the buck converter. The output voltage is adjustable based on the duty cycle of the switching transistor. The drawback in this network technology is that the switch of the converter is not grounded; this complicates the driving circuitry. However, this drawback is of no consequence if the power supply is isolated from the load circuit.

Principle of operation

The basic principle of the inverting buck-boost converter is fairly simple (see figure 2):

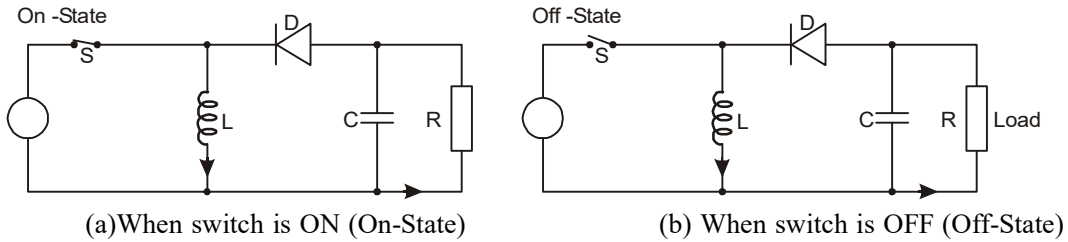


Fig. 5.18: The two operating states of a buck-boost converter

- When the switch is in the On-state, the input voltage source is directly connected to the inductor (L). This results in accumulation of energy in L in the form of magnetic field. In this stage, the energy is supplies to the load by the capacitor.
- When the switch is in the Off-state, the inductor is connected to the load and capacitor. Therefore, energy is supplied by the inductor L to load R and capacitor C .

In comparison to the buck and boost converters, the characteristics of the inverting buck-boost converter are mainly:

- polarity of the output voltage is opposite to that of the input, the output voltage can vary continuously from 0 to ∞ (for an ideal converter). The output voltage ranges for a buck and a boost converter are respectively V_i to 0 and V_i to ∞ .

A buck converter combined with a boost converter (four-switch topology)

The output voltage is typically of the same polarity of the input, and can be lower or higher than the input. Such a non-inverting buck-boost converter may use a single inductor which is used for both the buck inductor mode and the boost inductor mode. In this topology switches are used instead of diodes, that is why it is also called a “four-switch buck-boost converter”.

Principle of operation

In a 4-switch topology, the buck and boost converters are combined. It can operate in either the buck or the boost mode. In both the modes, at a time only one switch controls the duty cycle, another is for commutation and must be operated inversely to the former one, and the remaining two switches are in a fixed position.

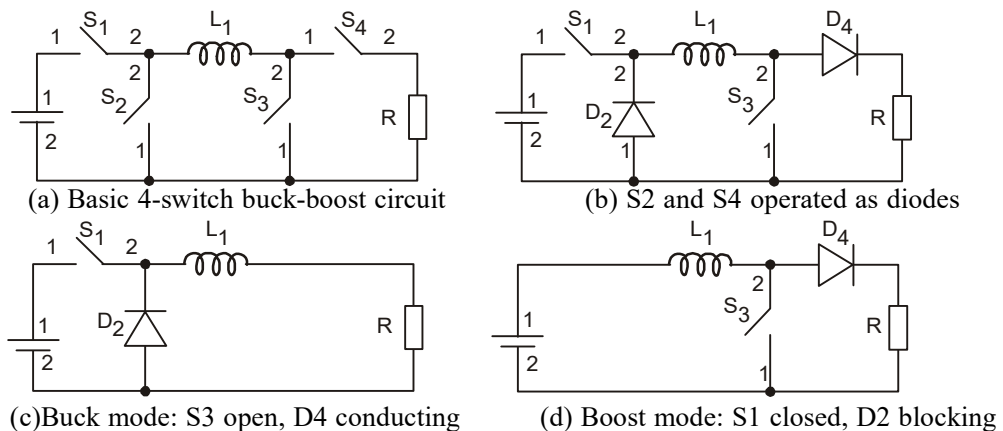


Fig. 5.19 : The basics of the 4-switch topology

A 2-switch buck-boost converter can be built with two diodes also as shown in Fig. 5.19. However, to upgrade the converters, diodes can be replaced with *FET* or *MOSFET*. It doesn't cost much extra but improves the efficiency and reduce the voltage drops.

Continuous and discontinuous mode

The buck-boost converters can also be operated in continuous as well as discontinuous mode similar to buck converters and boost converters. When the current through the inductor (I_L) never falls to zero during the commutation cycle, it is called a continuous mode but if it falls to for some duration then it is called as discontinuous mode.

Applications of Buck boost converter

- It is used in the self regulating power supplies.
- It is used in the Battery power systems.
- Power amplifier applications.
- It has consumer electronics.
- Adaptive control applications.

Advantages of Buck Boost Converter

- It gives higher output voltage.
- Low voltage on *MOSFETs*
- Low operating duct cycle.

5.6. DUTY CYCLE

The period or duration in which a signal or system remains active is called duty cycle.

Duty cycle is commonly expressed as a percentage or a ratio. A period is the time duration that a signal takes to complete an on-and-off cycle.

As a formula, a duty cycle (%) may be expressed as:

$$D = \frac{PW}{T} \times 100\%$$

Similarly, a duty cycle (ratio) may be expressed as:

$$D = \frac{PW}{T}$$

where D is the duty cycle, PW is the pulse width (pulse active time), and T is the total period of the signal.

For a converter, $D = V_{out} / V_{in}$

Accordingly, a 60% duty cycle means the signal is on 60% of the time but off 40% of the time.

Note: The “on time” for a 60% duty cycle could be a fraction of a second, a day, or even a week, depending on the length of the period.

Duty cycle is used to describe the percent time of an active signal in an electrical device (power converter etc.).

5.7. VOLTAGE SOURCE INVERTERS

*A circuit that operates from a stiff dc source and develops an ac output is usually known as **voltage source inverter**.*

If the input dc is a voltage source, the inverter is called a voltage source inverter (*VSI*). One can similarly

think of a current source inverter (*CSI*), where the input to the circuit is a current source. The *VSI* circuit has direct control over ‘output (ac) voltage’ whereas the *CSI* directly controls ‘output (ac) current’. Shape of voltage waveforms output by an ideal *VSI* should be independent of load connected at the output.

The simplest dc voltage source for a *VSI* may be a battery bank, which may consist of several cells in series-parallel combination. Solar photovoltaic cells can be another dc voltage source. An ac voltage supply, after rectification into dc will also qualify as a dc voltage source. A voltage source is called stiff, if the source voltage magnitude does not depend on load connected to it.

Voltage source inverters (*VSI*) are used in uninterruptible power supply (*UPS*) units, adjustable speed drives (*ASD*) for ac motors, electronic frequency changer circuits etc.

Most of us are more familiar with commercially available inverter units used in our houses and offices as stand-by units to power some essential ac loads in case the power supply gets interrupted. In such inverter units, battery supply is used as the input dc voltage source and the inverter circuit converts the dc into ac voltage of desired power frequency (50Hz). The achievable magnitude of ac voltage is limited by the magnitude of input (dc bus) voltage. In ordinary household inverters the battery voltage may be just 12 volt and the inverter circuit may be capable of supplying ac voltage of around 10 volts (rms) only. In such cases the inverter output voltage is stepped up using a transformer to meet the load requirement of, say, 230 volt.

5.8. CONVERSION OF DC INPUT TO AC OUTPUT

Schematic circuit

For conversion of dc into ac, two schematic circuits, using transistor-switches, are shown in Figs. 5.20(a) and 5.21(a). In both the circuits, the transistors work in common emitter configuration and are interconnected in push-pull manner. In order to have a single control signal for the transistor switches, one transistor is of *nnp* type and the other of *pnp* type and their emitters and bases are shorted as shown in the figures. A symmetrical bipolar dc supply is required for both the circuits. Collector of *nnp* transistor is connected to positive dc supply ($+E$), whereas, the collector of *pnp* transistor is connected to negative dc supply of same magnitude ($-E$). A resistive load is connected between the emitter shorting point and the power supply ground.

Working

When the transistors work in active (amplifier) mode

The circuit for the transistors working in active (amplifier) mode is shown in Fig. 5.20(a). When applied base signal is positive, the *pnp* transistor is reverse biased and the *nnp* transistor conducts the load current. Similarly for negative base voltage the *pnp* transistor conducts while *nnp* transistor remains reverse biased. A suitable resistor connected in series with the base signal will limit the base current and keeps it sinusoidal provided the applied (sinusoidal) base signal magnitude is much higher than the base to emitter conduction-voltage drop. Assuming constant gain of the transistor over its working range, the load current can be seen to follow the applied base signal. Fig. 5.20(b) shows a typical load voltage and base signal waveforms. The other transistor will also be dissipating identical power during its conduction.

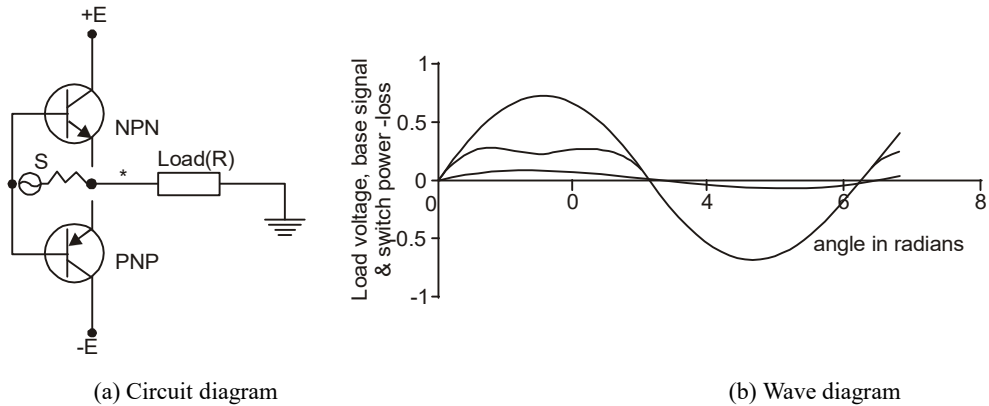


Fig. 5.20: Transistors working in active (amplifier) mode

When the transistors work in switched-mode

The circuit for the transistors working in switched-mode is shown in Fig. 5.21(a). The conducting switch remains fully on having negligible on-state voltage drop and the non-conducting switch remains fully off allowing no leakage current through it. The load voltage waveform output by switched-mode circuit of Fig. 5.21(b) is rectangular with magnitude $+E$ when the *nnp* transistor is on and $-E$ when *pnnp* transistor is

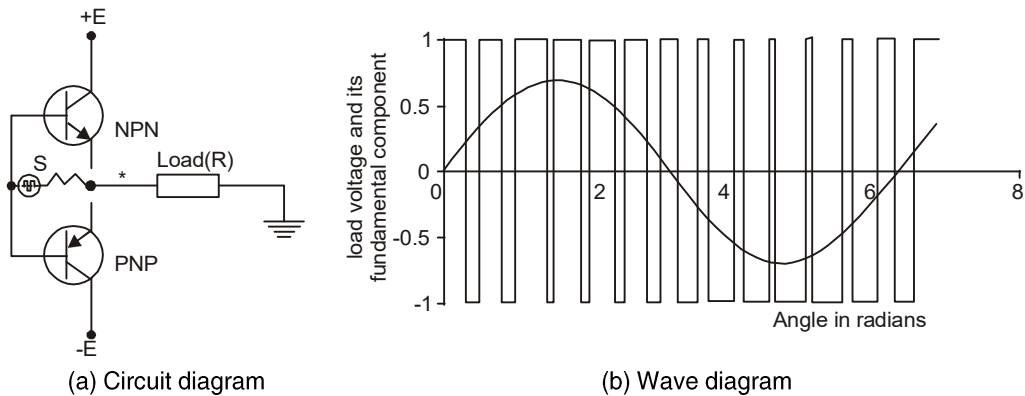


Fig. 5.21: Transistors working in switch mode

on. Such waveform is shown in Fig. 5.21(b). The on and off durations of the two transistors are controlled so that (i) the resulting rectangular waveform has no dc component (ii) has a fundamental (sinusoidal) component of desired frequency and magnitude and (iii) the frequencies of unwanted harmonic voltages are much higher than that of the fundamental component so that those can be filtered. The fundamental sine wave is also shown in Fig. 5.21 (b). This waveform is identical to the sinusoidal output voltage waveform of the system voltage.

Conclusion

Both amplifier mode and switched mode circuits are capable of producing ac voltages of controllable magnitude and frequency. However, the amplifier circuit is not acceptable in power-electronic applications due to high switching power loss. The switched mode circuit is acceptable although it generates significant amount of unwanted harmonic voltages along with the desired fundamental frequency voltage. These

high frequency voltage harmonics can easily be blocked by using small size filters. Thus, a desired quality of load voltage can be obtained.

5.9. GENERAL STRUCTURE OF VOLTAGE SOURCE INVERTERS (VSI)

Single-phase voltage source inverter

A typical power-circuit topologies of a single-phase voltage source inverter is shown in Fig. 5.22. For medium output power applications, only one dc source and the preferred devices are:

- (i) n-channel IGBTs (Q_1, Q_2, Q_3 etc.- act as fast and controllable switches)
- (ii) a large dc link capacitor (C_{dc})
- (iii) fast recovery diodes (D_1, D_2, D_3 etc.)

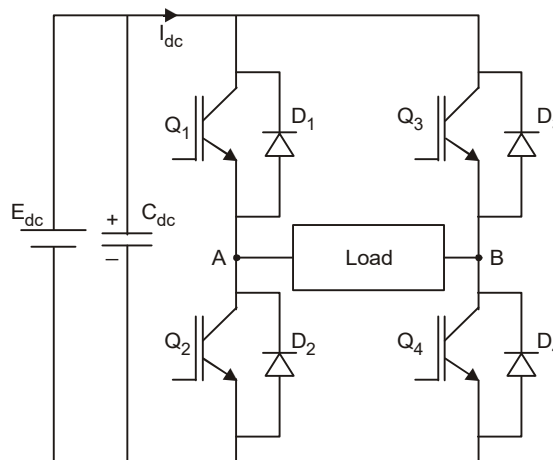


Fig. 5.22: Topology of a single-phase VSI

The current supplied by the dc bus to the inverter switches is referred as dc link current and has been shown as ' i_{dc} ' in Fig. 5.22. The magnitude of dc link current often changes in as the inverter switches (Q_1, Q_2, Q_3 and Q_4) are turned on and off. The inverter switches work in fully-on or fully-off mode to achieve reduced losses in the switches. The step change in instantaneous dc link current occurs even if the ac load at the inverter output is drawing steady power. However, average magnitude of the dc link current remains positive if net power-flow is from dc bus to ac load. The net power-flow direction reverses if the ac load connected to the inverter is regenerating. Under regeneration, the mean magnitude of dc link current is negative.

For an ideal input (dc) supply, with no series impedance, the dc link capacitor does not have any role. However a practical voltage supply may have considerable amount of output impedance. The supply line impedance, if not bypassed by a sufficiently large dc link capacitor, may cause considerable voltage spike at the dc bus during inverter operation. This may result in deterioration of output voltage quality, it may also cause malfunction of the inverter switches as the bus voltage appears across the non-conducting switches of the inverter. Moreover, in the absence of dc link capacitor, the series inductance of the supply line will prevent quick build up or fall of current through it and the circuit behaves differently from the ideal VSI where the dc voltage supply is supposed to allow rise and fall in current as per the demand of the inverter circuit.

Therefore, dc link capacitor should be applied to remove the ripples. These should be put very close to the switches so that it provides a low impedance path to the high frequency component of the switching currents. The capacitor itself must be of good quality with very low equivalent series resistor and inductor.

When switches are to be connected in bridge fashion, using n-channel *IGBTs*, the gate (base) signals to the *VSI* switches need to be isolated.

While framing the circuit, the leads that interconnect switches and diodes to the dc bus must be of minimum length to avoid insertion of significant amount of stray inductances in the circuit. The overall layout of the power circuit has a significant effect over the performance of the inverter circuit.

A diode in anti-parallel with each controlled switch, like *IGBT*, is used in *VSI* to allow a non-unity power factor load at the output.

Essentially, it is a full bridge circuit as shown in Fig. 5.22. The circuit has two legs of switches, each leg consisting of an upper switch and a lower switch. Junction point of the upper and lower switches is the output point of that particular leg. Voltage between output point of legs and the mid-potential of the dc bus is called as '**pole voltage**' referred to the mid potential of the dc bus. One may think of pole voltage referred to negative bus or referred to positive bus too but unless otherwise mentioned pole voltages are assumed to be referred to the mid-potential of the dc bus. The two pole voltages of the single-phase bridge inverter generally have same magnitude and frequency but their phases are 180° apart. Thus the load connected between these two pole outputs (between points 'A' and 'B') will have a voltage equal to twice the magnitude of the individual pole voltage.

Three-phase voltage source inverter

A typical power-circuit topologies of a three-phase voltage source inverter is shown in Fig. 5.23. For medium output power applications, only one dc source and the preferred devices are:

- (i) n-channel *IGBTs* ($Q_1, Q_2, Q_3, Q_4, Q_5, Q_6$ - act as fast and controllable switches)
- (ii) a large dc link capacitor (C_{dc})
- (iii) fast recovery diodes ($D_1, D_2, D_3, D_4, D_5, D_6$)

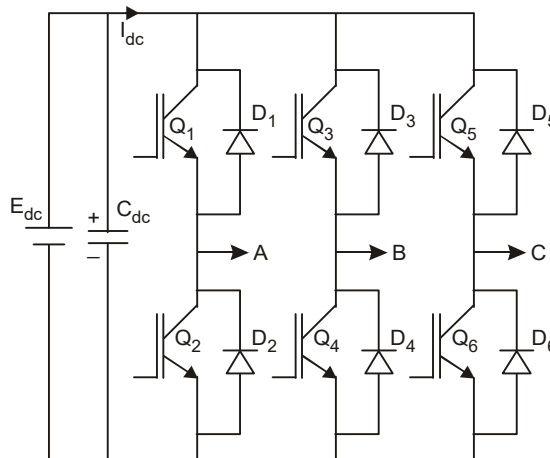


Fig. 5.23: Topology of a three-phase VSI

The working of 3-phase inverter bridge, shown in Fig. 5.23, is similar as that of 1-phase inverter. The only difference is that the pole voltages of the 3-phase inverter bridge are 120° phase apart across the terminals A , B and C .

5.10. MODULATION

*The process of varying some characteristic (e.g. amplitude, frequency or phase) of a carrier wave by the *modulating signal is called **modulation**.*

The audio (message) signals or waves have small power and cannot be transmitted to long distances. Therefore, these waves or signals are 'added' to the high frequency (carrier) waves because these have sufficient power to travel through long distances.

The carrier wave is usually represented by the expression ;

$$v_c = V_c \sin (\phi_c t + \phi)$$

The three variables in this equation are amplitude V_c ; frequency f_c (as $\omega_c = 2\pi f_c$) and phase angle ϕ . Therefore, the audio waves are *added* to the carrier waves in such a way that some characteristic (amplitude frequency or phase) of carrier varies in accordance with the signal. This process by which the carrier is *modified* in accordance with the signal is called ****modulation**.

5.11. NEED OF MODULATION

Modulation is extremely necessary in radio/TV communication, processing weak signals in instrumentation and in other electronic systems to

- (i) increases the operating range, (ii) transmit the signal without wire and (iii) reduces the size of transmitting antenna.

5.12. TYPES OF MODULATION

As discussed earlier, modulation is a process of varying some characteristic *i.e.* amplitude, frequency or phase of the carrier wave in accordance with the message signal. Accordingly, the modulation is of three types, namely ;

- (i) amplitude modulation (ii) frequency modulation (iii) phase modulation.

We shall confine our attention on the first two types of modulations *i.e.* amplitude modulation and frequency modulation. It is because in India, amplitude modulation is employed in radio broadcasting system, whereas, frequency modulation is employed for sound signals and amplitude is employed for picture (video) signals in *TV* transmission.

5.13. AMPLITUDE MODULATION

*The process by which the amplitude of a carrier wave is varied in accordance with the modulating signal is called **amplitude modulation**.*

Principle of amplitude modulation is represented in Fig. 5.24 The three waves shown in Fig. 5.24 are (a) modulating signal, (b) carrier wave and (c) the resultant of amplitude modulated wave. It may be noted that when a signal of frequency f_s is modulated with carrier wave of frequency f_c , a

* The modulating signal may be audio or video signal.

** In fact, the name modulation has come from modification.

resultant wave (modulated wave) is produced. It retains the frequency of carrier wave *i.e.* f_c , but its amplitude varies in accordance with the signal. The amplitude of the resultant wave varies in both the halves (positive and negative) simultaneously. It is because when the signal is increasing in the positive sense, the amplitude of the carrier wave also increases. On the other hand when the signal is changing in the negative sense, the amplitude of the carriers decreases. This modulation (mixing of two waves) is done with the help of an electron circuit using solid state devices or valves. The circuit is known as *modulator*.

The important points to be noted are ;

- (i) Amplitude of the modulated wave varies in accordance with message signal.
- (ii) Frequency of the modulated wave is the same (f_c) as that of the carrier frequency.
- (iii) While doing modulation, the amplitude of carrier varies on both the halves simultaneously in accordance with the signal.

5.14. MODULATION FACTOR AND ITS SIGNIFICANCE

We have seen that in amplitude modulation, the amplitude of the carrier increases during positive half cycle of the signal, whereas it decreases during the negative half-cycle of the signal (See Fig. 5.24). The extent to which the amplitude of carrier wave is changed by the signal is described by the factor called *modulation factor*. It may be defined as under :

The ratio of change in amplitude of carrier wave due to modulation to the original amplitude of the normal carrier wave is called modulation factor. It is generally represented by letter 'm'.

$$\text{Modulation factor, } m = \frac{\text{Change in amplitude of carrier}}{\text{amplitude of normal carrier}}$$

The above relation clearly shows that the modulation factor depends upon the amplitude of both the waves ; carrier and signal.

Significance of modulation factor : In amplitude modulation, the amplitude of the carrier wave varies as per the modulating signal wave. The degree of modulation factor shows the strength of message signal *i.e.* the greater the degree of modulation (m), the stronger and clear will be the message signal and vice-versa. Hence, for $m = 1$ or 100%, the message signal being transmitted will be the strongest. However, when the carrier is over modulated (*i.e.* $m > 1$ or 100%), the AM wave will be clipped off and a huge distortion will occur during reception. Therefore, degree of modulation should *never exceed* 100%.

5.15. ANALYSIS OF AMPLITUDE MODULATED WAVE

Let the carrier voltage wave be represented by the equation ;

$$v_c = V_c \sin (\omega_c t + \phi)$$

For simplicity, consider phase angle ϕ to be zero, then

$$v_c = V_c \sin \omega_c t \quad \dots(i)$$

where,

$$v_c = \text{Instantaneous value of carrier}$$

$$V_c = \text{amplitude of carrier}$$

$$\omega_c = 2\pi f_c = \text{angular velocity at carrier frequency } f_c.$$

Let this carrier is modulated with the modulating signal represented by the equation ;

$$v_s = V_s \cos \omega_s t \quad \dots(ii)$$

where,

v_s = instantaneous value of signal

V_s = amplitude of signal

$\omega_s = 2\pi f_s$ = angular velocity at signal frequency f_s

If m is the modulation factor, then

$$m = \frac{V_s}{V_c} \quad \text{or} \quad V_s = mV_c \quad \dots(iii)$$

Substituting the value of V_s in eqn. (ii), we get,

$$v_s = mV_c \cos \omega_s t \quad \dots(iv)$$

In amplitude modulation, the amplitude of the carrier wave (V_c) varies in accordance with the signal as shown in Fig. 5.24. Hence, the amplitude of the resultant modulated wave varies at signal frequency. Therefore, the amplitude of AM wave is given as ;

$$\begin{aligned} &= V_c + mV_c \cos \omega_s t \\ &= V_c (1 + m \cos \omega_s t) \quad \dots(v) \end{aligned}$$

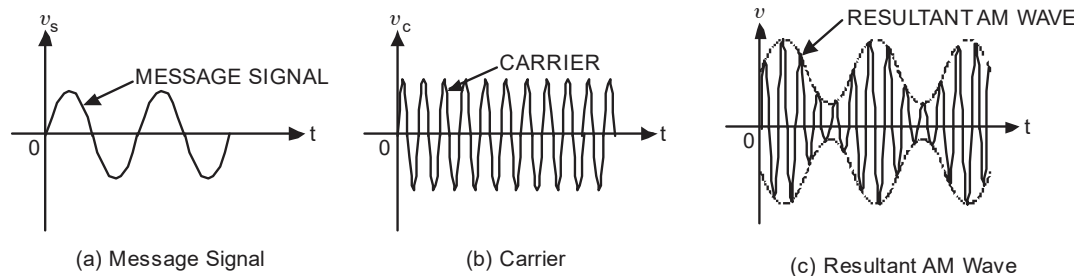


Fig. 5.24: Amplitude modulated wave.

Thus, the instantaneous value of the resultant modulated wave will be ;

$$\begin{aligned} v &= \text{Amplitude} \times \sin \omega_c t \\ &= V_c (1 + m \cos \omega_s t) \sin \omega_c t \\ &= V_c \sin \omega_c t + mV_c \sin \omega_c t \cos \omega_s t \\ &= V_c \sin \omega_c t + \frac{mV_c}{2} (2 \sin \omega_c t \cos \omega_s t) \\ &= V_c \sin \omega_c t + \frac{mV_c}{2} [\sin (\omega_c - \omega_s)t + \sin (\omega_c + \omega_s)t] \\ &= V_c \sin \omega_c t + \frac{mV_c}{2} \sin (\omega_c - \omega_s)t + \frac{mV_c}{2} \sin (\omega_c + \omega_s)t \quad \dots(vi) \end{aligned}$$

The following points may be noted from the expression (vi) of modulated voltage wave ;

* To make the calculation work simple, the signal is represented by cosine of the angle. This only shows that the reckoning point is taken at positive maximum position.

** Here, $f_c = \frac{\omega_c}{2\pi}$; $(f_c - f_s) = \frac{(\omega_c - \omega_s)}{2\pi}$ and $(f_c + f_s) = \frac{(\omega_c + \omega_s)}{2\pi}$

- (i) The *AM* waves is just a summation of the following three waves varying sinusoidally
 - (a) First having magnitude V_c and frequency f_c
 - (b) Second having magnitude $mV_c/2$ and frequency $(f_c - f_s)$
 - (c) Third having magnitude $mV_c/2$ and frequency $(f_c + f_s)$.
- (ii) The *AM* wave contains the fundamental frequency of carrier f_c and produces two more frequencies $(f_c - f_s)$ and $(f_c + f_s)$ known as side-band frequencies. Where, $(f_c - f_s)$ is called lower sideband frequency and $(f_c + f_s)$ is called the upper sideband frequency.

5.16. LIMITATIONS OF AMPLITUDE MODULATION

Amplitude modulation suffers from the following shortcomings :

1. **Poor efficiency** : In amplitude modulation, sidebands contain the signal, therefore, the power existing in the sidebands is only the useful power. The sideband power is only one-third (33.3%) of the total power of *AM* wave. Therefore, it is said that the amplitude modulation transmits signal at poor efficiency.
2. **Noisy reception** : In an *AM* wave, the amplitude variation in carrier contains the signal. Unfortunately, all the natural and man made noises consists of electrical disturbances. Moreover, radio receiver is such a device that it cannot distinguish between the amplitude variations that present due to desired signal or noise. Hence the reception is noisy. For instant, if we start a scooter or motor-cycle near the radio receiver, a noise. Hence the reception is noisy.
3. **Smaller operating range** : Owing to the poor efficiency of amplitude modulation, the transmitters employing this method have smaller range *i.e.* message (signal) cannot be transmitted to longer distances.
4. **Poor audio quality** : Because of more interference of the electrical amplitude disturbances, the audio quality obtained is poor when the signal a transmitter by amplitude modulation.

5.17. FREQUENCY MODULATION

The process by which the frequency of a carrier wave is varied in accordance with the modulating signal is called **frequency modulation**.

Principle of frequency modulation is represented in Fig. 5.25. The three waves shown in the figure are (a) signal, (b) carrier and (c) the resultant frequency modulated wave. It may be noted that when a signal of frequency f_s is modulated with carrier wave of frequency f_c , a resultant modulated wave is produced.

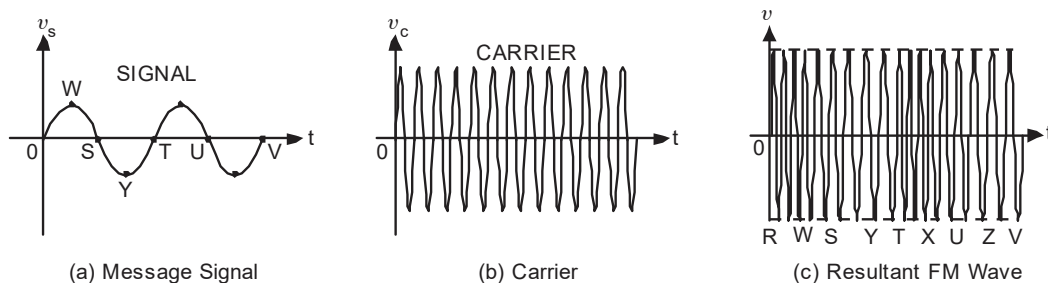


Fig. 5.25: Frequency modulated wave.

* In eqn. $v_c = V_c \sin (\omega_c t + \phi)$, if phase angle ϕ is neglected for simplicity, then $v_c = V_c \sin \omega_c t$.

It retains the amplitude of the carrier wave (*i.e.* V_c) but its frequency varies in accordance with the instantaneous magnitude of the signal. Thus, when the signal voltage is zero, frequency of the carrier wave is not modulated and remains the same (see position *RSTU* and *V* in Fig. 2.25-c). However, when the magnitude of signal is reaching its positive peak value, the frequency of carrier wave (after modulation) also increases as represented by closely spaced cycles (see position *W* and *X* in Fig. 5.25-c). Whereas, during negative peak value, the frequency of carrier decreases as represented by widely spaced cycles (see position *Y* and *Z* in Fig. 5.25-c).

Mathematically ;

In the carrier voltage is given by the equation ;

$$*v_c = V_c \sin \omega_c t$$

and the modulating wave or signal is given by the equation ;

$$v_s = V_s \cos \omega_s t$$

Thus, the instantaneous value of FM voltage is given as;

where V_c = amplitude of carrier wave

$$\omega_c = 2\pi f_c = \text{angular velocity at carrier frequency } f_c$$

$$\omega_s = 2\pi f_s = \text{angular velocity at signal frequency } f_s$$

$$\delta = \text{maximum frequency deviation}$$

$$= k V_s f_c \text{ where } k \text{ is proportionality constant and } V_s \text{ is amplitude of signal wave}$$

Modulation index for *FM*, m_f is defined as :

$$m_f = \frac{\text{max. frequency deviation}}{\text{modulating signal frequency}} = \frac{\delta}{f_s} \quad \dots(iv)$$

$$\text{Hence, } v = V_c \sin (\omega_c t + m_f \omega_s t) \quad \dots(v)$$

The following points are worth noting :

- (i) The amplitude of the modulated wave is the same as that of the carrier wave.
- (ii) The frequency of the modulated wave varies in accordance with the message signal.

Advantages

- (i) *High transmission efficiency* : Transmission efficiency of *FM* is very high as compared to *AM*. It is because in *AM* the transmitted power is governed by the modulation depth whereas in *FM* it is independent of modulation depth as the amplitude of *FM* wave is constant. Moreover, all the transmitted power in *FM* is useful, whereas in *AM* most of it is used in transmitting carrier which does not indicate any modulation change.

* *VHF* means Very High Frequency and

UHF means Ultra High Frequency

MF means Medium Frequency

HF means High Frequency

** Standard frequencies are allocated worldwide by the International Radio Consultative Committee (*CCIR*) of the *I.T.U.*

- (ii) *Noiseless reception* : *FM* receivers can be fitted with amplitude limiters to remove the amplitude variations caused by noise, therefore, *FM* receivers provide noiseless reception. Moreover, *FM* broadcasts operate in the upper *VHF* and *UHF* frequency range at which there happens to be less noise than in the *MF* and *HF* ranges occupied by *AM* broadcasts.
- (iii) *Better audio quality* : There is less adjacent-channel interference in *FM* than in *AM*. It is because ***Standard frequency allocations provide a guard band between commercial FM stations.*

Disadvantages

FM transmissions also suffer from some of the drawbacks, otherwise there would have been no *AM* transmission left. These drawbacks are listed below :

- (i) *Wider channel is needed* : A much wider channel is required by *FM*, upto 10 times as large as that needed by *AM*. This is one of the major disadvantage.
- (ii) *Equipment used is more complex and costly* : *FM* transmitting and receiving equipment particularly modulators and demodulators are more complex and costly.
- (iii) *Smaller area of reception* : In this case reception is limited to line of sight, therefore, area of reception for *FM* is much smaller than for *AM*. This property may be considered as an advantages for co-channel allocation otherwise it is true that it reduces the area of reception.

5.18. PHASE MODULATION

The process by which the phase angle of a carrier wave is varied in accordance with the modulating signal is called phase modulation.

In phase modulation, the phase deviation is proportional to the amplitude of the modulating signal (V_s) but is independent of its frequency (f_s). In this case, the phasor of the modulated wave leads the reference position during positive half-cycle of the modulating signal and lags the reference position during the negative half-cycle of the modulating signal. The angular displacement of the phasor of the modulated wave (f_s) is restricted within the limits by the modulating signal.

Mathematically

If carrier voltage is given by the equation :

$$v_c = V_c \sin (\omega_c t + \phi) \quad \dots(i)$$

and the modulating signal wave is given by the equation ;

$$v_s = V_s \cos \omega_s t \quad \dots(ii)$$

In phase modulation, the phase in eqn. (i) is varied in accordance with the instantaneous amplitude of the modulating voltage. The expression for the *PM* wave will be

$$v = V_c \sin (\omega_c t + \phi_s \sin \phi_s t) \quad \dots(iii)$$


where ϕ_s is the maximum value of phase change introduced by this particular modulating signal and is proportional to the maximum amplitude of this modulation. For the sake of uniformity, the above equation may be rewritten as ;

$$v = V_c \sin (\omega_c t + m_p \sin \omega_s t) \quad \dots(iv)$$

where

$$m_p = \phi_s = \text{modulation index for phase modulation}$$

PROJECT

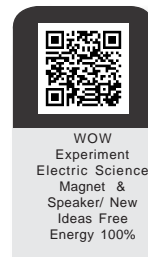

SUMMARY

1. *Power converter:* A power converter is an electrical or electro-mechanical or electronic device that converts electrical energy to mechanical, mechanical energy electrical, *DC* to *AC*, *AC* to *DC*, *DC* to *DC* of different voltage level, *AC* to *AC* of different voltage level or different frequency.
2. *Simple linear voltage regulator:* It is just a potential-divider.
3. *Buck converter:* It is a *DC-to-DC* power converter which steps down voltage and steps up the current simultaneously such that input power supply remains the same as that of the output (load).
4. *Applications of buck converters:* These are very useful for converting a computer's main (bulk) supply voltage (often 12V) down to lower voltages needed by *USB*, *RAM* and the *CPU* (1.8V or less).
5. *Boost converter:* It is a *DC-to-DC* power converter which steps up voltage and steps down the current simultaneously such that input power supply remains the same as that of the output (load).
6. *Applications of boost converters:* Two battery-powered applications that use boost converters are used in hybrid electric vehicles (*HEV*) and lighting systems.
7. *Buck-boost converter:* It is a type of *DC-to-DC* power converter that has the ability to step-down or step-up the output voltage (magnitude) and steps-up or step-down the current simultaneously such that input power supply remains the same as that of the output (load).
8. *Duty cycle:* The period or duration in which a signal or system remains active is called duty cycle.
9. *Voltage source inverter:* A circuit that operates from a stiff dc source and develops an ac output is usually known as voltage source inverter.
10. *Modulation:* The process by which the characteristics of one waveform (carrier) is modified in accordance with the variations in another wave (modulating signal wave) is called modulation.

11. *Equation for carrier wave:* The carrier wave is given by the equation :

$$v_c = V_c \sin (\omega t + \phi)$$

This wave has three variable characteristics i.e. amplitude V_c , frequency f_c ($\omega = 2\pi f_c$) and phase angle ϕ .

12. *Necessity of modulation:*

(i) to increase operating range (ii) to permit transmission without wire
(iii) to reduce the size of transmitting antenna.

13. *Amplitude modulation:* When the amplitude of a carrier wave is varied in accordance with the modulating signal the process is called amplitude modulation.

14. *Modulation factor:* The ratio of change in amplitude of carrier wave due to modulation to the original of the normal carrier wave is called modulation factor.

$$m = \frac{V_s}{V_c}$$

15. *Limitations of amplitude modulation:* (i) poor efficiency (ii) noisy reception (iii) smaller operating range (iv) poor audio quality.

16. *Frequency modulation:* The process by which the frequency of a carrier wave is varied in accordance with the modulating signal is called frequency modulation.

17. *Advantages to FM:* (i) High transmission efficiency (ii) Noiseless reception (iii) Better audio quality.

Disadvantages of FM: (i) Wider channel is needed (ii) Equipment used is more complex and costly (iv) Smaller area of reception.

18. *Phase modulation:* The process by which the phase angle of a carrier wave is varied in accordance with the modulating signal is called phase modulation.

SHORT ANSWER QUESTIONS

1. What is a power converter?
2. How does a power converter work?
3. What is the difference between an inverter and a converter?
4. How do you convert *DC* to *AC*?
5. What is the difference between a rectifier and an inverter?
6. How does a potential divider used to get reduced voltage?
7. Why buck converter is preferred over potential divider?
8. How does a buck converter work?
9. How current can be increased in a circuit?
10. How does boost converter work?
11. What is the use of a boost converter?

12. What is a buck boost converter?
13. How does a buck boost converter work?
14. How does a *DC* to *AC* inverter work?
15. What is the duty ratio?
16. What does 60% duty cycle mean?
17. What is a 100% duty cycle?
18. How does a voltage source inverter convert dc into ac?
19. Name the major components used in a *VSI*, draw its circuit.
20. What is difference between a 1-phase and 3-phase *VSI*?
21. What is the difference between a *UPS* and an inverter?
22. What is a sinusoidal modulator?
23. What are the different types of modulation?
24. What is meant by Over-modulation?
25. What is meant by under-modulation?
26. Where amplitude modulation is used?
27. What do you mean by amplitude modulation?
28. Why *FM* is better than *AM*?
29. How amplitude modulation is work?
30. What is amplitude modulation index?
31. What is *FM* signal?

MULTI-CHOICE QUESTIONS

1. A diode in anti-parallel with the controlled switch, like *IGBT*, is used in *VSI* to:
 - (A) prevent reversal of dc link current.
 - (B) allow a non-unity power factor load at the output.
 - (C) protect the circuit against accidental reversal of dc bus polarity.
 - (D) none of the above.
2. A large capacitor, put across *dc* bus of a voltage source inverter, is intended to:
 - (A) to protect against switch failure.
 - (B) to minimize high frequency current ripple through the ideal dc source.
 - (C) to maintain a constant dc link current.
 - (D) allow a low impedance path to the high frequency component of dc link current.
3. Gate (base) signals to the *VSI* switches, using n-channel *IGBTs*, need to be isolated to allow:
 - (A) protection of switches against short at the inverter output terminals.
 - (B) lower losses in the gate drive circuit.

- (C) switches to be connected in bridge fashion.
 - (D) a dc link voltage higher than the switch voltage rating.
4. The inverter switches work in fully-on or fully-off mode to achieve:
 - (A) reduced losses in the switches.
 - (B) minimum distortion in the output voltage waveform.
 - (C) easier gate control circuit for the switching devices.
 - (D) satisfactory operation for non-resistive load at the output.
 5. *AM* is a process by which
 - (A) the frequency of the carrier is varied in accordance with the signal.
 - (B) the amplitude of the carrier is varied in accordance with the signal.
 - (C) the phase of the carrier is varied in accordance with the signal.
 - (D) the frequency and amplitude both are varied in accordance with the signal.

TEST QUESTIONS

1. What do you mean by power converter? How will you classify them?
2. Explain the working of a buck converter with the help of a circuit diagram.
3. Draw the input and output wave-shapes of a buck converter working in continuous mode.
4. How will you differentiate between continuous and discontinuous mode of operation of buck converter?
5. Explain the working of a boost converter with the help of a circuit diagram.
6. Draw the input and output wave-shapes of a boost converter working in discontinuous mode.
7. How will you differentiate between continuous and discontinuous mode of operation of boost converter?
8. Mention the characteristics and important applications of buck converter and boost converter.
9. Explain the working of a buck-boost converter with the help of a circuit diagram.
10. What is the significance of duty cycle?
11. How dc is converted into ac with the help of a voltage source inverter (*VSI*)?
12. Why switch mode *VSI* is preferred over amplifier mode *VSI*?
13. Explain the working of a single-phase *VSI* with the help of a circuit diagram.
14. What is modulation ? State the need of modulation in communication system.

or

What do you mean by modulation ? Why is essential ?

15. Define *AM* and *FM*. Use sketches to explain these definitions. Where are these employed ?
16. What do you understand by modulation factor ? What is its significance ?

17. In what respect *FM* differ from that of *AM* ? Discuss relative merits and demerits of the two methods of modulation.
18. Define amplitude modulation and derive an expression for a sinusoidal carrier voltage, amplitude modulated by another sinusoidal voltage?

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes (1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												

ANSWERS TO MULTI-CHOICE QUESTIONS

Multi-Choice questions :

1. (B)
2. (D)
3. (C)
4. (A)
5. (B)



Experiment No. 8

Synchronous Machine operating as a generator - stand-alone operation with a load. Control of voltage through field excitation.

This experiment can be divided into two parts:

- (i) To plot relationship between no load terminal voltage and excitation current in a synchronous generator at constant speed.
- (ii) Determination of relationship between the voltage and load current of an alternator keeping excitation and speed constant.

Objective:

1. To show that the generated voltage in an alternator is proportional to excitation (field current) before saturation.
2. To show that the terminal voltage of an alternator falls with the increase in load (when the load is resistive or inductive).

Apparatus/Instruments/Components required:

- (i) Synchronous machine coupled with a dc motor of rating
- (ii) Field regulating resistance R_1 for dc motor to control speed.
- (iii) Ammeter dc of rating (max. field current rating)
- (iv) Voltmeter ac of rating (max. line voltage rating)
- (v) Tachometer.
- (vi) A.C. ammeter of range equal to full load current of alternator.
- (vii) 3-phase load.

Circuit diagram:

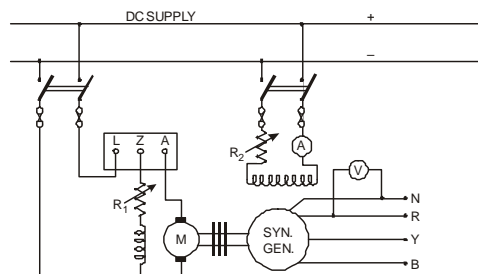


Fig. P8.1: Circuit diagram to observe the effect of field excitation on no load terminal voltage

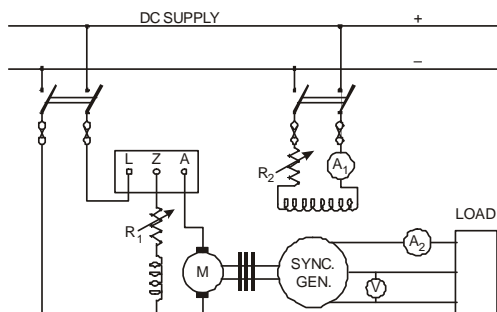


Fig. P8.2: Circuit diagram to observe the effect of load on terminal voltage

Theory:

The magnitude of induced e.m.f. per phase in an alternator is

$$E = 4.44 K_c K_d f \phi T \quad (\text{where } E \text{ is the terminal voltage per phase})$$

$$E \propto \phi f$$

When speed or frequency is kept constant

$$E \propto \phi \quad \text{or} \quad E \propto I_f \quad (\text{before saturation})$$

Where ϕ is the flux per pole and f is the frequency which in turn depends upon the speed of the alternator. The value of flux ϕ depends upon the field current and number of turns of field winding. Since the number of turns of field winding are fixed, therefore, the flux varies directly proportional to field current (I_f). The above conditions are true only upto the stage of saturation of magnetic circuit of the machine after which flux does not increase with the increase in field current. If the speed of alternator is kept constant, its e.m.f. varies directly in proportional to flux. The relation between the field current and the induced e.m.f. (phase value) when plotted on a graph paper gives the magnetisation characteristics or no-load characteristics of an alternator. Similar magnetisation characteristics can be drawn at different rotor speeds as shown in fig. 8.3.

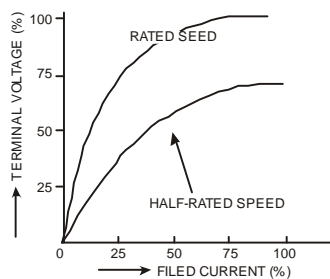


Fig. P8.3: Curve between I_f and V

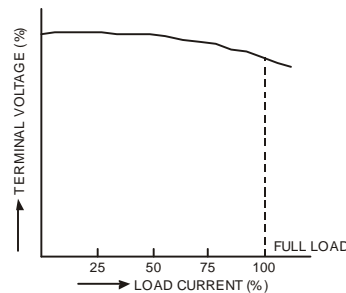


Fig. P8.4: Curve between I_L and V

The terminal voltage of an alternator drops with the increase in load (except for capacitive load which rarely occur on the system). In other words, it can be said that when full load is removed from the alternator, its terminal voltage increases as shown in fig. P8.4.

Procedure:

To perform no-load test/experiment, follow the steps given below:

1. Make the connections as per circuit diagram shown in fig.P8.1.
2. Get the connections checked by the teacher in-charge.
3. Start the dc motor coupled to alternator and adjust its speed to rated value keeping the field circuit of the alternator open.
4. Measure the value of the induced emf which will be very small (almost zero).
5. Now switch ON the field excitation of alternator and increase the field current I_f in steps. Note the values of field current I_f (ammeter reading A) at each step and the corresponding value of induced emf E (voltmeter reading V connected between one phase and neutral). Tabulate these readings.
6. Reduce the speed of the motor to one half of the rated value (check it with tachometer).
7. Reduce the excitation to zero and increase the field current I_f in steps. Note at each step the value of induced emf and tabulate the readings.

Procedure:

To perform load test/experiment, follow the steps given below:

1. Make the connections as per the circuit diagram shown in fig. P8.2.
2. Get the connections checked by the teacher in charge.
3. Start the d.c. motor and adjust its speed to the rated speed of alternator.
4. Switch on the excitation to alternator and adjust its value till rated terminal voltage is obtained.
5. Keeping the excitation constant, connect the load and increase it in steps, it will be observed that the voltage is decreasing but do not record any reading at this stage.
6. Increase the load to full load value and adjust the field current so that rated terminal voltage is obtained at rated speed.
7. Keeping the excitation fixed at this value, go on decreasing the load (i.e. load current). Note the value of load current (I_L) and terminal voltage (V) at each step, keeping the speed constant.
8. Switch OFF the load completely and record the terminal voltage at rated speed.
9. Draw the graph between load current (I_L) and terminal voltage (V).

Observation table: To draw curve between I_f and V

S.No.	Speed N1	Field Current I_f	Terminal voltage V	Speed N2	Field Current I_f	Terminal
1.						
2.						
3.						

Observation table: To draw curve between I_L and V

S.No.	Field Current I_f (A_1)	Speed N	Load current I_L (A_2)	Terminal Voltage V
1.				
2.				
3.				

Results:

1. The probable shape of curve is shown in fig. P8.3.
2. Plot a curve between I_f and V , the probable curves are shown in fig. P8.4.

6

Electrical Installations

RATIONALE

The rapid industrial growth is mainly due to utilisation of electrical energy in various fields. To-day, the dependence on electrical energy is so much that it has become a part and parcel of our daily life.

Electricity is a good servant but a bad master if not handled properly. Therefore, while working with electrical installation and handling electrical equipment, one should always take care of his own as well as of other's safety. A little carelessness may result in an accident which may be fatal. Therefore certain safety measures must be observed before dealing with electricity.

To provide safety to the operators and equipment various safety devices have been developed. In this chapter, we shall discuss various common safety devices, earthing etc.

UNIT OUTCOMES

U6-O1: Unit-6 Learning Outcome-1

To understand the meaning and functions of switchgear.

U6-O2: Unit-6 Learning Outcome-2

To differentiate between *LV*, *MV* and *HV* switchgear.

U6-O3: Unit-6 Learning Outcome-3

To analyse the working of *LV* switchgear devices such as Switch Fuse Unit (*SFU*), *MCB*, *ELCB/RCCB*, and *MCCB*.

U6-O4: Unit-6 Learning Outcome-4

To analyse various types of wiring installations and insulated wires/cables used in these installations.

U6-O5: Unit-6 Learning Outcome-5

Earthing and its purpose.

U6-O6: Unit-6 Learning Outcome-6

Construction, working and applications of a lead-acid battery.

UNIT SPECIFIC

- Switchgear and its function.
- LV, MV and HV switchgears and major devices or equipment employed in LV switchgear.

- Protection provided by LV switchgear devices such as Switch Fuse Unit (SFU), MCB, ELCB/RCCB, MCCB etc.
- Different types of cables used in wiring installations.
- Different types of wiring systems used in domestic, commercial and industrial installations.
- Selection of size of wires based on equipment to be used in the installation.
- Earthing and its importance.
- Constructional features and working of a lead-acid battery.
- Calculation of energy consumption charges and billing.

MAPPING THE UNIT OUTCOMES WITH THE COURSE OUTCOMES


Unit II Outcomes	EXPECTED MAPPING WITH COURSE OUTCOMES (1-weak Correlation; 2-Medium correlation; 3-Strong Correlation)		
	CO-1	CO-2	CO-3
U6-O1	1	--	3
U6-O2	1	--	3
U6-O3	1	--	3
U6-O4	1	--	3
U6-O5	1	--	3
U6-O5	1	--	3

Interesting facts

- The world's biggest light bulb is in Edison, New Jersey. It is 14 feet tall, weighs eight tons, and sits on top of the Thomas Edison Memorial Tower.
- Electricity is present in our bodies – our nerve cells use it to pass signals to our muscles.
- Iceland is the country that uses the most electricity annually. Their consumption is about 23% more than the U.S.

Video Resources

Videos Links for circuit

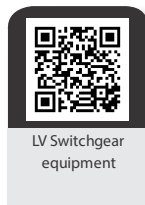



Cables used in
wiring
installations



Types of wiring
installations



Purpose of
Earthing



Types of
Earthing



Constructional
features and
working of a lead-
acid battery



Calculation
of energy
consumption
charges and
billing

6.1. SWITCHGEAR

In an electric power system, the combination of electrical switches, fuses or circuit breakers used to control, protect and isolate electrical equipment is called switchgear.

Switchgear is employed to improve the reliability of the electric supply.

Broadly, a switchgear has two types of components:

- Power conducting components, such as switches, circuit breakers, fuses, and lightning arrestors, that conduct or interrupt the flow of electrical power
- Controlling components, such as control panels, current transformers, potential transformers, protective relays, and associated circuitry, that monitor, control, and protect the power conducting components

Thus, the basic functions of switchgear is protection. It interrupts the short-circuit and overload fault

currents while maintain the service to unaffected circuits. Switchgear also provides isolation of circuits from power supplies. In power system, the electrical switchgears are categorized as HV, MV & LV switchgears.

HV Switchgears: The switchgear system that deals with voltage above 33 kV, is referred as high voltage switch gears. High voltage circuit breaker, is the main component of HV switchgear,

MV Switchgears: The switchgear system which is to handle voltages between 3 kV to 33 kV is categorized as medium voltage switchgear or MV switchgear. These switchgears are of many types.

LV Switchgears: Generally electrical switchgear rated upto 1 kV is termed as low voltage switchgear. The term LV Switchgear includes low voltage circuit breakers, switches, off load electrical isolators, HRC fuses, earth leakage circuit breaker, miniature circuit breakers (MCB) and molded case circuit breakers (MCCB) etc i.e. all the accessories required to protect the LV system.

6.2. LOW VOLTAGE SWITCHGEAR OR LV SWITCHGEAR

Rating Thermal	AC-23 Isolating Switch rating	AC-22 Fuse Switch rating	AC-23 Fuse Switch rating	Suggested Fuse Type	AC-23 Motor Switch rating	Mechanical Endurance (Operating Cycles)
63A	80A	80A	63A	H TS	28 KW	10,000
100A	125A	125A	100A	H TSD	45 KW	10,000
160A	200A	200A	160A	H TSF	80KW	8,000
200A	250A	250A	200A	H TSF	90 KW	8,000
320A	400A	320A	320A	H TSK	150 KW	5,000
400A	500A	460A	400A	H TSMF	185 KW	5,000
500A	630A	630A	500A	H TTM	225 KW	5,000
800A	800A	750A	630A	H TLM	300 KW	3,000

In LV switchgear system, electrical appliances are protected against short circuit and over load conditions by electrical fuses or electrical circuit breaker. However, the human operator is not adequately protected against the faults occurs inside the appliances. The problem can be overcome by using earth leakage circuit breaker. This operates on low leakage current. The earth leakage circuit breaker can detect leakage current as low as 100 mA and is capable of disconnecting the appliance in less than 100 m sec. Let us deal with the most popular switchgear devices such as Switch fuse Unit (SFU), MCB, ELCB, MCCB.

6.3. FUSE

*A short piece of metal wire, inserted in series with the circuit, which melts when more than rated value of current flows through it and breaks the circuit is called a **fuse**.*

A fuse is connected in series (see Fig. 6.1) with

the circuit to be protected and carries the load current without overheating itself under normal conditions. However, when abnormal condition occurs, an excessive current (more or equal to the predetermined value for which the fuse is designed) flows through it. This raises the temperature of the fuse wire to the extent that it melts and opens the circuit. This protects the machines or apparatus from damage which can be caused by the excessive current.

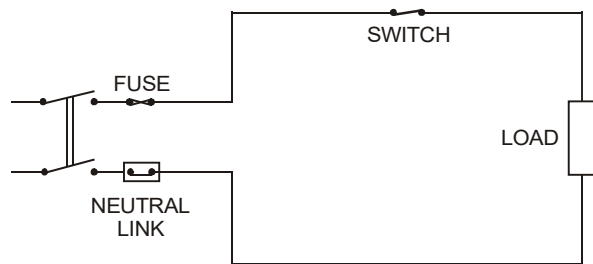


Fig. 6.1: Circuit with fuse

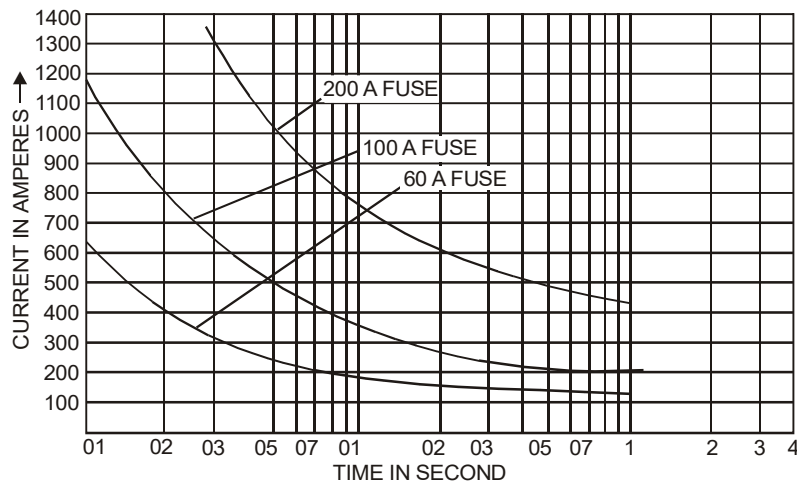


Fig. 6.2: Time-current characteristics of various fuses

Time-Current Characteristics : The time required to blow out a fuse depends upon the magnitude of excessive current. Larger the current, smaller is the time taken by the fuse to blow out. Hence a fuse has inverse time current characteristic as shown in Fig.6.2 which is desirable for a protective device.

Advantages

- (i) The cost of this protective device is very low.
- (ii) It requires no maintenance.
- (iii) It interrupts heavy current without noise or smoke.
- (iv) The smaller size of fuse element imposes a current limiting effect under short circuit.
- (v) The minimum time of operation can be predetermined by selecting proper material of the fuse wire.
- (vi) The inverse time-current characteristic makes it suitable for overcurrent protection.

Disadvantages

- (i) Considerable time is lost in re-wiring or replacing fuses after every operation.
- (ii) On short-circuit, determination between fuses in series can only be obtained if there is considerable difference in the relative sizes of the fuse concerned.

6.4. SWITCH FUSE UNIT (SFU)

Switch Fuse: Switch fuse Unit comprises of various porcelain rewireable fuses or *HRC* fuse fittings complete with their conducting parts. The switch is fitted with sturdy side operating handle with quick-break type mechanism, as shown in fig.6.3.

Contacts are made of electrolytic copper silver-plated. The fixed contacts are provided with removable shield. Switch Fuse units are provided with rewireable fuse or *HRC* Fuse Links. All these parts are assembled in an enclosure.

The Enclosure is made of sheet steel duly phosphatised and powder-coated. They are provided with conduit knock-outs. Door inter-lock is provided to prevent opening when the switch is in 'ON' condition.

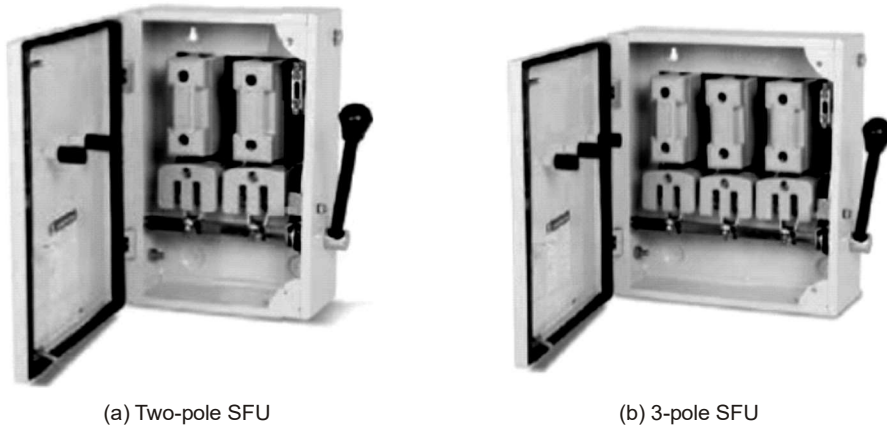


Fig. 6.3: Switch fuse Unit (SFU)

6.5. MINIATURE CIRCUIT BREAKER (MCB)

Miniature Circuit Breaker (*MCB*) is a device which ensures definite protection of wiring system and sophisticated equipment against over current and short circuit faults. The outer view and the internal details of a miniature circuit breaker are shown in Fig. 6.4 and 6.5 respectively.

Construction

Construction of an *MCB* can be explained by considering the following main parts:

- (i) *Outer body or housing* : The outer body or housing of an *MCB* is moulded from a special grade glass fibre reinforced polyster with the help of an injection moulding machine. The outer body and other polyster components of *MCB* are fire retardant, anti-tracking and non-hygroscopic. These polyster parts and housing have the ability to withstand high temperature and mechanical impacts.
- (ii) *Contacts* : The contacts of an *MCB* are made of pure silver. This provides definite advantages such as long contact life, low contact resistance, ensures quick arc removal and low heat generation.

- (iii) *Operating mechanism* : All the components of the operating mechanism are made of special plastic that they are self lubricating which eliminates wear and tear, rust and corrosion. These components are very light in weight and have low inertia thereby ensure snap make the break ability. The reliability and ruggedness of the operating mechanism is thus maintained.



MCB

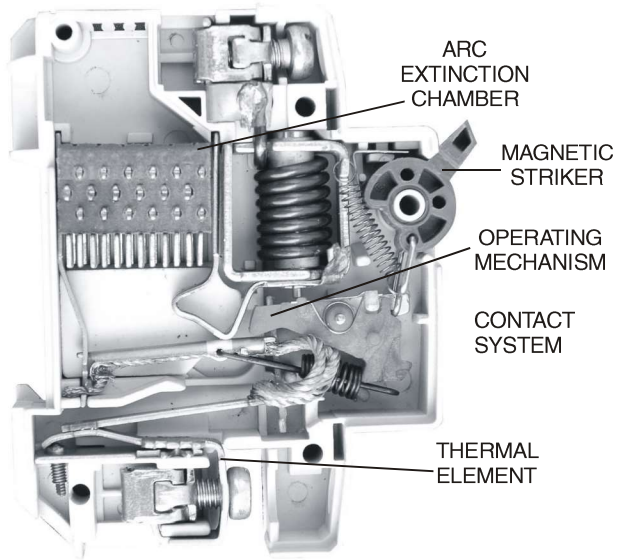


Fig. 6.4: Outer view of an MCB

Fig.6.5: Internal structure of MCB

- (iv) *Arc extinguishing Chamber* : The arc produced during breaking of circuit is extinguished abruptly by providing a special arc chute chamber.
- (v) *Fixing arrangement* : The *MCB* mounting clip gets easily snapped on to the Din-bar and can be removed easily by a simple operation with a screw driver. This saves the time which would have been required for fixing it with screws.
- (vi) *Mechanical interlocking of Multiple MCBs* : The levers of all the (3 or 4) multiple *MCBs* are connected internally. This ensures simultaneous tripping of all poles even if the fault develops in any one of the phases.

Working

MCB may operate under two different conditions :

- (i) *Moderate Overload Condition* : Detection of moderate overload conditions is achieved by the use of a thermo-metal which deflects in response to the current passing through it. The thermo-metal moves against the trip lever releasing the trip mechanism.
- (ii) *Short circuit conditions* : When the current flowing through the *MCB* reaches a pre-determined level (as per its setting or rating), it pushes the solenoid plunger which releases the trip mechanism and simultaneously separates the contacts.

Under short circuit conditions, the current limiting action is achieved by the use of a high speed, direct acting electro- magnetic mechanism.

This mechanism forcibly separates the contacts and simultaneously releases the trip mechanism. A high *arc voltage drop* is rapidly introduced which limits the fault current to a duration of few milliseconds and achieves almost instantaneous interruption (the facts are shown graphically in Fig.6.6).

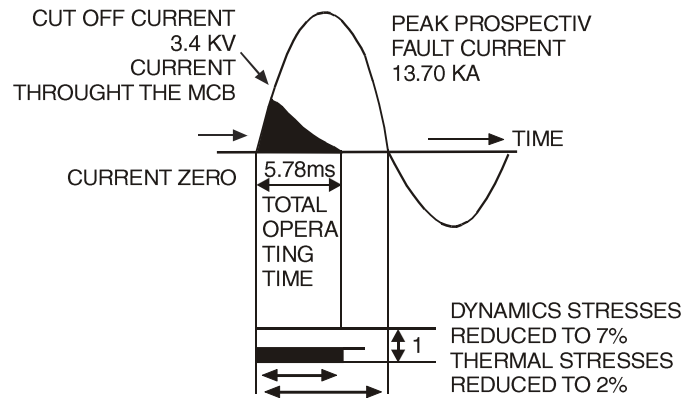


Fig. 6.6: Operating characteristics of an MCB

When the contacts are separated, the current still rises due to arc. This arc is extinguished quickly in the arc chute chamber and does not allow the current to reach theoretical maximum value. The total breaking time is reduced to less than 5 millisecond.

Applications

Since MCBs are available with different current ratings of 0.5, 1.6, 2, 2.5, 3, 4, 5, 6, 7.5, 10, 16, 20, 25, 32, 35, 40 and 63 ampere and voltage ratings of 240/415 volt ac and upto 220V dc. Moreover, they have very small breaking time (5 millisecond), therefore, these are generally employed to protect the important and sophisticated appliances used commercially and for domestic purposes such as computers, air conditioners, compressors, refrigerators and many others.

6.6. EARTH LEAKAGE CIRCUIT BREAKER (ELCB)

In the industrial, commercial and domestic building some times (usually in rainy season) leakage to earth occurs. This leakage may cause electric shock or fire. Hence, the leakage to earth is very dangerous and needs protection.

ELCB is a device which provides protection against earth leakage faults.

Construction and internal circuit details

The enclosures of the *ELCB* is moulded from high quality insulating material. The materials are fire retardant, anti-tracking, non-hygroscopic, impact resistant and can withstand high temperatures. The body contains spring loaded mounting arrangement on din-channel which ensures snap fitting of *ELCB* into position. However, these also have the facility to screw-on directly to any surface with

the help of two screws. A 2-pole *ELCB* is used for 1-phase supply and a 4-pole *ELCB* is used for 3-phase, 4 wire supply. A 4-pole *ELCB* is shown in Fig.6.7.

Internal wiring diagram of a 2-pole *ELCB* is shown in Fig.6.8. As shown in Fig.6.8 an *ELCB* contains a core balanced transformer (ferrite ring on which one or two turns of phase and neutral wire ; and a few turns of operating coil of relay are wound), and a relay. A test button is placed between phase and neutral in series with a limiting resistor. The terminal designation and connection diagram for a 2-pole and 4-pole *ELCB* are shown in Fig. 6.9 and Fig. 6.10 respectively.



Fig. 6.7: 4-pole ELCB

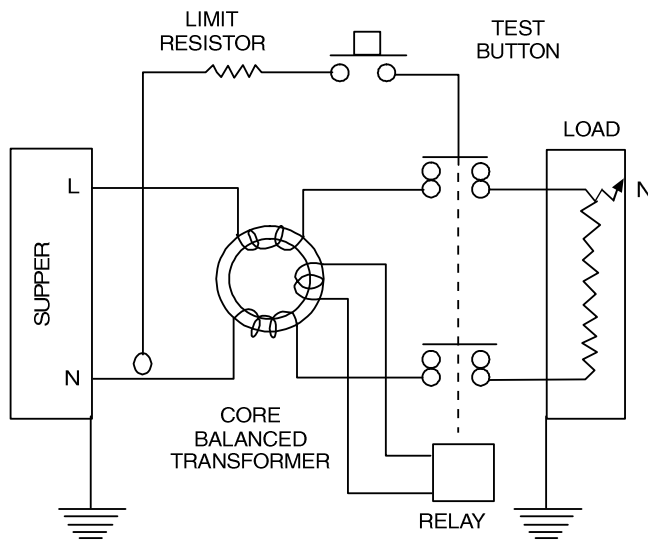


Fig. 6.8: Internal wiring diagram of a 2-pole ELCB

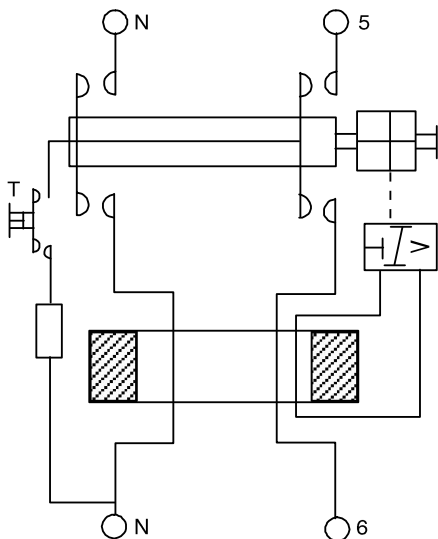


Fig. 6.9: Circuit for 2-pole ELCB

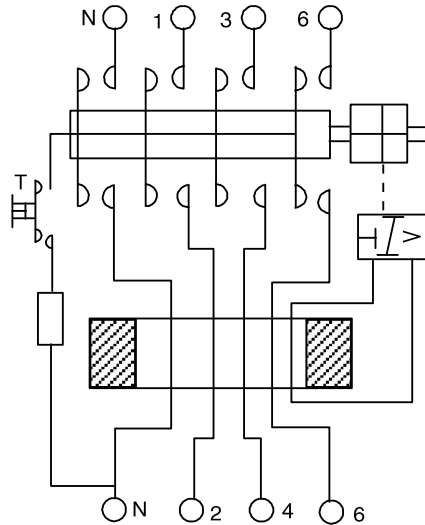


Fig.6.10: Circuit for 4-pole ELCB

Principle of operation

Under normal conditions, the magnitude of currents flowing through the phase wire and neutral are the same and core of the core balanced transformer does not carry any flux (*i.e.* two windings neutralise the flux). Thus, no e.m.f. is induced in the operating coil of the relay wound on the same core. However, when the earth fault (earth leakage) occurs, the current in the phase wire becomes more than the neutral wire. This unbalancing sets up flux in the core of the core balanced transformer which in turn induces an e.m.f. in the operating coil of the relay. Hence, relay is energised and the plunger of the *ELCB* goes to the off position or disconnects the load from the supply.

Thus, *ELCB* protects the system against leakage.

Use of test knob

A test knob is provided for periodic checking of the mechanism and function of *ELCB*.

6.7. MOULDED CASE CIRCUIT BREAKER (MCCB)

Molded case circuit breakers are the electrical protection device that is commonly used when load current exceed the capabilities of miniature circuit breakers. They are also used where the current rating are required to be adjusted by adjusting trip settings, which are not available in plug-in circuit breakers and MCBs.

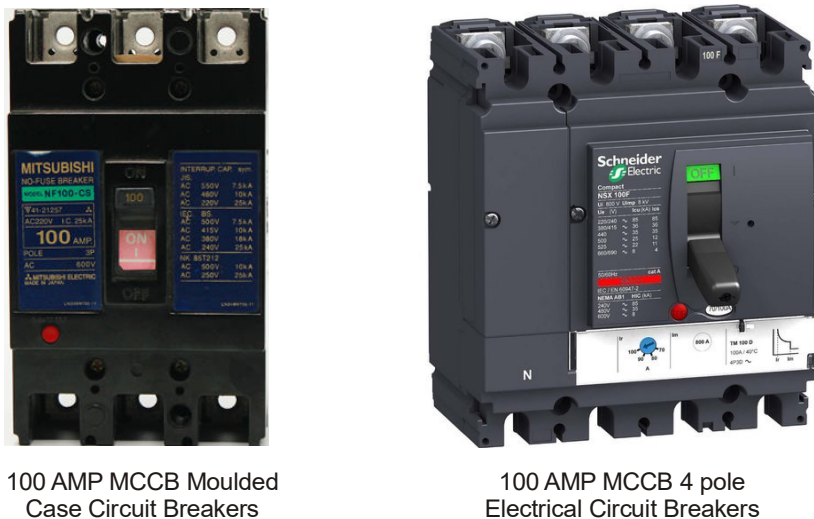


Fig.6.11: Moulded case circuit breakers

A molded case circuit breaker (*MCCB*) is a type of electrical protection device that can be used for a wide range of voltages, and frequencies of both 50 Hz and 60 Hz. The main distinctions between molded-case and miniature circuit breaker are that the *MCCB* can have current ratings of up to 2500 A, and its trip settings are normally adjustable. Moreover *MCCBs* are much larger in size than *MCBs*. It has the following three major functions:

- Protection against overload
- Protection against electrical faults
- Switching a circuit on and off

The wide range of current ratings available from molded-case circuit breakers allows them to be used in a wide variety of applications. *MCCBs* are available with current ratings that range from low values such as 15 A, to industrial ratings such as 2500 A. Their outer view is shown in fig 6.11.

Operating Mechanism

At its core, the protection mechanism employed by *MCCBs* is based on the same physical principles used by all types of thermal-magnetic circuit breakers.

Overload protection: It is accomplished by means of a thermal mechanism. *MCCBs* have a bimetallic contact that expands and contracts in response to changes in temperature. Under normal operating conditions, the contact allows electric current through the *MCCB*. However, as soon as the current exceeds the adjusted trip value, the contact will start to heat and expand until the circuit is interrupted.

Fault protection: On the other hand, fault protection is accomplished with electromagnetic induction, and the response is instant. Fault currents should be interrupted immediately, no matter if their duration is short or long. Whenever a fault occurs, the extremely high current induces a magnetic field in a solenoid coil located inside the breaker, this magnetic induction trips a contact and current is interrupted.

Manual operation: As with all types of circuit breakers, the *MCCB* includes a disconnection switch which is used to trip the breaker manually.

6.8. TYPES OF WIRES AND CABLES

Before considering the various types of wiring systems suitable for any installation, it is required to know about the various types of cables (insulated conductors) which are used for internal wiring systems.

A solid or stranded conductor covered with insulation is known as a cable.

The cable may be a single core or multi-core depending upon the number of conductors. Various types of insulating materials are employed for covering the conductors.

Accordingly, the cables (wiring conductors) may be classified as :

- (i) Vulcanised Indian Rubber (*V.I.R.*) cables.
- (ii) Poly-vinyl Chloride (*P.V.C.*) cables.
- (iii) Tough Rubber sheathed (*T.R.S.*) or Cab Tire Sheathed (*C.T.S.*) cables.
- (iv) Lead sheathed cables.
- (v) Weather proof cables.

6.8.1.Types of Wiring

The main types of wirings usually employed in residential buildings, commercial buildings and industries are :

1. Cleat Wiring ;
2. Casing and Capping Wiring ;
3. *C.T.S.* or *T.R.S.* Wiring ;
4. Metal Sheathed Wiring ;
5. Conduit Wiring.

- 1. Cleat Wiring :** In this system of wiring, usually *V.I.R.* or *P.V.C.* conductors are employed. The conductors are supported in porcelain cleats which are placed at least 6 mm above the walls. The porcelain cleats are made of two parts, the lower one is known as base being having two or three grooves for the accommodation of conductors and the upper one is known as cap as shown in Fig. 6.12. The conductors are run in the grooves, cap is placed over the base and the whole assembly is fixed on to the wall with the help of wooden screws and gutties (wooden or *P.V.C.* plugs) already cemented in the wall. The screw not only fixes the cleats on the wall but also tightens the grip of the wires between the two halves of the cleat.

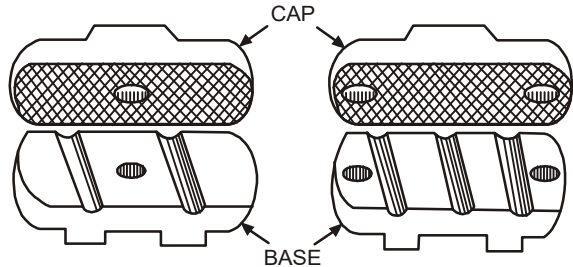


Fig. 6.12: Porcelain cleats

Advantages

- (i) It is cheapest system to wiring.
- (ii) A little skill is required to lay the wiring.
- (iii) This wiring can be installed very quickly.
- (iv) It is the most suitable system for temporary wiring.
- (v) The wiring can be dismantled very quickly and whole of the material is recovered.
- (vi) Inspection, alteration and additions can be made easily.

Disadvantages

- (i) It gives a rubbish look.
- (ii) It is rarely employed for permanent job.
- (iii) At the time of white washing or distempering the lime falls over the wires which may damage insulation.
- (iv) Oil and smoke are also injurious to *V.I.R.*
- (v) Mechanical injuries may damage the conductor since there is no protecting cover.

- 2. Casing and Capping Wiring :** In this system of wiring, generally *V.I.R.* wires are employed. The casing is just a base that consists of rectangular *P.V.C.* or wooden block of seasoned teak wood and has usually two grooves to accommodate wires. The casing is fixed on the wall with the help of wooden screws and gutties already cemented in the wall. The casing is usually placed 3 mm apart from the wall by means of porcelain discs in order to protect the casing from dampness.

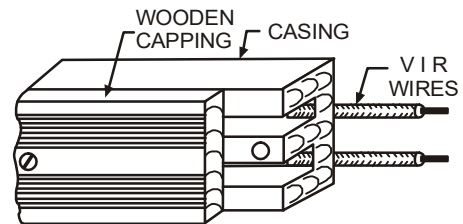


Fig. 6.13: Casing – capping

Then the wires of opposite polarity are laid in different grooves. After placing the wires in the grooves of casing at the top is covered by means of a rectangular strip of seasoned wood of the same width as the casing known as capping with the help of wooden screws. The assembled view of casing capping with the *V.I.R.* wires placed in the grooves is shown in Fig. 6.13.

Advantages

- (i) It gives better appearance than cleat wiring.
- (ii) Its cost is quite low as compared to other systems of wiring except cleat wiring.
- (iii) It is easy to install and repaired.
- (iv) Conductors are strongly insulated.
- (v) Capping provides protection against mechanical injury.

Disadvantages

- (i) It is not suitable in damp situations.
- (ii) There is a risk of fire.
- (iii) To make the job good looking highly skilled labour is required.

3. **C.T.S. or T.R.S. Wiring :** In this system of wiring, generally *C.T.S.* (Cab Tire Sheathed) or *T.R.S.* (Tough Rubber Sheathed) conductors are employed. The conductors are run on well seasoned, perfectly straight and well varnished teak wood batten of thickness 13 mm. The width of the batten is chosen depending upon the number of wires to be run on it. While doing this type of wiring, the batten is fixed on to the wall by means of wooden screws and gutties already cemented in the wall. The wires are held on the batten with the help of clips already fixed on the batten with the help of nails as shown in Fig. 6.14.

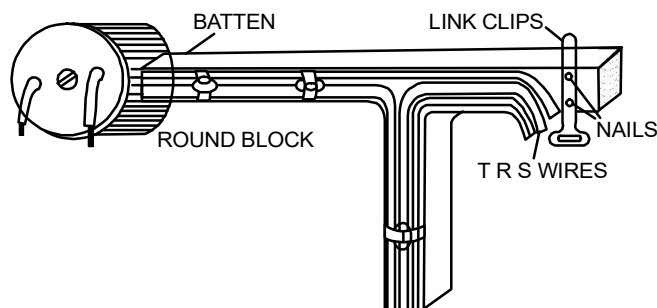


Fig. 6.14: CTS Wiring

Advantages

- (i) It is easy to install and repair.
- (ii) It gives nice appearance.
- (iii) The conductors have strong insulation, therefore, it has longer life.
- (iv) It is fire-proof up to some extent.
- (v) Chemicals do not affect the conductors insulation.

Disadvantages

- (i) The conductors are open and liable to mechanical injury, therefore, this type of wiring cannot be used in workshops.
- (ii) Its use in places open to sun and rain is restricted.
- 4. **Metal Sheathed Wiring** : This system of wiring is similar to *C.T.S.* or *T.R.S.* wiring. Only difference is that in this case *V.I.R.* conductors covered with lead alloy sheath (metal sheathed cable) are used. The metal sheathed cables are run on the wooden batten. The batten is fixed on the wall by means of screws and gutties already cemented into the wall. The cables are held on the batten with the help of link clips.

Advantages

- (i) The conductors are protected against mechanical injury.
- (ii) It can suitably employed under damp situations.
- (iii) It gives better appearance.
- (iv) It has longer life.
- (v) Conductors are protected against chemicals.
- (vi) It can be installed in open space.

Disadvantages

- (i) The metal sheathed cables are costlier than *C.T.S.* or *T.R.S.* wires.
- (ii) In case of leakage, there is every risk of shock.
- (iii) Skilled labour and proper supervision is required.
- 5. **Conduit Wiring** : In this system of wiring, *V.I.R.* or *T.R.S.* conductors are run in metallic or *P.V.C.* tubes called conduits. This system of wiring provides best mechanical protection, safety against fire and shock. Therefore, it is considered to be the most suitable system of wiring for workshops and commercial buildings.

The conduits can either be supported over the wall by means of saddles or can be buried under plaster. Accordingly there are two types of conduit wirings namely ;

- (i) Surface conduit wiring,
- (ii) Concealed conduit wiring.

In surface conduit wiring, the conduit is run over the wall supported by means of saddles as shown in Fig.6.15 Whereas, in concealed conduit wiring, the conduit is embedded in the walls and ceiling by placing it in the pre made cavity in them. After placing the conduit, the insulated conductors (or cables) are drawn into them by means of *G.I.* wire known as pilot wire. Number of inspection boxes (conduit boxes) are provided along the run of conduit to facilitate the drawing of wires.

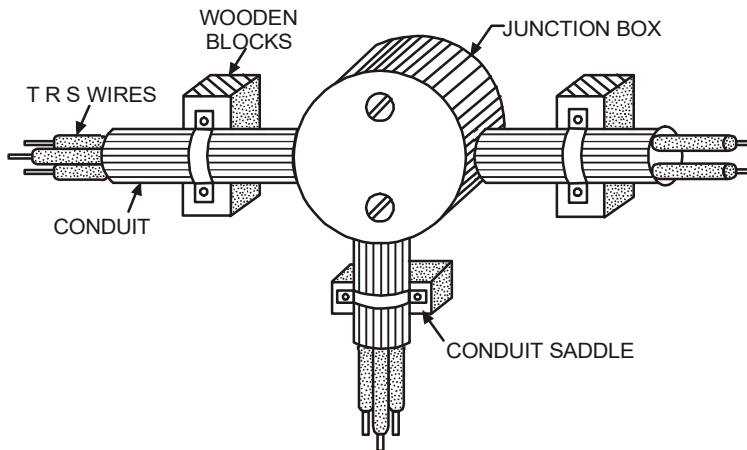


Fig. 6.15: Conduit wiring

Advantages

- (i) Conduit provides protection against mechanical injury and fire.
- (ii) Conduit provides protection against chemicals.
- (iii) Conductors are safely secured from moisture.
- (iv) This wiring has far better look.
- (v) It has a longer life.

Disadvantages

- (i) It is costly system of wiring
- (ii) It requires more time for erection.
- (iii) It requires highly skilled labour.

6.8.2. Power rating of Basic house-hold equipment:

To calculate the rating of the main switch and MCB_s / fuses to be used on the distribution board for a building and also for finalizing the size of the cable for service connection and internal wiring, it is necessary to assess the load of the building in ampere. For this purpose, following guidelines may be adopted after deciding the number and type of outlets installed in the building.

Incandescent light point (Bulb Point)	60 watt
Fluorescent tube 2 feet long (0.6 m)	20 watt
4 feet long (1.2 m)	40 watt
Ceiling fans	60 watt
Socket outlets (5A)	100 watt
15 ampere socket outlet (Power Socket)	1000 watt
Exhaust fan	100 watt
CFL/LED lamp	40 watt

Selection of cable or insulated wires used in wiring installations.

To find out the correct size of wire to be used at an installation, it is necessary to find out the load in ampere to be carried by the cables.

The following tables help us for selection of correct size of insulated wire based upon current and voltage drop of the conductors. Table shows only the copper wires used in the internal wiring system upto a current carrying capacity of 28 ampere, although, larger size wires are also available:

Table . Current Rating of Copper Conductor Single Core Cables

(VIR, PVC or Polythene insulated including tough rubber sheathed, PVC or lead sheathed cables)

Size of conductors		Two cables d.c. or single phase a.c.		Three or four cable balanced three phase a.c	
Nominal area mm ²	No. and dia of wire (mm)	Current Rating (A)	Approximate length of run for one volt drop (metre)	Current Rating (A)	Approximate length of run for one volt drop (metre)
1.0	1/1.12	5	2.9	3	2.8
1.5	3/0.737	10	3	10	3.7
2.5	3/1.06	15	3.4	13	4.3
4.0	7/0.737	20	3.7	15	4.8
6.0	7/1.06	28	4.0	25	5.2

Aluminium core cable or insulated wires can also be used as per the current rating and size given in the following table. But aluminium core cable are avoided in the internal wiring of the buildings since they have poor mechanical strength. However, these are commonly used in service connections.

Table . Current Rating of Aluminium Conductor Single Core Cables

(VIR, PVC or Polythene insulated including tough rubber sheathed, PVC or lead sheathed cables)

Size of conductor		Two cables d.c. or single phase a.c.		Three or four cables balanced three phase		Four cables d.c. or single phase a.c.	
Nominal area mm ²	No. and dia. of wire (mm)	Current Rating (A)	Approx run for one volt drop (m)	Current Rating (A)	Approx run for one volt drop (m)	Current Rating (A)	Approx run for volt drop (m)
1.5	1/1.40	10	2.3	9	2.9	9	2.5
2.5	1/1.80	15	2.5	12	3.6	11	3.4
4	1/2.24	20	2.9	17	3.9	15	4.1
6	1/2.80	27	3.4	24	4.3	21	4.3
10	1/3.55	34	4.3	31	5.4	27	5.4
16	7/1.70	43	5.4	38	7.0	35	6.8
25	7/2.24	59	6.8	54	8.5	48	8.5
35	7/2.50	69	7.2	62	9.8	55	9.0
50	7/3.00	91	7.9	82	10.1	69	10.0
50	19/1.80	91	7.9	82	10.1	69	10.0
70	19/2.24	134	8.0	131	9.5	—	—
95	19/2.50	153	8.8	152	10.0	—	—

6.9. CLASSIFICATION OF CABLES

Underground cables are usually classified according to the voltage for which these are manufactured. Hence these are classified as :


- (i) Low tension (L T) cables—for operating voltages upto 1000V
- (ii) High tension (H T) cables—for operating voltages upto 11 kV
- (iii) Super tension (S T) cables—for operating voltages from 22 kV to 33 kV
- (iv) Extra high tension (EHT) cables—for operating voltages from 33 kV to 66 kV
- (v) Extra super voltage cables—for operating voltages from 66 kV to 132 kV and above.

Low Tension (LT) Cables

These cables are employed for system voltages upto 1000 volt. Generally these cables are used for distribution of electric power at 400 V. The cables are of two types *viz* single-core and multi-core cables. Due to economic reasons 4-core cable is mostly employed for distribution of electric power at low voltages.

The low voltage cables do not have special attention for their construction since in these cables the electrostatic stresses are small. Moreover, their thermal conductivity is quite sufficient to dissipate heat. Fig.6.16 represents the construction of a four-core cable. The conductors are insulated with rubber or polyvinyl chloride. Around all the four conductors a layer of fibrous compounded material is provided.

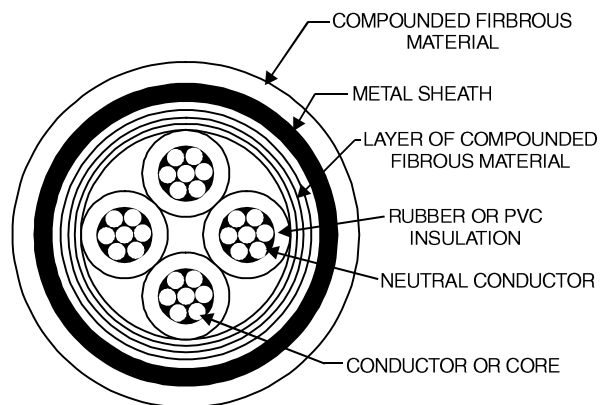Above this layer a lead sheath is provided to restrict the moisture to enter the core of the cable. The lead sheath is covered with a compounded fibrous material. In this case, wire armoured cover may or may not be provided, however if it is provided, it is covered with a layer of serving.



FOUR CORE L.T. CABLE

Fig.6.16: Cross-section of a four core LT cable

6.10. EARTHING

*The process of connecting metallic bodies of all the electrical apparatus and equipment to the huge mass of earth by a wire of negligible resistance is called **earthing**.*

When a body is earthed, it is basically connected to the huge mass of earth by a wire having negligible resistance. Thus, the body attains zero potential *i.e.*, potential of earth. This ensures that whenever a live conductor comes in contact with the outer body, the charge is released to the earth immediately.

6.10.1. Purpose Of Earthing

The basic purpose of earthing is to protect the human body (operator) from electric shock.

To illustrate the purpose of earthing consider an electrical circuit shown in Fig. 6.17 where an electrical appliance of resistance R is connected to the supply through a fuse and a switch. When an operator touches the metallic body of the apparatus [see Fig. 6.17(a)] having perfect insulation, the equivalent circuit is shown in Fig. 6.17 (b). Where two parallel paths are formed. Since the insulation resistance R_i is very high as compared to appliance resistance R , whole of the current flows through appliance resistance and no current flows through human body (operator's body) resistance.

When earth fault occurs, the live (phase) wire directly comes in contact with the outer body and the insulation resistance reduces to zero as shown in Fig. 6.17 (c). Now the body resistance is just in parallel with the appliance resistance. A heavy current flows through the human body and operator gets a severe shock.

However, if the metallic body or outer frame of the appliance is properly earthed then under earth fault condition, the circuit will be as shown in Fig. 6.17 (d). Where earth resistance R_e is just in parallel with the appliance resistance R and body resistance R_b . Since earth resistance is very small as compared to body resistance, almost whole of the fault current flows through the earth resistance and no current flows through the human body. *Thus, the operator is protected from electric shock.* Moreover, the

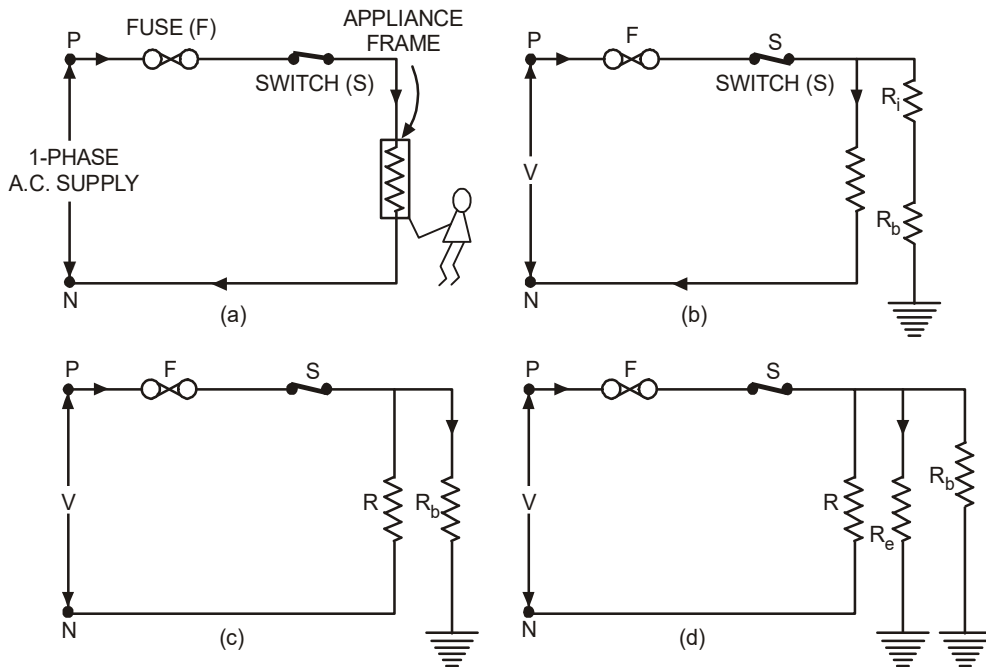


Fig.6.17: Earthing protects the operator

fault current is much more than the full load current of the circuit which melts the fuse. Hence, the appliance is disconnected automatically from the supply mains.

6.10.2. Equipment Earthing

According to Rule 61 of Indian Electricity Rules 1956, it is obligatory to earth the following points and apparatus used in the power system, where the voltage is more than 125 V :—

- (i) All the metal frames of motors, generators, transformers and controlling equipment.
- (ii) The steel tower and steel tubular or rail poles carrying over head conductors.
- (iii) The metal frames of portable electrical equipment such as heaters, table fans, electric iron, refrigerator, air conditioners, vacuum cleaners etc.
- (iv) Other metal parts such as conduits, switch gear casings etc.
- (v) Earth terminal of all the 3-pin outlet sockets.
- (vi) In case of concentric cables, external conductor *i.e.* armouring of such cables.
- (vii) Stay wires of overhead lines if stay insulator is not provided.

In case of insulation failure, the primary object of connecting all the above points and apparatus to earth is to release the charge accumulated on them immediately to earth so that the person coming in contact may not experience electric shock. The other object is that a heavy current when flows through the circuit that operates the protective devices (*i.e.* fuse or miniature circuit breaker) which opens the circuit.

Generally, the following values of earth resistance must be achieved while earthing :

Equipment to be earthed	Max. value of resistance under worst conditions
(i) Large power stations	0.5 ohm
(ii) Major sub-station	1.0 ohm
(iii) Small sub-stations	2.0 ohm
(iv) Factories sub-stations	1.0 ohm
(v) Lattice steel towers	3.0 ohm
(vi) Industrial machines and equipment	0.5 ohm

The earth resistance depends upon the moisture contents in the soil and varies from month to month. Therefore, earth resistance must be checked periodically by earth tester and maximum permissible value be obtained by pouring water into the funnel.

6.10.3. System Earthing

A proper system has to be adopted while earthing. In fact, all the heavy power equipment should be earthed by two separate distinct earth wires following the different routes. The two earth connections are applied to improve the reliability. If one of the earth wires breaks or fails to carry the fault current, the other carries that current and provides the required protection. Moreover, in factories and substations where more than one equipment is to be earthed, parallel connections should invariably be used. In no case series connections are done, as even a single bad contact or break in the earthing-lead will disconnect all the succeeding equipment from the earth.

Thus, for proper earthing of heavy power equipment, double earthing system has to be adopted. Moreover, the number of apparatus must be connected in parallel to the earth.

- 4. Pipe Earthing :** Taking into consideration the factors such as initial cost, inspection, resistance measurement etc., G.I. pipe earthing is best form of ground connection. Iron is the cheapest material and remains serviceable even if put in salty mass of earth. The pipe used as earth electrode is galvanised and perforated. Its diameter is 38.1 mm and length is 2 metre. The length may be increased to 2.75 metre in case of dry soil. The diameter of pipe has very little effect on the resistance of the earth connection. To facilitate the driving in of the pipe into ground, it is provided with the tapered casting at the lower end. Another pipe of 19.05 mm diameter and of length 2.45 metre is connected at the top of the above said pipe. The connection between these pipes is made through a reducing socket, as shown in Fig. 6.18.

The earthing lead should be soldered and connected to the pipe. Alternate layers of charcoal and salt are provided around the G.I. pipe to keep the surroundings moist enough. The salt is poured at the bottom and thereafter alternate layers of charcoal and salt are arranged.

- 5. Plate Earthing :** In this type of earthing, a copper or G.I. plate of dimensions not less than 60 cm × 60 cm × 3.18 mm or 60 cm × 60 cm × 6.35 mm is used as earth electrode instead of G.I. pipe. The plate is buried into ground in such a way that its face is vertical and the top is not less than 3 metres below the ground level. The G.I. wire is used for G.I. plate and copper wire for copper plate earthing. The size of wire is selected according to the installation and fault current. The earthing lead is suitably protected placing it under-ground in a pipe, as shown in Fig. 6.19.

Alternate layers of charcoal and salt are used around the plate. The layers of charcoal shall be placed immediately over the plate and thereafter successive layers of salt and charcoal are laid to keep the surroundings sufficiently moist.

Note : Pipe earthing and plate earthing are considered to be the best as they have reasonably low value of earth resistance.

6.10.5. Double Earthing

For providing better safety it is advisable to provide two separate earth wires, from two separate earth electrodes, connected to same metallic body of the equipment at two different points. This is known as double earthing. Double earthing is essential, as per Indian Electricity Rule, for metallic bodies of large rating equipment such as transformer, motors etc. working at 400 V and above.

Advantages of double earthing are :

1. Surety of safety, because if at any time one earthing is ineffective, then another will provide earth path to fault current.
2. As the two earth wires are in parallel so the effective resistance from equipment to earth electrode is reduced.

6.11. BATTERY

*A series, parallel or series-parallel grouping of cells is called a **battery**.*

Generally, a cell can deliver a small current at low voltage. For a circuit, if higher voltage is required – a battery containing number of cells connected in series is applied; if higher current is required a battery containing number of cells connected in parallel is applied; if larger current at higher voltage is required a battery containing number of cells in series further connected in parallel is applied.

*Usually, a number of cells connected in series placed in a single container is called a **battery**.*

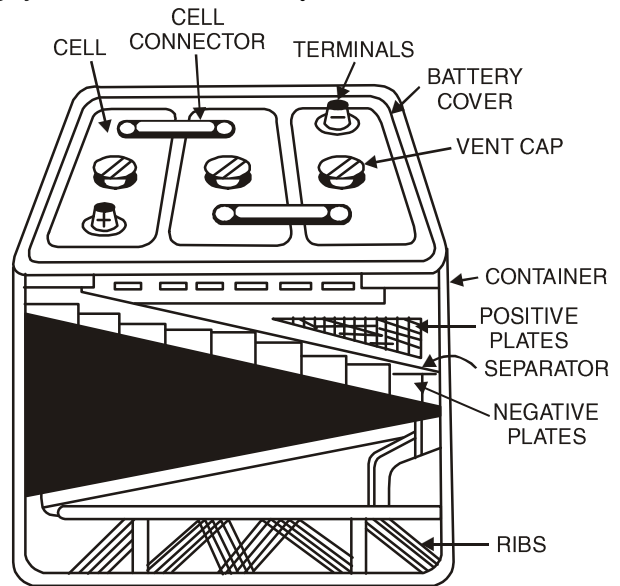


Fig. 6.20 : Lead-acid battery

6.11.1. lead-Acid Battery

Fig. 6.20 shows the cut-away view of 6V commercial lead-acid battery. The following are the important parts of the battery.

1. **Container :** It is the outer body of the battery. It is made of a hard rubber or plastic material and is sealed at the top to prevent spilling of the electrolyte. A large space is left at the bottom of the container so that the sediments that drop from the plates are collected here and may not short circuit the positive and negative plates.
2. **Plates :** Generally, alloy of lead-antimony sheets covered with lead-peroxide and spongy lead forming positive and negative plates respectively are used as electrodes. To increase the capacity of the battery, we use a large number of plates in each cell instead of only two plates. The number of positive and negative plates (*i.e.* 11, 13, 15 or 17) of each cell are alternatively placed and sandwiched with an insulator called *separator* as shown in fig. 6.21. One group of positive and negative plates forms a cell which develops an e.m.f. of 2.0 volt. A separate compartment is provided for each cell in the container of the battery.

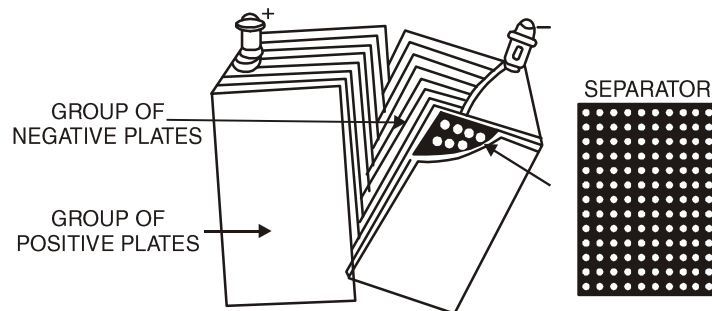


Fig. 6.21: Battery plates and separator

3. **Separator** : To reduce the internal resistance of the cell and to save the space, the plates are placed very close to each other. To prevent the plates touching each other if they wrap or buckle, they are separated by a rubber sheet (non-conducting material) having large number of small holes called *separator* [see fig. 6.21].
4. **Electrolyte** : Dilute sulphuric-acid (H_2SO_4) is used as an electrolyte in lead-acid batteries. Sulphuric-acid is added to water in such a proportion that with a fully charged battery, its specific gravity is about 1.28 to 1.29.
5. **Battery cover** : Each cell compartment is covered usually with a molded hard rubber and the joints between covers and container are sealed with an acid-resistance material. In each cell cover openings are provided — two for positive and negative terminals, and third for a vent. The whole container is fitted with a leak proof cover.
6. **Vent caps** : The vent-cap has a vent hole to allow free exit of the gases formed in the cell during charging. The vent caps can be easily removed for adding water. The vent cap is also removed to insert the nozzle of hydrometer for checking the specific gravity of electrolyte to check the battery charge condition.
7. **Inter-cell connector** : The cells, placed in the same container are connected in series with a lead alloy link called inter-cell connector.
8. **Cell terminals** : Each cell has two terminals which are generally made of lead as it does not corrode due to the electrolyte. The positive terminal of the battery is marked with a red colour or by a large positive (+) sign.

6.11.2. Capacity of a Battery

*The quantity of electricity which a battery can delivery during single discharge until its terminal voltage falls to 1.8V/cell is called the **capacity** of a battery.*

The capacity of a battery or cell is commercially expressed in ampere-hour and is generally denoted by A-H.

Capacity of a battery or cell = $I_d T_d$ ampere-hour
 where, I_d = discharging current in ampere
 T_d = discharging time of battery or cell in hour.

6.11.3. Efficiency of a Battery

The efficiency of a battery (or cell) can be defined in the following two ways :

- (i) **Quantity or A-H efficiency** : *The ratio of output ampere-hour during discharging to the input ampere-hour during charging of the battery is called **quantity or ampere-efficiency** of the battery.*

Mathematically, $\eta_{AH} = \frac{I_d T_d}{I_c T_c}$

where, I_d = discharging current in ampere : T_d = discharging time in hour.
 I_c = charging current in ampere, T_c = charging time in hour.

- (ii) **Energy or W-H efficiency :** *The ratio of output watt-hour during discharging to the input watt-hour during charging of the battery is called **energy or watt-hour efficiency** of the battery.*

Mathematically,
$$\eta_{WH} = \frac{I_d T_d V_d}{I_c T_c V_c}$$

where, V_d = Average terminal voltage during discharging,
 V_c = Average terminal voltage during charging

Battery Back-up

*The time (in hrs) for which a battery can deliver the desired current is called **battery back-up** of the bank.*

Example 6.1. : *An alkaline cell is discharged at a steady current of 4 A for 12 hour, the average terminal voltage being 1.2 V to restore it to its original state of voltage, a steady current of 3 A for 20 hour is required, the average terminal voltage being 1.44 V. Calculate the ampere-hour and watt-hour efficiencies in this particular case.*

Solution :

Ampere-hour efficiency,
$$\eta_{AH} = \frac{I_d T_d}{I_c T_c} \times 100$$

where, $I_d = 4\text{ A}$; $T_d = 12\text{ hour}$; $I_c = 3\text{ A}$; $T_c = 20\text{ hour}$;

$$\eta_{AH} = \frac{4 \times 12}{3 \times 20} \times 100 = \mathbf{80\% (Ans.)}$$

Watt-hour efficiency,
$$\eta_{WH} = \frac{I_d T_d V_d}{I_c T_c V_c} \times 100 \quad \text{where, } V_d = 1.2\text{ V} ; V_c = 1.44\text{ V} ;$$

$$\eta_{WH} = \frac{4 \times 12 \times 1.2}{3 \times 20 \times 1.44} \times 100 = \mathbf{66.67\% (Ans.)}$$

Example 6.2. : *A discharged battery is put on charge at 5A for 4 hour at a mean charging voltage of 13.5 V. It is then discharged in 6 hour at a constant terminal voltage of 12 V through a resistance of R ohm. Calculate the value of R for an ampere-hour efficiency of 85%.*

Solution : Ampere-hour efficiency,
$$\eta_{AH} = \frac{I_d T_d}{I_c T_c} \times 100$$

where, $\eta_{AH} = 85\%$; $T_d = 6\text{ hour}$; $I_c = 5\text{ A}$; $T_c = 3.5\text{ hour}$.

$$\therefore 85 = \frac{I_d \times 6}{5 \times 3.5} \times 100 \quad \text{or} \quad I_d = 2.48\text{ A} \quad \text{and} \quad R = \frac{V_d}{I_d} = \frac{12}{2.48} = \mathbf{4.84\text{ ohm (Ans.)}}$$

6.11.4. Charge Indications of a lead-acid Battery or Cell

The charge condition of a battery is usually checked by checking the specific gravity of the electrolyte (H_2SO_4). For a fully charged battery, the specific gravity of H_2SO_4 is 1.28 to 1.29. However, when the specific gravity falls below 1.15, the battery is fully discharged. In fact, to increase the life of battery, it should be recharged when the specific gravity of the electrolyte is found to be less than 1.18. The values of specific gravity for different condition of charge are given below :

<i>Specific gravity</i>	<i>Condition</i>
1.280 to 1.290	100% charged
1.230 to 1.250	75% charged
1.190 to 1.200	50% charged
1.150 to 1.160	25% charged
below 1.130	fully discharged

To check the specific gravity of H_2SO_4 , an instrument called *hydrometer* is used (see fig. 6.22) which works on Archmedeies principle. In common use, the decimal point is omitted from the value of specific gravity *i.e.* 1.280 specific gravity is spoken as 1280 and so on.

However, the state of a battery can also be checked by checking.

- (i) **Voltage** : When the terminal voltage of the battery on load is 2.1 to 2.5 V per cell, the battery is said to be fully charged. Whereas, when the voltage of battery falls to below 1.8 V per cell, the battery is considered to be fully discharged and it is immediately put on charging.
- (ii) **Colour of plates** : When a lead-acid cell or battery is fully charged, its anode is PbO_2 which is *chocolate brown* in colour and cathode is of Pb

which is *grey* in colour. However, when the battery is fully discharged, both the plates attain $PbSO_4$ as active material which is whitish in colour.

Characteristics of Lead-acid Battery

- (i) The e.m.f. of a fully charged lead-acid cell is 2.2 V which decreases to 2.0 V rapidly. However, the average e.m.f. of the cell is 2.0 V which decreases to 1.8 V when fully discharged.
- (ii) The internal resistance of this cell is quite low.
 - The A-H efficiency of this cell is nearly 80% whereas, the W-H efficiency is 60%.
 - The specific gravity of electrolyte is 1280 to 1290 but to 1150 when the battery is fully discharged.

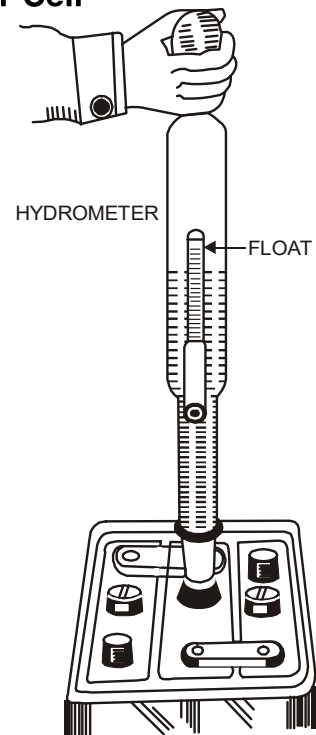


Fig. 6.22: Checking of electrolyte

6.11.5. Charging of lead-acid Battery

Whenever, terminal voltage of a battery falls below 1.8V per cell, it is put under recharging. The following points must be kept in mind while charging a battery :

- (i) Only a d.c. voltage source is applied for recharging.

6.11.6. Care and Maintenance of lead-acid Batteries

The average life of a lead-acid battery is two to four years depending upon its manufacturing qualities and technique. However, to obtain longer life and efficient service, the following points must be kept in view :

1. The battery should not be allowed to use when the e.m.f. of the battery falls to 1.8 V per cell. Otherwise, the lead sulphate of the plates partly changes to non-active lead sulphate and reduces the life of the battery.
2. The specific gravity to the electrolyte should not be allowed to falls below 1.15.
3. The battery should never be left standing in a discharged condition, otherwise sulphation will occur and the battery cells are permanently damaged.
4. When not in use, the battery must be fully charged and stored in a cool and dry place.
5. Great care should be taken that the acid used as electrolyte should not contain any substantial impurity. It should be colourless when viewed through a 12 cm column.
6. The electrodes must remain completely immersed in the electrolyte, preferably the level of electrolyte should always be about 10 mm above the electrodes.
7. Whenever the level of the electrolyte decreases due to evaporation or gassing, distilled water should be added so as to keep the same concentration of electrolyte.
8. The battery should be charged and discharged at low rate so that its temperature may not rise above 45 °C. The high temperature may buckle the plates and damage the separators and the battery may be totally damaged.
9. The battery terminals should never be short circuited.
10. While charging the polarity must be checked carefully.
11. The room where the batteries are charged should be well ventilated as the atmosphere near the batteries would be charged with corresponding acid fumes.
12. The flames must be kept away form the vent of the battery, otherwise hydrogen and oxyzen produced with in the battery cells may get fire.
13. The battery terminals should always be kept clean and periodically greased with vaseline to prevent corrosion.

6.11.7. Applications of lead-acid Batteries

Lead-acid batteries have innumerable commercial applications. Some of the important application are given below :

1. Used in automobiles for starting and lighting.
2. For lighting on steam and diesel railway trains.

3. Used at generating stations and sub-stations for operation of protective devices and for emergency lighting.
4. Used at telephone exchanges.
5. Used for emergency lighting at important places such as hospitals, theaters, banks etc.
6. Used for lighting purposes in remote rural areas.

6.12. NICKEL-IRON ALKALINE CELL

It is also known as Edison-cell as it was developed by an American scientist Thomson A Edison in 1909.

Construction

It contains two plates *i.e.* a positive plate (anode) and a negative plate (cathode). The active material of anode is $Ni(OH)_4$ and of cathode is iron (Fe) when fully charged. The two plates are immersed in the electrolyte, a solution of potassium hydroxide (KOH). A small quantity of lithium hydrate ($LiOH$) is also added to the electrolyte which increases the capacity and life of the cell. The specific gravity of the electrolyte is 1.2. In this case, the container is made of nickel-plated iron to which negative plates are connected. This cell is quit compact as small quantity of electrolyte is used.

Electrical characteristics

- (i) The e.m.f. of a fully charged cell is 1.4 V which decreases to 1.3 V rapidly. However, the average e.m.f. of the cell is 1.2 V which decreases to 1.0 V when fully discharged.
- (ii) The internal resistance of this cell is quite high nearly 5 times to that of a lead-acid cell.
- (iii) The A-H efficiency of this cell is nearly 80% whereas, the W-H efficiency is 60%.

Advantages

It has the following advantages in comparison to that of a lead-acid cell.

- (i) Longer life – about 5 year
- (ii) Its electrolyte (KOH) is not harmful if spilled away.
- (iii) The specific gravity of its electrolyte does not change when discharged, therefore, it can be left in a fully discharged condition for a considerable period of time without damage.
- (iv) Lower weight – nearly half to that of lead-acid cell.
- (v) It can be discharged and recharged at higher rate for longer period without damage.
- (vi) It can withstand higher temperature.
- (vii) It is more rugged and can withstand more mechanical and electrical stresses.

Disadvantages

- (i) Higher cost-nearly double.
- (ii) Higher cost-nearly double.
- (iii) As the e.m.f. developed per cell is less (only 1.2V), more number of cells are required for a particular voltage.

- (iv) Higher internal resistance-nearly 5 times. Therefore, it can not provide large current and is unsuitable for automobile starting.
- (v) Lower efficiency.

6.13. CALCULATIONS FOR ENERGY CONSUMPTION

Electrical energy is supplied to a consumer by the supplier. To charge the electrical energy consumed by a consumer, an energy meter is installed to its quantity. The reading of the energy meter is taken every month. The difference between the fresh reading and the previous reading tell about the consumption of electrical energy in that month. This quantity of energy is multiplied by the rate (or tariff) fixed by the supplier to prepare an electricity bill. However, some other charges such as meter rent, GST, other taxes applicable etc. are also added in the bill.

Example 6.3. : A building has (i) 12 light points of 60 watt each burning 4 hour a day, (ii) a fan point of 75 watt each running 10 hour a day, (iii) a plug point for a 750 watt heater is used one hour a day. (iv) one radio 80 watt used 6 hour a day and (v) a 1/2 H.P. pump of 80% efficiency running 2 hour a day. Calculate the total connected load in kilowatt, maximum possible current, the daily consumption of energy and monthly bill. The supply is given at 230 volt and energy costs Rs. 5.15 per unit. The rent for a meter is Rs. 50 per month. Assume the month of 30 days.

Solution :

Load Points	Connected Load	Energy Consumed/Day
(i) 12 lights of 60W each 4 hr/day	$12 \times 60 = 720 \text{ W}$	$\frac{720 \times 4}{1000} = 2.88 \text{ kWh}$
(ii) 4 fan points of 75W each – 10 hr/day	$4 \times 75 = 300 \text{ W}$	$\frac{300 \times 10}{1000} = 3.00 \text{ kWh}$
(iii) 1 plug point of 750W heater – 1 hr/day	$1 \times 750 = 750 \text{ W}$	$\frac{750 \times 1}{1000} = 0.75 \text{ kWh}$
(iv) 1 radio of 80W – 6 hr/ day	$1 \times 80 = 80 \text{ W}$	$\frac{80 \times 6}{1000} = 0.48 \text{ kWh}$
(v) 1/2 H.P. Pump 80% eff. – 2 hr/day	$\frac{1}{2} \times \frac{735 \cdot 5}{80} \times 100 = 460 \text{ W}$	$\frac{460 \times 2}{1000} = 0.92 \text{ kWh}$
Total	2310 W	8.03 kWh




Therefore connected load,
Maximum possible current,
Energy consumption/day
Energy consumption/month
Rate of energy/month
Energy cost/month
Meter rent/month
Therefore monthly bill

$P = 2310 \text{ W} = 2.31 \text{ kW (Ans.)}$
 $I = P/V = 2310/230 = 10.043 \text{ A (Ans.)}$
 $= 8.03 \text{ kWh (Ans.)}$
 $= 8.03 \times 30 = 240.9 \text{ kWh (Ans.)}$
 $= \text{Rs. } 5.15$
 $= 5.15 \times 240.9 = \text{Rs. } 1240.60$
 $= \text{Rs. } 50.00$
 $= 50 + 1240.60 = \text{Rs. } 1290.60 \text{ (Ans.)}$

PRACTICE EXERCISE

1. An alkaline cell is discharged at a steady current of 4 A for 12 hour, the average terminal voltage being 1.2 V to restore it to its original state of voltage, a steady current of 3 A for 20 hour is required, the average terminal voltage being 1.44 V. Calculate the ampere-hour and watt-hour efficiencies in this particular case. (Ans, 80%; 66.67%)
2. A discharged battery is put on charge at 5A for 4 hour at a mean charging voltage of 13.5 V. It is then discharged in 6 hour at a constant terminal voltage of 12 V through a resistance of R ohm. Calculate the value of R for an ampere-hour efficiency of 85%. (Ans, 4.84 ohm)
3. A building has (i) 12 light points of 60 watt each burning 4 hour a day, (ii) a fan point of 75 watt each running 10 hour a day, (iii) a plug point for a 750 watt heater is used one hour a day. (iv) one radio 80 watt used 6 hour a day and (v) a 1/2 H.P. pump of 80% efficiency running 2 hour a day. Calculate the total connected load in kilowatt, maximum possible current, the daily consumption of energy and monthly bill. The supply is given at 230 volt and energy costs Rs. 5.15 per unit. The rent for a meter is Rs. 50 per month. Assume the month of 30 days. (Ans, 2.31 kW; 10.043 A; 240.9 kWh; 1290.60)

PROJECT

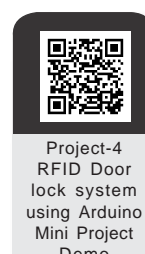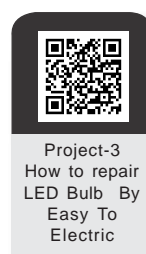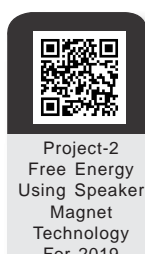

SUMMARY

1. **Switchgear:** In an electric power system, the combination of electrical switches, fuses or circuit breakers used to control, protect and isolate electrical equipment is called switchgear.
2. **Power conducting components:** All the switches, circuit breakers, fuses, and lightning arrestors, that conduct or interrupt the flow of electrical power come under this category.
3. **Controlling components:** All the control panels, current transformers, potential transformers, protective relays, and associated circuitry, that monitor, control, and protect the power conducting components come under this category.

4. *HV, MV & LV switchgears*: In power system, the electrical switchgears are categorized as *HV, MV & LV* switchgears.
5. *HV Switchgears*: High voltage circuit breaker, is the main component of *HV switchgear*,
6. *MV Switchgears*: The switchgear system which is to handle voltages between 3 kV to 33 kV is categorized as medium voltage switchgear or *MV switchgear*. These switchgears are of many types.
7. *LV Switchgears*: Generally electrical switchgear rated upto 1 kV is termed as low voltage switchgear. The term *LV Switchgear* includes low voltage circuit breakers, switches, off load electrical isolators, *HRC* fuses, earth leakage circuit breaker, miniature circuit breakers (*MCB*) and molded case circuit breakers (*MCCB*) etc i.e. all the accessories required to protect the LV system.
8. *Switch Fuse Unit (SFU)*: It comprises of a porcelain or *HRC* fuse and switch. The switch is operated manually with the help of a handle.
9. *Miniature Circuit Breaker (MCB)*: It is a device which ensures definite protection of wiring system and sophisticated equipment against over current and short circuit faults.
10. *ELCB or RCCB*: Earth Leakage Circuit Breaker or Residue Current Circuit Breaker is a device which provides protection against earth leakage faults.
11. *Molded case circuit breakers*: Molded case circuit breaker is the electrical protection device that is commonly used when load current exceed the capabilities of miniature circuit breakers.
12. *Wires and Cables*: A solid or stranded conductor covered with insulation is known as a insulated wire or cable.
13. *Low Tension (LT) Cables*: These cables are employed for system voltages upto 1000 volt. Generally, these cables are used for distribution of electric power at 400 V. The cables are of two types viz single-core and multi-core cables.
14. *Earthing* : The process of connecting metallic bodies of all the electrical apparatus and equipment to the huge mass of earth by a wire of negligible resistance is called *earthing*.
15. *Purpose of earthing* : The basic purpose of earthing is to *protect the human body* (operator) from electric shock.
16. *Equipment earthing* : According to Indian Electricity Rules, it is obligatory to earth the metallic bodies of all the electrical equipment/apparatus/appliance which is operated at 125 V or more than this.
17. *System earthing* : All the electrical equipment/apparatus/appliance operated at 125 V or more must be properly earthed atleast at two places called double earthing.
18. *Methods of earthing* : The following method may be employed for earthing (i) strip earthing (ii) Earthing through water mains (iii) Rod earthing (iv) Pipe earthing (v) Plate earthing. Pipe earthing is considered the best method.
19. *Battery* : A number of cells connected in series, placed in single container is called a *battery*.
20. *Capacity of battery* : The quantity of electricity (in Ah) which a battery can deliver in single discharge is called its *capacity*.

21. *Efficiency of a cell or battery :*

$$\eta_{AH} = \frac{I_d T_d}{I_c T_c}; \quad \eta_{WH} = \frac{I_d T_d V_d}{I_c T_c V_c}$$

22. *Charge indications of a lead-acid cell or battery :*

(i) Specific gravity of electrolyte : 1.280 to 1.290 – 100% charged

(ii) Voltage : more than 2V – fully charged ; below 1.8 V – fully discharged.

(iii) Colour of plates : anode – chocolate brown and cathode – grey fully charged ; both whitish – fully discharged.

23. *Nickle – Iron alkaline cell :* Anode – $Ni(OH)_4$; Cathode – Fe ; Electrolyte – KOH

Electrical characteristics : (i) E.M.F. of a fully charged cell is 1.4 V which decreases rapidly to 1.3 V. Average e.m.f. of the cell is 1.2 V which decreases to 1.0 V when fully discharged.

(ii) High internal resistance – 5 times to lead-acid cell.

(iii) η_{AH} – 80% (App) ; η_{WH} – 60% (App.)

24. *Calculations for energy consumption:* The quantity of electrical energy consumed by the consumer in a specified period is multiplied by the rate (or tariff) fixed by the supplier to prepare an electricity bill.

SHORT ANSWER QUESTIONS

1. What do you mean by switchgear?
2. What are the important elements of *LT* switchgear?
3. What is the function of *SFU*?
4. Why *MCB* is preferred over *SFU*?
5. What is the major function of *ELCB*?
6. How will you differentiate between *MCCB* and *MCB*?
7. What is *CTS* and *VIR* wire ?
8. Name the various types of wiring systems commonly used in residential and commercial buildings.
9. What do you mean by earthing ?
10. How earth resistance can be kept low in dry summer season ?
11. What do you mean by double earthing ?
12. Which type of earthing will you prefer pipe earthing or plate earthing ? Give reasons.
13. How the outer metallic bodies of electrical appliances are connected to earth?
14. What is the function of container of a lead-acid battery.
15. Why large number of holes are provided in the separator.
16. Mention five important applications of a lead-acid battery.

17. While checking the conditions of battery it is seen that the float dips at different levels at different specific gravity of electrolyte, why ?
18. What are the charge indications of a lead-acid battery ?
19. What do you mean by capacity of a battery ? What are its units ?
20. Define ampere-hour efficiency of a battery.
21. What do you mean by capacity of a battery, what are the factors on which it depends ?
22. How do we care a lead-acid battery ? Write five major points.
23. What are the applications of lead-acid batteries ?
24. Name the important components of a Nickel-iron alkaline cell.
25. What are the electrical characteristics of a nickel-iron cell ?
26. How will you calculate the charges of electrical energy used by a consumer?
27. Mention the charge indications of a lead-acid battery.

NUMERICAL FOR PRACTICE

1. An alkaline cell is discharged at a steady current of 5 A for 12 hour, the average terminal voltage being 1.2 V to restore it to its original state of voltage, a steady current of 4 A for 20 hour is required, the average terminal voltage being 1.44 V. Calculate the ampere-hour and watt-hour efficiencies in this particular case. *(Ans. 75%, 62.5%)*
2. A discharged battery is put on charge at 6A for 4 hour at a mean charging voltage of 13.5 V. It is then discharged in 6 hour at a constant terminal voltage of 12 V through a resistance of R ohm. Calculate the value of R for an ampere-hour efficiency of 85%. *(Ans. 3.53 Ω)*
3. Calculate the ampere-hour and watt-hour efficiencies of a secondary cell having 20 hour charge rate of 10 A and delivery rate of 5A for 36 hour with mean terminal voltage of 1.96 V. The terminal voltage during charging has a mean value of 2.35 V. *(Ans. 90% ; 75.06%)*
4. A building has (i) 20 light points of 60 watt each lighting 5 hour a day, (ii) 10 fan point of 70 watt each running 18 hour a day, (iii) a plug point with a 750 watt heater is used two hour a day. (iv) two TVs each of 80 watt used 6 hour a day and (v) a 1/2 H.P. pump motor having 80% efficiency running 2 hour a day. Calculate the total connected load in kilowatt, maximum possible current, the daily consumption of energy and monthly bill. The supply is given at 230 volt and energy costs Rs. 6.00 per unit. The rent for a meter is Rs. 80 per month. Assume the month of 30 days. *(Ans. 3.285 kW, 14.28 A, 22.01 kWh, Rs. 3961.80)*

MULTI-CHOICE QUESTIONS

1. In motor wiring installations, double earthing is required.
 (A) Single (B) double (C) tripple (D) all of these

2. *The material used for fuse element is*
(A) copper (B) Aluminium (C) Tin-lead alloy (D) any of a, b or c
3. *The material used for fuse must have*
(A) low melting point and low specific resistance
(B) low melting point and high specific resistance.
(C) high melting point and low specific resistance
(D) low melting point with any specific resistance.
4. *Fuse is always connected*
(A) in series with the circuit to be protected
(B) in parallel with the circuit to be protected
(C) either (a) or (b)
(D) none of these
5. *Fuse is always connected in*
(A) neutral (B) earth (C) phase (D) any (a), (b) or (c).
6. *The basic purpose of earthing is that*
(A) it avoids faults
(B) it allows the current to flow in the circuit
(C) it protects the operator from electric shock
(D) it stops current to flow in the circuit.
7. *For proper earthing, according to I.E. Rules, of heavy power equipment :*
(A) single earthing is sufficient
(B) double earthing system has to be adopted
(C) half earthing is sufficient
(D) any one of above.
8. *Earth resistance should be very low*
(A) very low (B) 10 ohm (C) 100 ohm (D) very high
9. *The capacity of a cell depends upon*
(A) nature of plates material and electrolyte
(B) size of plates and quantity of electrolyte
(C) both *a* and *b*
(D) none of above
10. *A 12 V lead-acid battery used in a car contains*
(A) 10 cells connected in series (B) 10 cells connected in parallel
(C) 6 cells connected in parallel (D) 6 cells connected in series.

11. To check the specific gravity of an electrolyte, the name of the instrument used is
(A) hydrometer (B) lactometer (C) barometer (D) voltameter
12. The electrolyte used in a Nickel-iron battery is
(A) H_2SO_4 (B) $K(OH)_2$ (C) $NaCl$ (D) none of above
13. When lead-acid battery is fully charged.
(A) The colour of positive plates will be chocolate brown
(B) The colour of negative plates will be whitish
(C) the specific gravity of electrolyte will be 1.15.
(D) All above
14. When a nickel-iron cell is fully charged
(A) the active material of positive and negative plates will be $Ni(OH)_2$ and Fe respectively.
(B) the p.d. across the terminal of the cell be 1.4 V
(C) The specific gravity of the electrolyte (KOH) will be 1.2.
(D) All above.

TEST QUESTIONS

1. What do you mean by electrical switchgear? How will you categorise it?
2. What do you mean by LV switchgear? What are the various a SFU.
3. Explain the construction and working of an MCB.
4. How an MCB is different to fuse?
5. What do you mean by MCCB? How it is different to MCB?
6. Explain the construction and working of an ELCB.
7. How does a fuse protect and maintain the life of an electrical equipment ?
8. Classify the cables (or wires) use in domestic installations
9. Explain with the help of a neat sketch the construction of 4-core LV cable.
10. What is earthing. What is its purpose ?
11. Explain system earthing and equipment earthing.
12. What are the various methods of earthing ? Explain pipe earthing.
13. What do understand by double earthing ?

14. Explain the construction and working of a lead-acid storage battery.
15. How hydrometer is used to determine the charged condition of a lead acid cell ? Explain.
16. Write a note on care and maintenance of a lead-acid battery.
17. Explain the important characteristics of a Lead-acid battery and Nickle-iron battery.
18. State the precautions to be observed in the use of a lead-acid cell.
19. Explain the constructional feature of a typical nickel-iron alkaline cell.
20. Give atleast five important application of a lead-acid battery.
21. How will you calculate the electricity bill of a consumer?

ATTAINMENT & GAP ANALYSIS

Attainment of the Programme Outcomes will be compiled in the table below to make a Gap Analysis and work out remedial measures:

Course Outcome	Attainment of the Programme Outcomes											
	(1- Weak Correlation; 2- Medium correlation; 3- Strong Correlation)											
	PO-1	PO-2	PO-3	PO-4	PO-5	PO-6	PO-7	PO-8	PO-9	PO-10	PO-11	PO-12
CO-1												
CO-2												
CO-3												
CO-4												
CO-5												

ANSWERS TO MULTI-CHOICE QUESTIONS

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (B) | 2. (D) | 3. (A) | 4. (A) | 5. (C) |
| 6. (C) | 7. (B) | 8. (A) | 9. (B) | 10. (D) |
| 11. (A) | 12. (D) | 13. (A) | 14. (D) | |



Experiment No. 9

Demonstration of (a) dc-dc converters (b) dc-ac converters – PWM waveform (c) the use of dc-ac converter for speed control of an induction motor and (d) Components of LT switchgear.

Objective:

1. To show that the generated voltage in an alternator is proportional to excitation (field current) before saturation.
2. To show that the terminal voltage of an alternator falls with the increase in load (when the load is resistive or inductive) i.e. determination of regulation of alternator by direct loading method.

Theory:

(a) DC-DC Power Converters

DC-DC power converters are employed in a variety of applications such as power supplies for personal computers, laptop, office equipment, spacecraft power systems, telecommunications equipment, dc motor drives etc. The input to a dc-dc converter is an unregulated dc voltage and it produces a regulated output voltage of different magnitude. Classification of Converters

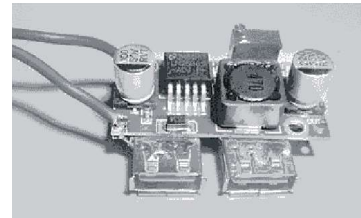


Fig. P9.1: Pictorial view of buck converter
Classification of Converters

The dc-dc converters may be classified as:

Buck Converter: These are step down converters, their output voltage is less than the dc input voltage.

Boost converter: These are step up converters, their output voltage is more than the dc input voltage.

Buck-Boost converter: Their output voltage can be either higher or lower than the dc input voltage.

Buck Converters

Working

The two circuit configurations of a buck converter i.e. On-state, when the switch is closed, and Off-state, when the switch is open are shown in Fig. P9.2 and P9.3 respectively. The arrows indicate the direction of flow of conventional current.

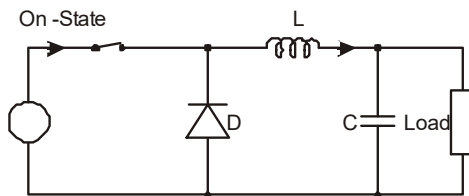


Fig. P9.2: On-state

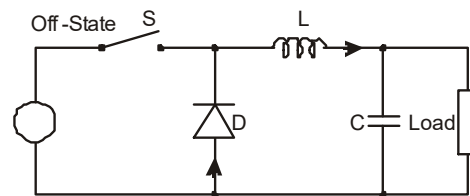


Fig. P9.3: Off-state

The functioning of buck converter is best understood in terms of the relation between current and voltage of the inductor. BUCK CONVERTERS

On-state

- When at first instant the switch is closed (on-state), as shown in Fig. P9.2, the current will begin to increase, and the inductor will produce an opposing voltage across its terminals in response to the changing current. This voltage drop counteracts the voltage of the source and therefore reduces the net voltage across the load.
- If the switch is opened while the current is still changing, then there will always be a voltage drop across the inductor, so the net voltage at the load will always be less than the input voltage i.e. source voltage.

Off-state

- When the switch is opened again (off-state), as shown in Fig. P9.3, the current will start decreasing. The decreasing current will produce a voltage drop across the inductor which will be opposite to the drop at on-state and hence, the inductor becomes a Current Source. The stored energy in the inductor's magnetic field is released which supports the current flow through the load. This off-state current is added to the current flowing during on-state, hence, the total current becomes greater than the average input current (being zero during off-state).
- Thus, during off-state, there is reduction in voltage, but this reduction is compensated by the increase in average current. Ideally, it preserves the power provided to the load. It all happens only because during off-state, the inductor is discharging its stored energy into the rest of the circuit.

Hence, a reduced voltage is obtained across the load, thus a buck converter decreases the dc voltage at the output.

Boost Converters

Boost converter is a DC-to-DC power converter which steps up voltage and steps down the current simultaneously such that input power supply remains the same as that of the output (load). Boost converter is a DC-to-DC power converter which steps up voltage and steps down the current simultaneously such that input power supply remains the same as that of the output (load).

Conventional circuit

The block diagram (conventional circuit) and pictorial view of a boost converter is shown in Fig. P9.4 and P9.5 respectively. It essentially consists of;

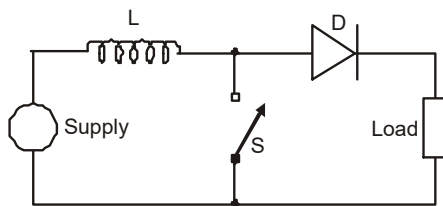


Fig. P9-4: Boost converter circuit diagram.

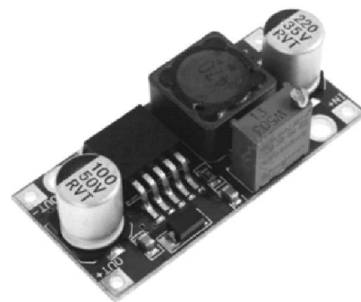


Fig. P9-5: Pictorial view of boost converter

- At least two semiconductors – a diode and a transistor, however, in modern buck converters usually diode is replaced with a transistor and transistor is replaced with a MOSFET or IGBT.
- At least one energy storage element – a capacitor, inductor or the two in combination.
- Extra capacitors (or sometimes a combination of capacitors and inductors) – these are used to filter ripples. These components are normally added to output (load-side) and input (supply-side); not shown here for simplicity.

Principle:

The basic principle of a boost converter is the tendency of an inductor to oppose the changes in current by creating and destroying a magnetic field. In this converter, the output voltage is always higher than the input voltage. A schematic of a boost power stage is shown in Fig. P9.6.

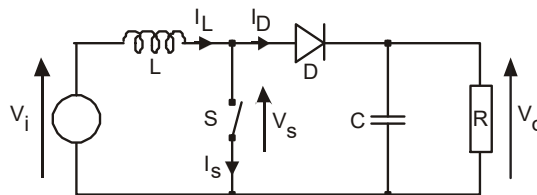


Fig.P9-6: Boost converter schematic

On-state

- When the switch is closed (On-state), current flows through the inductor in clockwise direction, a magnetic field is developed, and some energy is stored in it and the inductor attain a polarity.

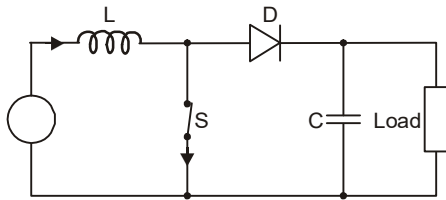


Fig. P9-7: On-state

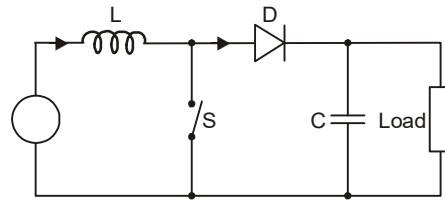


Fig. P9-8: Off-state

Off-state

- When the switch is opened (Off-state), current will reduce since the impedance is higher. The magnetic field previously created will collapse to maintain the current towards the load. Thus, the emf of the two sources will be in series causing a higher voltage to charge the capacitor through the diode D.

Hence, a higher voltage and reduced current is obtained across the load, thus a boost converter increases the dc voltage but decreases current at the output.

Procedure:

To demonstrate a dc-dc converters:

1. Make the connections as per the converter available in the lab.
2. Get the connections checked by the teacher in-charge.
3. Measure the input and output dc voltage and observe wave shape at the input and output on CRO.

(b) dc-ac Converters – PWM waveform

Principle: Pulse Width Modulation

Pulse Width Modulation (PWM) is a digital technology that is employed to change the amount of power delivered to a device. A pulse width modulator generates analogue signals by using a digital source. A PWM signal is basically a square wave which is switched between on and off state. The duty cycle and frequency of a PWM signal determine its behaviour.

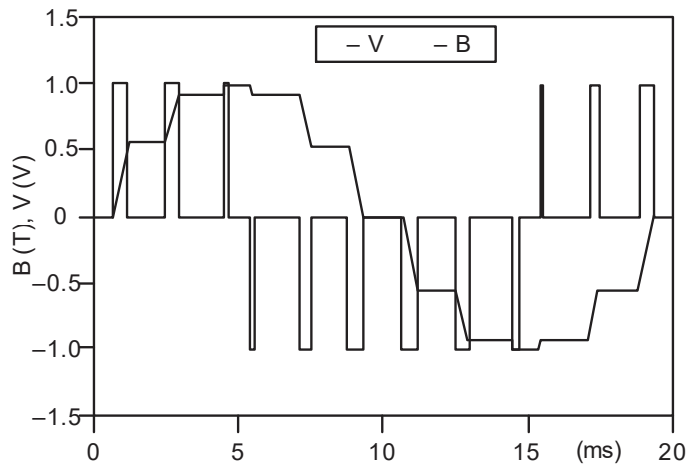


Fig. P9-9: Wave shape of a Pulse Width Modulation (PWM)

An example of PWM in an idealized inductor driven by a voltage source modulated as a series of pulses, resulting in a current in the inductor like a sine wave. The rectangular voltage pulses nonetheless result in a more and more smooth current waveform, as the switching frequency increases. Note that the current waveform is the integral of the voltage waveform.

(c) The use of dc-ac converter for speed control of an induction motor

Single-phase voltage source inverter

A typical power-circuit topologies of a single-phase voltage source inverter is shown in Fig. P9.10. For medium output power applications, only one dc source and the preferred devices are:

- (i) n-channel IGBTs (Q1, Q2, Q3 etc.- act as fast and controllable switches)
- (ii) a large dc link capacitor (C_{dc})
- (iii) fast recovery diodes (D1, D2, D3 etc.)

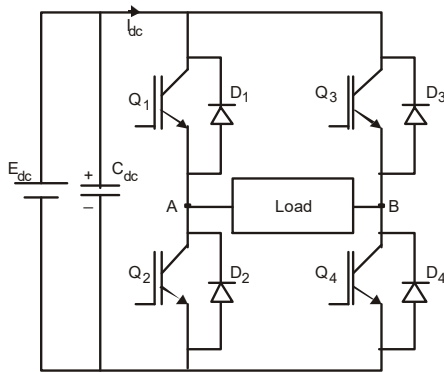


Fig. P9.10: Topology of a single-phase VSI

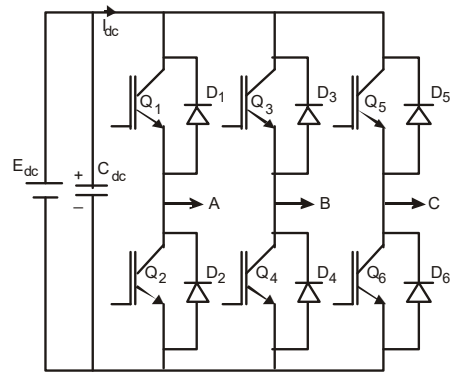


Fig. P9.11: Topology of a three-phase VSI

Three-phase voltage source inverter

A typical power-circuit topologies of a three-phase voltage source inverter is shown in Fig. P9.11. For medium output power applications, only one dc source and the preferred devices are:

- (i) n-channel IGBTs ($Q1, Q2, Q3, Q4, Q5, Q6$ - act as fast and controllable switches)
- (ii) a large dc link capacitor (C_{dc})
- (iii) fast recovery diodes ($D1, D2, D3, D4, D5, D6$)

Procedure:

1. A dc-ac converter is just an inverter which converts dc into ac, used at our domestic installations, offices etc. The same inverter can be used for experiment or make the connections as per circuit shown in fig. 9.10 and 9.11.
2. Get the connections checked by the teacher in-charge.
3. Measure the input dc voltage and output ac voltage, observe wave shapes at the input and output on CRO.

(d) Components of LT switchgear

Some of the important components of LT switchgear are mentioned below:

1. Switch Fuse Unit (SFU)

Switch Fuse: Switch fuse Unit comprises of various porcelain rewirable fuses or HRC fuse fittings complete with their conducting parts. The switch is fitted with sturdy side operating handle with quick-break type mechanism, as shown in fig.P9.12. It is used to connect or disconnect the main supply to the load.

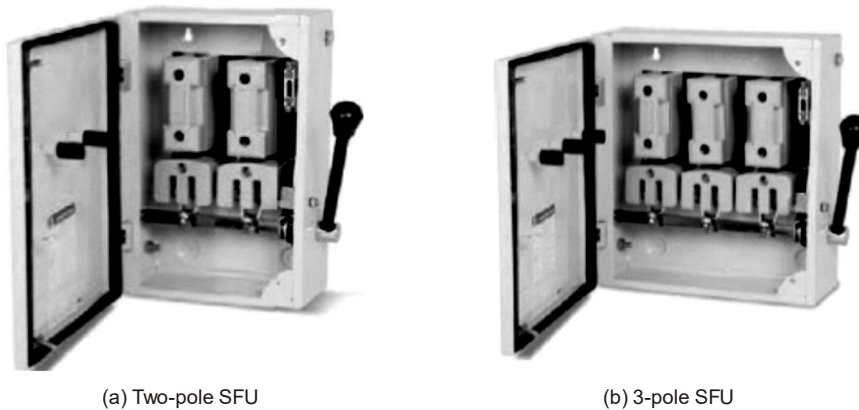


Fig. P9.12: Switch Fuse Unit (SFU)

2. Miniature Circuit Breaker (MCB)

Miniature Circuit Breaker (MCB) is a device which ensures definite protection of wiring system and sophisticated equipment against over current and short circuit faults. The outer view and the internal details of a miniature circuit breaker are shown in Fig. P9.13 and P9.14 respectively.



Fig. P9.13: Outer view of an MCB

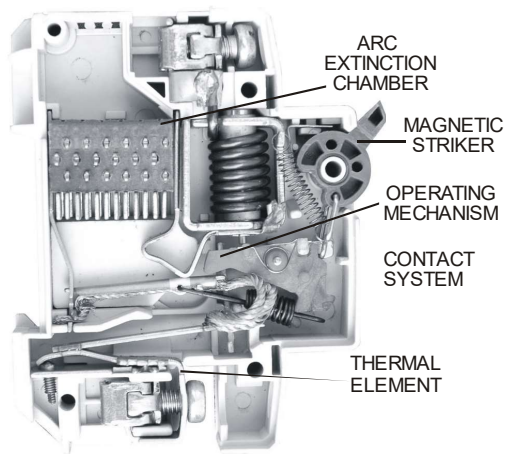


Fig.P9.14: Internal structure of MCB

3. Earth Leakage Circuit Breaker (ELCB)

In the industrial, commercial and domestic building sometimes (usually in rainy season) leakage to earth occurs. This leakage may cause electric shock or fire. Hence, the leakage to earth is very dangerous and needs protection.

ELCB is a device which provides protection against earth leakage faults.

A 2-pole ELCB is used for 1-phase supply and a 4-pole ELCB is used for 3-phase, 4 wire supply. A 4-pole ELCB is shown in Fig.P9.15.

Internal wiring diagram of a 2-pole ELCB is shown in Fig.P9.16.



Fig. P9.15: 4-pole ELCB

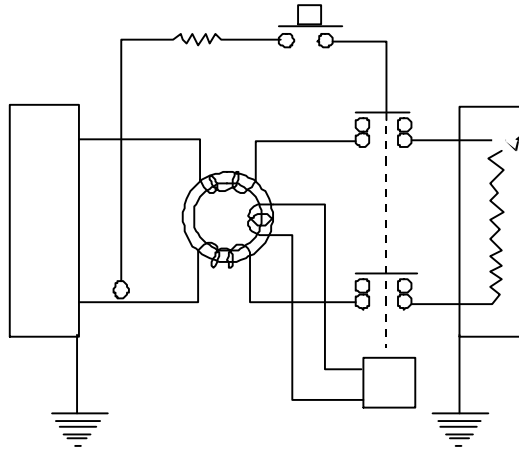


Fig. P9.16: Internal wiring diagram of a 2-pole ELCB

4. Moulded Case Circuit Breaker (MCCB)

Moulded case circuit breakers are the electrical protection device that is commonly used when load current exceed the capabilities of miniature circuit breakers. They are also used where the current rating are required to be adjusted by adjusting trip settings, which are not available in plug-in circuit breakers and MCBs.



100 AMP MCCB Moulded
Case Circuit Breakers



100 AMP MCCB 4 pole
Electrical Circuit Breakers

Fig.P9.17: Moulded case circuit breakers

Two such Moulded case circuit breakers are shown in fig. P9.17.

