



K. K. Wagh Institute of Engineering Education & Research, Nashik
(An Autonomous Institute From A.Y. 2022-23)

WINTER-2025	
Exam Seat No.:	
Academic Year:2025-2026	Semester:III
Class:SY	Program:B.Tech
Branch Code:ROB	Pattern:2022
Name of Course:Electrical and Electronics Systems	Course Code:ROB222003
Max. Marks:60	Duration:2.30 Hrs.

Instructions: Candidates should read carefully the instructions printed on the Question Paper and on the cover page of the Answer Book, which is provided for their use.

1. This question paper contains 02page(s).
2. Answer to each new question is to be started on a new page.
3. Assume suitable data wherever required, but justify it.
4. Draw the neat labelled diagrams, wherever necessary.
5. The last columns indicates the Course Outcome and level of Blooms Taxonomy of the Question/sub-question.

Marks CO

Question No. 1

- 1a) Explain the working of NPN transistor with diagram (6) CO1, CO2

Question No. 2

- 2a) Explain Dfferentiator with diagram (6) CO3, CO4

Question No. 3

- 3a) Explain working of SCR with diagram (8) CO1, CO2

OR

- 3b) Explain construction and working FET. (8) CO3

- 3c) Explain working of opto- isolator (8) CO3

OR

- 3d) Explain different signal conditioning method with diagram (8) CO4

Question No. 4

- 4a) Derive the EMF equation of DC generator (8) CO3

OR

- 4b) Explain the working of DC series motor with diagram (8) CO3

- 4c) Explain the regenerative braking method of DC motor. (8) CO3, CO4

OR

- 4d) State the different industrial application of DC motor. (8) CO3

Question No. 5

5a) Explain the construction and working principle of stepper motor (8) CO5

OR

5b) Explain Torque slip characteristics of induction motor: (8) CO5

5c) Explain construction and working principle Servo motor (8) CO5

OR

5d) Explain any two method of speed control of Induction motor. (8) CO5

..... End of question paper.....