



**K. K. Wagh Institute of Engineering Education & Research, Nashik**  
(An Autonomous Institute From A.Y. 2022-23)

WINTER-2025	
Exam Seat No.:	
Academic Year:2025-2026	Semester:IV
Class:SY	Program:B.Tech
Branch Code:ELE	Pattern:2023
Name of Course:Power Electronics	Course Code:2306213
Max. Marks:60	Duration:2.30 Hrs.

**Instructions:** Candidates should read carefully the instructions printed on the Question Paper and on the cover page of the Answer Book, which is provided for their use.

1. This question paper contains 03 page(s).
2. Answer to each new question is to be started on a new page.
3. Assume suitable data wherever required, but justify it.
4. Draw the neat labelled diagrams, wherever necessary.

**Marks CO**

**Question No. 1**

- 1a) A single phase fully controlled converter fed from AC supply is used to control DC voltage across with RL load where inductance is very high to maintain constant current, If AC source voltage is 200V rms, calculate the firing angle to produce average output voltage (6) CO2
- (i) 100V
- (ii) -100V

**Question No. 2**

- 2a) (i) Compare MOSFET with IGBT. (3 Marks) (6) CO1
- (ii) Compare SCR with TRIAC. (3 Marks)

**Question No. 3**

- 3a) In a buck-boost converter show that (8) CO2
- $$\frac{V_0}{V_s} = \frac{D}{1-D}$$
- with the help of circuit diagram and waveform.

**OR**

- 3b) In a boost converter show that (8) CO2
- $$\frac{V_0}{V_s} = \frac{1}{1-D}$$
- with the help of circuit diagram and waveform.

- 3c) Design a buck converter with following specifications (8) CO4  
Input voltage=36V  
Output voltage=24V  
Output power=100W  
Allowable ripple in output voltage 1% of average output voltage  
Allowable ripple in inductor current is 15% of load current.  
Switching frequency=75kHz

**OR**

- 3d) Design a buck-boost converter to transfer battery to motor of electric vehicle with following specifications (8) CO4  
Battery output voltage=48V.  
Motor specification= 200W at 36V  
Allowable ripple in output voltage 2% of average output voltage  
Allowable ripple in inductor current is 15%.  
Switching frequency=75kHz

**Question No. 4**

- 4a) A step down chopper is having input 200V and it used to control a motor of 100V. If switching frequency is 10kHz, calculate (8) CO3
- (i) Duty cycle (1 Marks)
  - (ii) Pulse width (1 Marks)
  - (iii) Output voltage, if the pulse width is reduced to half keeping switching frequency constant. (3 Marks)
  - (iv) Pulse width required, if the required output voltage is 150V with same switching frequency. (3 Marks)

**OR**

- 4b) A step up chopper is having input 75V and it used to control a motor of 100V. If on time of chopper is 100 $\mu$ sec, calculate (8) CO3
- (i) Duty cycle (1 Marks)
  - (ii) Switching frequency (1 Marks)
  - (iii) Output voltage, if the pulse width is reduced to half keeping switching frequency constant. (3 Marks)
  - (iv) Pulse width required, if the required output voltage is 150V with same switching frequency. (3 Marks)
- 4c) Draw the circuit diagram of single phase AC voltage regulator connected to RL load. Explain the working with the help of waveform. (8) CO3

**OR**

- 4d) A single phase AC voltage regulator is used in R load. (8) CO3
- (i) Derive the rms output voltage current and power for given circuit. (5 marks)
  - (ii) If input voltage is 230V, 50Hz and load is 1000W at unity power factor, calculate rms output voltage and current. Firing angle is 45 degree. (3 marks)

**Question No. 5**

- 5a) Derive the instantaneous output voltage of single phase half bridge inverter using Fourier analysis and show that only odd harmonics are present in the output. (8) CO3

**OR**

- 5b) For a single phase full bridge voltage source inverter is used to control resistive load of 1000W from a battery of 100V. Calculate: (8) CO3
- (i) rms output voltage (2 Marks)
  - (ii) fundamental rms output voltage (2 Marks)
  - (iii) fundamental output current (2 Marks)
  - (iv) Total harmonic distortion (THD) (2 Marks)

- 5c) Draw the circuit diagram and waveform for three voltage source inverter with 180 degree of conduction. Explain the working of the same. (8) CO2

**OR**

- 5d) Draw the circuit diagram and explain working of cascaded multilevel inverter (8) CO2

**..... End of question paper.....**